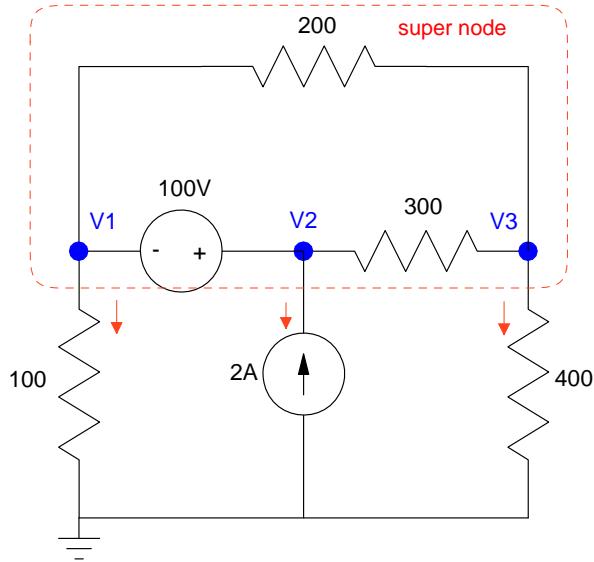


# ECE 320 - Homework #1

EE 206 Review, Phasors. Due Monday, January 14, 2019

## 1. Voltage Nodes:



- a) Write the voltage node equations for the following circuit

$$V_2 - V_1 = 100 \quad \text{voltage source}$$

$$\left(\frac{V_3 - V_2}{300}\right) + \left(\frac{V_3 - V_1}{200}\right) + \left(\frac{V_3 - 0}{400}\right) = 0 \quad \text{current from node } V_3 \text{ must sum to zero}$$

$$\left(\frac{V_1}{100}\right) - 2 + \left(\frac{V_3}{400}\right) = 0 \quad \text{current from the supernode must sum to zero}$$

*note: Other supernodes are also OK. As long as the supernode forms a closed region, the sum from that region must sum to zero.*

- b) Solve using Matlab (or similar program)

Group terms

$$V_2 - V_1 = 100$$

$$\left(\frac{-1}{200}\right)V_1 + \left(\frac{-1}{300}\right)V_2 + \left(\frac{1}{200} + \frac{1}{300} + \frac{1}{400}\right)V_3 = 0$$

$$\left(\frac{1}{100}\right)V_1 + \left(\frac{1}{400}\right)V_3 = 2$$

Place in matrix form

$$\begin{bmatrix} -1 & 1 & 0 \\ \left(\frac{-1}{200}\right) & \left(\frac{-1}{300}\right) & \left(\frac{1}{200} + \frac{1}{300} + \frac{1}{400}\right) \\ \left(\frac{1}{100}\right) & 0 & \left(\frac{1}{400}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 2 \end{bmatrix}$$

Solve in Matlab (or similar program. I like SciLab: it's free. I like free.)

```
A = [-1, 1, 0 ; -1/200,-1/300,1/200+1/300+1/400 ; 1/100,0,1/400]
```

```
- 1.      1.      0.  
- 0.005  - 0.0033333  0.0108333  
 0.01      0.      0.0025
```

```
B = [100;0;2]
```


```
100.  
0.  
2.
```

```
V = inv(A)*B
```

```
v1    161.29032  
v2    261.29032  
v3    154.83871
```

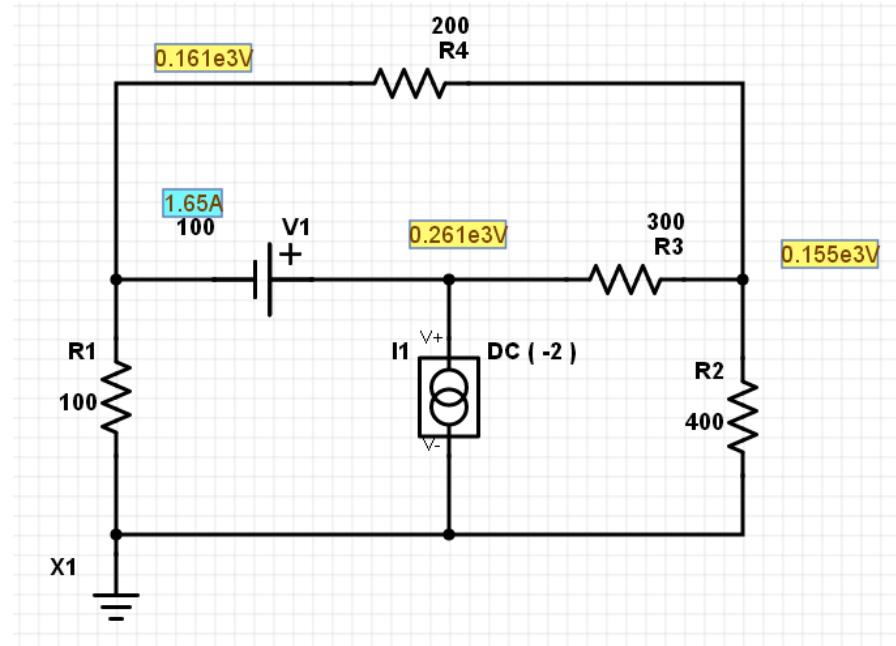c) Check your answers in PartSim (or similar circuit simulator)


*note: The current source in PartSim has an odd symbol where it's not obvious which way the current flows. So, I have a 50/50 shot at getting the direction correct. Turns out the current flows out of the minus terminal (or make the current negative if it comes out of the + terminal)*



Comparing the results, calculations match simulation results.

	Computed part b	Simulated part c
V1	161.29032	161V
V2	261.29032	261V
V3	154.83871	155V

## 2. Current Loops:

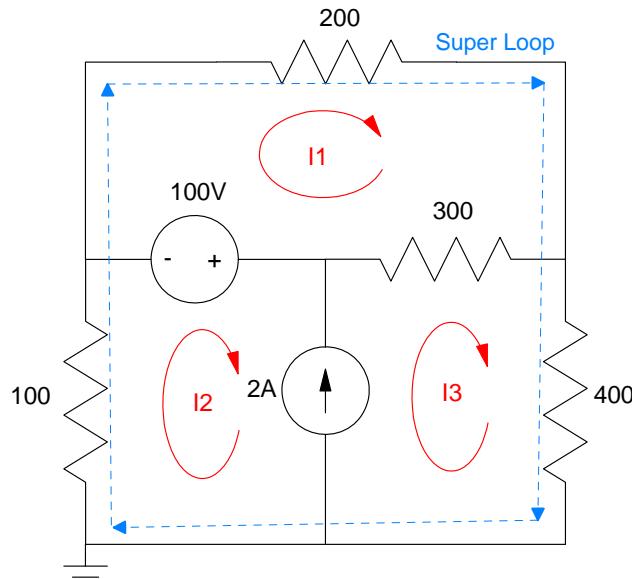

a) Write the current loop equations for the following circuit

$$I_3 - I_2 = 2 \quad \text{current source}$$

$$200I_1 + 300(I_1 - I_3) + 100 = 0 \quad \text{sum of voltages around loop } I_1 \text{ must equal zero}$$

$$100I_2 + 200I_1 + 400I_3 = 0 \quad \text{sum of voltages around super loop must equal zero}$$

*Note: There are multiple solutions. As long as you have three independent equations you can solve for three unknowns.*

b) Solve using Matlab (or similar program)

Group terms

$$I_3 - I_2 = 2$$

$$500I_1 - 300I_3 = -100$$

$$100I_2 + 200I_1 + 400I_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 0 & -1 & 1 \\ 500 & 0 & -300 \\ 200 & 100 & 400 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2 \\ -100 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
A = [0,-1,1 ; 500,0,-300 ; 200,100,400]
```

```
0.      - 1.      1.  
500.    0.      - 300.  
200.    100.    400.
```

```
B = [2 ; -100 ; 0]
```

```
2.  
- 100.  
0.
```

```
I = inv(A)*B
```


```
I1    0.0322581  
I2   - 1.6129032  
I3    0.3870968
```

Sidelight: To compare this to PartSim, you have to do some computations

$$I_1 = \left( \frac{161V - 155V}{200\Omega} \right) = 0.03A$$


$$I_2 = \left( \frac{0V - 161V}{100\Omega} \right) = -1.61A$$

$$I_3 = \left( \frac{155V}{400\Omega} \right) = 0.387A$$

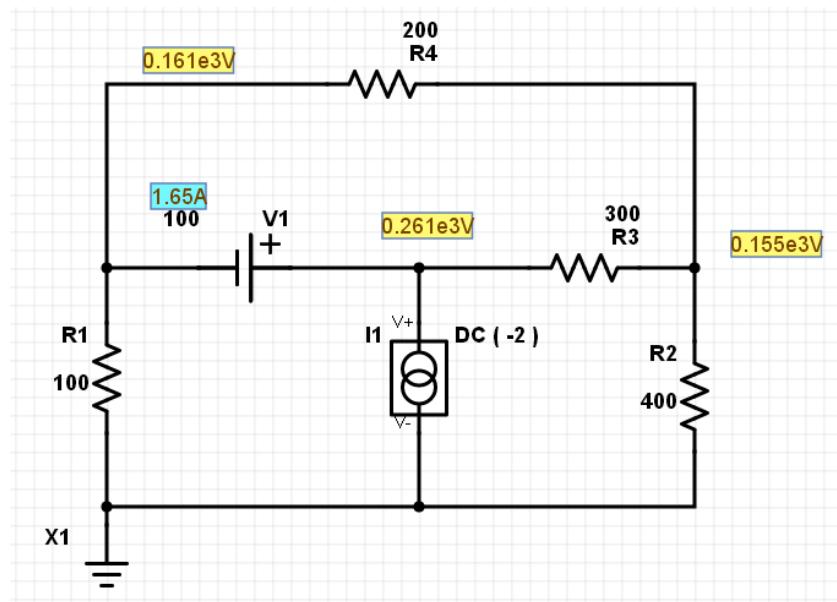

Problem 1 - 2

### 3. Voltage Nodes:

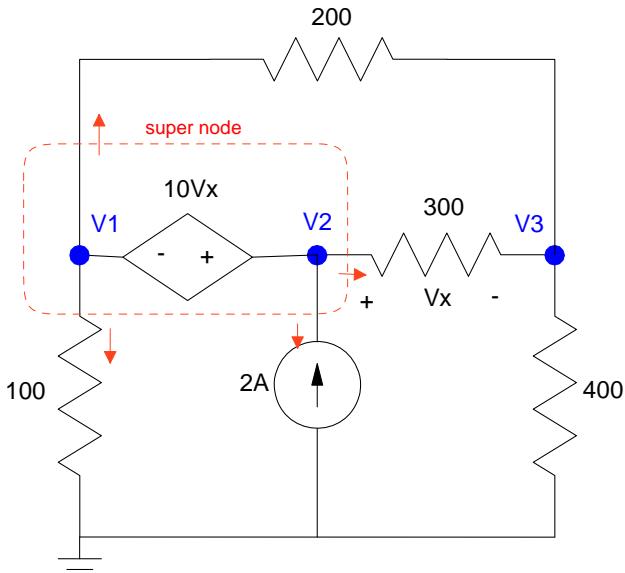

a) Write the voltage node equations for the following circuit

$$V_x = V_2 - V_3$$

*define  $V_x$  (gives a 4th equation)*

$$V_2 - V_1 = 10V_x$$

*dependent voltage source*

$$\left(\frac{V_3 - V_1}{200}\right) + \left(\frac{V_3 - V_2}{300}\right) + \left(\frac{V_3}{400}\right) = 0$$

*sum of current from node  $V_3$  is zero*

$$\left(\frac{V_1 - V_3}{200}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{V_2 - V_3}{300}\right) - 2 = 0$$

*sum of current from the supernode is zero*

b) Solve using Matlab (or similar program)

Group terms

$$V_2 - V_3 - V_x = 0$$

$$V_2 - V_1 - 10V_x = 0$$

$$\left(\frac{-1}{200}\right)V_1 + \left(\frac{-1}{300}\right)V_2 + \left(\frac{1}{200} + \frac{1}{300} + \frac{1}{400}\right)V_3 = 0$$

$$\left(\frac{1}{200} + \frac{1}{100}\right)V_1 + \left(\frac{1}{300}\right)V_2 - \left(\frac{1}{200} + \frac{1}{300}\right)V_3 = 2$$

Place in matrix form

$$\begin{bmatrix} 0 & 1 & -1 & -1 \\ -1 & 1 & 0 & -10 \\ \left(\frac{-1}{200}\right) & \left(\frac{-1}{300}\right) & \left(\frac{1}{200} + \frac{1}{300} + \frac{1}{400}\right) & 0 \\ \left(\frac{1}{200} + \frac{1}{100}\right) & \left(\frac{1}{300}\right) & -\left(\frac{1}{200} + \frac{1}{300}\right) & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 2 \end{bmatrix}$$

Solve in Matlab

```

a1 = [0,1,-1,-1];
a2 = [-1,1,0,-10];
a3 = [-1/200,-1/300,1/200+1/300+1/400,0];
a4 = [1/200+1/100,1/300,-1/200-1/300,0];
A = [a1;a2;a3;a4]

0.          1.          - 1.          - 1.
- 1.          1.          0.          - 10.
- 0.005    - 0.0033333  0.0108333  0.
0.015      0.0033333  - 0.0083333  0.

B = [0;0;0;2]


0.
0.
0.
2.

V = inv(A)*B

v1      172.06704
v2      105.02793
v3      111.73184
vx     - 6.7039106

```

#### 4. Current Loops:

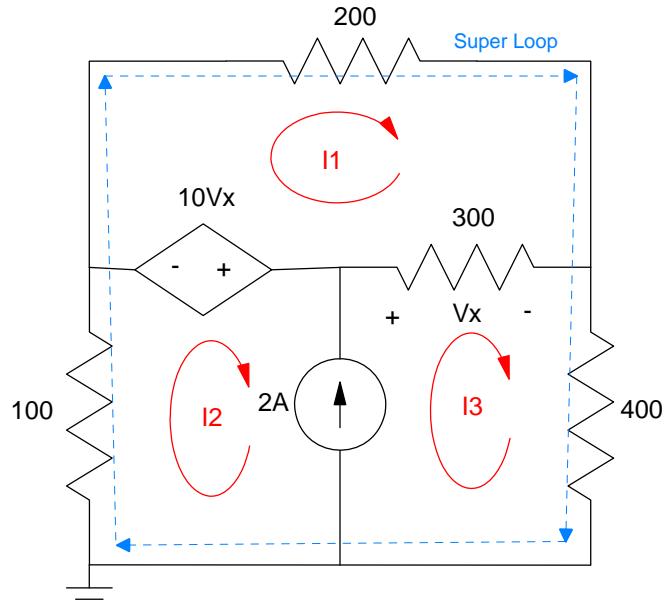

a) Write the current loop equations for the following circuit

$$V_x = 300(I_3 - I_1) \quad \text{define the control voltages in terms of } I_1, I_2, I_3$$

$$I_3 - I_2 = 2 \quad \text{current source}$$

$$200I_1 + 300(I_1 - I_3) + 10V_x = 0 \quad \text{voltages around loop } I_3 \text{ must sum to zero}$$

$$100I_2 + 200I_1 + 400I_3 = 0 \quad \text{voltages around the super loop must sum to zero}$$

b) Solve using Matlab (or similar program). Group terms

$$300I_3 - 300I_1 - V_x = 0$$

$$I_3 - I_2 = 2$$

$$500I_1 - 300I_3 + 10V_x = 0$$

$$100I_2 + 200I_1 + 400I_3 = 0$$

Place in matrix form

$$\begin{bmatrix} -300 & 0 & 300 & -1 \\ 0 & -1 & 1 & 0 \\ 500 & 0 & -300 & 10 \\ 200 & 100 & 400 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```

A = [-300,0,300,-1 ; 0,-1,1,0 ; 500,0,-300,10 ; 200,100,400,0]
- 300.      0.      300.    - 1.
  0.      - 1.      1.      0.
  500.      0.      - 300.    10.
  200.     100.     400.    0.

B = [0;2;0;0]

  0.
  2.
  0.
  0.

I = inv(A)*B


  0.3016760
- 1.7206704
  0.2793296
- 6.7039106

```

As a check

$$V_1 = -100I_2 = 172.06V \quad \text{matches voltage calculations}$$
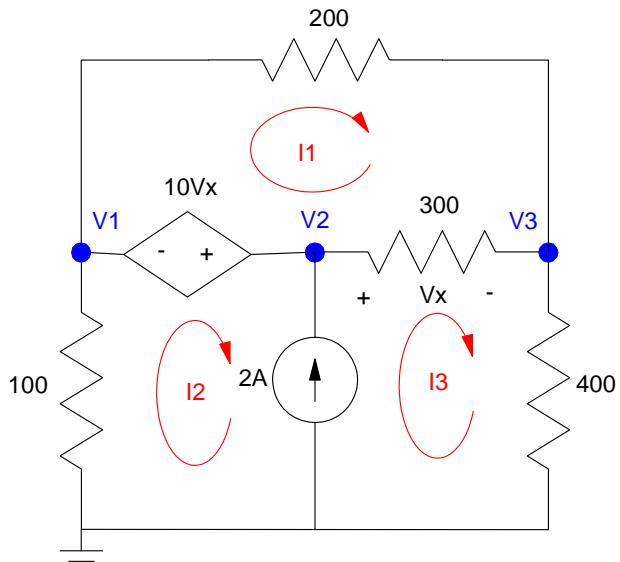
$$V_3 = 400I_3 = 111.728V \quad \text{matches voltage calculations}$$



Problem 3 & 4

5) Assume Vin contains a DC and 1.6Hz (10 rad/sec) signal:

$$V_{in} = 10 + 3 \sin(10t)$$


- a) Determine the impedances of the inductor, capacitor, and resistor at DC and 10 rad/sec
- b) Determine the voltage, Y, using phasor analysis

### DC Analysis

$$V_{in} \rightarrow 10 + j0$$

$$L \rightarrow j\omega L = 0$$
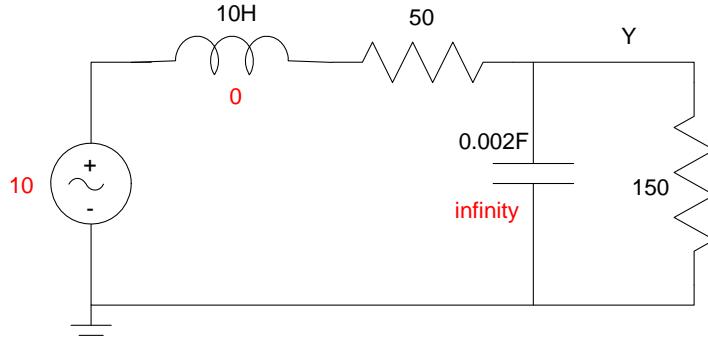
$$C \rightarrow \frac{1}{j\omega C} = \infty$$



By voltage division

$$Y = \left( \frac{150}{150+50} \right) \cdot 10 = 7.5V$$


### AC Analysis

$$\omega = 10$$

$$V_{in} \rightarrow 0 - j3 \quad \text{real} = \cosine, \ -\text{imag} = \sinus$$

$$L \rightarrow j\omega L = j100$$
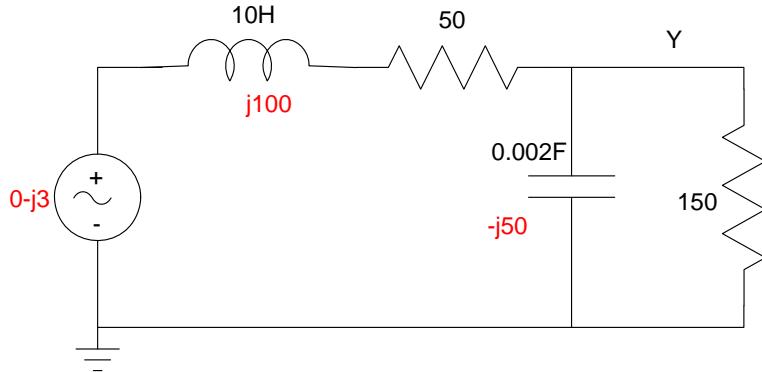
$$C \rightarrow \frac{1}{j\omega C} = -j50$$



Combine the resistor and capacitor in parallel

$$150|| -j50 = \left( \frac{1}{150} + \frac{1}{-j50} \right)^{-1} = 15 - j45$$

By voltage division

$$Y = \left( \frac{(15-j45)}{(15-j45)+(50+j100)} \right) (0 - j3)$$

$$Y = -1.5517 + j0.6207$$

meaning

$$y(t) = -1.5517 \cos(10t) - 0.6207 \sin(10t)$$

The total answer is the DC term plus the AC term

$$y(t) = DC + AC$$

$$y(t) = 7.5 - 1.5517 \cos(10t) - 0.6207 \sin(10t)$$

Note: If you prefer polar form

$$Y = 1.6713 \angle 158.2^\circ$$

meaning



$$y(t) = 1.6713 \cos(10t + 158.2^\circ)$$

The total answer (in polar form) is then...

$$y(t) = 7.5 + 1.6713 \cos(10t + 158.2^\circ)$$

Both answers are correct

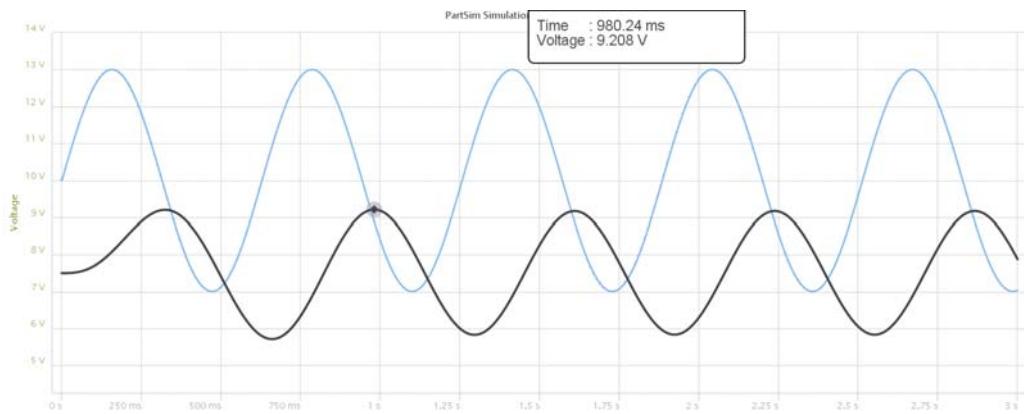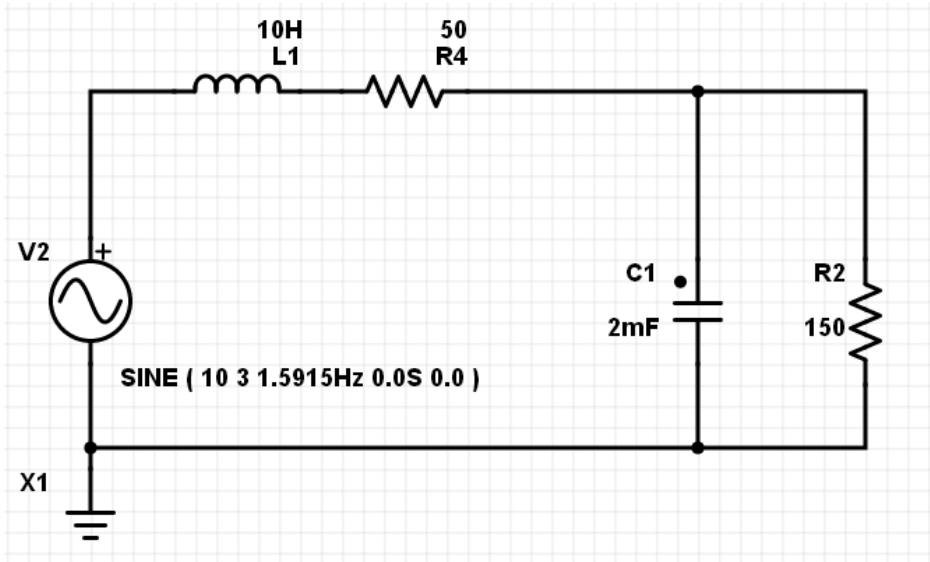c) Check your answer using PartSim (or similar program)




Comparing to calculations:

	Calculated part b	Simulated part c
DC Level	7.5V	7.5V
AC (Vpp)	3.3426Vpp	3.338Vpp

6) Assume Vin contains a DC and 16Hz (100 rad/sec) signal:

$$V_{in} = 10 + 3 \sin(100t)$$

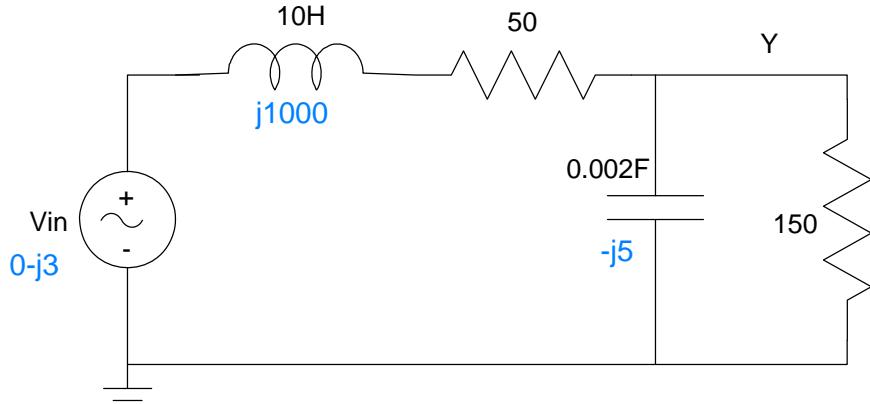- a) Determine the impedances of the inductor, capacitor, and resistor at DC and 100 rad/sec
- b) Determine the voltage, Y, using phasor analysis



Problem 5 & 6:

DC: No change from problem 5

$$Y = 7.5V$$

AC:  $V_{in} = 3 \sin(100t)$

$$V_{in} \rightarrow 0 - j3$$

$$L \rightarrow j\omega L = j1000$$

$$C \rightarrow \frac{1}{j\omega C} = -j5$$

Add the 150 Ohms and the capacitor in parallel

$$150 \parallel -j5 = 0.1665 - j4.9945$$

By voltage division

$$Y = \left( \frac{(0.1665 - j4.9945)}{(0.1665 - j4.9945) + (50 + j1000)} \right) (0 - j3)$$

$$Y = -0.0013 + j0.0015$$

$$Y = 0.0150 \angle 94.8^\circ$$



meaning

$$y(t) = 0.0150 \cos(100t + 94.8^\circ)$$

The total answer is the DC and AC term

$$y(t) = 7.5 + 0.0150 \cos(100t + 94.8^\circ)$$

c) Check your answer in PartSim

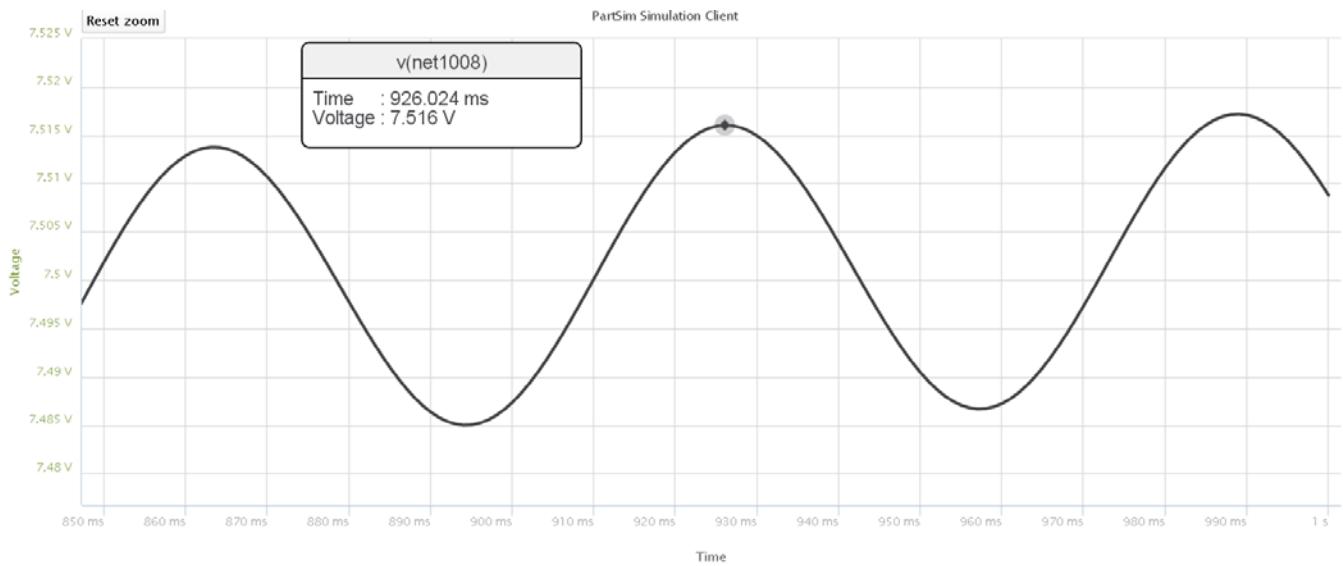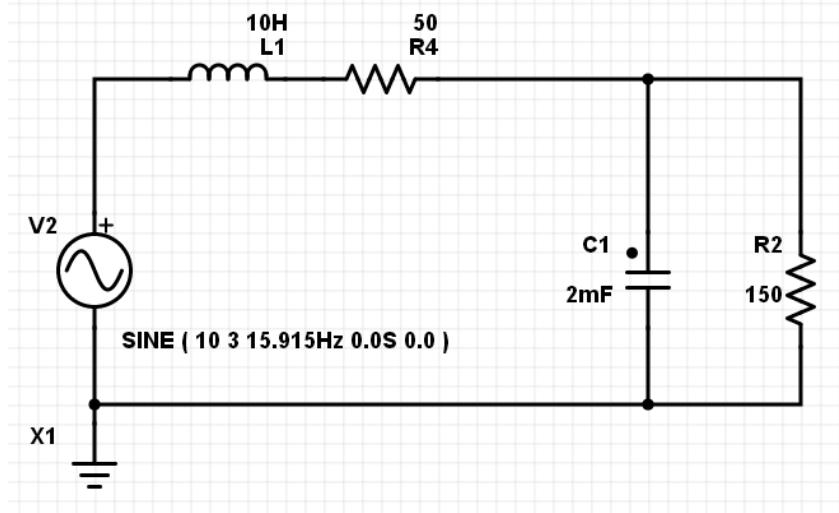

Comparing simulation to calculation results:

	Calculated part b	Simulated part c
DC Level	7.5V	7.5V
AC (Vpp)	0.0301 Vpp	0.032 Vpp