ECE 320 - Homework #6

H Bridge, DC to DC Converters, Fourier Transform. Due Wednesday, February 20, 2019

H-Bridge

Assume a TIP112 and TIP117 transistor for the following H-bridge (Darlington pairs)

- $\beta = 1000$
- $V_{be} = 1.4V$
- $\min(|V_{ce}|) = 0.9V$
- 1) Determine the voltages V1 and V2 for the following H-bridge



$$I_2 = \left(\frac{12-1.4}{40k}\right) = 265 \mu A$$
 $\beta I_2 = 265 m A$

Assuming both transistors are satuated...

$$I_3 = \left(\frac{12 - 0.9 - 0.9}{25}\right) = 408mA$$

The actual current, I3, is the smallest of these

$$I_3 = \min(1.6A , 408mA , 265mA) = 265mA$$

meaning that transistor 1 is saturated, transistor 2 is active

$$V_4 = 12 - 0.9V = 11.1V$$
$$V_3 = V_2 - 25\Omega \cdot 265mA = 4.475V$$

- 2) Modify this circuit to meet the following requirements
 - Input: A,B,C,D. 0/12V binary signals, capable of 20mA
 - Output: 50 Ohm resistor
 - Relationship: By varying A,B,C,D, the voltage across the 50 Ohm resistor can be set to +12V, -12V, and 0V (+/-1V)

The current you're trying to drive through a 50 Ohm resistor is

$$I_3 = \left(\frac{12V - 0.9V - 0.9V}{50\Omega}\right) = 204mA$$

To saturate each transistor, you need

$$\beta I_b > I_c$$
$$I_b > \frac{204mA}{1000} = 204\mu A$$

Let Ib = 1mA. Then

$$R_b = \left(\frac{12V - 1.4V}{1mA}\right) = 10.6k$$

Let Rb = 10k



DC to DC Converters (Buck converter)

3) For the following Buck converter, determine the votlages at V1 and V2 (DC and AC)



$$V_1 = 0.4 \cdot 20V + 0.6 \cdot (-0.7V) = 7.58V$$
$$V_2 = \left(\frac{100}{100+10}\right)V_1 = 6.89V$$

AC

$$V_{1} = 20.7V_{pp}$$

$$V_{2} = \left(\frac{9.21 - j28.91}{(9.21 - j28.91) + (10 + j68.20)}\right) \cdot 20.7V_{pp}$$

$$V_{2} = 16.12V_{pp}$$

4) Simulated your design for problem #3 in PartSim (or similar program) to verify the DC and AC voltages at V2



	V1		V2	
	DC	AC	DC	AC
Calculated	7.58 V	20.7 Vpp	6.89 V	14.36 Vpp
Simulated	?	20.67 Vpp	11.67 V	10.96 Vpp

- 5) Modify this circuit so that the votlage at V2 is
 - 5V (DC)
 - 250mVpp (AC)

```
DC:
```

$$V_{2} = 5V$$

$$V_{1} = \left(\frac{100+10}{100}\right)V_{2} = 5.50V$$

$$5.50V = \alpha \cdot 20V + (1 - \alpha)$$

$$\alpha = \left(\frac{5.50+0.7}{20+0.7}\right) = 0.2995$$

Duty Cycle = 29.95%

AC:

Pick L to reduce the ripple by 10x (ripple becomes 2.07 Vpp)

$$|j\omega L| = 10 \cdot R_{load} = 1000\Omega$$
$$L = 159mH$$

Pick C to reduce the ripple down to 250mVpp

$$\left|\frac{1}{j\omega C}\right| = \left(\frac{250mV_{pp}}{2.07V_{pp}}\right) \cdot 100\Omega = 12.08\Omega$$
$$C = 13.18\mu F$$

Checking in PartSim (not required)





	V1		V2	
	DC	AC	DC	AC
Calculated	5.50 V	20.7 Vpp	5.00 V	250mVpp
Simulated	?	20.67 Vpp	4.95 V	246mVpp

Fourier Transform:

6) Find the Fourier transform for V1 (problem #3) out to the 5th harmonic. (a 40% duty cycle square wave at 1kHz)

$$V_1(t) = \begin{cases} 20V & 0 < t < 400 \mu s \\ -0.7V & 400 \mu s < t < 1ms \end{cases}$$

In Matlab (actually SciLab)

```
t = [0:0.0001:1]';
x = 20*(t < 0.4) - 0.7*(t >= 0.4);
t = t * 2*pi;
c0 = mean(x);
c1 = 2 * mean(x .* exp(-j*t));
c2 = 2*mean(x .* exp(-j*2*t));
c3 = 2 * mean(x .* exp(-j*3*t));
c4 = 2*mean(x .* exp(-j*4*t));
c5 = 2*mean(x .* exp(-j*5*t));
[c0;c1;c2;c3;c4;c5]
Ν
       C(N)
    7.5791721
0
1
    3.8761426 -11.917231i
  -3.1316587 -2.2781891i
2.0899225 -1.5155117i
-0.9645298 -2.9808269i
-0.0001400 -3.540D-16i
2
3
4
5
```

This means

$$x(t) = 7.579 + 3.876 \cos (6280t) + 11.917 \sin (6280t)$$

-3.131 cos(2 · 6280t) + 2.278 sin (2 · 6280t)
+2.089 cos(3 · 6280t) + 1.155 sin (3 · 6280t)
-0.964 cos(4 · 6280t) + 2.980 sin (4 · 6280t)
+0.000 cos(5 · 6280t) + 0.000 sin (5 · 6280t)

Plotting this in MatLab

```
xf = c0;
xf = xf + real(c1)*cos(t) - imag(c1)*sin(t);
xf = xf + real(c2)*cos(2*t) - imag(c2)*sin(2*t);
xf = xf + real(c3)*cos(3*t) - imag(c3)*sin(3*t);
xf = xf + real(c4)*cos(4*t) - imag(c4)*sin(4*t);
xf = xf + real(c5)*cos(5*t) - imag(c5)*sin(5*t);
t0 = t/(2*pi);
plot(t0,x,t0,yf);
xlabel('Time (ms)');
ylabel('Volts');
```



x(t) (blue) and its Fourier approximation taken out to the 5th harmonic (red)

7) Using the results from problem #6, find V2(t) in terms of its Fourier Trasnform out to the 5th harmonic.

Sample Calculations:

n = 3 $\omega = n \cdot 6280 = 18,840 \frac{\text{rad}}{\text{sec}}$ $V_1 = 2.0899 - j1.5155$ $L \rightarrow j\omega L = j188.4\Omega$ $C \rightarrow \frac{1}{j\omega C} = -j10.61\Omega$ $100\Omega \mid\mid -j10.61\Omega = 1.114 - j10.497\Omega$ $V_2 = \left(\frac{(1.114 - j10.497\Omega)}{(1.114 - j10.497\Omega) + (10 + j188.4)}\right) \cdot (2.0899 - j1.5155)$ $V_2 = 0.1370 + j0.0678$

Repeating for all five terms

n	V1	gain	V2
0	7.58	0.9090909	6.8901564
1	3.876 -j11.917	-0.5292 - j0.5715	4.762 - j8.523
2	-3.131 -j2.278	-0.137 -j0.038	0.342 + j0.430
3	2.089 -j1.515	-0.058 - j0.010	-0.137 + j0.068
4	-0.964 -j2.980	-0.032 - j0.004	0.019 + j0.100
5	0.000 -j0.000	-0.021 -j 0.002	0

