ECE 320 - Homework #6

DC to DC Converters, Schmitt Triggers, Fourier Transforms. Due Monday, February 24th

DC to DC Converters

- 1) Determine the voltages (both DC and AC) for V1 and V2.
- 2) Simulate this circuit in PartSim and determine the voltages at V1 and V2 (both DC and AC)



3) Change the duty cycle and C so that

- The DC voltage at V2 = 5.00V
- The ripple at V2 is 100mVpp

Schmitt Triggers

4) A thermistor has the following resistance vs. temperature relationship

$$R = 1000 \cdot \exp\left(\frac{3905}{T} - \frac{3905}{298}\right) \,\Omega$$

where T is the temperature in degrees Kelvin (Celsius + 273). Design a circuit which outputs

- +10V when T > 5C
- 0V when T < 0C
- No change for 0C < T < 5C

5) Design a circuit which turns on and off a DC motor based upon temperature

- The motor turns on when T > 5C
- The motor turns off when T < 0C
- No change for 0C < T < 5C

Assume the motor draws 400mA @ 10V when on.

6) (Lab): Build the circuit you designed for problem #5.

Fourier Transforms

The voltage V1 in problem #1 is a 40% duty cycle square wave

$$V_{1}(t) = V_{1}(t + 1ms)$$
 V1 is periodic in 1ms - i.e. it's a 1kHz square wave
$$V_{1}(t) = \begin{cases} +20V & 0 < t < 400 \mu s \\ -0.7V & 400 \mu s < t < 1000 \mu s \end{cases}$$

7) Determine the first five terms for the Fourier transform for V1(t)

$$V_1(t) = a_0 + a_1 \cos(\omega_0 t) + b_1 \sin(\omega_0 t) + a_2 \cos(2\omega_0 t) + b_2 \sin(2\omega_0 t)$$

- 8) Determine V2(t) at each frequency
 - DC
 - 1kHz
 - 2kHz

9) How do your answers for problem #1 and problem #8 compare?

	Problem #1	Problem #8
V2(DC)		
V2 1kHz term		
V2 2kHz term		

note: The 1kHz term is V1pp for problem #1. This is related to problem #8 as

$$2|a_1 - jb_1| = V_{pp} \qquad \text{at 1kHz}$$

The 2kHz term is V1pp for problem #1 is 0Vpp (we ignored it). This is related to problem #8 as

$$2|a_2 - jb_2| = V_{pp} \qquad \text{at } 2\text{kHz}$$