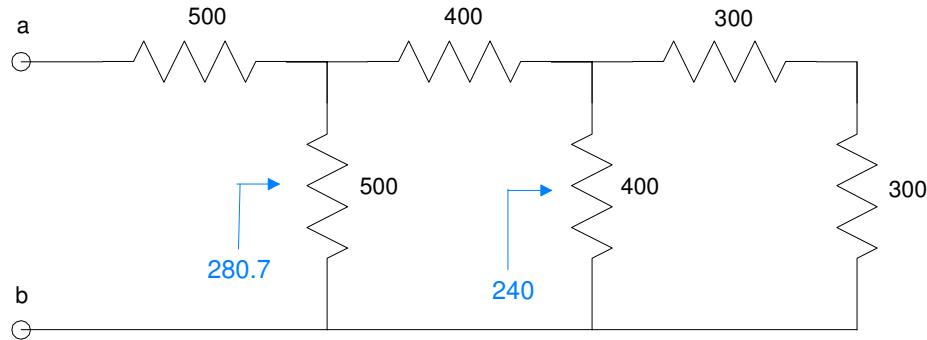


ECE 320 - Quiz #1 - Name _____

EE 206 Review. January 24, 2020

- 1) Determine the resistance R_{ab}

$R_{ab} = 780.702$



$$300 + 300 = 600$$

$$600 \parallel 400 = 240$$


$$240 + 400 = 640$$

$$640 \parallel 500 = 280.702$$

$$280.702 + 500 = 780.702$$

2) Determine the resistance R_{ab} (it will be a complex number)

$$R_{ab} = 324.159 + j468.419$$

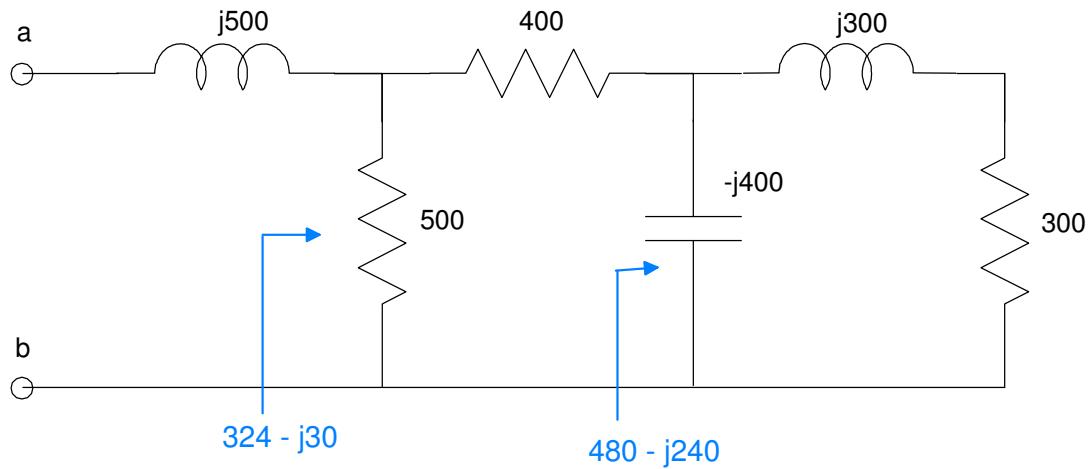

$$300 + j300 = 300 + j300$$


$$(300 + j300) \parallel (-j400) = 480 - j240$$

$$(480 - j240) + (400) = 880 - j240$$

$$(880 - j240) \parallel 500 = 324.159 - j30.581$$


$$(324.159 - j30.581) + (j500) = 324.159 + j468.419$$

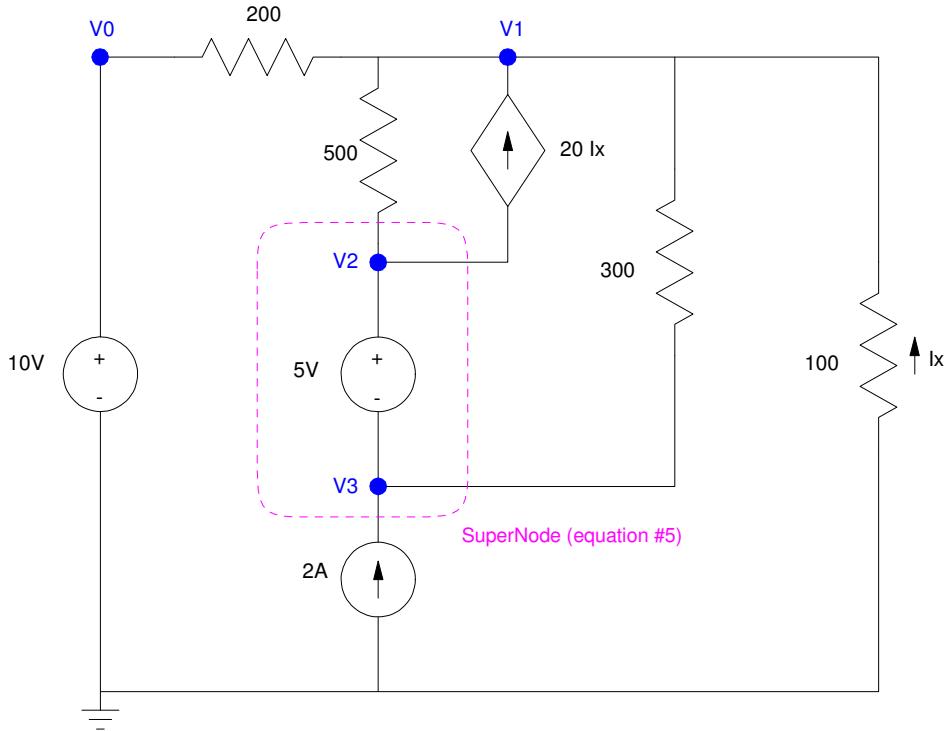3) Give N voltage node equations to solve for the N unknown voltages.



- $V_0 = 10$
- $V_2 - V_3 = 5$
- $I_x = \left(\frac{0 - V_1}{100} \right)$
- $\left(\frac{V_1 - V_0}{200} \right) + \left(\frac{V_1 - V_2}{500} \right) - 20I_x + \left(\frac{V_1 - V_3}{300} \right) + \left(\frac{V_1}{100} \right) = 0$
- $\left(\frac{V_2 - V_1}{500} \right) + 20I_x + \left(\frac{V_3 - V_1}{300} \right) - 2 = 0$

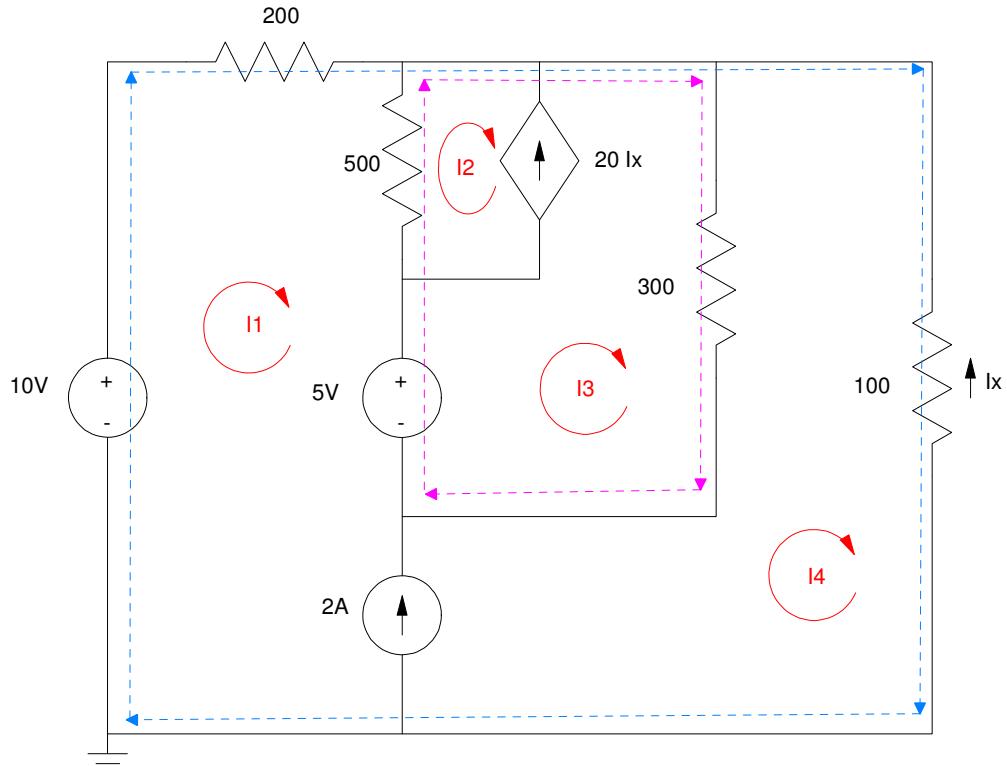
4) Give N current loop equations to solve for the N unknown currents



- $I_x = -I_4$
- $I_4 - I_1 = 2$
- $I_3 - I_2 = 20I_x$
- $-5 + 500(I_2 - I_1) + 300(I_3 - I_4) = 0 \quad \text{pink superloop}$
- $-10 + 200I_1 + 100I_4 = 0 \quad \text{blue superloop}$

5) Signals X and Y are displayed on an oscilloscope. Give the phasor representation for these two voltages

Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase
66.67 hz	8.2Vp 16.4Vpp 5.8Vrms	-72 deg	6.2Vp 12.4Vpp 4.38Vrms	-124 deg

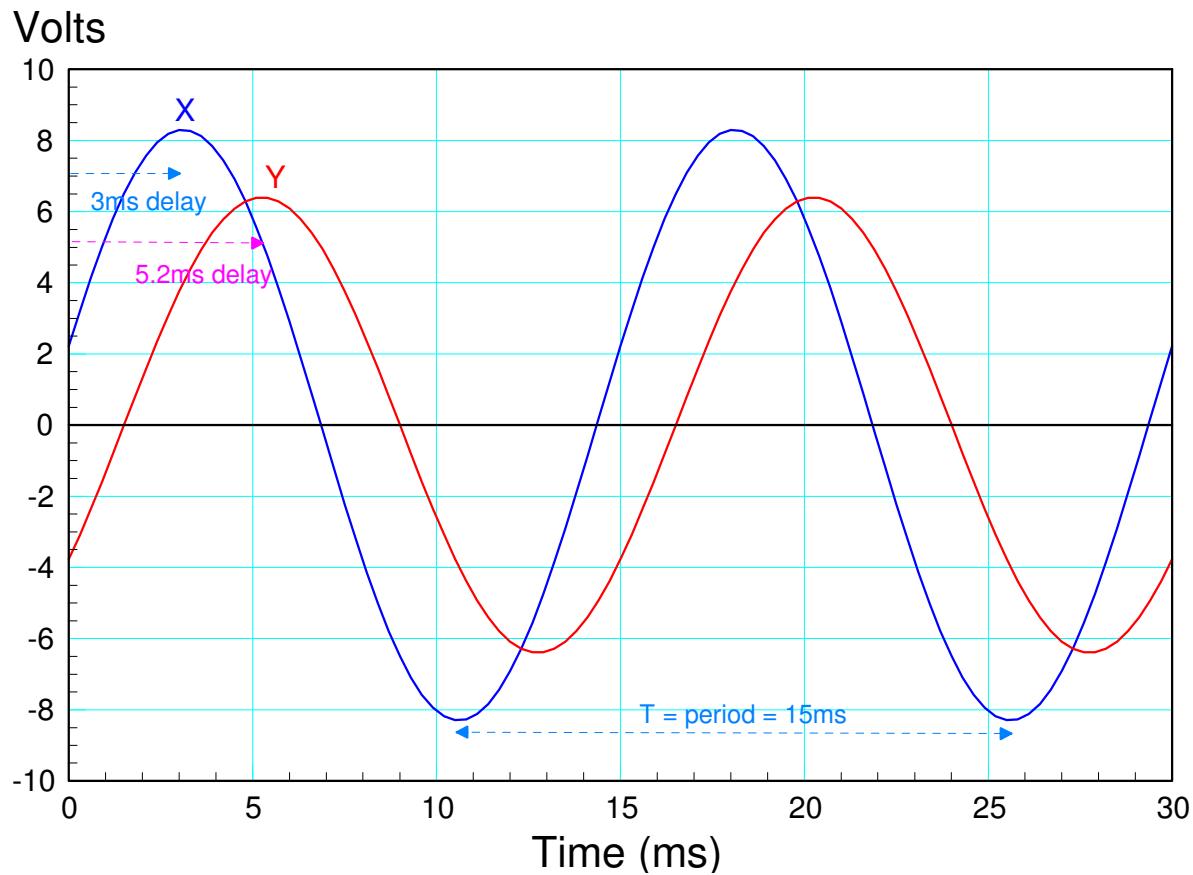

$$f = \frac{1}{\text{period}} = \frac{1}{15\text{ms}} = 66.67\text{Hz}$$


$$\theta_x = -\left(\frac{\text{delay}}{\text{period}}\right) 360^\circ = -\left(\frac{3\text{ms}}{15\text{ms}}\right) 360^\circ = -72^\circ$$

$$\theta_y = -\left(\frac{\text{delay}}{\text{period}}\right) 360^\circ = -\left(\frac{5.2\text{ms}}{15\text{ms}}\right) 360^\circ = -124^\circ$$

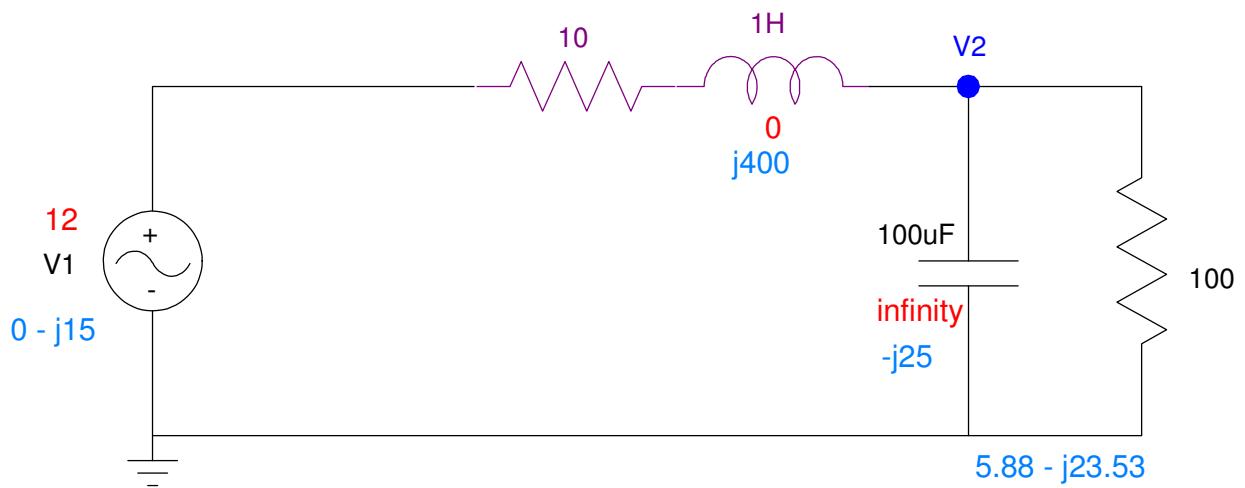6) Determine $V_2(t)$ assuming

$$V_1(t) = 12 + 15 \sin(400t)$$

$$\boxed{V_2(t) = 10.909 - 0.273 \cos(400t) - 0.926 \sin(400t)}$$



DC (red)

$$V_2 = \left(\frac{100}{100+10} \right) 12 = 10.909V$$

AC (blue)

$$100 || (-j25) = 5.88 - j23.53$$

$$V_2 = \left(\frac{(5.88-j23.53)}{(5.88-j23.53)+(10+j400)} \right) (0-j15)$$

$$V_2 = -0.273 + j0.926$$

real = cosine, -imag = sine

Bonus! Bernie Sanders Trivia!!! Which is the oldest (circle one)?

- The oldest edible cheese (Bleeder): 18 years old (Bitto Storico), 40 years (Wisconsin Cheddar)
- **The oldest (drinkable) champaign:** 170 years (found in a ship wreck in the Baltic Sea)
- Godzilla (first movie): Released 1954, making Godzilla 66 years old
- Bernie Sanders: 78 years old