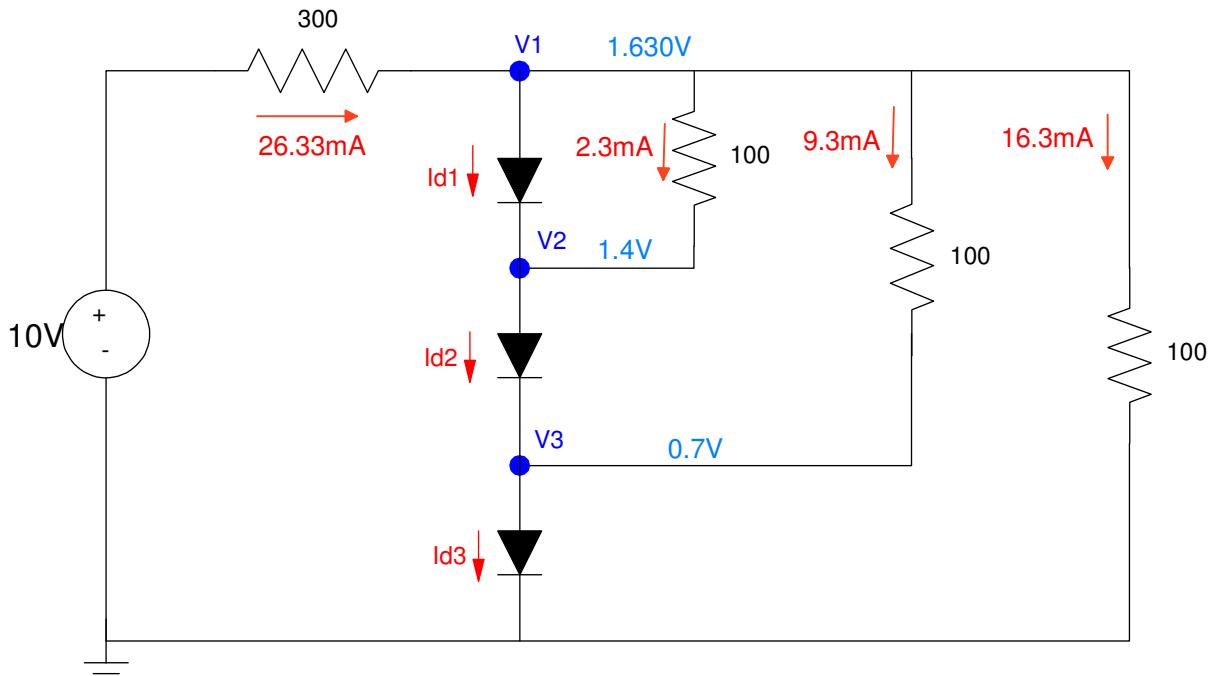


# ECE 320 - Quiz #3 - Name \_\_\_\_\_

Diodes, AC to DC Converters - Spring 2020

- 1) Determine the voltages and currents for the following circuit. Assume ideal silicon diodes ( $V_f = 0.7V$ ).

V1	V2	V3	Id1	Id2	Id3
<b>1.630V</b>	<b>1.40V</b>	<b>0.70V</b>	<b>0mA</b>	<b>2.30mA</b>	<b>11.60mA</b>



If all three diodes are on, you draw too much current for diode1 to be on

Assume diode1 is off

$$\left(\frac{V_1-10}{300}\right) + 0 + \left(\frac{V_1-1.4}{100}\right) + \left(\frac{V_1-0.7}{100}\right) + \left(\frac{V_1}{100}\right) = 0$$

$$V_1 = 1.630V$$


$$I_{d1} = 0 \quad \text{off}$$

$$I_{d2} = \left(\frac{V_1-V_2}{100}\right) = 2.30mA$$

$$I_{d3} = I_{d2} + \left(\frac{V_1-V_3}{100}\right) = 11.6mA$$

2) Determine the voltages and currents for the following circuit. Assume ideal silicon diodes ( $V_f = 0.7V$ ).

V1	V2	V3	Id1	Id2	Id3
<b>1.40V</b>	<b>1.12V</b>	<b>0.70V</b>	<b>0mA</b>	<b>38.1mA</b>	<b>39.5mA</b>

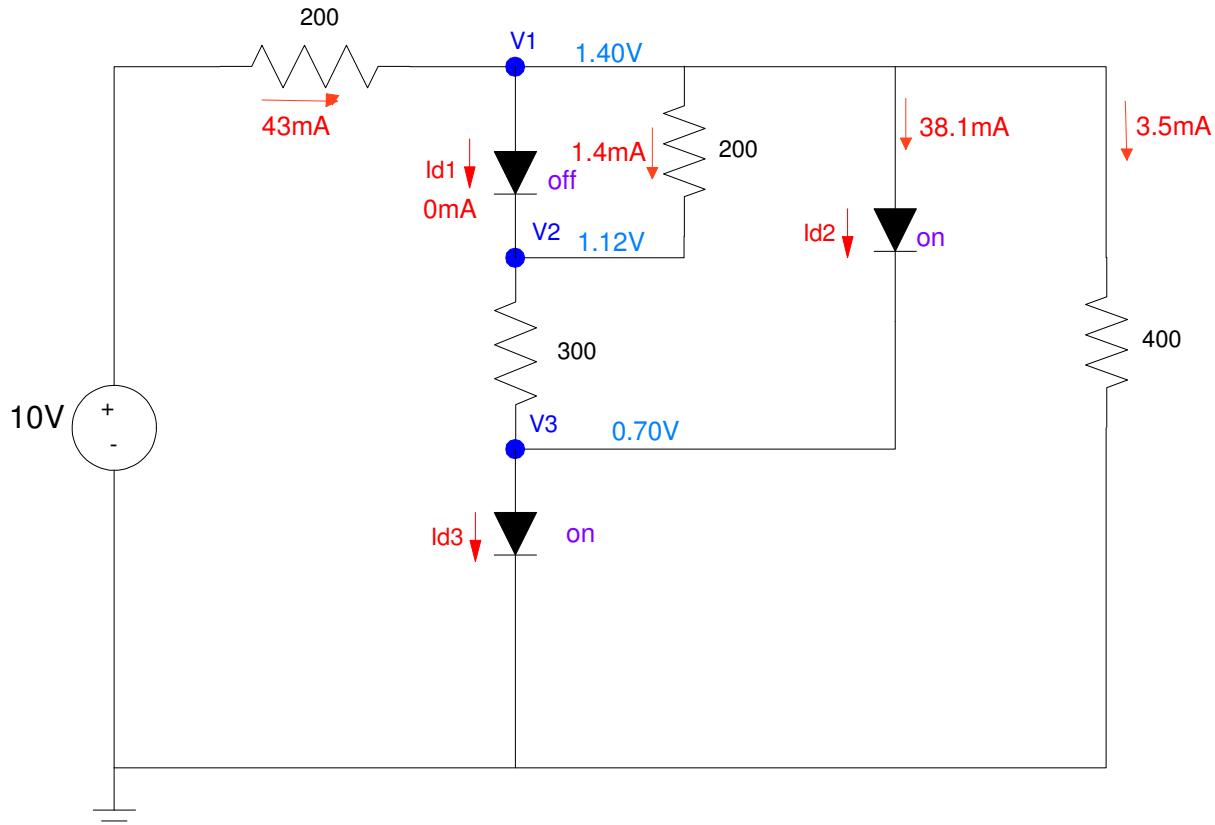

Diode2 and Diode3 are on - making  $V_1 = 1.4V$

$$V_3 = 0.7V$$

$$\left(\frac{10-1.4}{200}\right) = I_{d1} + \left(\frac{V_1-V_3}{500}\right) + I_{d2} + \left(\frac{V_1}{400}\right)$$

$$I_{d2} = 38.1mA$$

$$I_{d3} = I_{d2} + \left(\frac{V_1-V_3}{500}\right) = 39.5mA$$

$$V_2 = V_3 + \left(\frac{V_1-V_3}{500}\right) 300 = 1.12V$$

3) Determine the resistances so that the following RGB LED outputs baby blue:

- Red = 7800 mcd
- Green = 9570 mcd
- Blue = 9410 mcd


The specifications for the RGB LED are:

color	Vf	mcd @ 20mA
red	2.0V	10,000
green	3.0V	10,000
blue	3.2V	10,000

Rr	Rg	Rb
<b>512.8</b>	<b>365.7</b>	<b>361.3</b>

$$I_r = \left( \frac{7,800 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 15.6 \text{ mA}$$

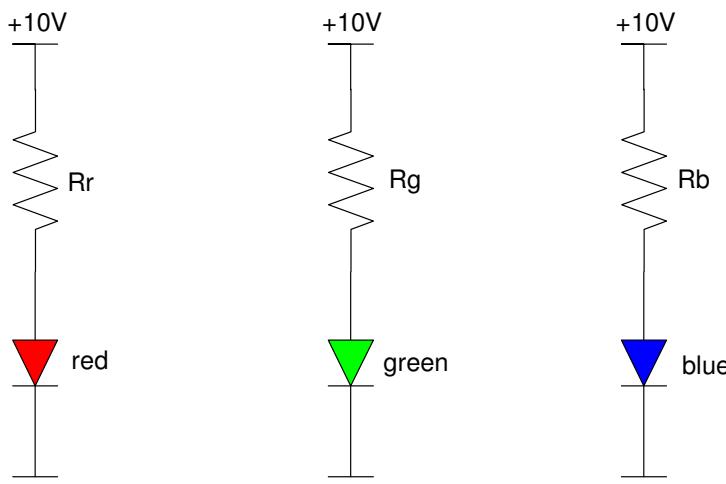
$$R_r = \left( \frac{10V - 2V}{15.6 \text{ mA}} \right) = 512.8 \Omega$$



4) Determine the voltage V1 and the currents through the red, green, and blue LED

color	Vf	mcd @ 20mA
red	2.0V	10,000
green	3.0V	10,000
blue	3.2V	10,000

V1	Ir	Ig	Ib
<b>2.0V</b>	<b>80mA</b>	<b>0mA</b>	<b>0mA</b>
<b>10.0V</b>	<b>0mA</b>	<b>0mA</b>	<b>0mA</b>

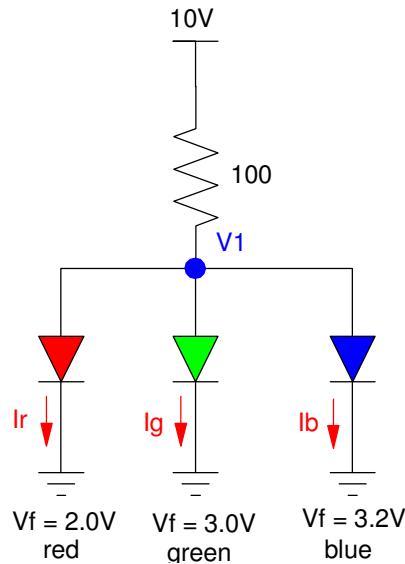

The red LED sets the voltage to 2.00V

The green and blue LED turn off.

The current is then

$$I_r = \left( \frac{10V - 2V}{100\Omega} \right) = 80mA$$

This then burns out the red LED. All the current goes to the green LED (lowest  $V_f$ )


This then burns out the green LED. All the current goes to the blue LED

This then burns out.

The net result is three dead LEDs, no current, and  $V_1 = 10V$ .

5) Determine the voltages V1 and V2 (both DC and AC)

V1		V2	
DC (mean(V1))	AC (V1pp)	DC (mean(V2))	AC (V2pp)
<b>16.83V</b>	<b>4.949Vpp</b>	<b>12.94V</b>	<b>0.683Vpp</b>

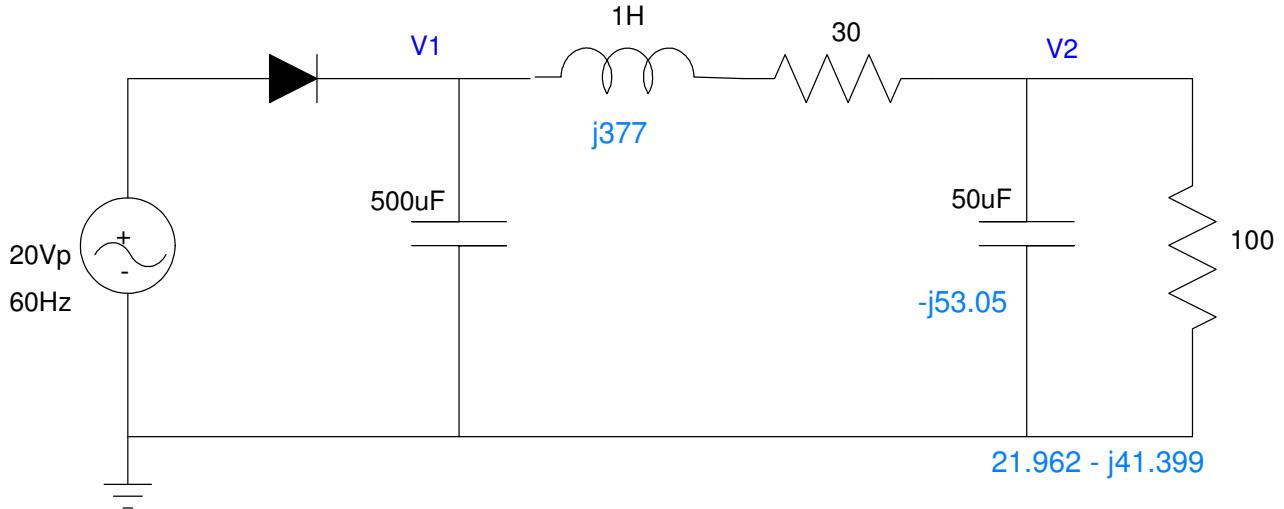

$$\text{DC: } V1(\text{peak}) = 19.3V$$

$$I \approx \left( \frac{19.3V}{130\Omega} \right) = 148.5mA$$

$$I = C \frac{dV}{dt}$$

$$148.5mA = 500\mu F \cdot \frac{dV}{1/60s}$$

$$dV = 4.949V_{pp} \quad (\text{AC})$$

$$V_1 = 19.3V - \frac{1}{2} \cdot 4.949V = 16.83V \quad (\text{DC})$$


$$V_2 = \left( \frac{100}{100+30} \right) 16.83V = 12.94V \quad (\text{DC})$$

$$V_2 = \left( \frac{(21.962-j41.399)}{(21.962-j41.399)+(30+j377)} \right) 4.949V_{pp} = 0.683V_{pp} \quad (\text{AC} - \text{just use the magnitude})$$

6) Determine R, C1, and C2 so that

- The DC current through R is 200mA
- The ripple at V1 is 3Vpp and
- The ripple at V2 = 0.2Vpp

C1	C2	R
<b>1111μF</b>	<b>102μF</b>	<b>59 Ohms</b>

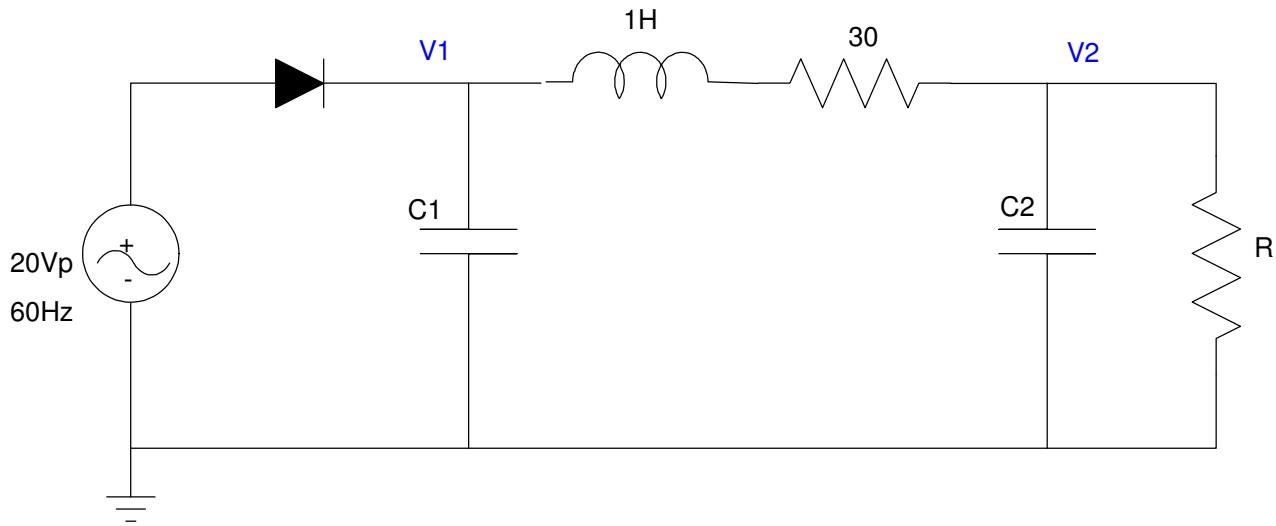

$$V_1(DC) = 19.3V - \frac{1}{2} \cdot 3V_{pp} = 17.8V$$

$$I = 200mA = \left( \frac{17.8V}{R+30} \right)$$

$$R = 59\Omega$$

$$I = C_1 \frac{dV}{dt}$$

$$200mA = C_1 \cdot \frac{3V_{pp}}{1/60s}$$

$$C_1 = 1111\mu F$$

Assume C2 = 0

$$V_2 = \left( \frac{1000}{1000+30+j377} \right) 3V_{pp} = 0.4569V_{pp}$$

To make the ripple 0.200Vpp

$$\left| \frac{1}{j\omega C_2} \right| = \left( \frac{0.2V}{0.4569V} \right) \cdot 59\Omega = 25\Omega$$

$$C_2 = 102\mu F$$

Bernie Sanders Bonus! Bernie Sanders and Quicksilver (of the X-men) leave Iowa to go to New Hampshire. Bernie flies an SR-71 (the world's fastest airplane) at 6 times the speed of sound. Quicksilver runs. Who gets to New Hampshire first?

answer: Quicksilver (approx 1 million mph)

SR71: Mach-6 (3600 mph)