

ECE 320 - Quiz #5 - Name _____


Transistors, H-Bridges, Schmitt Triggers, Buck Converters. February 27, 2020

Transistor Switch

Determine R_b and R_c so that a function generator can turn on and off a 5W LED at 1.00A. Assume

- LED: $V_f = 3.0V @ 1.67A$
- Transistor: $V_{be} = 1.4V$, $V_{ce} = 0.9V$, $\beta=1000$ (TIP112)
- Input: 0V / 5V binary, capable of up to 20mA

| Min value for R_b | Max value of R_b | R_c |
|---------------------|--------------------|-----------------|
| 180 Ohms | 3600 Ohms | 6.1 Ohms |

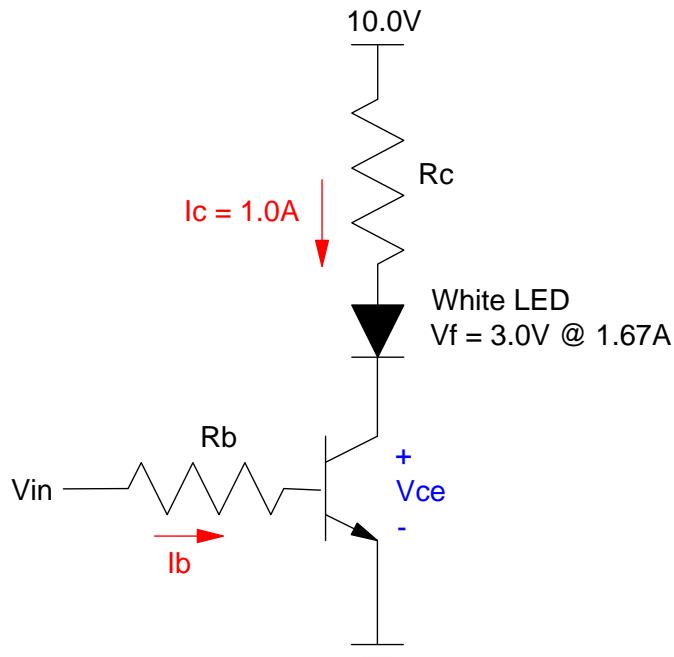

R_c :

$$R_c = \left(\frac{10V - 3V - 0.9V}{1A} \right) = 6.1\Omega$$

R_b : $1mA < I_b < 20mA$

$$\beta I_b > I_c = 1A$$

$$I_b > 1mA$$

$$R_b = \left(\frac{5V - 1.4V}{1mA} \right) = 3600\Omega \quad \text{upper limit}$$


$$R_b = \left(\frac{5V - 1.4V}{20mA} \right) = 180\Omega \quad \text{lower limit}$$

H-Bridge (analysis)

2) Determine the voltages and currents for the following H-bridge. Assume TIP transistors:

- $|V_{be}| = 1.4V$
- $|V_{ce}| = 0.9V$ when saturated
- $\beta = 1000$

| I1 | I2 | I3 | V1 | V2 |
|--------------|--------------|--------------|--------------|---------------|
| 86 uA | 43 mA | 43 uA | 9.1 V | 8.24 V |

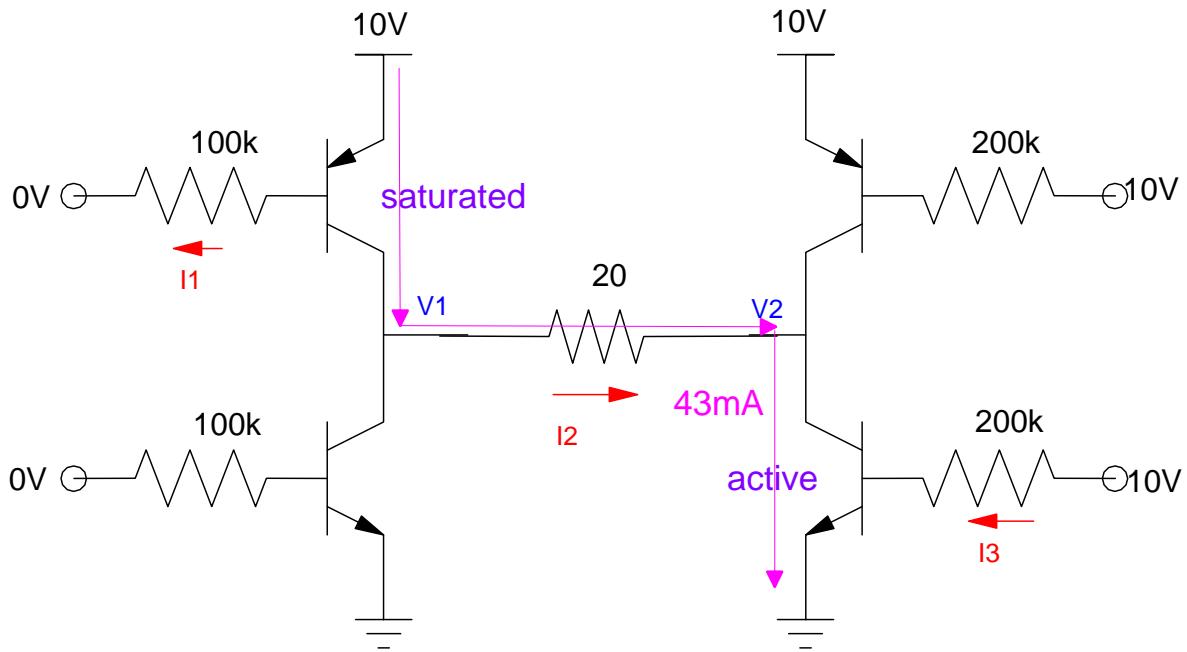

$$I_1 = \left(\frac{10-1.4}{100k} \right) = 86\mu A \quad \left(\frac{10V-0.9V-0.9V}{20} \right) = 410mA \quad I_3 = \left(\frac{10-1.4}{200k} \right) = 43\mu A$$

$$\beta I_1 = 86mA$$

$$\beta I_3 = 43mA$$

smallest current wins (43mA)

This means T1 is saturated ($V_{ce} = 0.9V$) and T4 is active ($0.9V < V_{ce} < 9.1V$)

$$V_1 = 10 - 0.9 = 9.1V$$


$$V_2 = V_1 - 43mA \cdot 20\Omega$$

H-Bridge (design)

3) Specify R1 and R2 so that the following H-bridge has transistors which are either off or saturated. For these values of R1 and R2, determine the currents. Assume

- $|V_{be}| = 1.4V$
- $|V_{ce}| = 0.9V$ when saturated
- $\beta = 1000$
- I_1 and I_3 can be 20mA (or less)

| R1 | R2 | I1 | I2 | I3 |
|-------------|-------------|------------|--------------|------------|
| 8.6k | 8.6k | 1mA | 410mA | 1mA |

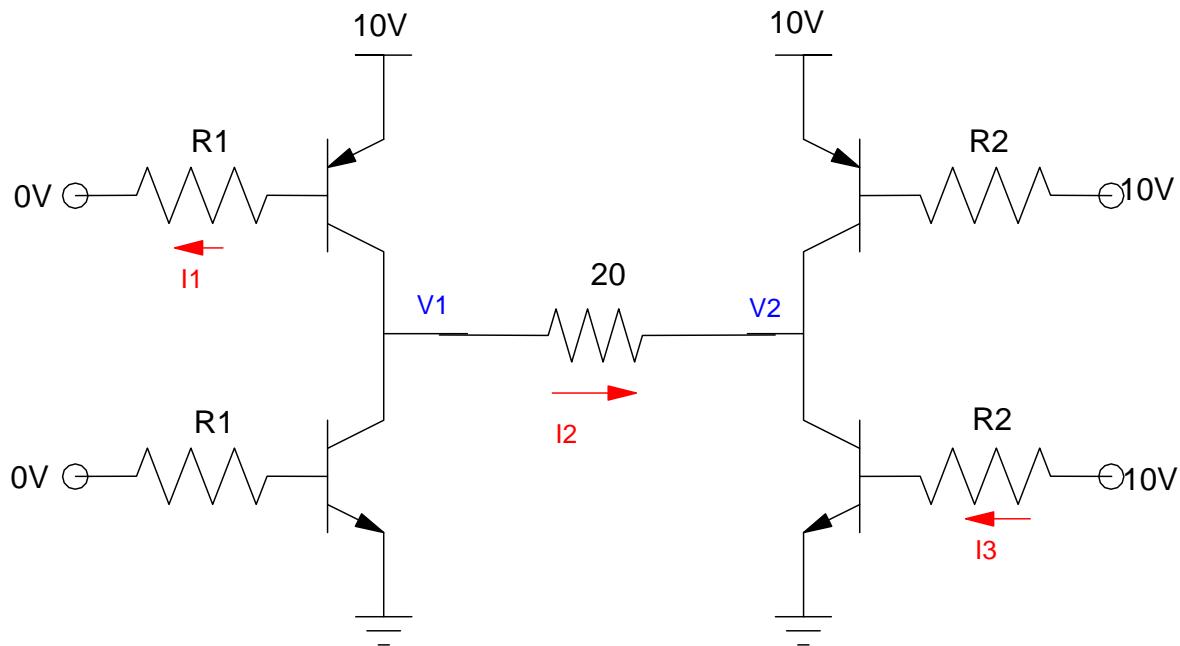

Ideally, all transistors are either off or saturated

$$I_2 = \left(\frac{10 - 0.9 - 0.9}{20} \right) = 410mA$$

To saturate the transistors

$$\beta I_b > I_c$$

$$I_b > 410\mu A$$

Pick a current in the range of

$$410\mu A < I_b < 20mA$$

Let $I_b = 1mA$


$$R_1 = \left(\frac{10V - 1.4V}{1mA} \right) = 8.6k\Omega$$

ditto for R2

Schmitt Trigger (design)

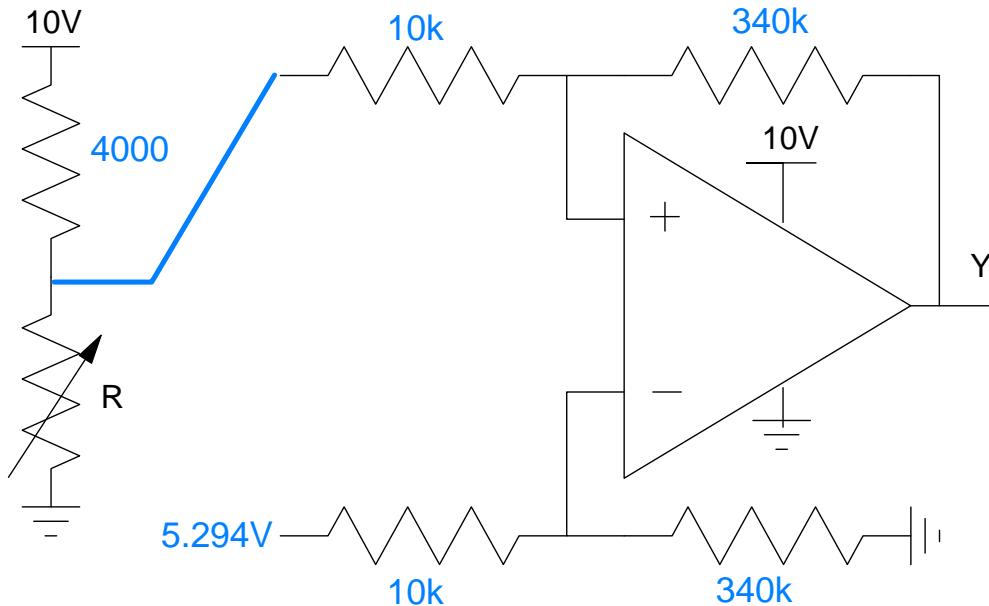4) Design a Schmitt Trigger so that the output (Y) is

- Y = 0V when R < 4000 Ohms
- Y = 10V when R > 4500 Ohms
- No change (0V or 10V) when 4000 < R < 4500 Ohms



When R = 4000 (Y = 0V)

$$X = \left(\frac{4000}{4000+4000} \right) 10V = 5.00V$$

When R = 4500 (Y = 10V)

$$X = \left(\frac{4500}{4500+4000} \right) 10V = 5.294V$$

When X goes up, Y goes up. Connect to the + input

When Y = 0, you switch at X = 5.294V. Make the offset 5.294V

The gain needed is


$$gain = \left(\frac{\text{change in output}}{\text{change in input}} \right) = \left(\frac{10V-0V}{5.294V-5.000V} \right) = 34.0$$

Make the resistor ratio 34.0 : 1

Buck Converter (analysis)

5) Determine the voltages (V1 and V2, both DC and AC) for the following Buck converter (DC to DC)

| V1 | | V2 | |
|----------------|-----------------|----------------|------------------|
| V1(DC) | V1(AC) | V2(DC) | V2(AC) |
| 15.86 V | 20.7 Vpp | 13.22 V | 2.131 Vpp |

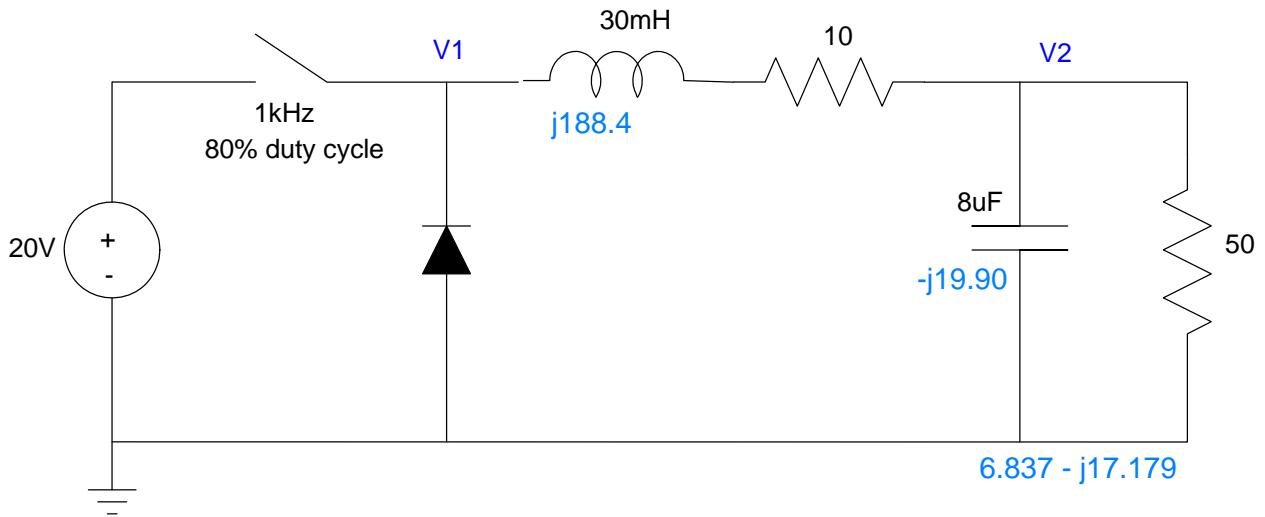

DC:

$$V_1 = (0.8)(20V) + (0.2)(-0.7V) = 15.86V$$

$$V_2 = \left(\frac{50}{50+10} \right) V_1 = 13.22V$$

AC:

$$V_1 \approx 20.7V_{pp}$$

$$V_2 = \left(\frac{(6.387-j17.179)}{(6.387-j17.179)+(10+j188.4)} \right) \cdot 20.7V_{pp}$$


$$V_2 = 2.131V_{pp}$$

take the magnitude & ignore the phase.

Buck Converter (design)

6) Design a Buck converter so that the output is 5.00V DC with a ripple of 1Vpp

| DC Voltage at V1 | Duty Cycle (% on) | C |
|------------------|-------------------|--------------------------------|
| 6.00 V | 32.4 % | 17.05 μF |

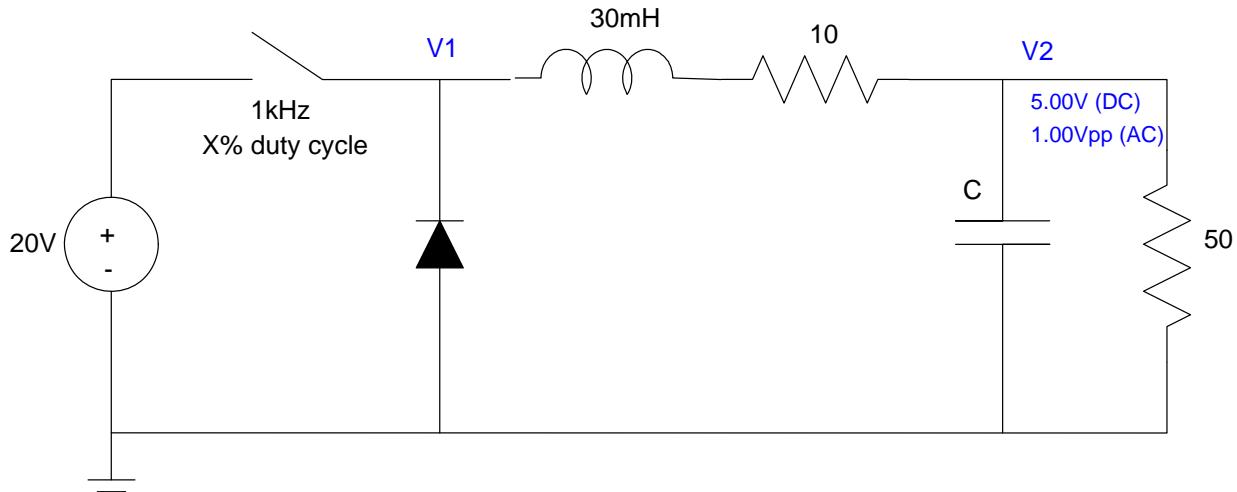

If $V_2 = 5.00V$

$$V_1 = \left(\frac{50+10}{50} \right) V_2 = 6.00V$$

The duty cycle is

$$\alpha \cdot 20V + (1 - \alpha)(-0.7V) = 6.00V$$

$$\alpha = \left(\frac{6.7V}{20.7V} \right) = 32.4\%$$

From problem #5, if $C = 8\mu F$, the ripple at V_2 is 2.131Vpp

To make the ripple 1.000Vpp

$$C_2 = \left(\frac{2.131}{1.000} \right) 8\mu F = 17.05\mu F$$

Bernie Sanders Bonus!!! This is more

- The number of votes Bernie Sanders got in the Nevada primary (6,788 votes), or
- The number of voles you'll have if you start with one breeding pair and wait one year?

Bernie Votes: 6,788

Voiles: 6,338