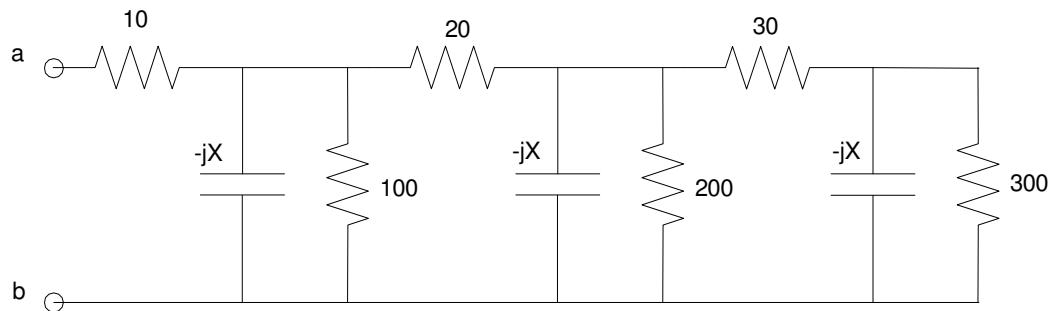


ECE 320 - Homework #1

EE 206 Review, Phasors. Due Wednesday, January 22nd

Resistors in series and parallel

- 1) Assume $X = \infty$ (DC analysis). Determine the resistance R_{ab}



Goint right to left...

$$300 + 30 = 330$$

$$330 \parallel 200 = 124.528$$

$$124.528 + 20 = 144.528$$

$$144.528 \parallel 100 = 59.105$$

$$59.105 + 10 = 69.105$$

answer:

69.205 Ohms

- 2) Assume $-jX = -j100$. Determine the resistance R_{ab} (it will be a complex number)

Goint right to left

$$300 \parallel -j100 = 30 - j90$$

$$(30 - j90) + 30 = 60 - j90$$

$$(60 - j90) \parallel 200 \parallel -j100 = 24.370 - j42.571$$

$$(24.370 - j42.571) + 20 = 44.370 - j42.571$$

$$(44.370 - j42.571) \parallel 100 \parallel -j100 = 23.513 - j22.999$$

$$(23.513 - j22.999) + 10 = 33.513 - j22.999$$


answer:

33.513 - j22.999 Ohms

Voltage Nodes & Current Loops

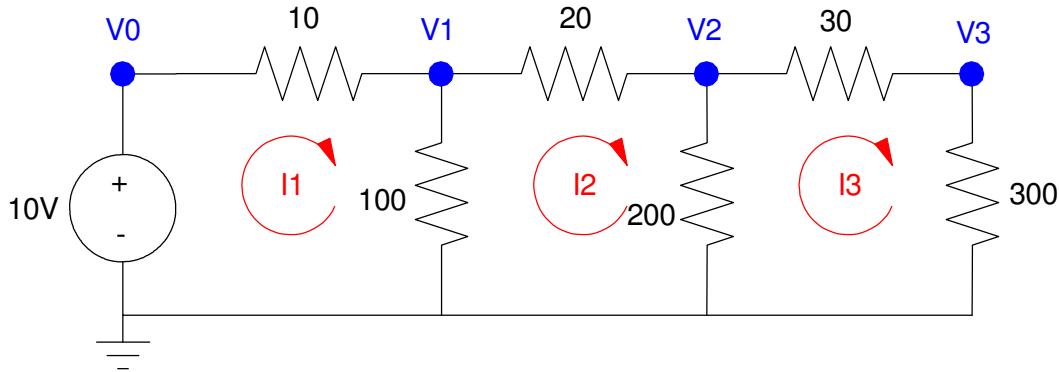3) (Voltage Nodes): For the following circuit

Write the voltage node equations (sum the current to zero at each node)



$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{V_1 - V_2}{20}\right) = 0$$

$$\left(\frac{V_2 - V_1}{20}\right) + \left(\frac{V_2}{200}\right) + \left(\frac{V_2 - V_3}{30}\right) = 0$$

$$\left(\frac{V_3 - V_2}{30}\right) + \left(\frac{V_3}{300}\right) = 0$$

Group terms

$$\left(\frac{1}{10} + \frac{1}{100} + \frac{1}{20}\right)V_1 - \left(\frac{1}{20}\right)V_2 = \left(\frac{1}{10}\right)V_0$$

$$\left(\frac{-1}{20}\right)V_1 + \left(\frac{1}{20} + \frac{1}{200} + \frac{1}{30}\right)V_2 + \left(\frac{-1}{30}\right)V_3 = 0$$

$$\left(\frac{-1}{30}\right)V_2 + \left(\frac{1}{30} + \frac{1}{300}\right)V_3 = 0$$


Place in matrix form

$$\begin{bmatrix} \left(\frac{1}{10} + \frac{1}{100} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) & 0 \\ \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{200} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) \\ 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{300}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \left(\frac{1}{10}\right)V_0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab (or similar program)


```
A = [1/10+1/100+1/20, -1/20, 0 ; -1/20, 1/20+1/200+1/30, -1/30 ; 0,-1/30,1/30+1/300]  
0.16 - 0.05 0.  
- 0.05 0.0883333 - 0.0333333  
0. - 0.0333333 0.0366667  
  
B = [1/10;0;0]  
0.1  
0.  
0.  
  
V = inv(A) *B*10  
8.5529254  
7.3693613  
6.6994194
```

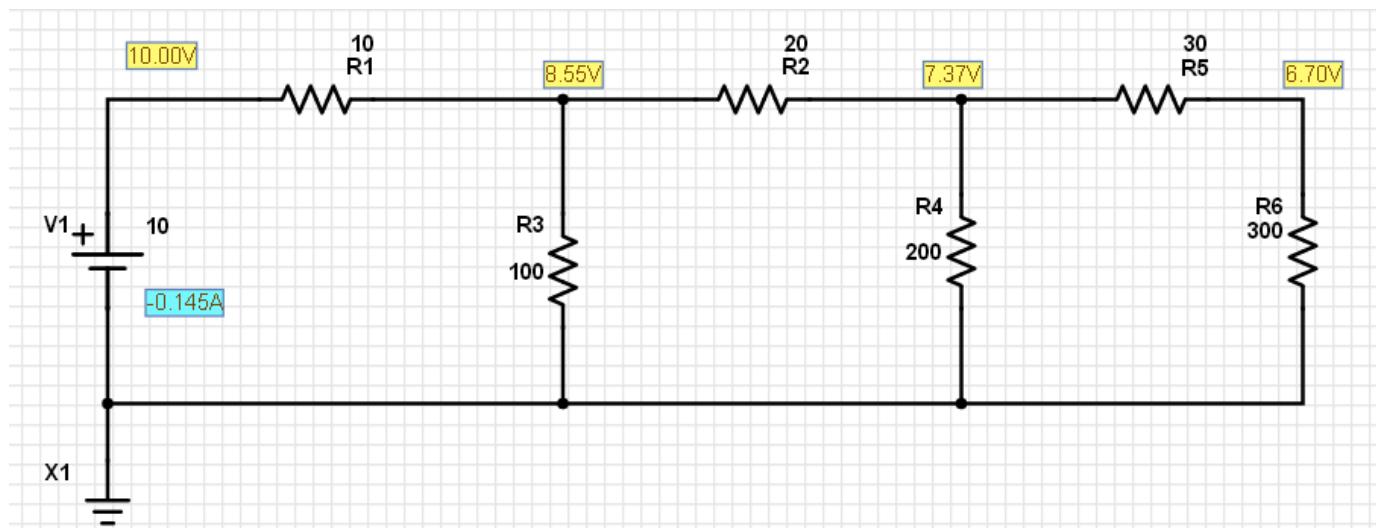Check your answers in PartSim (or similar circuit simulator)



The voltages match...

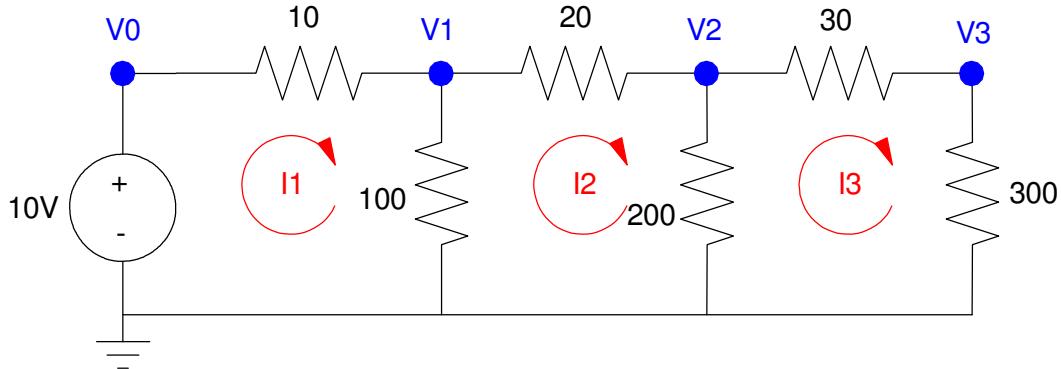4) (Current Loops) For the following circuit



Write the current loop equations (the sum of the voltages around any closed path must sum to zero)

$$-100 + 10I_1 + 100(I_1 - I_2) = 0$$

$$100(I_2 - I_1) + 20I_2 + 200(I_2 - I_3) = 0$$

$$200(I_2 - I_3) + 30I_3 + 300I_3 = 0$$

Group terms

$$110I_1 - 100I_2 = 100$$

$$-100I_1 + 320I_2 - 200I_3 = 0$$

$$-200I_2 + 530I_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 110 & -100 & 0 \\ -100 & 320 & -200 \\ 0 & -200 & 530 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab (or similar program)

$$A = [110, -100, 0 ; -100, 320, -200 ; 0, -200, 530]$$

$$\begin{array}{ccc} 110. & -100. & 0. \\ -100. & 320. & -200. \\ 0. & -200. & 530. \end{array}$$


$$B = [10 ; 0 ; 0]$$

$$\begin{array}{c} 10. \\ 0. \\ 0. \end{array}$$

$I = \text{inv}(A) * B$

0.1447075
0.0591782
0.0223314

This matches PartSim's answer

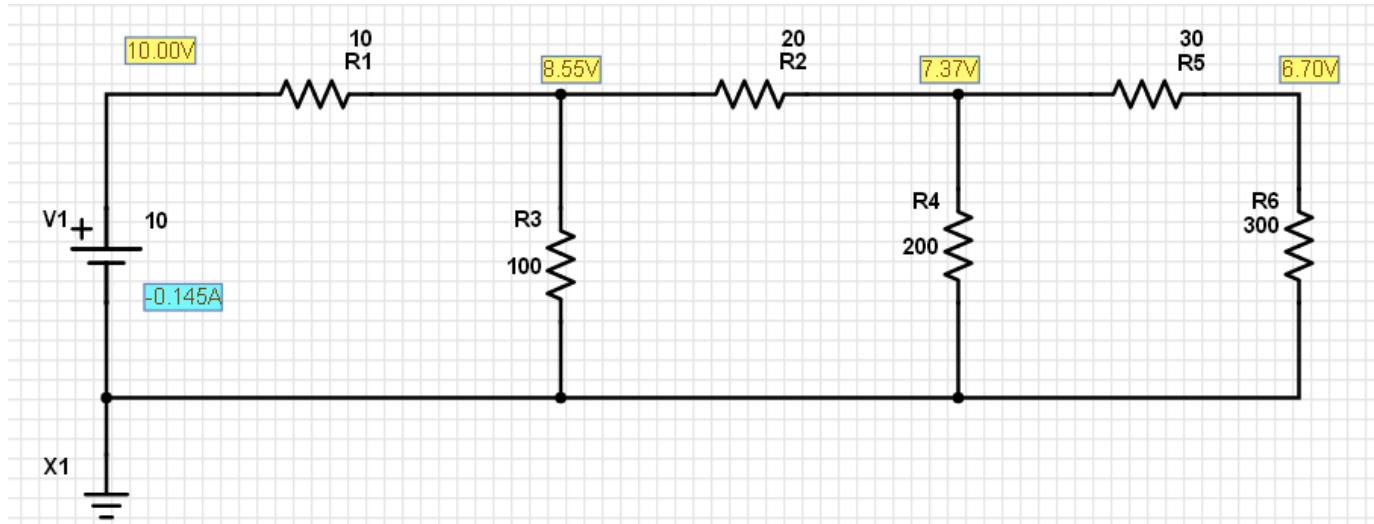


$$I_1 = \left(\frac{1-8.55}{10} \right) = 0.145 \quad \text{vs. } 0.1447074$$

$$I_2 = \left(\frac{8.55-7.37}{20} \right) = 0.059 \quad \text{vs. } 0.0591782$$

$$I_3 = \left(\frac{6.70}{300} \right) = 0.022 \quad \text{vs. } 0.0223314$$

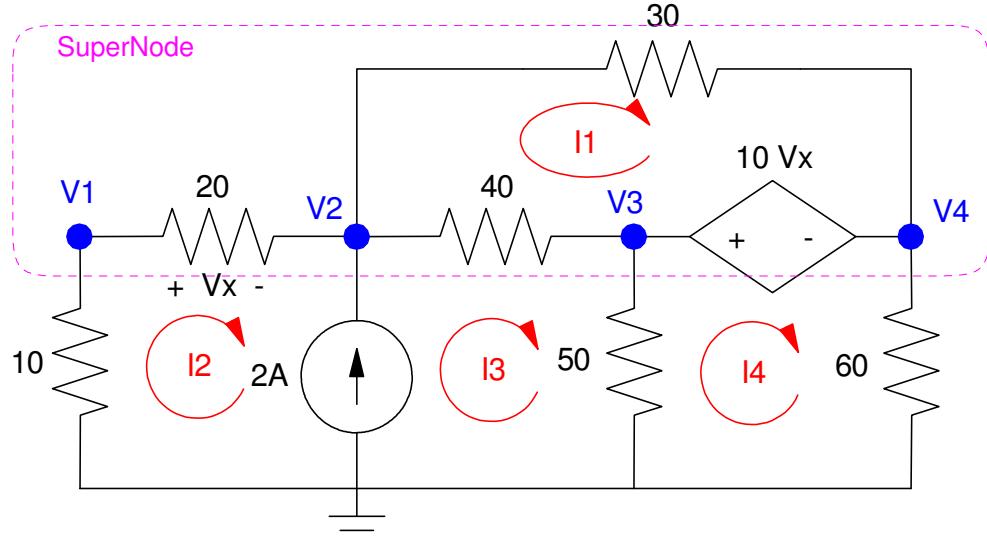5) (Voltage Nodes): For the following circuit



Write the voltage node equations

$$V_x = V_1 - V_2$$

$$10V_x = V_3 - V_4$$

$$\left(\frac{V_1}{10}\right) + \left(\frac{V_1 - V_2}{20}\right) = 0$$

$$\left(\frac{V_2 - V_1}{20}\right) + \left(\frac{V_2 - V_4}{30}\right) + \left(\frac{V_2 - V_3}{40}\right) - 2 = 0$$

Supernode:

$$\left(\frac{V_1}{10}\right) - 2 + \left(\frac{V_3}{50}\right) + \left(\frac{V_4}{60}\right) = 0$$

Group terms

$$V_1 - V_2 - V_x = 0$$

$$V_3 - V_4 - 10V_x = 0$$

$$\left(\frac{1}{10} + \frac{1}{20}\right)V_1 - \left(\frac{1}{20}\right)V_2 = 0$$

$$-\left(\frac{1}{20}\right)V_1 + \left(\frac{1}{20} + \frac{1}{30} + \frac{1}{40}\right)V_2 - \left(\frac{1}{40}\right)V_3 - \left(\frac{1}{30}\right)V_4 = 2$$

$$\left(\frac{1}{10}\right)V_1 + \left(\frac{1}{50}\right)V_3 + \left(\frac{1}{60}\right)V_4 = 2$$

Place in matrix form

$$\left[\begin{array}{ccccc} 1 & -1 & 0 & 0 & -1 \\ 0 & 0 & 1 & -1 & -10 \\ \left(\frac{1}{10} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) & 0 & 0 & 0 \\ \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{30} + \frac{1}{40}\right) & \left(\frac{-1}{40}\right) & \left(\frac{-1}{30}\right) & 0 \\ \left(\frac{1}{10}\right) & 0 & \left(\frac{1}{50}\right) & \left(\frac{1}{60}\right) & 0 \end{array} \right] \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 2 \\ 2 \end{bmatrix}$$

Solve using Matlab (or similar program)

```
A = [1,-1,0,0,-1 ; 0,0,1,-1,-10 ; 1/10+1/20,-1/20,0,0,0]
A = [A ; -1/20,1/20+1/30+1/40,-1/40,-1/30,0];
A = [A ; 1/10,0,1/50,1/60,0]
```

```
1.      - 1.          0.          0.          - 1.
0.          0.          1.          - 1.          - 10.
0.15      - 0.05       0.          0.          0.
- 0.05      0.10833333  - 0.025      - 0.03333333  0.
0.1          0.          0.02        0.0166667   0.
```


```
B = [0;0;0;2;2]
```

```
0.
0.
0.
2.
2.
```

```
V = inv(A) *B
```

```
V1    17.40458
V2    52.21374
V3   -151.14504
V4    196.94656
Vx   -34.80916
```

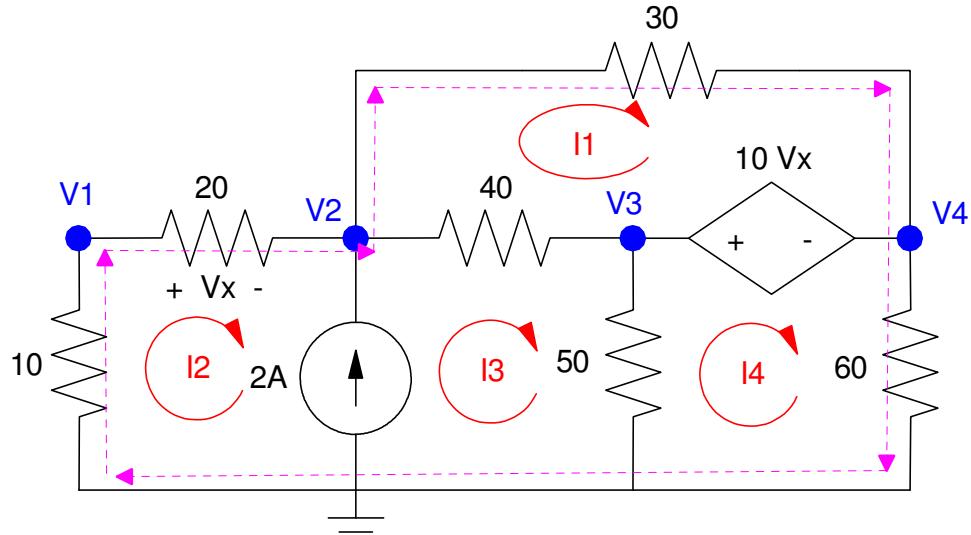6) (Current Loops) For the following circuit



a) Write the current loop equations

$$V_x = 20I_2$$

$$I_3 - I_2 = 2$$

$$30I_1 - 10V_x + 40(I_1 - I_3) = 0$$

$$50(I_4 - I_3) + 10V_x + 60I_4 = 0$$

SuperLoop

$$10I_2 + 20I_2 + 30I_1 + 60I_4 = 0$$

Group terms

$$20I_2 - V_x = 0$$

$$I_3 - I_2 = 2$$

$$70I_1 - 40I_3 - 10V_x = 0$$

$$-50I_3 + 110I_4 + 10V_x = 0$$

$$30I_1 + 30I_2 + 60I_4 = 0$$

Place in matrix form

$$\begin{bmatrix} 0 & 20 & 0 & 0 & -1 \\ 0 & -1 & 1 & 0 & 0 \\ 70 & 0 & -40 & 0 & -10 \\ 0 & 0 & -50 & 110 & 10 \\ 30 & 30 & 0 & 60 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

b) Solve using Matlab (or similar program)

```
A = [0,20,0,0,-1 ; 0,-1,1,0,0 ; 70,0,-40,0,-10 ; 0,0,-50,110,10 ; 30,30,0,60,0]
```

```
0.      20.      0.      0.      - 1.  
0.      - 1.      1.      0.      0.  
70.      0.      - 40.      0.      - 10.  
0.      0.      - 50.      110.      10.  
30.      30.      0.      60.      0.
```

```
B = [0;2;0;0;0]
```

```
0.  
2.  
0.  
0.  
0.
```


```
I = inv(A)*B
```

```
I1   -4.8244275  
I2   -1.740458  
I3   0.2595420  
I4   3.2824427  
Vx  -34.80916
```

Vx matches the previous solution. It's probably correct.

7) Assume Vin contains a DC and 500 rad/sec (79.57Hz) signal:

$$V_{in} = 10 + 3 \sin(500t)$$

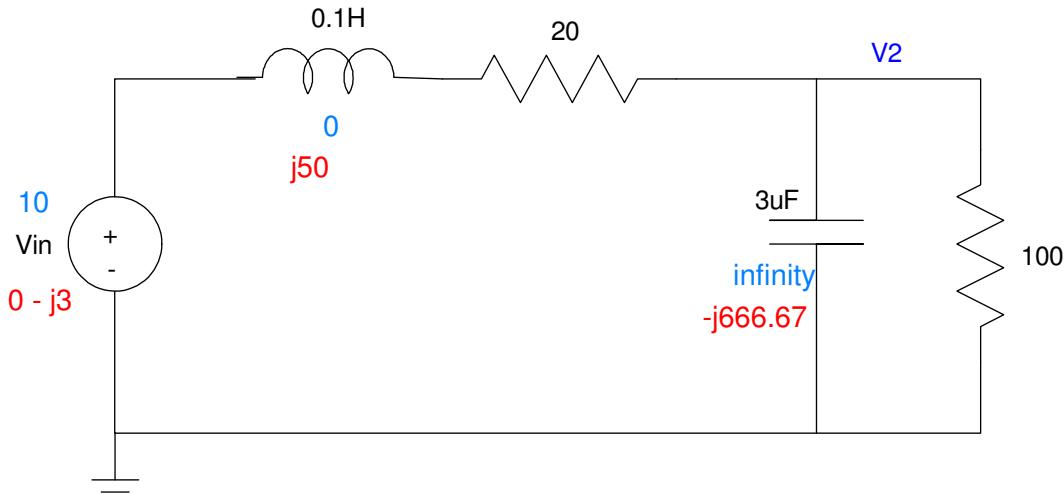

a) Determine the impedances of the inductor, capacitor, and resistor at DC and 1000 rad/sec shown in blue (DC) and red (AC)

b) Determine the voltage, V_2 , using phasor analysis

DC (blue)

$$V_{in} = 10 + j0$$

$$V_2 = \left(\frac{100}{100+20}\right)(10+j0)$$

$$V_2 = 8.333$$

$$v_2(t) = 8.333$$

AC (red)

$$V_{in} = 0 - j3$$

$$100 \parallel (-j666.67) = 97.80 - j14.67$$

$$V_2 = \left(\frac{97.80 - j14.67}{(97.80 - j14.67) + (20 + j50)}\right)(0 - j3)$$


$$V_2 = 1.028 - j2.182$$

$$v_2(t) = 1.028 \cos(500t) + 2.182 \sin(500t)$$


The total answer is then

$$v_2(t) = 8.333 + 1.028 \cos(500t) + 2.182 \sin(500t)$$

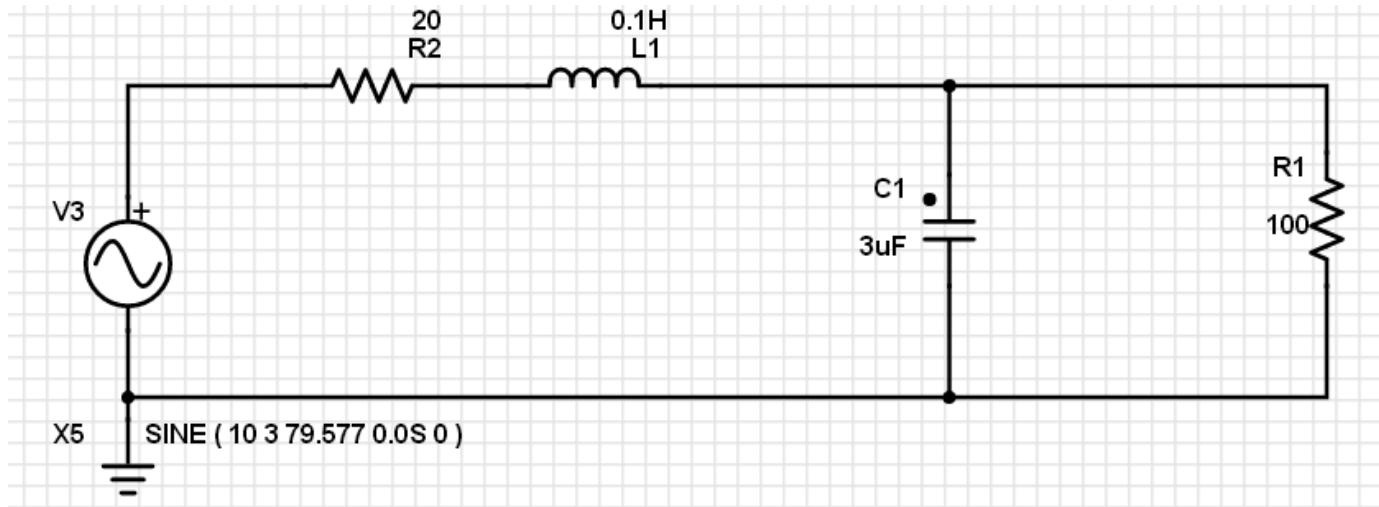c) Check your answer using PartSim (or similar program)



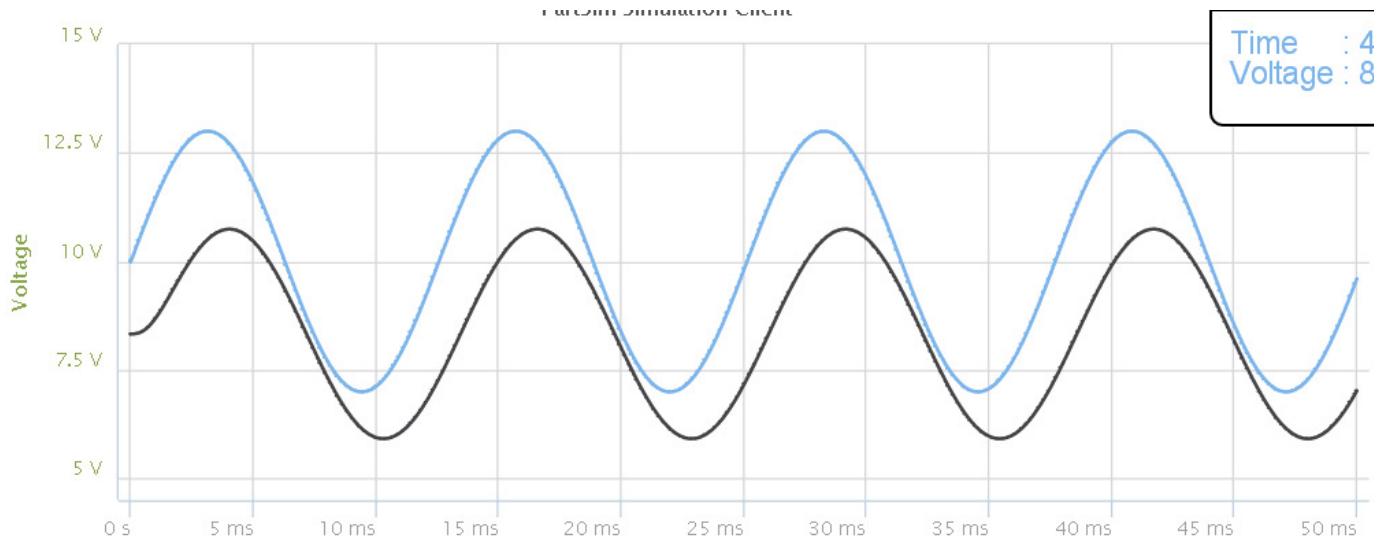PartSim circuit. Note that 500 rad/sec is 79.577 Hz



From the simulation

$$\max(V_2) = 10.742V$$

$$\min(V_2) = 5.923V$$

$$V_2(\text{DC}) = (\max + \min) / 2 = 8.333V \quad \text{same as calculated}$$

$$V_2(\text{AC}) = (\max - \min) = 4.819\text{Vpp} = 2.410\text{Vp}$$

$$|1.028 - j2.182| = 2.142\text{Vp} \quad \text{same as the simulation results}$$