

# ECE 320 - Homework #2 Solution

Semiconductors, PN Junction, Diode VI Characteristics. Due Wednesday, January 27th

Please make the subject "ECE 320 HW#2" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## Semiconductors

- 1) Why does the resistance of silicon decrease as temperature goes up?

*As temperature goes up, more thermal electron / hole pairs (charge carriers) are created.*

*As the number of charge carriers goes up, the resistance goes down.*

- 2) What doping of Boron (p-type) do you need to make an 0805 resistor have a resistance of 2000 Ohms? The dimensions of an 0805 resistor are

$$L = 2.0\text{mm}, W = 1.25\text{mm}, H = 0.95\text{mm}$$

$$R = \frac{\rho L}{A}$$

$$2000\Omega = \frac{\rho \cdot 0.2\text{cm}}{0.125\text{cm} \cdot 0.095\text{cm}}$$

$$\rho = 118.75 \Omega \text{ cm}$$

$$\sigma = \frac{1}{\rho} = 0.008421 \frac{1}{\Omega \text{ cm}} = n_p q \mu_p + n_n q \mu_n$$

$$0.008421 \approx n_p \cdot 1.6 \times 10^{-19} \cdot 500$$

$$n_p = 1.05 \times 10^{14} \frac{\text{atoms}}{\text{cc}}$$

- 3) A thermistor has the following resistance - voltage relationship

$$R = 1000 \exp\left(\frac{3905}{T} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees Kelvin. What is the resistance you'll read at

- +96.1F (hottest day in Fargo in 2019)
- -32.8F (coldest day in Fargo in 2019)
- +43.1F (average temperature in Fargo in 2019)

$$96.1\text{F} = 35.61\text{C}$$

$$\mathbf{R = 637 \text{ Ohms}}$$

$$-32.8\text{F} = -36.00\text{C}$$

$$\mathbf{R = 29,159 \text{ Ohms}}$$

$$+43.1\text{F} = 6.167\text{C}$$

$$\mathbf{R = 2420 \text{ Ohms}}$$

## PN Junction

4) Why can current flow p to n but not n to p?

Any of the following are valid answers:

*Current flowing p to n uses majority carriers. A large number of carriers means low resistance.*

*Current flowing n to p uses minority carriers. A small number of carriers means a very high resistance*

*Voltage from p to n reduces the size of the depletion zone. At 0.7V for silicon, the depletion zone is squeezed down to zero, at which point current flows.*


*Voltage n to p just makes the depletion zone larger.*

*If you apply enough voltage to overcome the potential energy barrier (0.7V for silicon), current flows.*

## Diode VI Characteristics

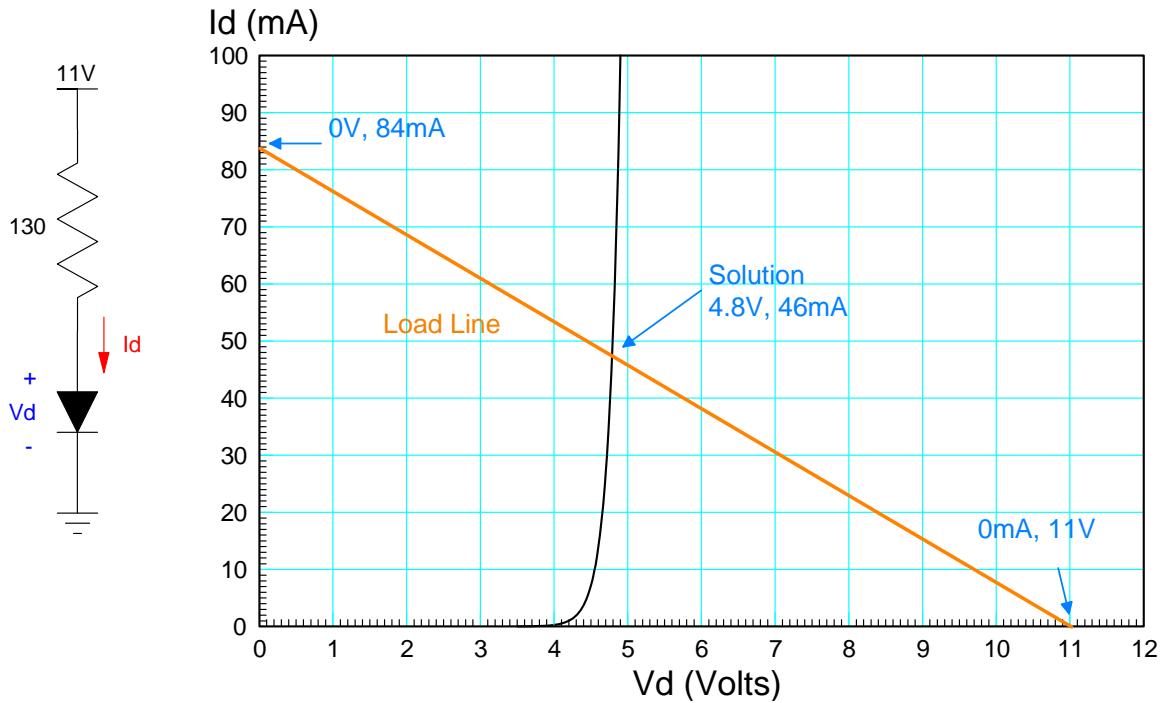5) Draw the load line for the following circuit and compute Id and Vd. The diode VI curve is shown on the graph.


- If  $Id = 0$  (the x-axis),  $Vd = 11V$
- If  $Vd = 0$ ,  $Id = 11V / 130 \text{ Ohms} = 84\text{mA}$



Assume the VI characteristics for a diode are

$$V_d = 0.052 \cdot \ln\left(\frac{I_d}{10^{-8}} + 1\right) \quad I_d = 10^{-8} \left( \exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

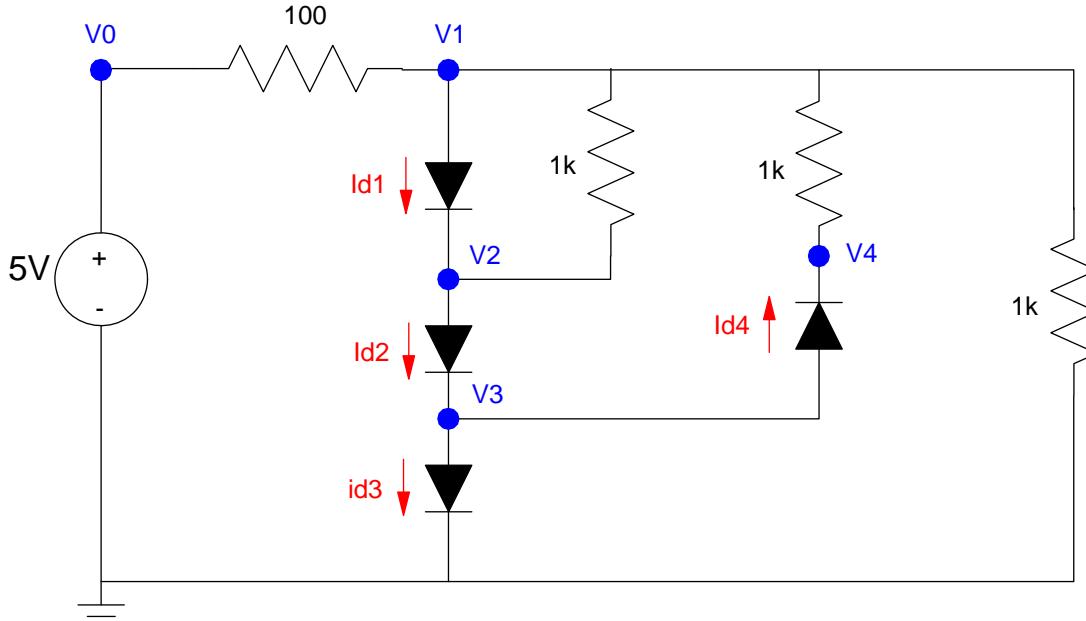6) Write the voltage node equations for the following circuit. Solve for V1 .. V4



Start with the diode equations

$$I_{d1} = 10^{-8} \left( \exp\left(\frac{V_1 - V_2}{0.052}\right) - 1 \right)$$

$$I_{d2} = 10^{-8} \left( \exp\left(\frac{V_2 - V_3}{0.052}\right) - 1 \right)$$

$$I_{d3} = 10^{-8} \left( \exp\left(\frac{V_3 - 0}{0.052}\right) - 1 \right)$$

$$I_{d4} = 10^{-8} \left( \exp\left(\frac{V_3 - V_4}{0.052}\right) - 1 \right)$$

Write the voltage node equations

$$\left(\frac{V_1 - V_0}{100}\right) + I_{d1} + \left(\frac{V_1 - V_2}{1000}\right) + \left(\frac{V_1 - V_4}{1000}\right) + \left(\frac{V_1}{1000}\right) = 0$$

$$-I_{d1} + I_{d2} + \left(\frac{V_2 - V_1}{1000}\right) = 0$$

$$-I_{d2} + I_{d3} + I_{d4} = 0$$

$$-I_{d4} + \left(\frac{V_4 - V_1}{1000}\right) = 0$$

Solve in Matlab using fminsearch

```
function [ J ] = cost_diode4( z )
V1 = z(1);
V2 = z(2);
V3 = z(3);
V4 = z(4);

Idss = 1e-8;
nVt = 0.052;

Id1 = Idss* exp( (V1 - V2)/nVt - 1 );
Id2 = Idss* exp( (V2 - V3)/nVt - 1 );
Id3 = Idss* exp( (V3 - 0)/nVt - 1 );
Id4 = Idss* exp( (V3 - V4)/nVt - 1 );

e1 = (V1 - 5)/1000 + Id1 + (V1-V2)/1000 + (V1-V4)/1000 + (V1/1000);
e2 = (V2-V1)/1000 - Id1 + Id2;
e3 = -Id2 + Id3 + Id4;
e4 = -Id4 + (V4-V1)/1000;

J = e1^2 + e2^2 + e3^2 + e4^2;

end
```

The solution is

```
[v,e] = fminsearch('cost_diode4',[2.1,1.4,0.7,2.1])

v =      2.4404      1.6281      0.8141      2.4403


e =      1.1022e-006

[v,e] = fminsearch('cost_diode4',v)

      v1          v2          v3          v4
v =    2.6168      1.7450      0.8725      2.6169

e =      4.9504e-015
```

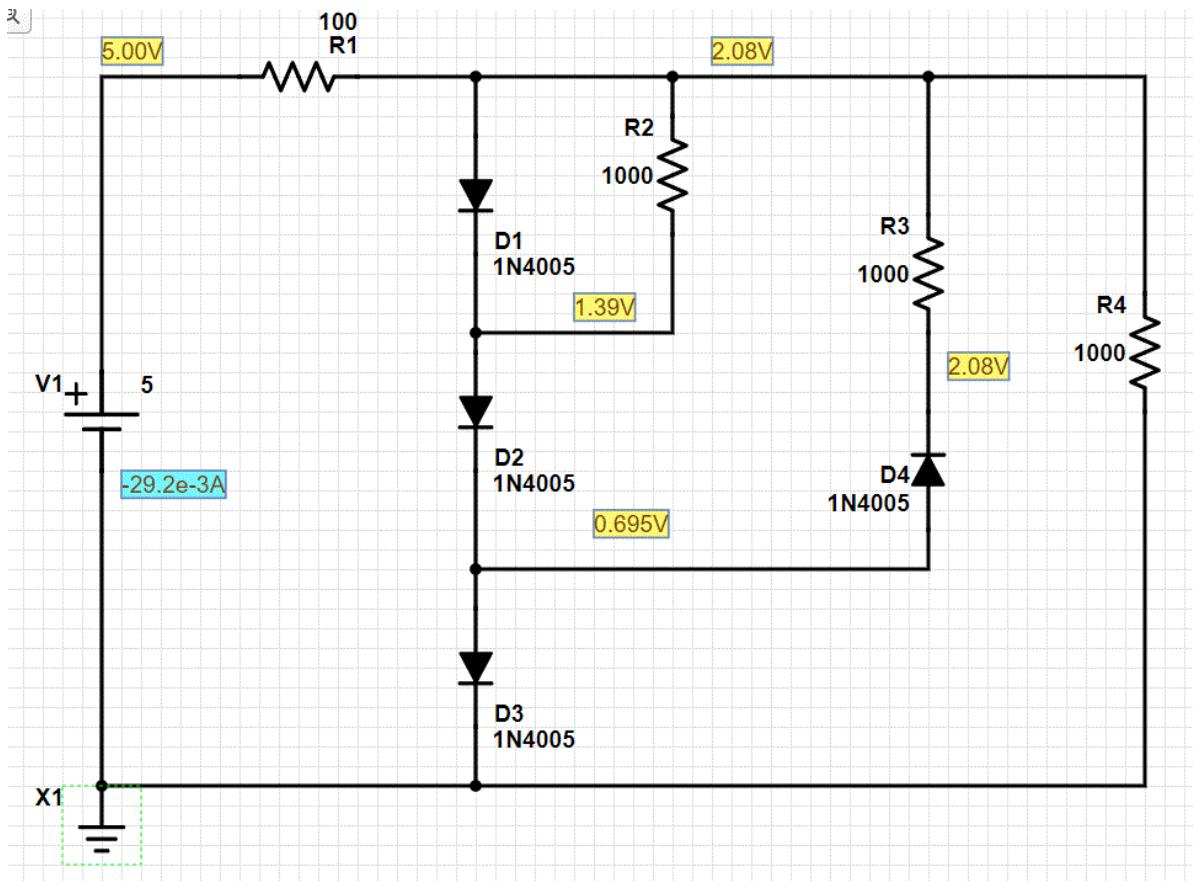
7) Check your results in PartSim. (use Fairchild, Rectifier Diode, 1N4005)



8) Build this circuit and measure the voltages V1, V2, and V3. Use a 4004 diode (in room 211 - or any silicon diode)

	Calculations problem 6	Simulation problem 7	Measured (lab) problem 8
V1	2.4404 V	2.08 V	2.22
V2	1.6281 V	1.39 V	1.48
V3	0.8141 V	0.695 V	0.74
V4	2.4403 V	2.08 V	2.21

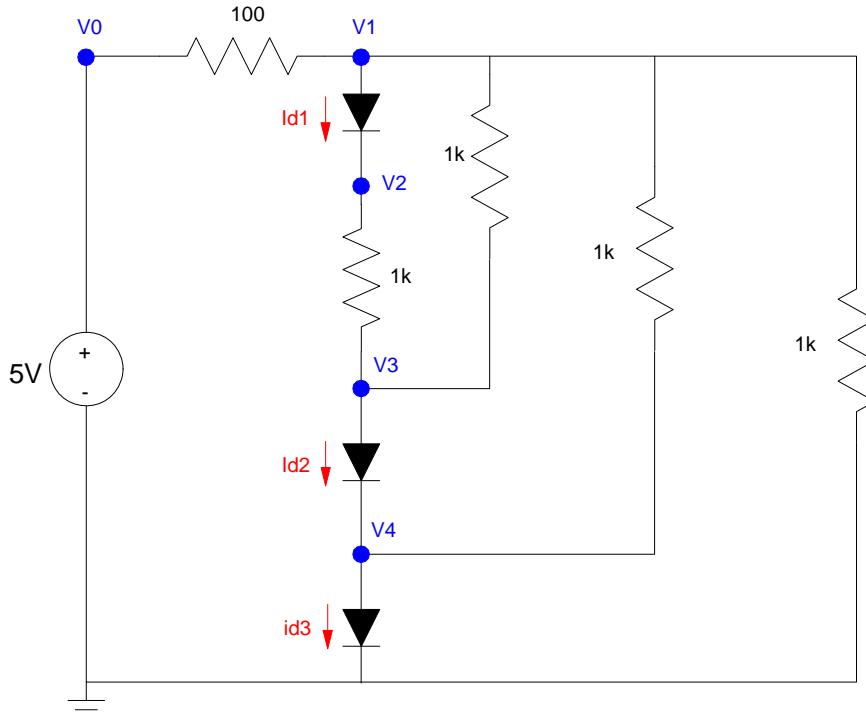9) Write the voltage node equations for the following circuit. Solve for { V1, V2, V3, V4 }



Start with the diode equations

$$I_{d1} = 10^{-8} \left( \exp \left( \frac{V_1 - V_2}{0.052} \right) - 1 \right)$$

$$I_{d2} = 10^{-8} \left( \exp \left( \frac{V_3 - V_4}{0.052} \right) - 1 \right)$$

$$I_{d3} = 10^{-8} \left( \exp \left( \frac{V_4 - 0}{0.052} \right) - 1 \right)$$

Write the voltage node equations

$$\left( \frac{V_1 - V_0}{100} \right) + I_{d1} + \left( \frac{V_1 - V_3}{1000} \right) + \left( \frac{V_1 - V_4}{1000} \right) + \left( \frac{V_1}{1000} \right) = 0$$

$$-I_{d1} + \left( \frac{V_2 - V_3}{1000} \right) = 0$$

$$\left( \frac{V_3 - V_1}{1000} \right) + \left( \frac{V_3 - V_2}{1000} \right) + I_{d2} = 0$$

$$\left( \frac{V_4 - V_1}{1000} \right) - I_{d2} + I_{d3} = 0$$

Solve using Matlab

### Function in Matlab

```
function [ J ] = cost_diode4( z )
V1 = z(1);
V2 = z(2);
V3 = z(3);
V4 = z(4);

Idss = 1e-8;
nVt = 0.052;

Id1 = Idss* exp( (V1 - V2)/nVt - 1 );
Id2 = Idss* exp( (V3 - V4)/nVt - 1 );
Id3 = Idss* exp( (V4 - 0)/nVt - 1 );

e1 = (V1 - 5)/100 + Id1 + (V1-V3)/1000 + (V1-V4)/1000 + (V1/1000);
e2 = (V2-V3)/1000 - Id1;
e3 = (V3-V1)/1000 + (V3-V2)/1000 + Id2;
e4 = (V4-V1)/1000 - Id2 + Id3;

J = e1^2 + e2^2 + e3^2 + e4^2;

end
```


Solution:

```
[V,e] = fminsearch('cost_diode4',[2.1,1.4,0.7,0.7])

      v1          v2          v3          v4
v =    3.8849    3.2058    1.4783    0.7538

e =  2.0161e-013
```

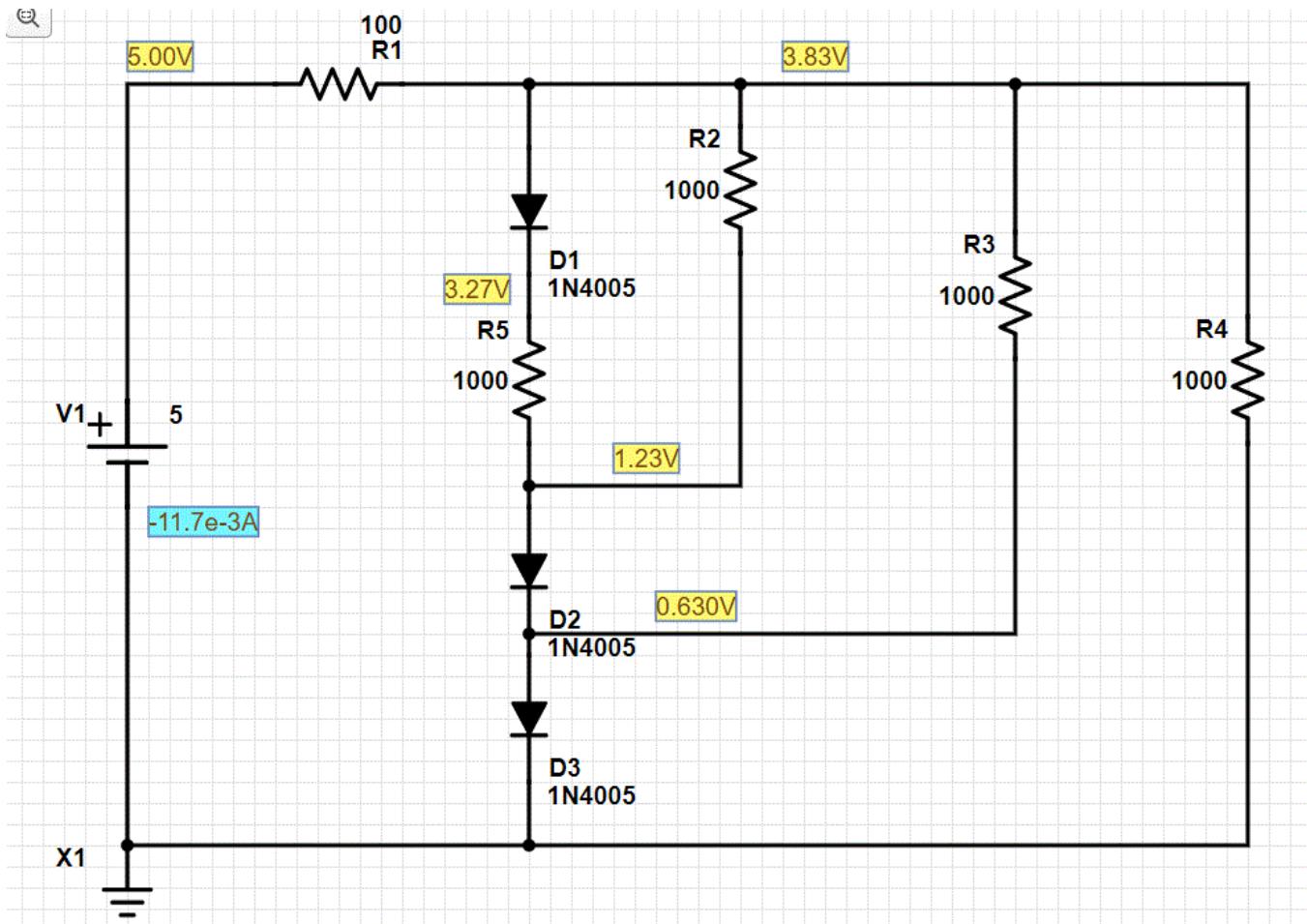10) Check your results in PartSim. (use Fairchild, Rectifier Diode, 1N4005)



11) Build this circuit and measure the voltages, Use a 4004 diode (in room 211 - or any silicon diode)

	Calculations problem 9	Simulation problem 10	Measured (lab) problem 11
V1	3.8849 V	3.83 V	3.87
V2	3.2058 V	3.27 V	3.22
V3	1.4783 V	1.23 V	1.48
V4	0.7538 V	0.63 V	0.82