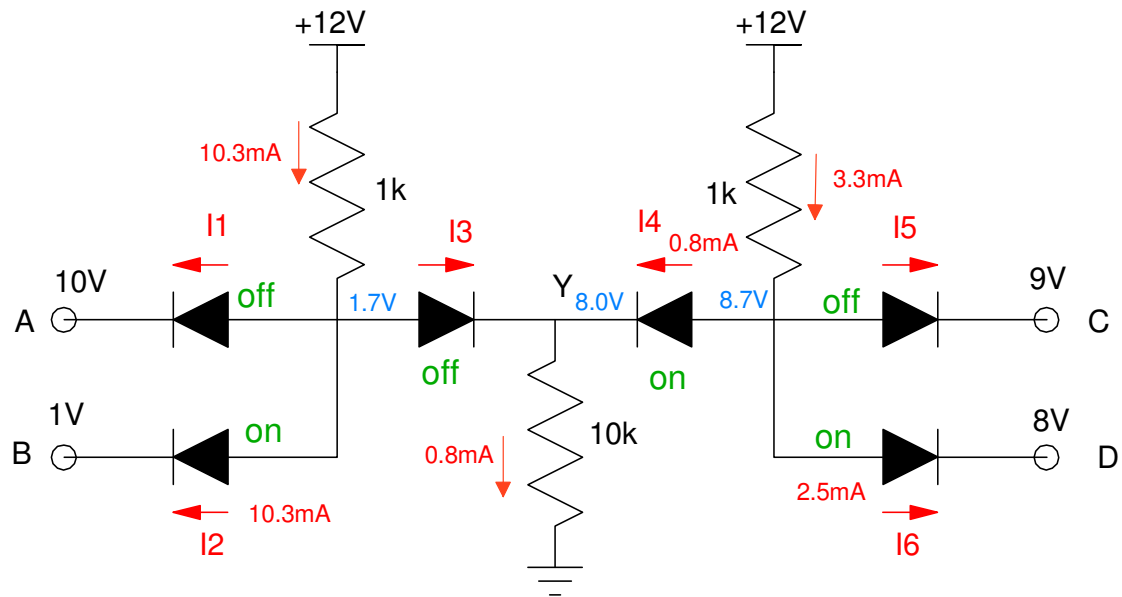


ECE 320 - Homework #4 Solution


Max/Min Circuits, Clipper Circuits, Transistor Theory. Due Monday, Feb 10th

Max/Min:

1) Determine the voltages and currents for the following max/min circuit. What function does this circuit implement? $Y = f(A, B, C, D)$



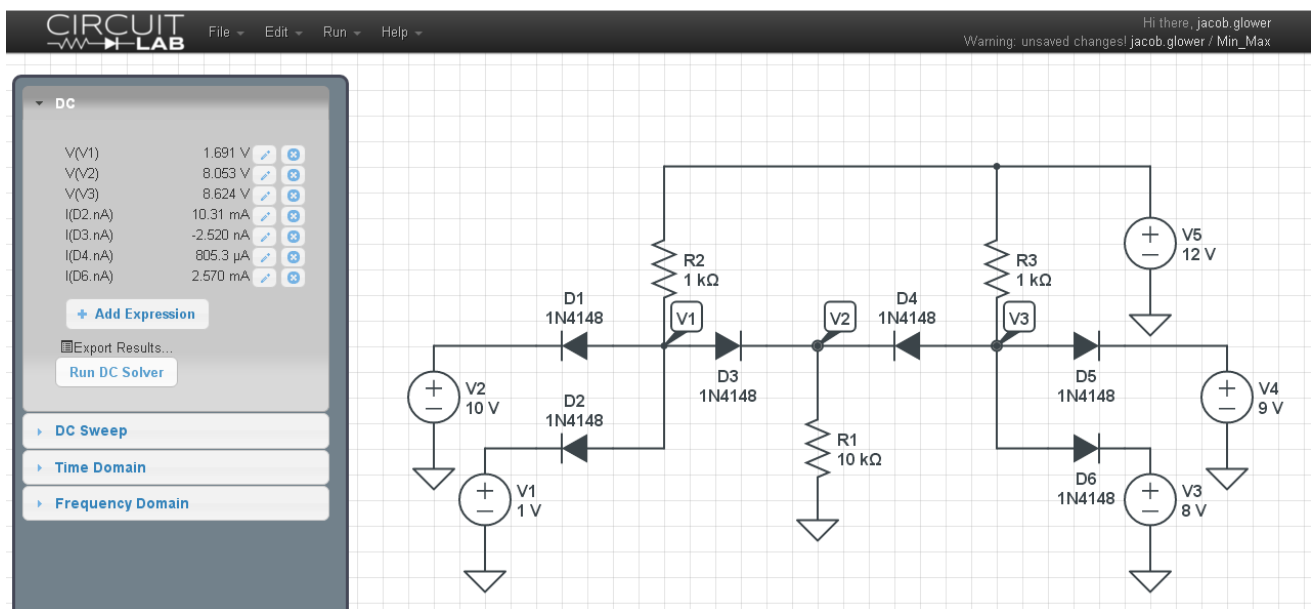
2) Check your results in PartSim (or similar program)



Clipper Circuits:

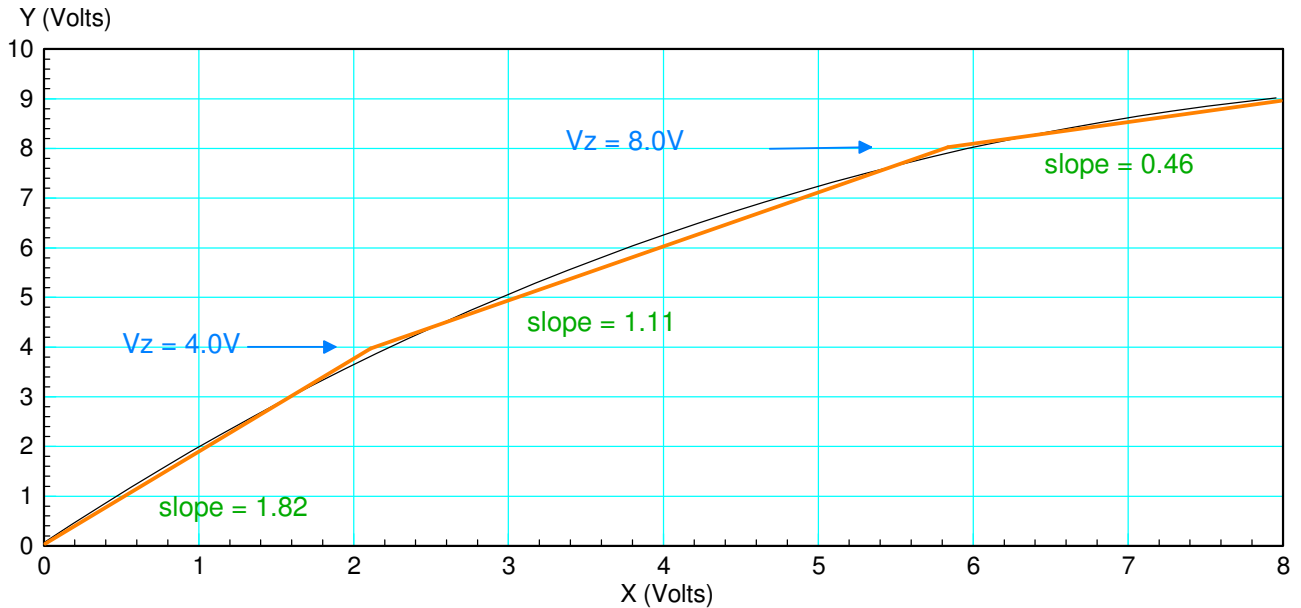3) Design a circuit to approximate the following function subject to the following requirements:

- Input: 0 .. 10V, capable of 100mA
- Output: 100k resistor
- Relationship: Graph below, +/- 200mV



Op-Amp: To get an initial gain of 1.81, add an op-amp with a gain of 1.81

$$gain = 1 + \frac{R_{16}}{R_{17}}$$

Let $R_{17} = 1k$

$$R_{16} = 810$$

Stage 1: Zener voltage = 4.0V

$$gain = \left(\frac{R_{19}}{R_{19} + R_{18}} \right) \cdot 1.81 = 1.11$$

$$\left(\frac{R_{19}}{R_{19} + 1k} \right) = \frac{1.11}{1.81} = 0.613$$

$$R_{19} = \left(\frac{0.613}{1 - 0.613} \right) 1k = 1586\Omega$$



Stage 2: Zener voltage = 8.0V

$$gain = \left(\frac{R_{net}}{R_{net} + R_{18}} \right) \cdot 1.81 = 0.46$$

$$R_{net} = 341\Omega = R_{19} || R_{20}$$

$$R_{20} = 430\Omega$$


4) Check your design in PartSim

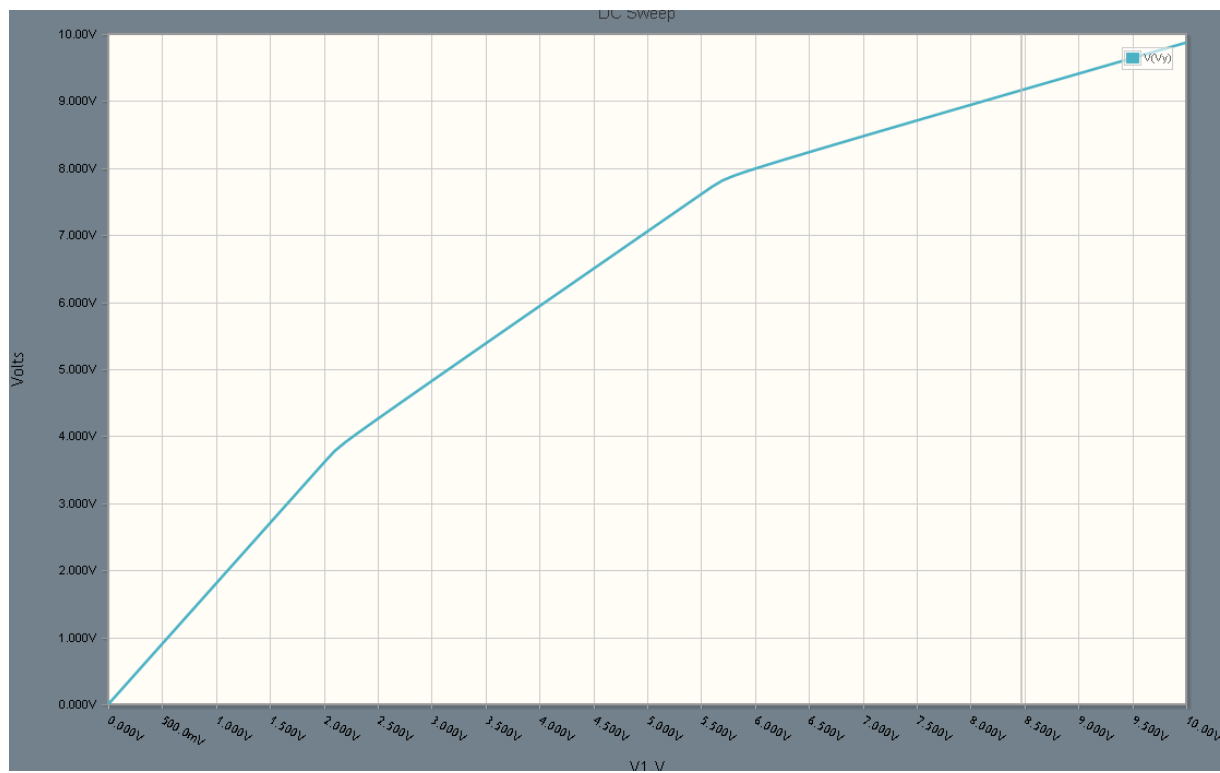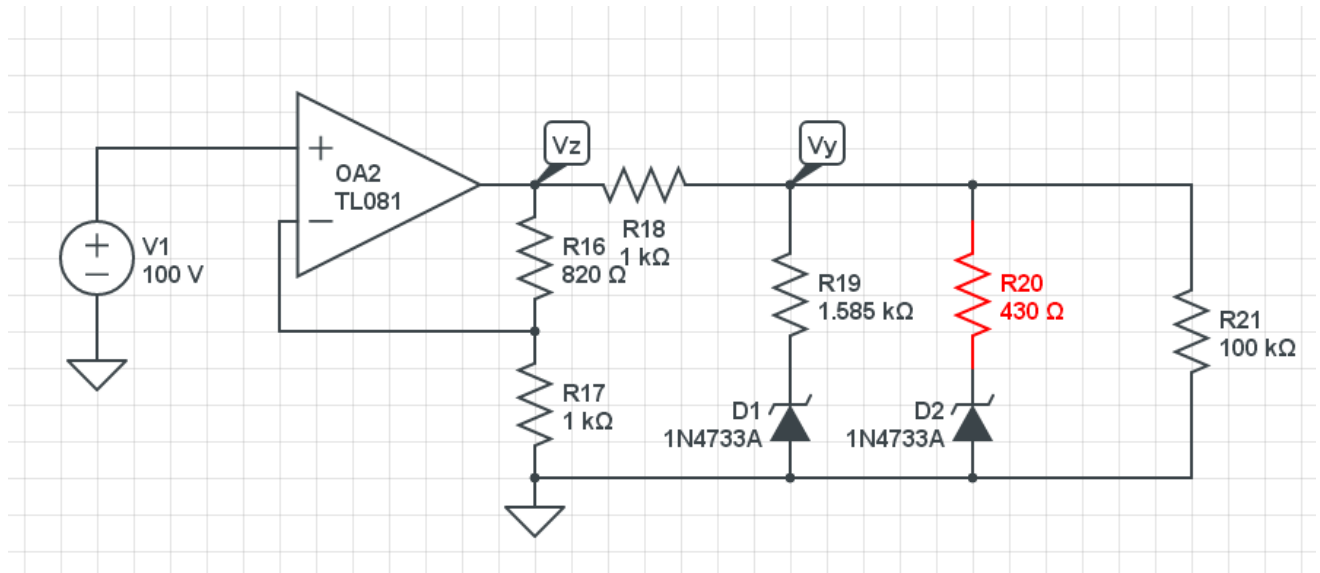

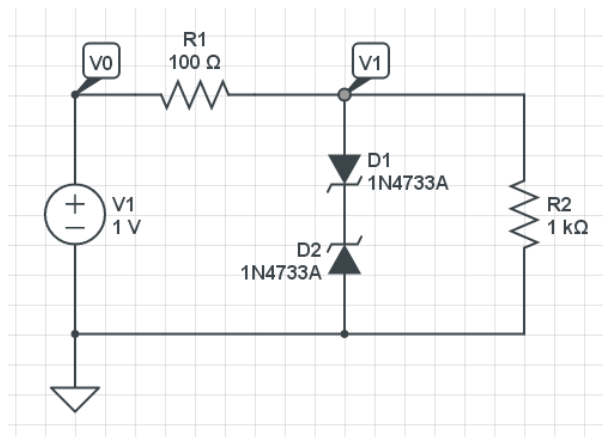
5) Design a circuit which meets the following requirements:

- Input: $-10 \text{ V} \dots +10 \text{ V}$, capable of 100 mA
- Output: $1 \text{ k}\Omega$ resistor
- Relationship:

$$V_{out} = \begin{cases} +5 \text{ V} & V_{in} > +5 \text{ V} \\ V_{in} & -5 \text{ V} < V_{in} < +5 \text{ V} \\ -5 \text{ V} & V_{in} < -5 \text{ V} \end{cases}$$




Both diodes are 4.3V zeners

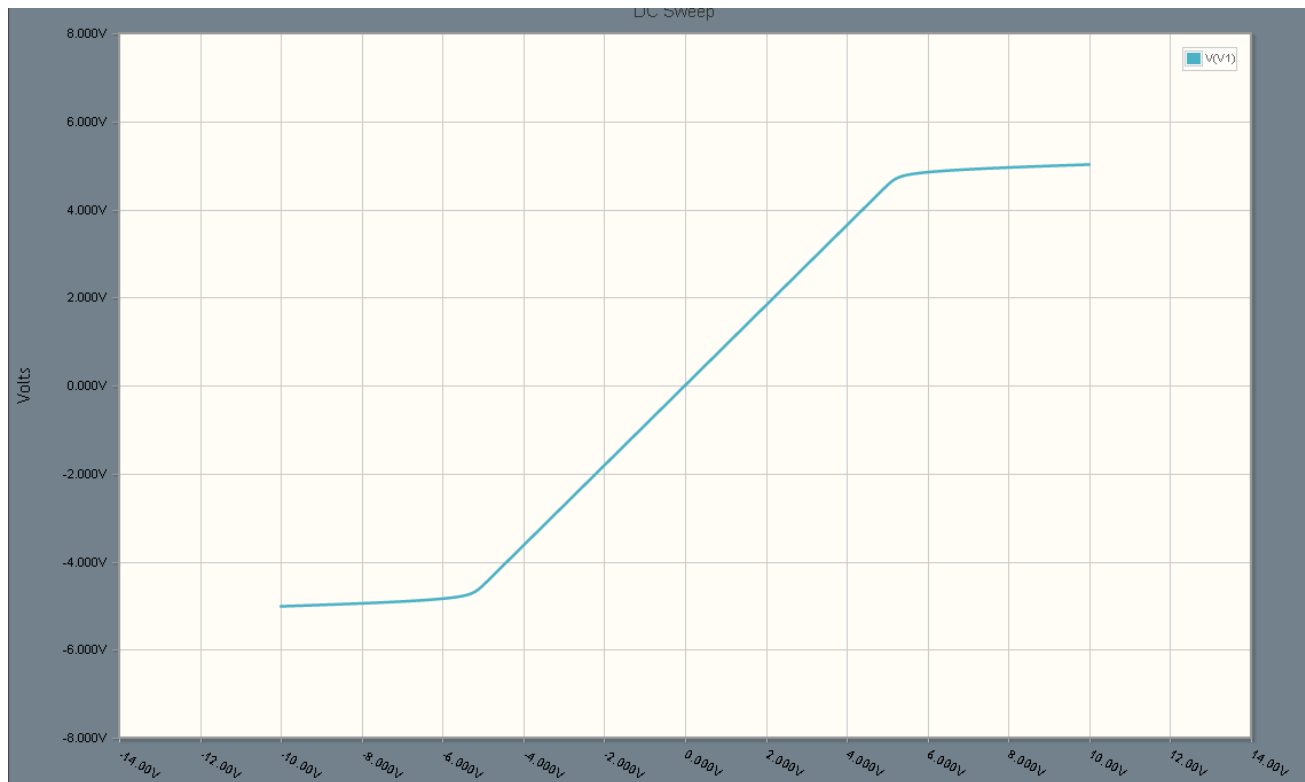

Transistors

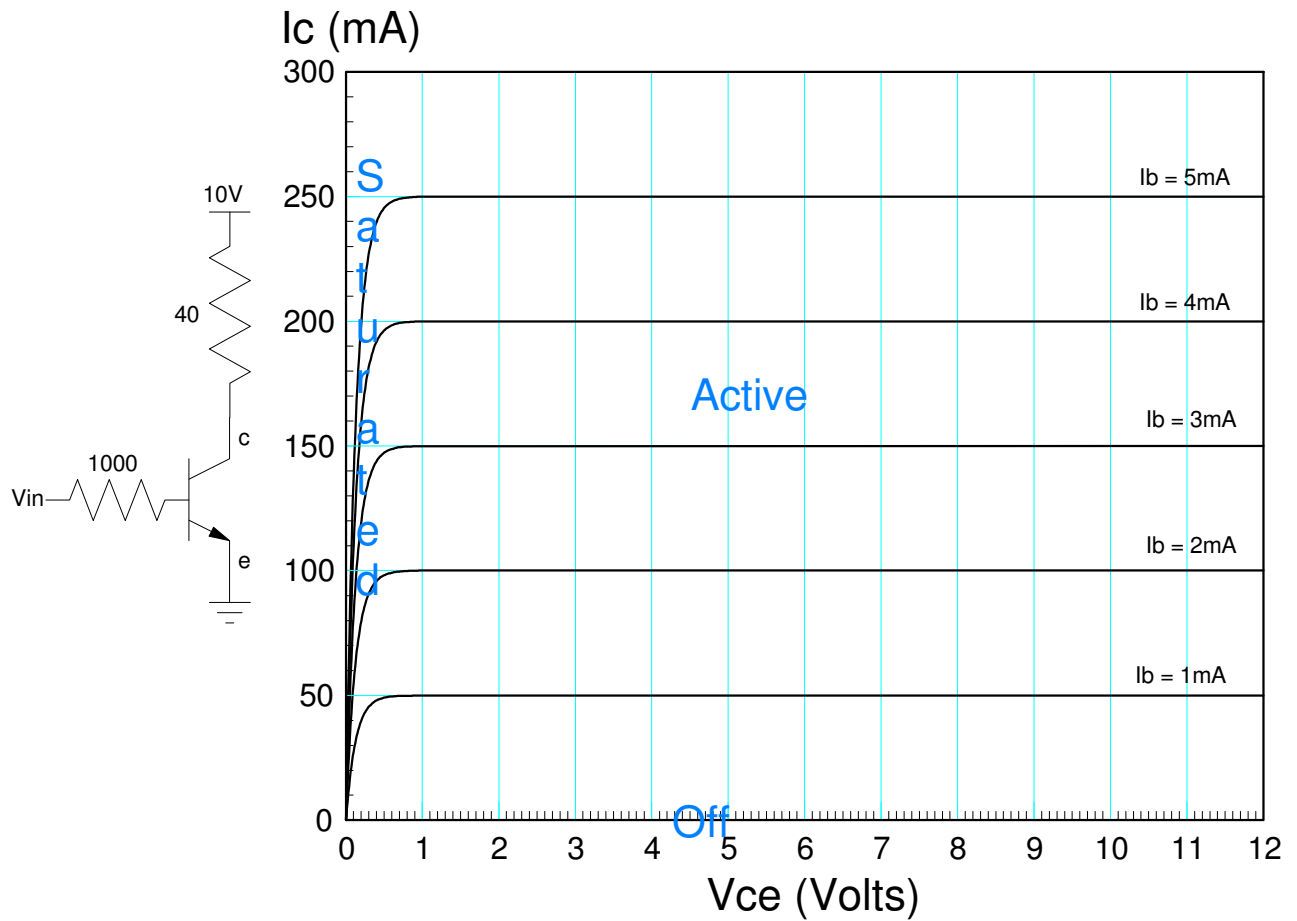6) Determine the current gain, β , for the transistor show below. Also label the off, active, and saturated regions.

$$\beta = \left(\frac{250mA}{5mA} \right) = 50$$



7) Draw the load-line and determine the Q-point for

$V_{in} = 0V$

- $I_b = 0$
- $I_c = 0$
- Q-Point: (10V, 0mA) *off*

$V_{in} = 3V$

$$I_b = \left(\frac{5V - 0.7V}{1000\Omega} \right) = 2.3mA$$

$$\beta I_b = 115mA$$

Q-Point: (5.4V, 115mA) *active*

$V_{in} = 6V$

$$I_b = \left(\frac{6V - 0.7V}{1000\Omega} \right) = 5.3mA$$

$$\beta I_b = 265mA > \frac{10V - 0.2V}{40\Omega} = 245mA$$

Q-Point: (0.2V, 245mA) *saturated*

