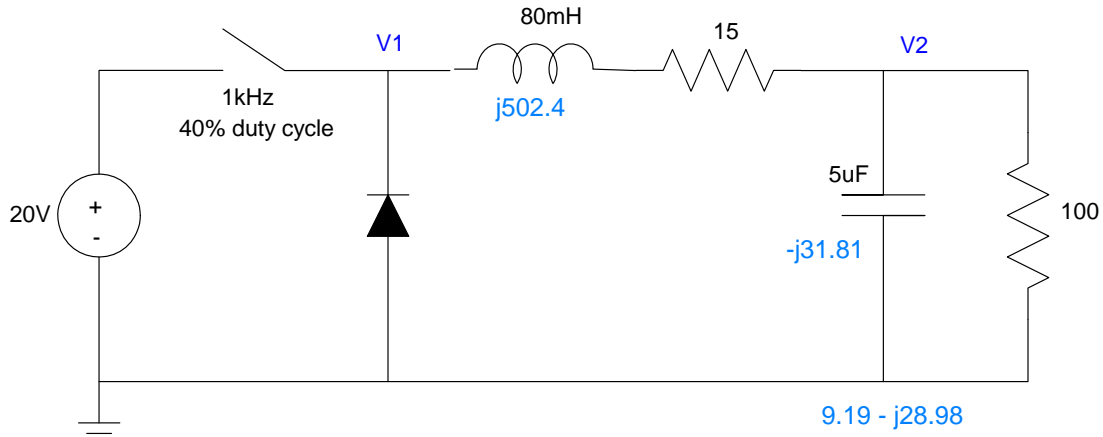


# ECE 320 - Homework #6

DC to DC Converters, Schmitt Triggers, Fourier Transforms. Due Monday, February 24th

## DC to DC Converters

1) Determine the voltages (both DC and AC) for V1 and V2.



V1

$$(DC) \quad V_1 = 0.4 \cdot 20V + 0.6 \cdot (-0.7V) = 7.58V$$

$$(AC) \quad V_1 = 20.7V_{pp}$$



V2:

$$(DC) \quad V_2 = \left( \frac{100}{100+15} \right) 7.58V = 6.59V$$

$$(AC) \quad V_2 = \left( \frac{9.19-j28.98}{(9.19-j28.98)+(15+j502.4)} \right) \cdot 20.7V_{pp}$$

$$V_2 = 1.32V_{pp}$$

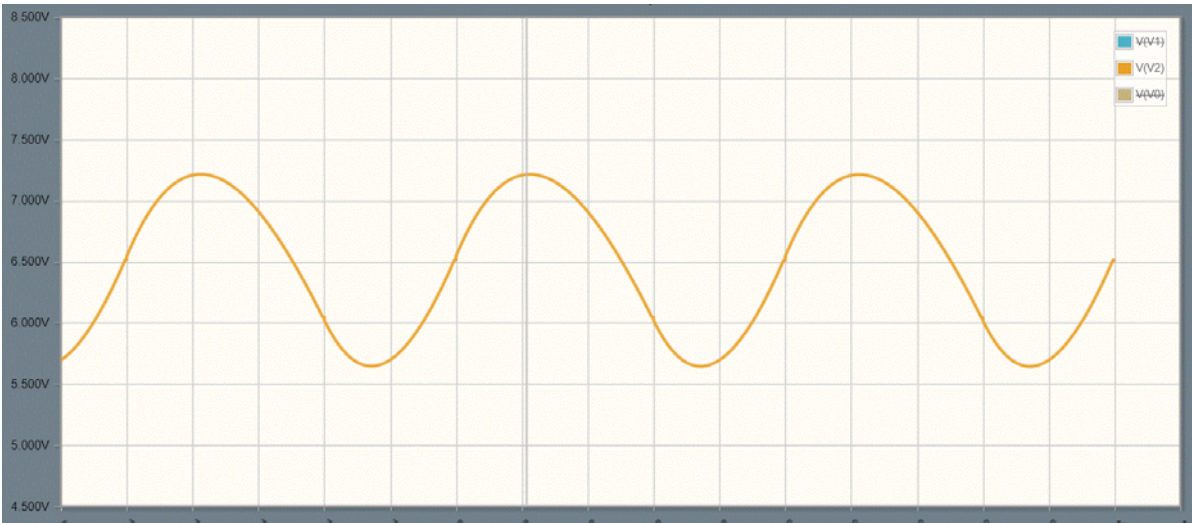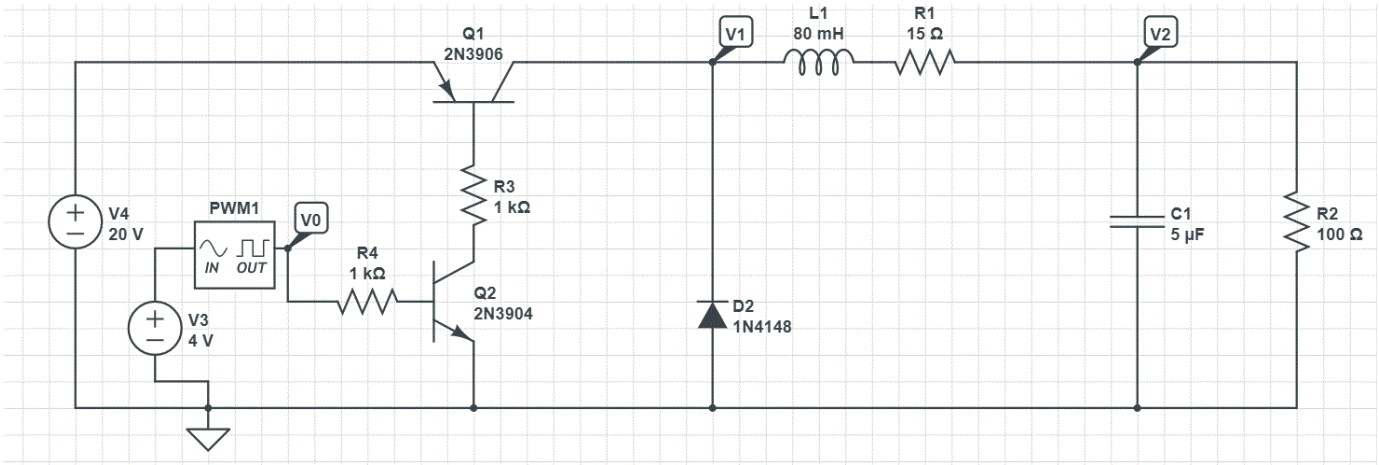2) Simulate this circuit in CircuitLab and determine the voltages at V1 and V2 (both DC and AC)



	V1		V2	
	DC	AC	DC	AC
Calculated	7.58V	20.7Vpp	6.59 V	1.32 Vpp
Simluated	9.65V	20.7Vpp	6.285 V	1.569 Vpp

3) Change the duty cycle and C so that

- The DC voltage at V2 = 5.00V
- The ripple at V2 is 100mVpp

The voltage at V1 should be

$$V_2 = 5.00V = \left( \frac{100}{100+15} \right) V_1$$

$$V_1 = 5.75V$$

The duty cycle should then be

$$\alpha = \left( \frac{5.75+0.7}{20+0.7} \right) = 0.31159$$

Make the duty cycle 31.16%

For a 100mVpp ripple

Without C2, the ripple is

$$V_2 = \left( \frac{100}{100+(15+j502.4)} \right) \cdot 20.7V_{pp}$$

$$V_2 = 4.016V_{pp}$$

For a ripple of 100mVpp,

The ripple needs to be 40.16x smaller

Zc = 40.16 times smaller than 100 Ohms

$$\left| \frac{1}{j\omega C_2} \right| = \left( \frac{1}{40.16} \right) 100\Omega = 2.49\Omega$$

$$C_2 = 63.94\mu F$$

## Schmitt Triggers

4) A thermistor has the following resistance vs. temperature relationship

$$R = 1000 \cdot \exp\left(\frac{3905}{T} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees Kelvin (Celsius + 273). Design a circuit which outputs

- +10V when  $T > 5^\circ\text{C}$
- 0V when  $T < 0^\circ\text{C}$
- No change for  $0^\circ\text{C} < T < 5^\circ\text{C}$

Assume a 2k resistor for a voltage divider.

At  $5^\circ\text{C}$  (on)

- $R = 2567 \text{ Ohms}$
- $V_a = 5.62\text{V}$

At  $0^\circ\text{C}$  (off)

- $R = 3320 \text{ Ohms}$
- $V_a = 6.24\text{V}$


The output increases as  $V_a$  decreases. Connect to the minus input.


When the output is 0V, you switch at  $5.62\text{V}$ . Make the offset  $5.62\text{V}$ .

The gain is

$$\text{gain} = \left( \frac{\text{change in output}}{\text{change in input}} \right) = \left( \frac{10\text{V} - 0\text{V}}{6.24\text{V} - 5.62\text{V}} \right) = 16.13$$

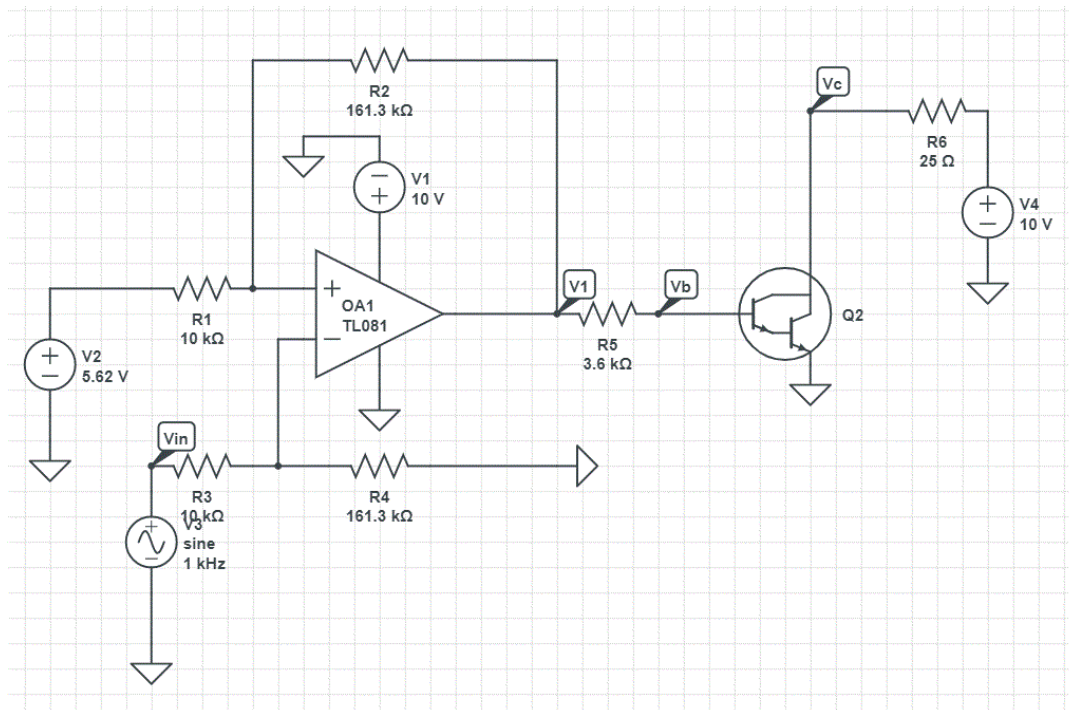Pick the resistors to be in a 16.13 : 1 ratio



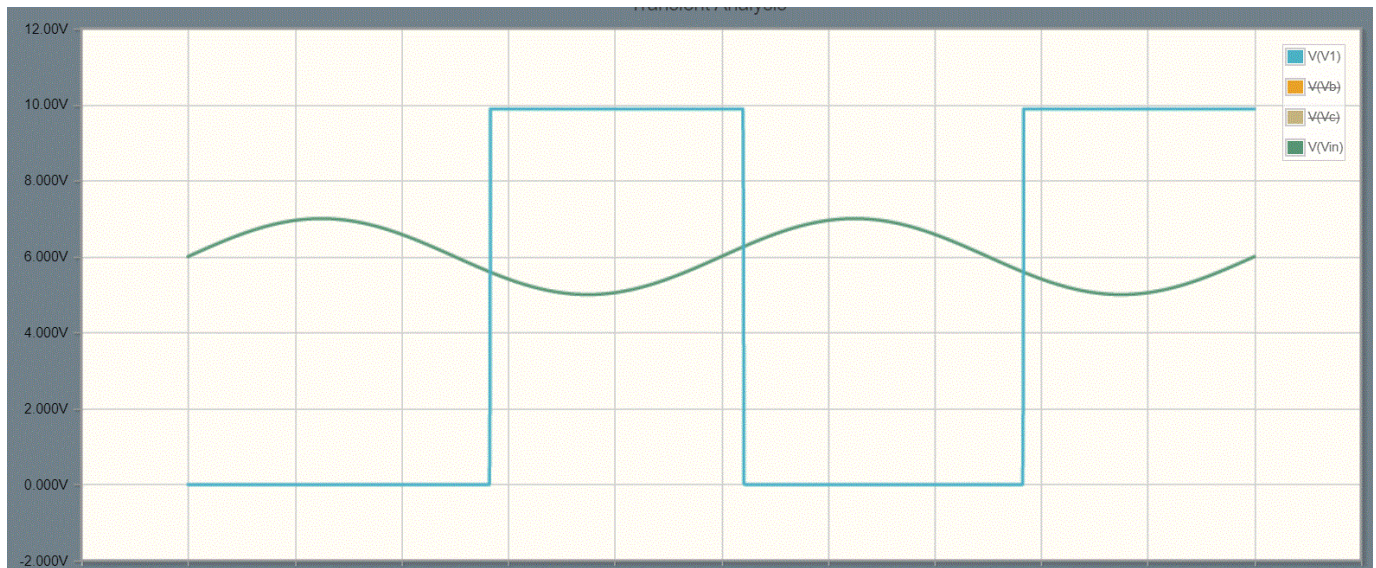

Checking in simulation, V1 turns on and off at

	Calculated	Simulated
On Voltage	5.62V	5.597 V
Off Voltage	6.24V	6.246 V

5) Design a circuit which turns on and off a DC motor based upon temperature

- The motor turns on when  $T > 5^{\circ}\text{C}$
- The motor turns off when  $T < 0^{\circ}\text{C}$
- No change for  $0^{\circ}\text{C} < T < 5^{\circ}\text{C}$

Assume the motor draws 400mA @ 10V when on.

Use the previous circuit and add a transistor as a switch. To make sure the transistor saturates

$$\beta I_b > I_c$$


$$I_b > \frac{I_c}{\beta} = \frac{400\text{mA}}{1000} = 400\mu\text{A}$$

Let  $I_b = 1\text{mA}$

$$R_b = \left( \frac{10\text{V} - 1.4\text{V}}{1\text{mA}} \right) = 8.6\text{k}\Omega$$



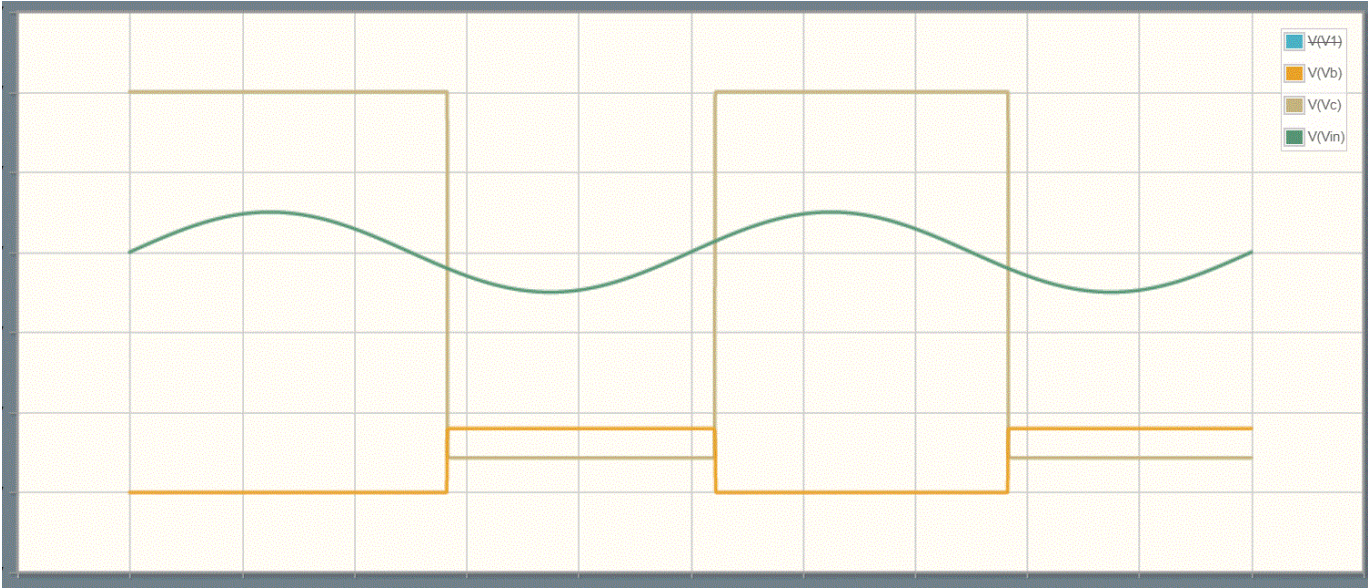6) (Lab): Build the circuit you designed for problem #5.



		Calculated	Simulated
Motor On	Vb	1.40 V	1.5940 V
	Vc	0.90 V	0.8637 V
Motor Off	Vb	0V	432uV
	Vc	10V	10.00 V

## Fourier Transforms

The voltage  $V_1$  in problem #1 is a 40% duty cycle square wave


$$V_1(t) = V_1(t + 1\text{ms}) \quad V_1 \text{ is periodic in } 1\text{ms} - \text{i.e. it's a } 1\text{kHz square wave}$$

$$V_1(t) = \begin{cases} +20\text{V} & 0 < t < 400\mu\text{s} \\ -0.7\text{V} & 400\mu\text{s} < t < 1000\mu\text{s} \end{cases}$$

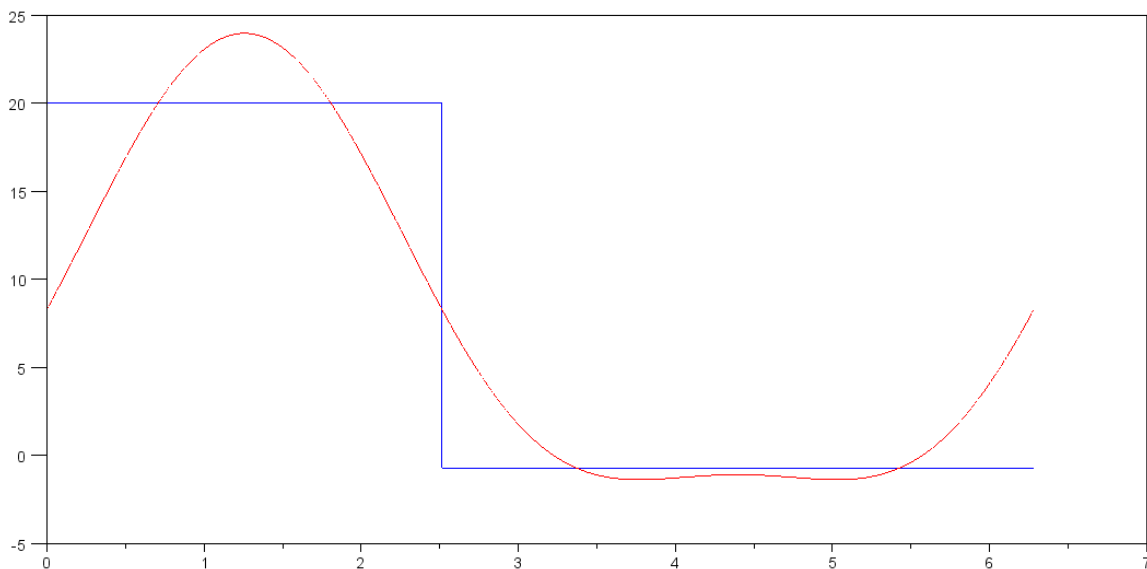7) Determine the first five terms for the Fourier transform for  $V_1(t)$

$$V_1(t) = a_0 + a_1 \cos(\omega_0 t) + b_1 \sin(\omega_0 t) + a_2 \cos(2\omega_0 t) + b_2 \sin(2\omega_0 t)$$

```
t = [0:0.0001:1]';  
V1 = 20*(t<0.4) - 0.7*(t>=0.4);  
t = t * 2*pi;  
  
a0 = mean(V1)  
  
a0 = 7.5791721  
  
a1 = 2*mean(V1 .* exp(-j*t))  
  
a1 = 3.8761426 - 11.917231i  
  
a2 = 2*mean(V1 .* exp(-j*2*t))  
  
a2 = -3.1316587 - 2.2781891i  
  
plot(t,V1,'b',t,real(a0 + a1*exp(j*t) + a2*exp(j*2*t)),'r');
```



8) Determine  $V_2(t)$  at each frequency

- DC
- 1kHz
- 2kHz

```
C = 5e-6;  
L = 0.08;
```

```
w = 0;  
Zrc = 1/(j*w*C + 1/100)
```

```
Zrc = 100.
```

```
y0 = Zrc / (Zrc + 15 + j*w*L) * a0
```

```
y0 = 6.5905844
```

```
w = 2*pi*1000;  
Zrc = 1/(j*w*C + 1/100)
```

```
Zrc = 9.1999668 - 28.902548i
```

```
y1 = Zrc / (Zrc + 15 + j*w*L) * a1
```

```
y1 = -0.4998887 + 0.6262359i
```


```
w = 2*pi*2000;  
Zrc = 1/(j*w*C + 1/100)
```

```
Zrc = 2.4704523 - 15.52231i
```

```
y2 = Zrc / (Zrc + 15 + j*w*L) * a2
```

```
y2 = 0.0426440 + 0.0442968i
```
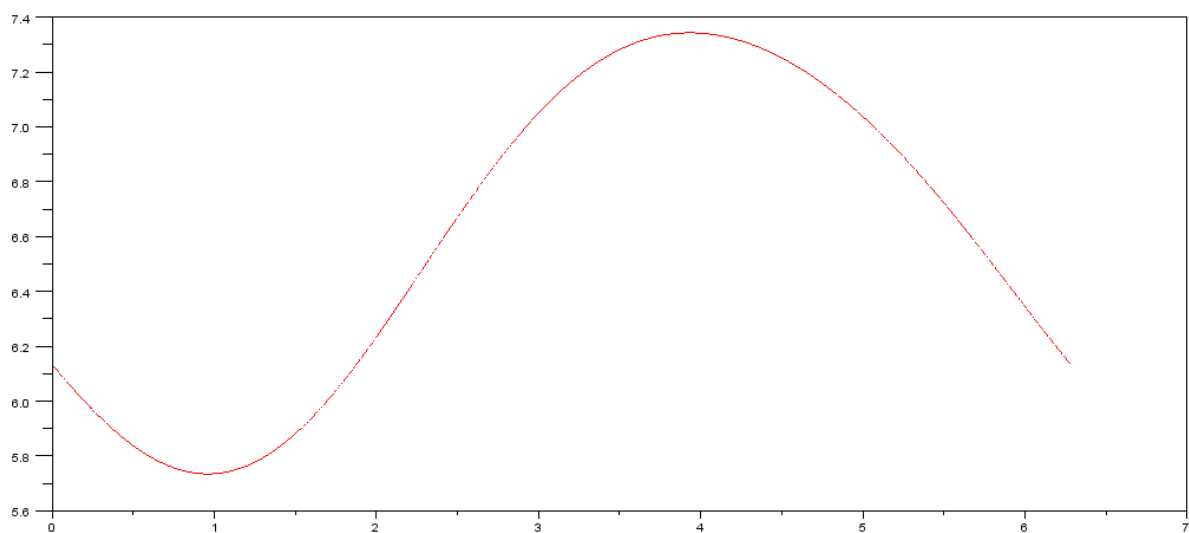
```
plot(t,real(y0 + y1*exp(j*t) + y2*exp(j*2*t)),'r');
```





9) How do your answers for problem #1 and problem #8 compare?

	Problem #1 calculated	Problem #2 simulated	Problem #8
V2(DC)	6.59 V	6.428 V	6.590 V
V2 1kHz term	1.32 Vpp	1.569 V	1.602 Vpp
V2 2kHz term	0 Vpp		0.123 Vpp

note: The 1kHz term is V1pp for problem #1. This is related to problem #8 as

$$2|a_1 - jb_1| = V_{pp} \quad \text{at 1kHz}$$

The 2kHz term is V1pp for problem #1 is 0Vpp (we ignored it). This is related to problem #8 as

$$2|a_2 - jb_2| = V_{pp} \quad \text{at 2kHz}$$

```
V2 = real(y0 + y1*exp(j*t) + y2*exp(j*2*t));
```

```
mean(V2)
```

```
ans = 6.5905387
```

```
max(V2) - min(V2)
```

```
ans = 1.6079241
```