

# ECE 320 - Quiz #5 - Name \_\_\_\_\_

555 Timers, Transistor Switch, Comparitors, Schmitt Triggers - February 19, 2021


1) 555 Timers. Determine R1, R2, and C so that the 555 timer outputs a 5% duty cycle 50Hz square wave:

$$t_{on} = R_1 \cdot C \cdot \ln(2.58) = 1.0ms$$

$$t_{off} = R_2 \cdot C \cdot \ln(2) = 19.0ms$$

Let R1 be your birthday day (1000 + 100\*Month + Day. May 14th would be 1514 Ohms)

R1 1000 + 100*Month + Day	R2	C

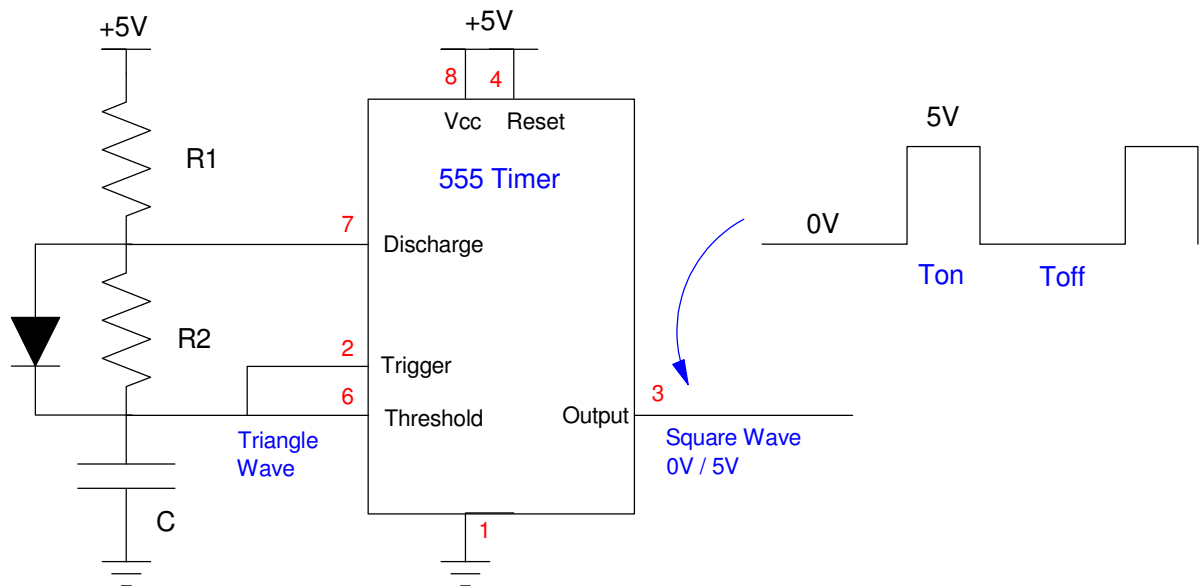


2) Transistor Switch: Design. Specify R1 and R2 so that when  $V_{in} = 5.00V$ ,

- $I_c = (1000 + 100 \cdot \text{Birth Month} + \text{Birth Day}) \text{ mA}$ . May 14th would be 1514mA (1.514A)
- The transistor is saturated, and
- $I_b < 25\text{mA}$  (the maximum output of a 555 timer)

Assume 6144 transistors

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.36V$  when saturated
- $\beta = 200$

$I_c \text{ (mA)}$ $1000 + 100 \cdot (\text{Mo}) + (\text{Day})$	$R_c$	min value of $R_b$	max value of $R_b$

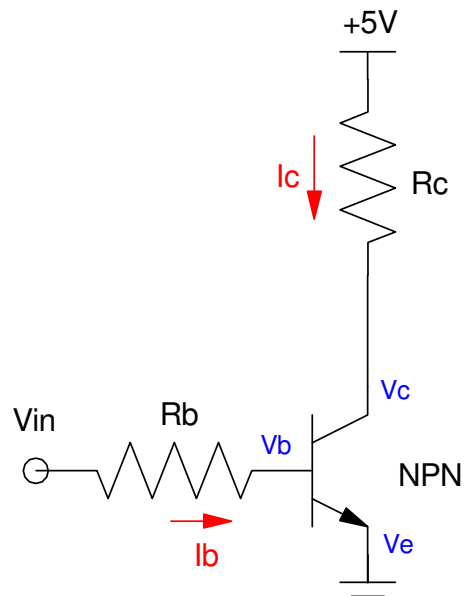


3) Darlington Pair (analysis). Assume two 6144 NPN transistors are connected as a Darlington pair.

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.36V$  when saturated
- $\beta = 200$

Let  $R_b$  be  $1000 + 100(\text{Birth Month}) + \text{Birth Day}$ . (May 14 = 1514 Ohms). Find the currents and voltages.



$R_b$ $1000 + 100 * Mo + Day$	I1	I2	I3
	V1	V2	V3

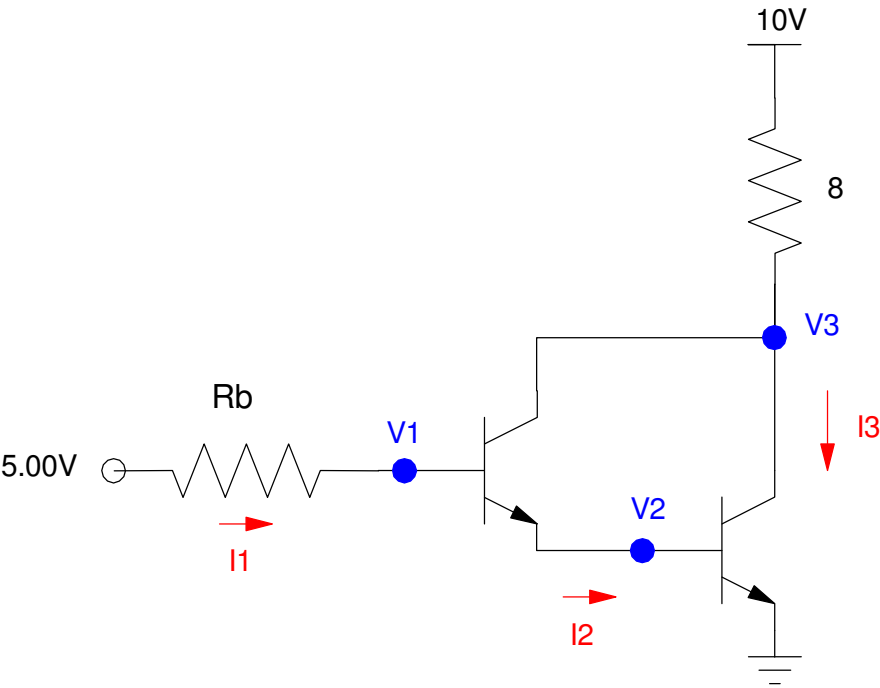

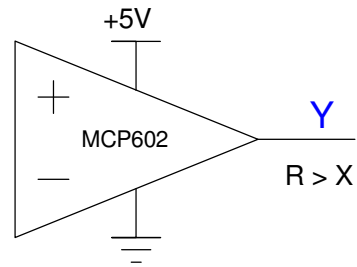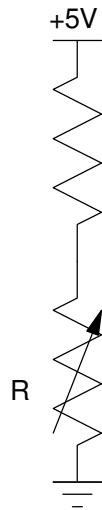4) Comparitor: Design a circuit which output

- 0V when  $R > X$  Ohms
- 5V when  $R < X$  Ohms



where  $X$  is  $1000 + 10 * (\text{Birth Month}) + (\text{Birth Day})$ .



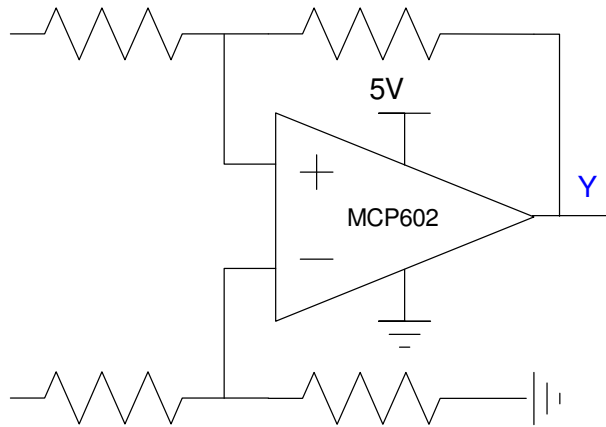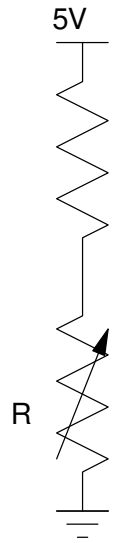5) Schmitt Trigger: Design a circuit which output

- 5V when  $R < X$  Ohms
- 0V when  $R > X + 200$  Ohms
- No change for  $X < R < X + 200$  Ohms

Let  $X$  be  $1000 + 10(\text{Birth Month}) + (\text{Birth Date})$ .



6) Schmitt Trigger: Analysis. Determine the voltages and resistance where the following Schmitt trigger turns on and off. Assume  $R_x$  is  $1000 + 10 * (\text{Birth Month}) + (\text{Birth Day})$ . May 14th gives  $R_x = 1514$  Ohms.

<div>R<sub>x</sub></div> <div>1000 + 10*Mo + Day</div>	On (V2 = +5V)		Off (V2 = 0V)	
	V1	R	V1	R

