

ECE 320 - Homework #2

Semiconductors, PN Junction. Due Monday, January 24th

Please make the subject "ECE 320 HW#2" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

Semiconductors

1) Why does current flow p-to-n but not n-to-p across a pn junction?

2) What doping of Phosphorus (n-type) do you need to make an 1206 resistor have a resistance of 1200 Ohms? The dimensions of an 1206 resistor are

$$L = 3.20\text{mm}, W = 1.60\text{mm}, H = 0.95\text{mm}$$

3) A thermistor has the following resistance - voltage relationship

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees C. What is the resistance at

- 0F Recommended temperature of a freezer
- +40F Recommended temperature of a refrigerator
- +68F Temperature of cold tap water (varies)
- +120F Temperature of hot tap water (varies)

Diode VI Characteristics

Assume the VI characteristics for a diode are (1N4004 diode in CircuitLab)

- $n = 1.45$
- $n V_t = 0.0377$
- $I_{dss} = 7.69e-11$

$$V_d = 0.0377 \cdot \ln\left(\frac{I_d}{7.69 \cdot 10^{-11}} + 1\right) \quad I_d = 7.69 \cdot 10^{-11} \left(\exp\left(\frac{V_d}{0.0377}\right) - 1\right)$$



4) For the 1-diode circuit (next page - 100 Ohms is brown - black - brown)

- a) Draw the load-line for the following circuit (next page). Determine V_d and I_d from the graph.
- b) Write the voltage node equations and solve for V_d and I_d assuming the VI equations above

5) Build this circuit in CircuitLab and solve for V_d and I_d . (Use a 1N4004 diode)

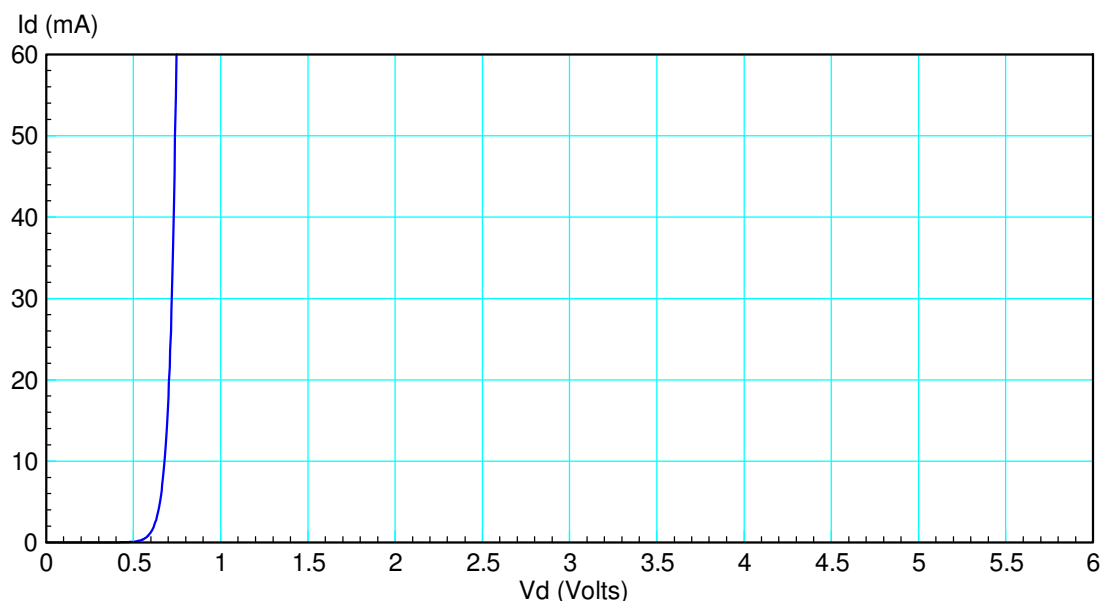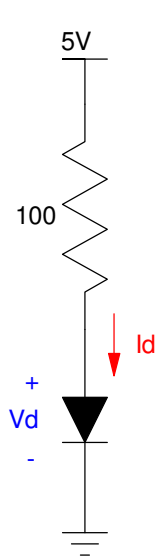6) Build this circuit on your breadboard and measure V_d . From this, compute I_d

- Include a photo to receive credit for this problem



	Vd	Id
4a) Graphical solution		
4b) Numeric Solution		
5) Simulation (CircuitLab)		
6) Lab (experimental)		

Problem 4 to 7

Problem 8 - 10: *Note: If you don't have four 100 Ohm resistors (brown - black - brown), replace the resistors with ones you ***do*** have - ideally all the same and close to 100 Ohms. Do problems 8 - 10 using the resistors you use for the experimental results (problem #10).*


8) Write the voltage node equations assuming nonlinear diodes. Solve for $\{V_1, V_2, \text{ and } V_3\}$ using Matlab.

9) Simulate this circuit in CircuitLab to determine $\{V_1, V_2, \text{ and } V_3\}$

10) Build this circuit with your breadboard and measure $\{V_1, V_2, V_3\}$

- Include a photo to receive credit for problem #10

	V1	V2	V3
8) Numeric Solution			
9) Simulation (CircuitLab)			
10) Lab (experimental)			

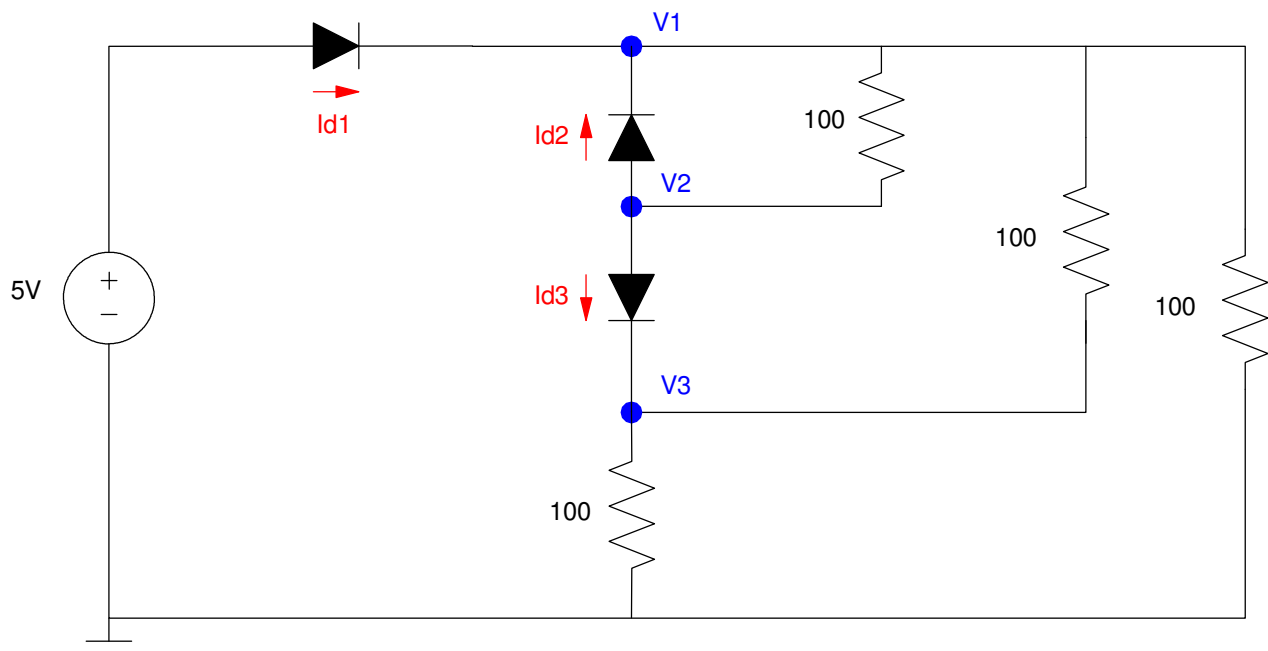

Problem 8-11. Change the resistors if you don't have four 100 Ohm resistors available