

ECE 320 - Quiz #2 - Name _____

Semiconductors, pn Junction, ideal diodes - Spring 2022

1a) What are holes and electrons?

Electrons: negatively charged particles that form covalent bonds and move around to carry current.

Holes: A missing electron in a covalent bond. A missing negative charge behaves like a positive charge.

1b) The voltage drop across a silicon diode is about 0.7V.

- Does this voltage go up or down as temperature goes up?
- Why does this happen?

Voltage goes down.

The voltage across a pn junction is a function of the doping level / the intrinsic carrier concentration level

$$V_d = V_T \cdot \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

As temperature goes up, the number of thermal holes and electrons (n_i) goes up. This makes the doping level less significant, making the diode pn-junction less distinct, reducing the voltage.

2) An 0603 resistor has the following dimensions

- $L = 0.06\text{cm}$
- $W = 0.03\text{cm}$
- $H = 0.02\text{cm}$

Determine the doping required to make a resistance of R ohms where

- $R = 1200 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.
- For example, May 14th would give $R = 1714$ Ohms

R 1200 + 100*(your birth month) + (your birth date)	Required Doping of Boron atoms / cc
1714	7.29e14

$$R = \left(\frac{\rho L}{A} \right)$$

$$1714\Omega = \left(\frac{\rho \cdot 0.06\text{cm}}{(0.03\text{cm})(0.02\text{cm})} \right)$$

$$\rho = 17.14 \Omega \cdot \text{cm}$$

$$\sigma = \frac{1}{\rho} = 0.0583 = n_n \cdot q \cdot \mu_n$$

$$0.0583 = n_n \cdot (1.6 \cdot 10^{-19}) \cdot (500)$$

$$n_n = 7.29 \cdot 10^{14} \frac{\text{atoms}}{\text{cc}}$$


3) Thermistors: Assume the VI characteristics of a thermistor are

$$R_T = 2000 \exp \left(\frac{4350}{T+273} - \frac{4350}{298} \right) \Omega$$

where T is the temperature in degrees C. Determine R_T and the temperature if $V_1 = 7.3V$

- Let R be $1200 + (\text{your birth month}) * 100 + \text{your birthday}$. (March 14th would give $R = 1714 \text{ Ohms}$)

R 1200 + 100*Month + Day	R_T (Ohms) Thermistor	Temperature (C)
1714 Ohms	2662 Ohms	19.27 C

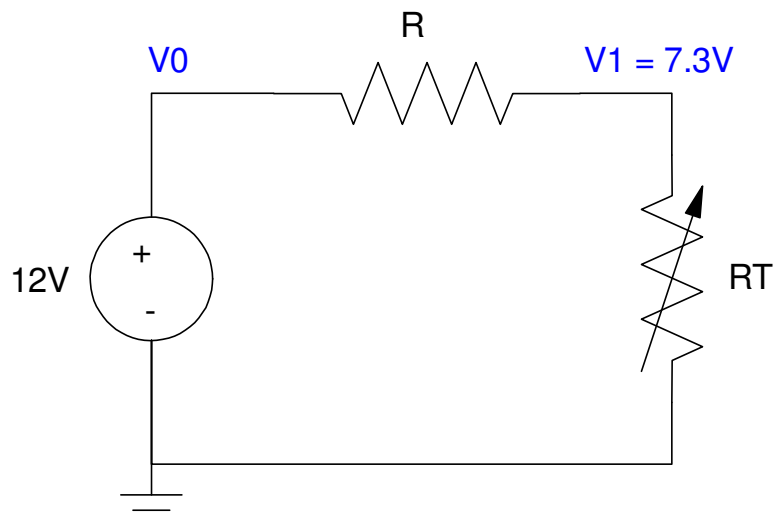

$$V_1 = 7.3V = \left(\frac{R_T}{R_T + 1714} \right) 12V$$

$$R_T = \left(\frac{7.3V}{12V - 7.3V} \right) 1714 \Omega$$


$$R_T = 2662.17 \Omega$$

$$T = 19.27^\circ C$$

4) Load Lines: The VI characteristic for a diode is show on the graph below. Draw the load line for the following circuit and from the graph, determine Vd and Id

- Let R be 1200 + 100*(Birth Month) + (Birthday)

R 1200 + 100*Month + Day	Load Line x-intercept	Load Lie y-intercept	Vd	Id
1714	10V	5.83mA	3.3V	3.8mA

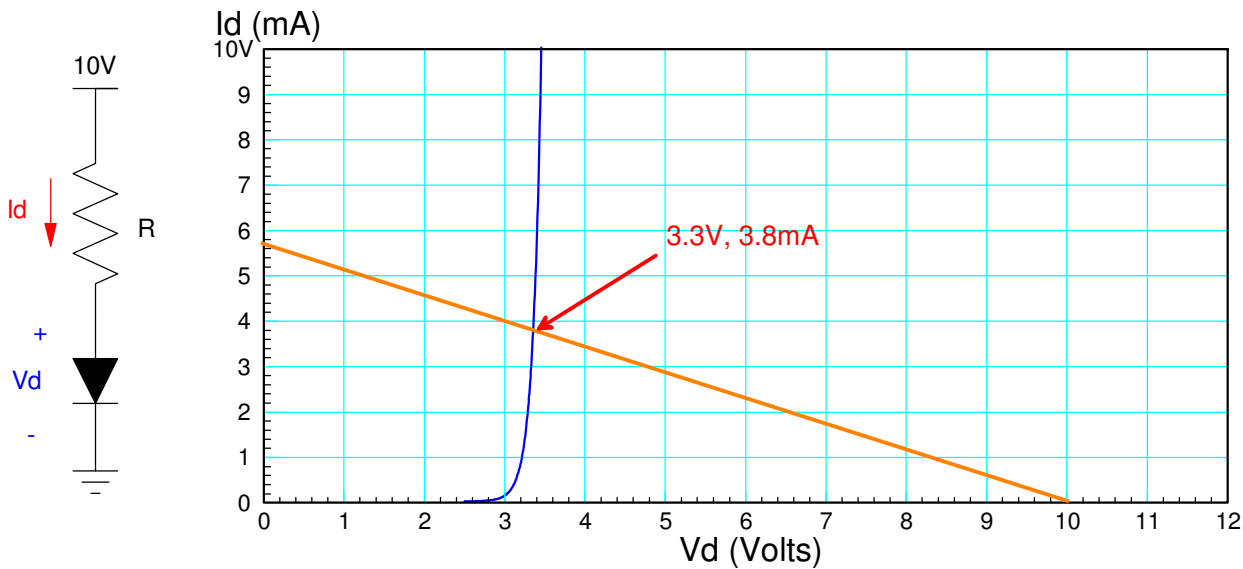

5) Diodes (nonlinear equations): Assume


- The VI characteristics of a diode are

$$I_d = 10^{-11} \cdot \left(\exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

- $R = 1200 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.

Write 7 equations to solve for 7 unknowns: $V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}$

- note: don't solve.

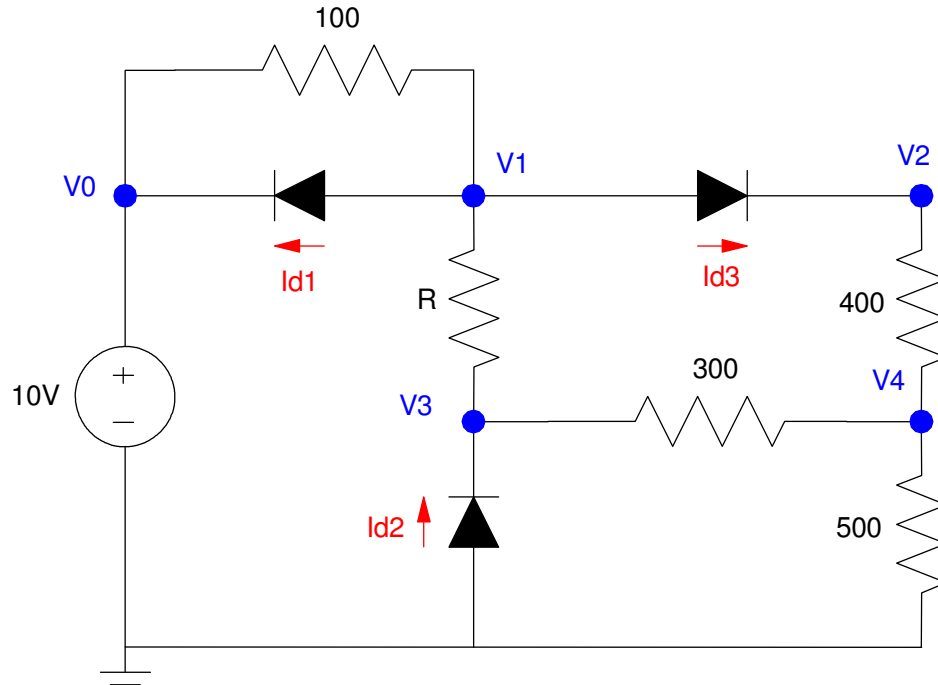

$$I_{d1} = 10^{-11} \cdot \left(\exp\left(\frac{V_1 - V_0}{0.038}\right) - 1 \right)$$

$$I_{d2} = 10^{-11} \cdot \left(\exp\left(\frac{0 - V_3}{0.038}\right) - 1 \right)$$

$$I_{d3} = 10^{-11} \cdot \left(\exp\left(\frac{V_1 - V_2}{0.038}\right) - 1 \right)$$

$$\left(\frac{V_1 - 10}{100} \right) + I_{d1} + \left(\frac{V_1 - V_3}{R} \right) + I_{d3} = 0$$

$$-I_{d3} + \left(\frac{V_2 - V_4}{400} \right) = 0$$

$$\left(\frac{V_3 - V_1}{R} \right) - I_{d2} + \left(\frac{V_3 - V_4}{300} \right) = 0$$

$$\left(\frac{V_4 - V_2}{400} \right) + \left(\frac{V_4 - V_3}{300} \right) + \left(\frac{V_4}{500} \right) = 0$$

6) Diodes (nonlinear equations): Assume


- The VI characteristics of a diode are

$$I_d = 10^{-11} \cdot \left(\exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

- $R = 1200 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.

Write 7 equations so solve for 7 unknowns: V_1 , V_2 , V_3 , I_{d1} , I_{d2} , I_{d3} , I_{d4}

- note: don't solve.

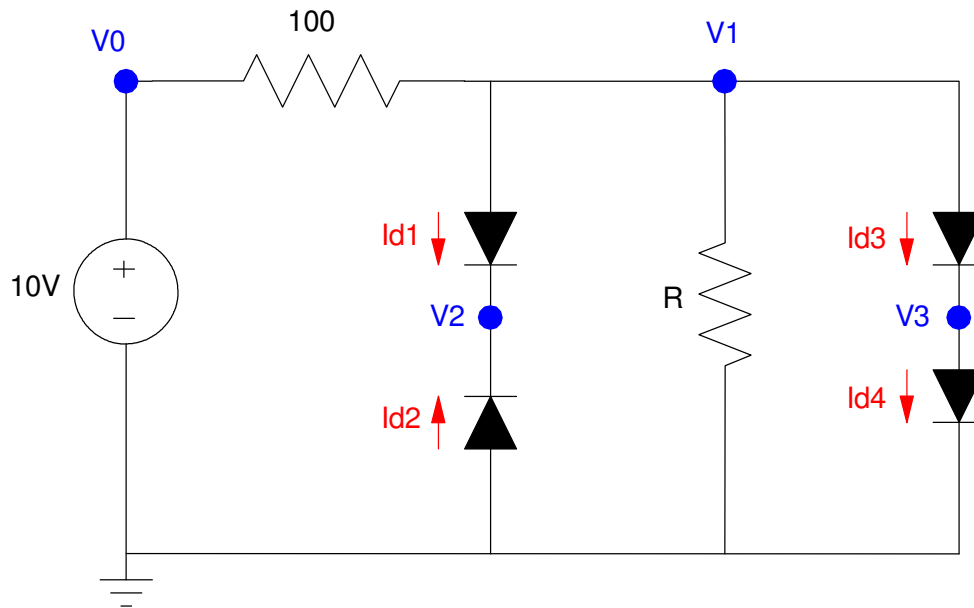

$$I_{d1} = 10^{-11} \cdot \left(\exp\left(\frac{V_1 - V_2}{0.038}\right) - 1 \right)$$

$$I_{d2} = \left(\exp\left(\frac{0 - V_2}{0.038}\right) - 1 \right)$$

$$I_{d3} = 10^{-11} \cdot \left(\exp\left(\frac{V_1 - V_3}{0.038}\right) - 1 \right)$$

$$I_{d4} = 10^{-11} \cdot \left(\exp\left(\frac{V_3 - 0}{0.038}\right) - 1 \right)$$

$$\left(\frac{V_1 - 10}{100} \right) + I_{d1} + \left(\frac{V_1}{R} \right) + I_{d3} = 0$$

$$I_{d1} = -I_{d2}$$

$$I_{d3} = I_{d4}$$

