


# ECE 320 - Homework #1

EE 206 Review, Phasors. Due Wednesday, January 19th

Please submit as a Word or pdf file if submitting on Blackboard or emailing to Jacob\_Glower@yahoo.com with subject ECE 320 HW#1

## Resistors in series and parallel

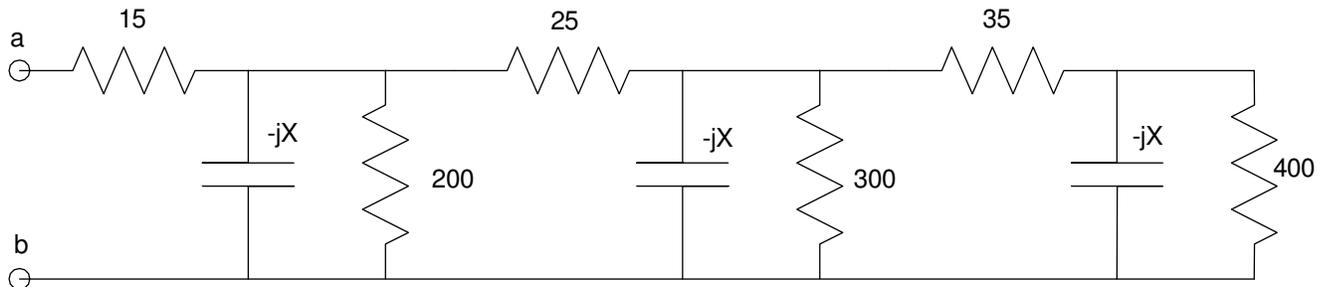1) Assume  $X = \text{infinity}$  (DC analysis). Determine the resistance  $R_{ab}$  (it will be a real number)



$$400 + 30 = 435 \text{ Ohms} \quad \text{series}$$

$$435 \parallel 300 = 177.55 \text{ Ohms} \quad \text{parallel}$$

$$177.55 + 25 = 202.55 \text{ Ohms} \quad \text{series}$$

$$202.55 \parallel 200 = 100.63 \text{ Ohms} \quad \text{parallel}$$

$$100.63 + 15 = 115.63 \text{ Ohms} \quad \text{series}$$

**ans: 115.63 Ohms**

2) Assume  $-jX = -j100$ . Determine the resistance  $R_{ab}$  (it will be a complex number)

$$400 \parallel -j100 = 23.529 - j94.118 \quad \text{parallel}$$

$$(23.529 - j94.118) + (35) = 58.529 - j94.118$$

$$(58.529 - j94.118) \parallel (300) \parallel (-j100) = 21.451 - j46.784$$

$$(21.451 - j46.784) + (25) = 46.451 - j46.784$$

$$(46.451 - j46.784) \parallel (200) \parallel (-j100) = 23.164 - j30.660$$


$$(23.164 - j30.660) + (15) = 38.164 - j30.660$$

**ans: 38.164 - j30.660**

## Voltage Nodes & Current Loops

3) (Voltage Nodes): For the following circuit

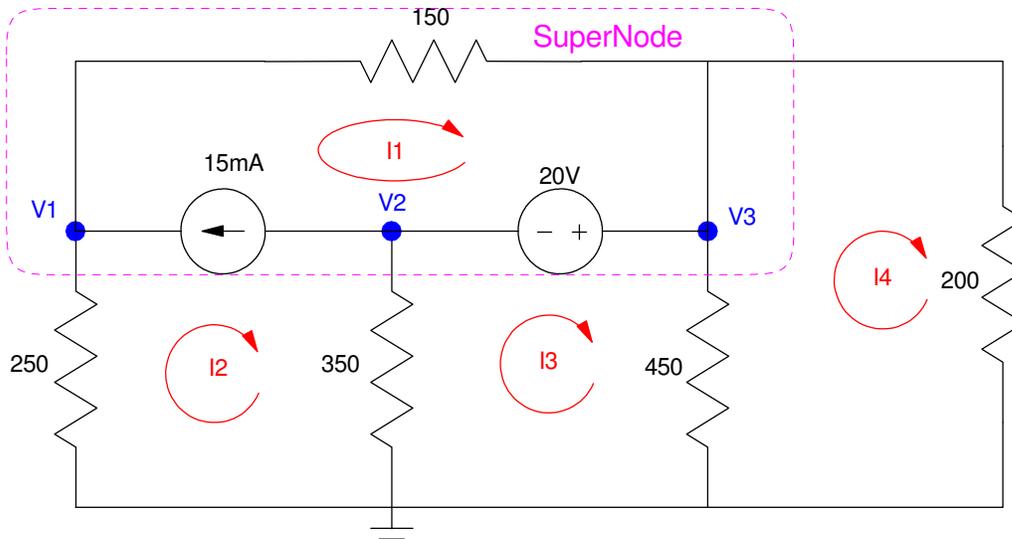- a) Write the voltage node equations
- b) Solve using Matlab (or similar program)
- c) Check your answers in CircuitLab (or similar circuit simulator)



Voltage Node Equations

$$V_3 - V_2 = 20$$

$$\left(\frac{V_1}{250}\right) - 15mA + \left(\frac{V_1 - V_3}{150}\right) = 0$$

SuperNode (others also work)

$$\left(\frac{V_1}{250}\right) + \left(\frac{V_2}{350}\right) + \left(\frac{V_3}{450}\right) + \left(\frac{V_3}{200}\right) = 0$$

Group terms

$$V_3 - V_2 = 20$$

$$\left(\frac{1}{250} + \frac{1}{150}\right)V_1 - \left(\frac{1}{150}\right)V_3 = 15mA$$

$$\left(\frac{1}{250}\right)V_1 + \left(\frac{1}{350}\right)V_2 + \left(\frac{1}{450} + \frac{1}{200}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 0 & -1 & 1 \\ \left(\frac{1}{250} + \frac{1}{150}\right) & 0 & \left(\frac{-1}{150}\right) \\ \left(\frac{1}{250}\right) & \left(\frac{1}{350}\right) & \left(\frac{1}{450} + \frac{1}{200}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0.015 \\ 0 \end{bmatrix}$$

## Solve using Matlab

```
>> A = [0,-1,1 ; 1/250+1/150,0,-1/150 ; 1/250,1/350,1/450+1/200]
```

```
      0   -1.0000    1.0000
  0.0107    0   -0.0067
  0.0040    0.0029    0.0072
```

```
>> B = [20;0.015;0]
```



```
20.0000
 0.0150
 0
```

```
>> V = inv(A)*B
```

```
V1    3.9659
V2   -15.9046
V3    4.0954
```


>>

Check in CircuitLab: The answers match

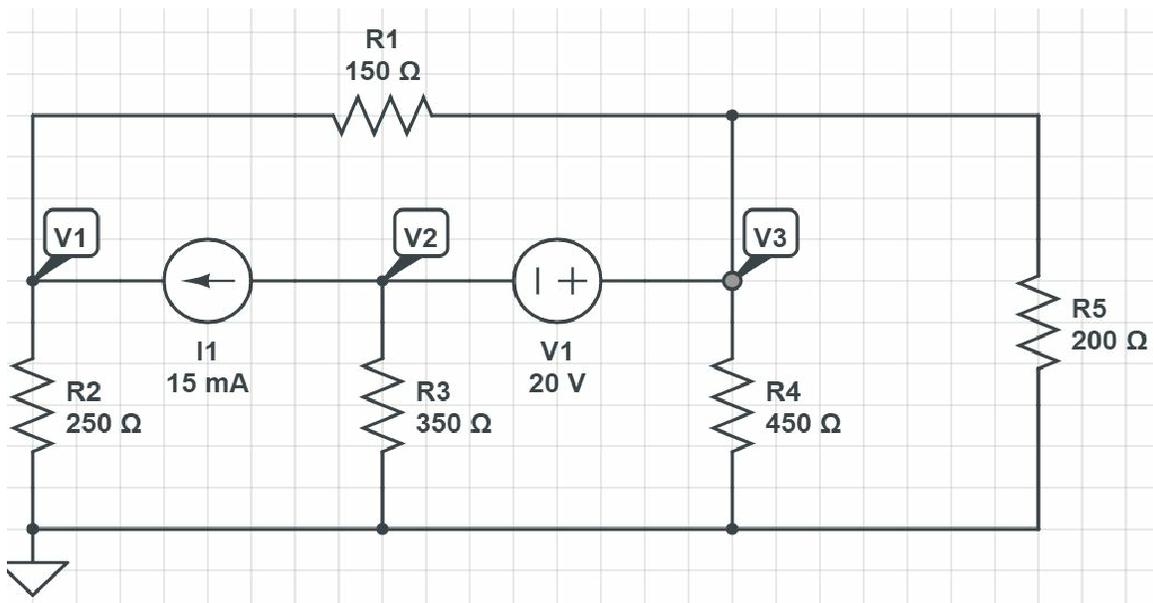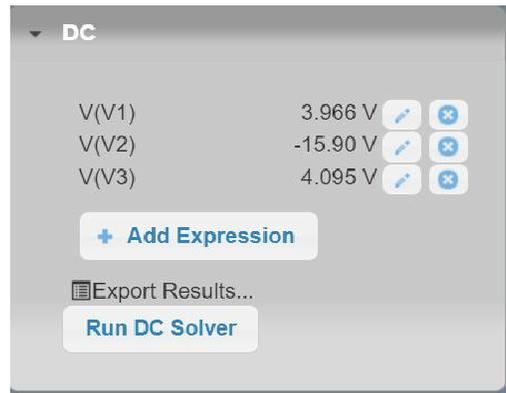

4) (Current Loops) For the following circuit

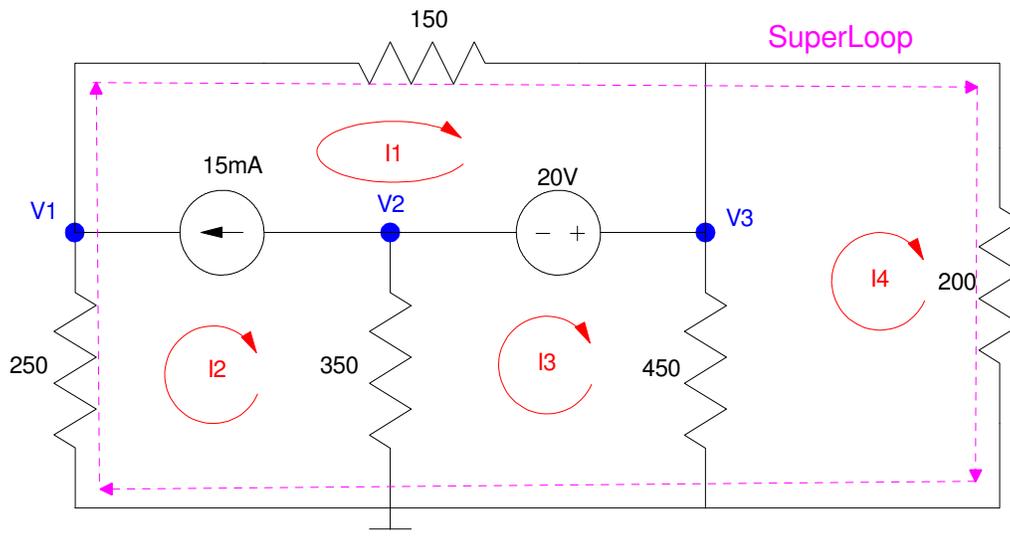- a) Write the current loop equations
- b) Solve using Matlab (or similar program)
- c) Check your answers in CircuitLab (or similar circuit simulator)



Problem 3 & 4

$$I_1 - I_2 = 15mA$$

$$350(I_3 - I_2) - 20 + 450(I_3 - I_4) = 0$$

$$450(I_4 - I_3) + 200I_4 = 0$$

SuperLoop ( other superloops also work)

$$250I_2 + 150I_1 + 200I_4 = 0$$

Group terms

$$I_1 - I_2 = 15mA$$

$$-350I_2 + 800I_3 - 450I_4 = 20$$

$$-450I_3 + 650I_4 = 0$$

$$250I_2 + 150I_1 + 200I_4 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & -350 & 800 & -450 \\ 0 & 0 & -450 & 650 \\ 150 & 250 & 0 & 200 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0.015 \\ 20 \\ 0 \\ 0 \end{bmatrix}$$

## Solve

```
>> A = [1,-1,0,0 ; 0,-350,800,-450 ; 0,0,-450,650 ; 150,250,0,200]
```

```
    1    -1     0     0
    0  -350   800  -450
    0     0  -450   650
   150   250     0   200
```

```
>> B = [0.015 ; 20 ; 0 ; 0]
```


```
    0.0150
   20.0000
     0
     0
```

```
>> I = inv(A)*B
```

```
I1   -0.0009
I2   -0.0159
I3    0.0296
I4    0.0205
```
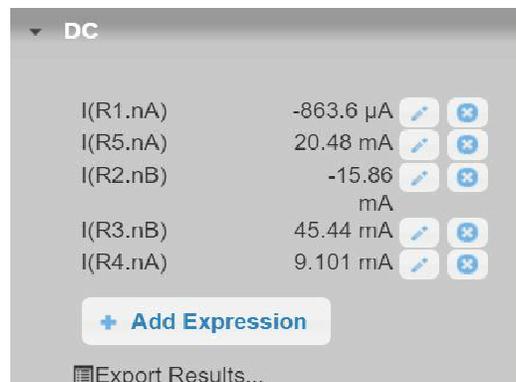
## Check in CircuitLab


- I1 is the current through R1 (-863.6 $\mu$ A = -0.0009A rounded)
- I2 is the current through R2 (-15.86mA rounded to -15.9mA)
- I4 is the current through R5 (20.48mA rounded to 20.5mA)
- (I3 - I4) is the current through R4 (9.101mA)



5) Assume  $V_{in}$  contains a DC and 400 rad/sec (63.66Hz) signal:

$$V_{in} = 10 + 6 \cos(450t) + 4 \sin(450t)$$

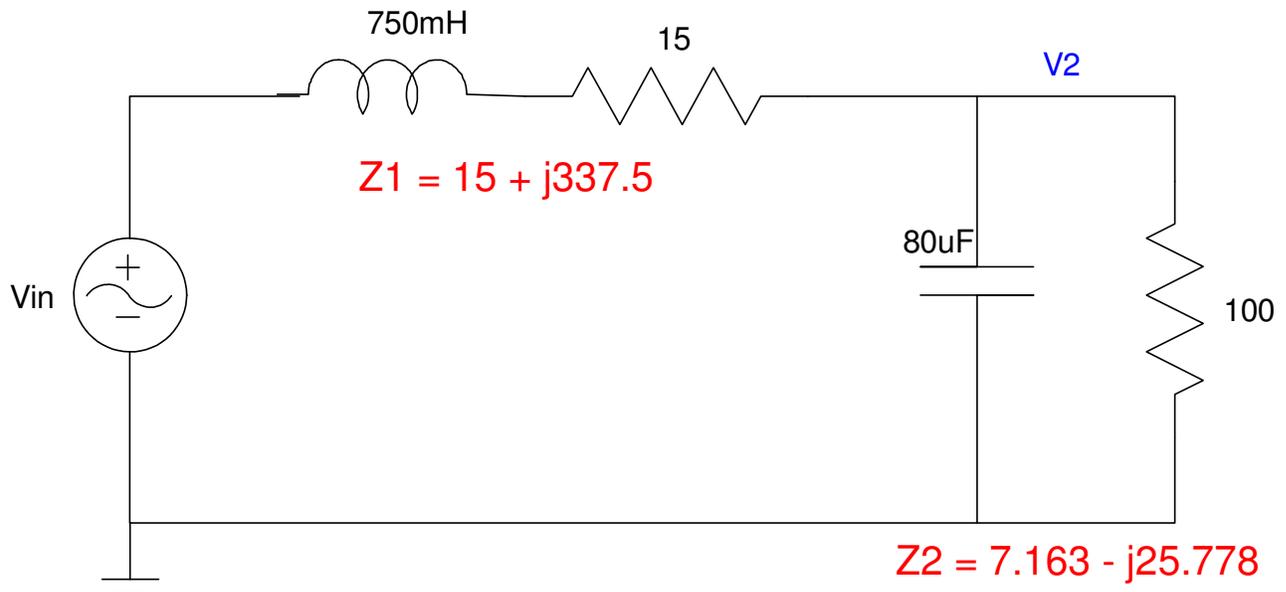- a) Determine the voltage,  $V_2$ , using phasor analysis
- b) Check your answer using CircuitLab (or similar program)



Use superposition: treat this as two separate problems

- $V_{in} = 10$
- $V_{in} = 6 \cos(450t) + 4 \sin(450t)$

DC:  $V_{in} = 10$

$$L = 0$$

$$C = \text{infinity}$$

$$V_2 = \left( \frac{100}{100+15} \right) 10 = 8.696V$$

AC:  $V_{in} = 6 \cos(450t) + 4 \sin(450t)$

$$\omega = 450$$

$$L \rightarrow j\omega L = j337.5\Omega$$

$$C \rightarrow \frac{1}{j\omega C} = -j27.778\Omega$$

$$V_{in} \rightarrow 6 - j4 \quad \text{real} = \text{cosine}, \text{-imag} = \text{sine}$$

$$(100\Omega) \parallel (-j27.778\Omega) = (7.163 - j25.788)\Omega$$

$$V_2 = \left( \frac{Z_2}{Z_1 + Z_2} \right) V_{in}$$

$$V_2 = \left( \frac{(7.163-j25.778)}{(7.163-j25.778)+(15+j337.5)} \right) (6-j4) = -0.599 + j0.150$$

$$V_2 = -0.599 + j0.150$$

or in polar form

$$V_2 = 0.618 \angle 165.9^\circ$$

### Check in CircuitLab

The voltage source is 450 rad/sec

$$f = \frac{\omega}{2\pi} = \frac{450}{2\pi} = 71.62 \text{ Hz}$$

The amplitude using cosine as the base function is:


$$V_{in} = 6 - j4 = 7.211 \angle -33.69^\circ$$

$$V_{in} = 7.211 \cos(450t - 33.69^\circ)$$


CircuitLab uses sine-waves as the reference

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$
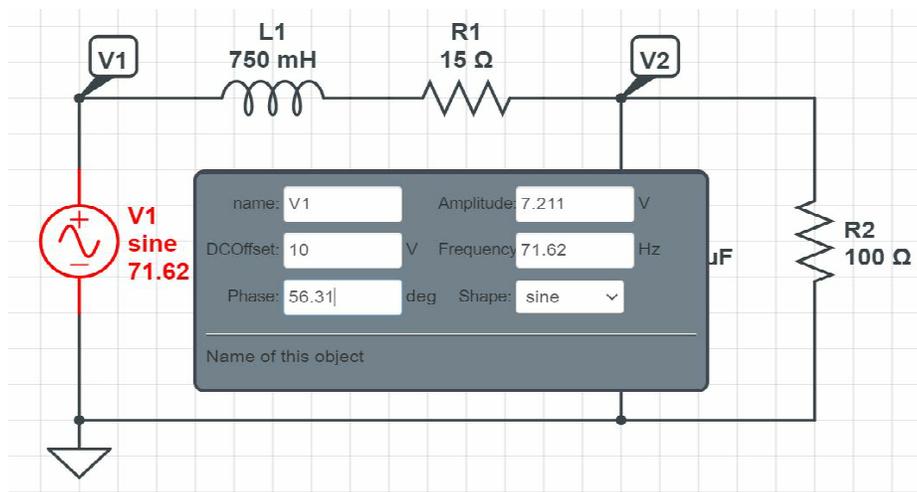
$$V_{in} = 7.211 \sin(450t + 56.31^\circ)$$



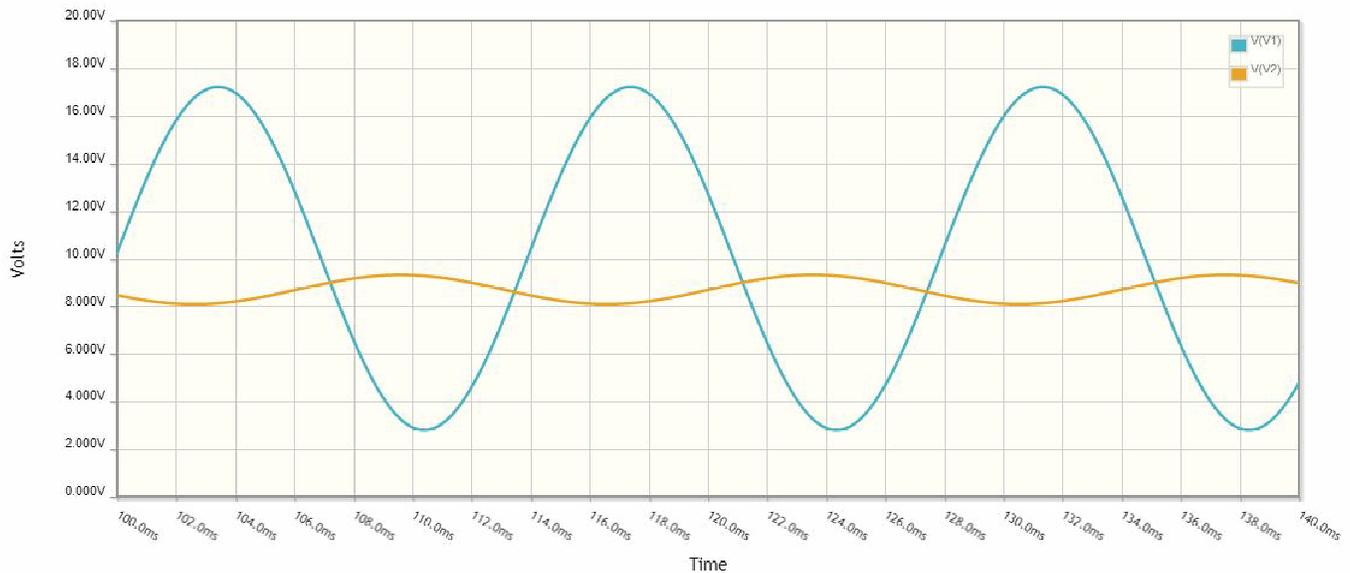Running a Time Domain simulation from 100ms to 140ms (3 cycles at 71Hz) gives



V1 (blue) & V2 (orange)

Checking the results:

- $\max(V2) = 9.311V$
- $\min(V2) = 8.079V$

DC

$$DC = \left( \frac{\max + \min}{2} \right) = 8.695V$$

$$\text{calculated} = 8.696V$$

AC

$$\begin{aligned} AC &= (\max - \min) = 1.232V_{pp} \\ &= 0.616V_p \\ &= 0.436V_{rms} \end{aligned}$$

Calculations were

$$V_2 = 0.618 \angle 165.9^\circ$$

This is the peak voltage ( 0.616V<sub>p</sub> vs. 0.618V<sub>p</sub> )

The phase shows up in the time delay

$$V_1 = 7.211 \angle -33.69^\circ$$

$$V_2 = 0.618 \angle 165.9^\circ = 0.618 \angle -194.1^\circ$$

V2 is delayed by 160.4 degrees from V1 (shows up in the graph)

