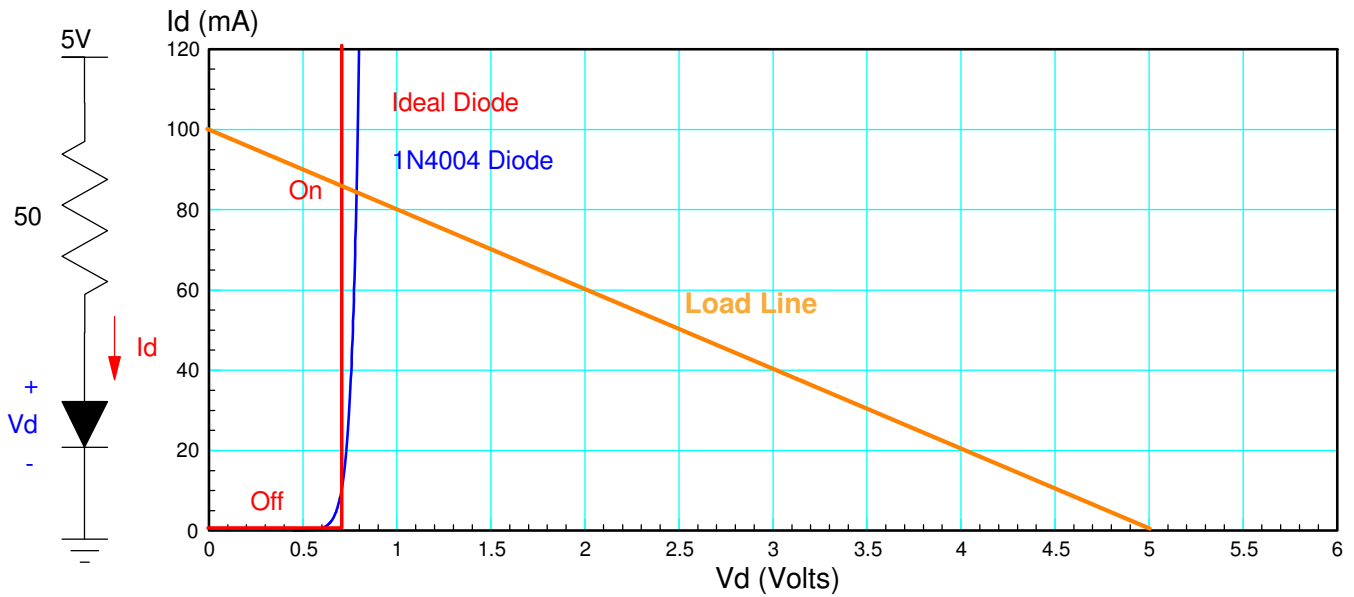


# ECE 320 - Homework #3

Ideal Diodes, LEDs, AC to DC Converters. Due Monday, January 31st

## Ideal Diodes:

1) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages and currents for the following circuit



The diode is probably on (more than 0.7V is applied), meaning

$$V_d = 0.7V$$

$$I_d = \left( \frac{5V - 0.7V}{50\Omega} \right) = 86.0mA$$


Note

- The results are close to what we found in homework #2, but
- Ideal diode model is *much* easier to use

	$V_d$	$I_d$
HW3: Ideal Diode	700mV	86.00mA
HW2) Graphical solution	800mV	85mA
HW2) Numeric Solution	821.1mV	83.58mA
HW2) Simulation (CircuitLab)	779.1mV	84.42mA
HW2) Lab (experimental)	757mV	83.20mA

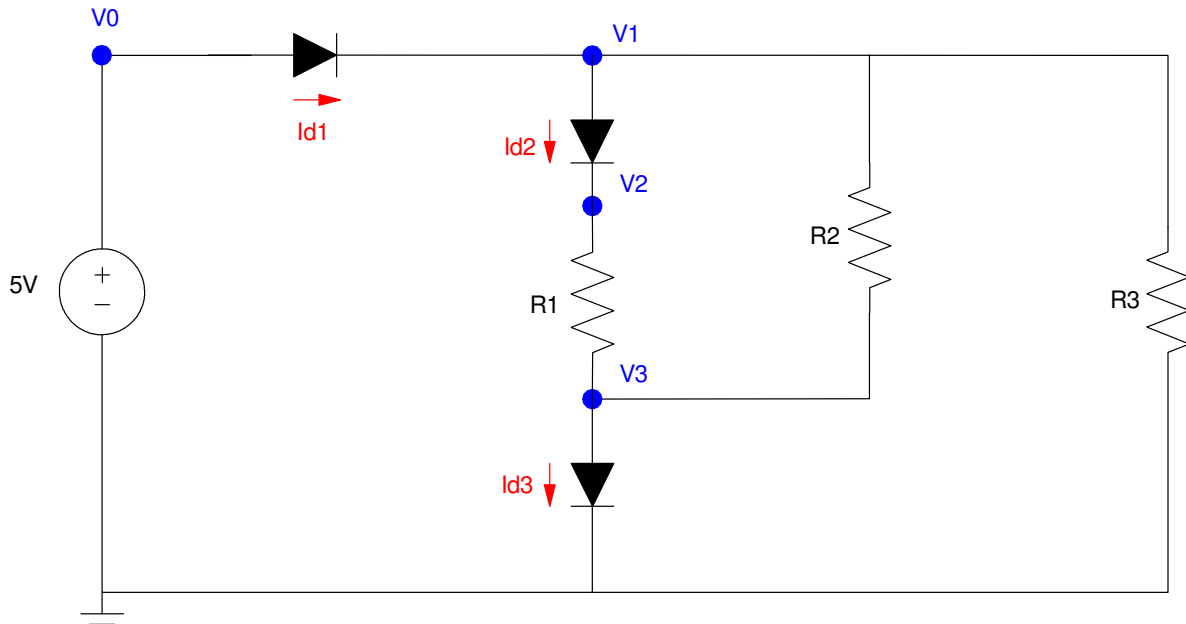2) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages and currents for the following circuit

- $R_1, R_2, R_3$  are the same that you used in homework #2



There are eight permutations of on & off. Assume

- $D_1, D_3$  are on
- $D_2$  is off

this gives

$$V_0 = 5V$$

$$V_1 = V_0 - 0.7V = 4.3V$$

$$V_2 = V_1 - 0.7V = 3.6V$$

$$V_3 = 0.7V$$

Comparing to homework #1

- The ideal diode model is close but a little off

	V0	V1	V2	V3
Ideal Diode	5.00V	4.30V	3.60V	700mV
Numeric Solution	5.00V	4.1955V	3.4172V	801.8mV
Simulation (CircuitLab)	5.00V	4.229V	3.494V	758.5mV
Lab (experimental)	4.92V	4.14V	3.40V	755mV

## LEDs

The specifications for a Piranah RGB LED are

Color	Vf @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

3) Design a circuit to drive these LEDs with a 5V source to produce olive green:

- Red = 6901 mcd (176/255)
- Green = 7686 mcd (196/255)
- Blue = 2313 mcd (59/255)

Current is proportional to brightness

$$I_r = \left( \frac{6901 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 13.802 \text{ mA}$$


$$R_r = \left( \frac{5 \text{ V} - 2.0 \text{ V}}{13.802 \text{ mA}} \right) = 311.5 \Omega$$

$$I_g = \left( \frac{7686 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 15.372 \text{ mA}$$

$$R_g = \left( \frac{5 \text{ V} - 3.2 \text{ V}}{15.372 \text{ mA}} \right) = 117.1 \Omega$$

$$I_b = \left( \frac{2313 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 4.626 \text{ mA}$$
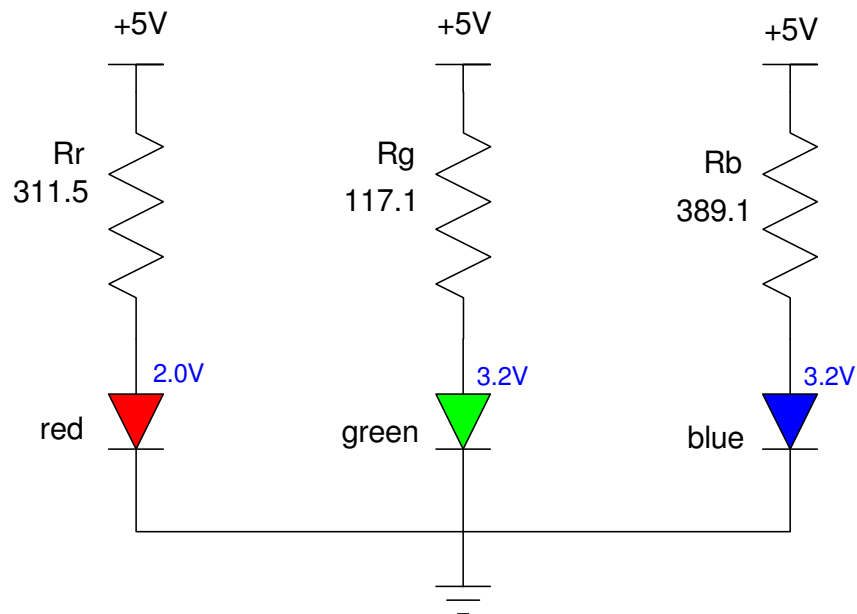
$$R_b = \left( \frac{5 \text{ V} - 3.2 \text{ V}}{4.626 \text{ mA}} \right) = 389.1 \Omega$$



4) Design a circuit to drive these LEDs with a 5V source producing salmon pink:

- Red = 6666 mcd (170/255)
- Green = 3333 mcd (85/255)
- Blue = 5490 mcd (140/255)

$$I_r = \left( \frac{6666 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 13.333 \text{ mA}$$

$$R_r = \left( \frac{5\text{V} - 2.0\text{V}}{13.333 \text{ mA}} \right) = 225.0 \Omega$$

$$I_g = \left( \frac{3333 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 6.667 \text{ mA}$$


$$R_g = \left( \frac{5\text{V} - 3.2\text{V}}{6.667 \text{ mA}} \right) = 270.0 \Omega$$

$$I_b = \left( \frac{5490 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 10.98 \text{ mA}$$

$$R_b = \left( \frac{5\text{V} - 3.2\text{V}}{10.980 \text{ mA}} \right) = 163.9 \Omega$$

Other colors can be obtained from

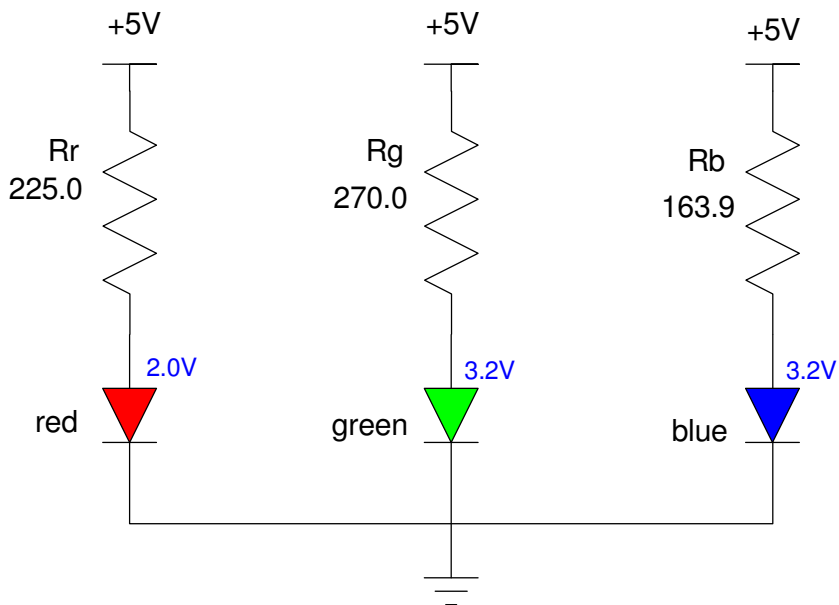
<https://www.rapidtables.com/web/color/color-wheel.html>



## AC to DC Converters

For the circuit below:

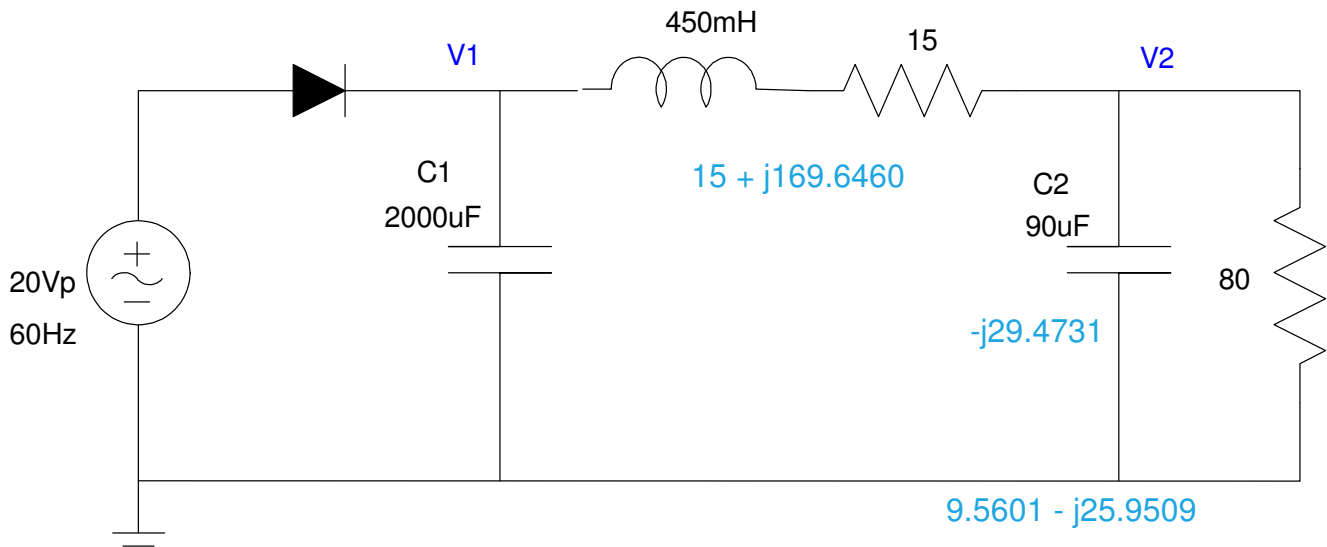5) Determine the voltages at V1 and V2 (DC and AC)



V1:

$$\max(V1) = 19.3V$$

$$I \approx \left( \frac{19.3V}{80\Omega + 15\Omega} \right) = 203.2mA \quad \text{worst case}$$

$$I = C \frac{dV}{dt}$$

$$203.2mA = 2000\mu F \cdot \left( \frac{dV}{1/60s} \right)$$

$$dV = 1.6930V$$

$$V_1(AC) = 1.6930V_{pp}$$

$$V_1(DC) = 19.3V - \frac{1}{2}V_{1pp} = 18.45V$$

V2:

$$V_2(DC) = \left( \frac{80\Omega}{80\Omega + 15\Omega} \right) \cdot V_1(DC)$$

$$V_2(DC) = 15.5398V$$

$$V_2(AC) = \left( \frac{(9.5607 - j25.9509)}{(9.5607 - j25.9509) + (15 + j169.6460)} \right) \cdot V_1(AC)$$

$$|V_2(AC)| = 0.3232V_{pp}$$

6) Build the circuit in CircuitLab (or similar program) and verify your calculations for problem #5


From CircuitLab


- $\max(V1) = 19.11V$
- $\min(V1) = 17.62V$
- $\max(V2) = 15.56V$
- $\min(V2) = 15.37V$

$DC = (\max + \min)/2$

$AC = (\max - \min) Vpp$

	V1		V2	
	DC	AC	DC	AC
Calculated	18.45V	1.693Vpp	15.5398V	0.3232Vpp
Simulated	18.365V	1.490Vpp	15.465V	0.190Vpp

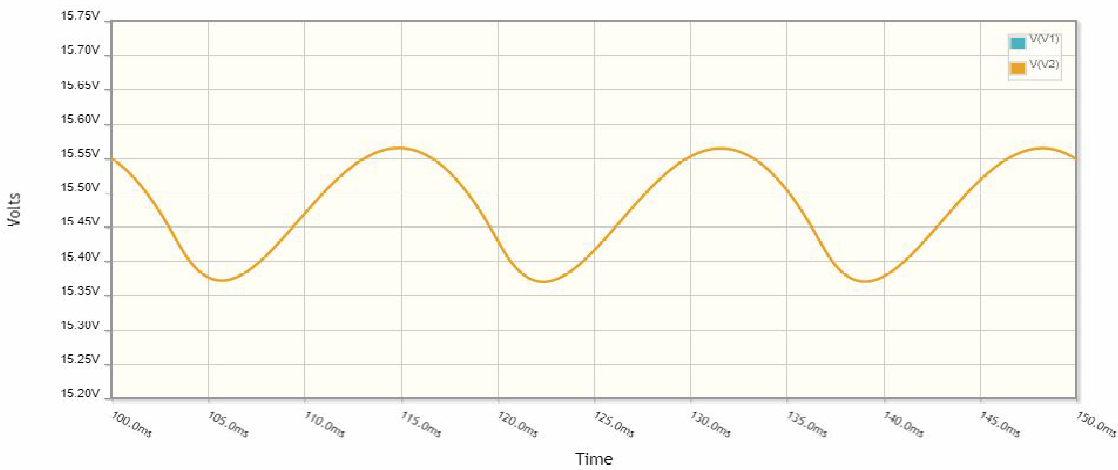

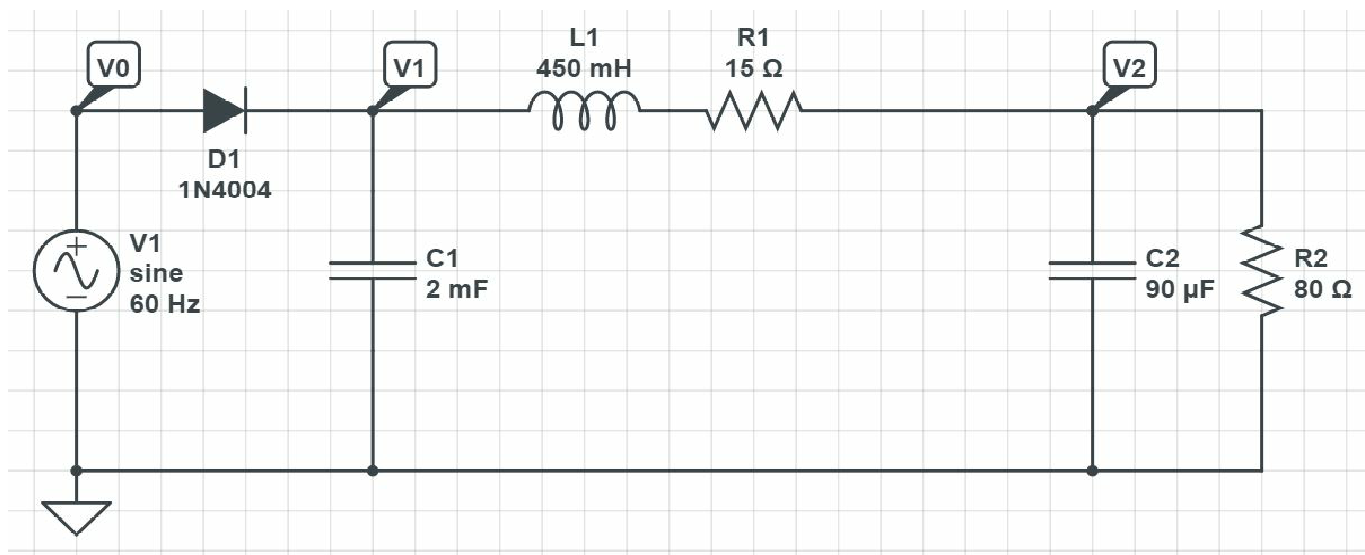

Problem 6: CircuitLab Simulation

7) Determine C1 and C2 so that AC voltages are:  $V_1 = 2V_{pp}$  and  $V_2 = 250mV_{pp}$ .

$$V_1(AC) = 2V_{pp}$$

$$\max(V_1) = 19.3V$$

$$V_1(DC) = 19.3V - \frac{1}{2}V_1(AC)$$

$$V_1(DC) = 18.3V$$

$$I = \left( \frac{18.3V}{80\Omega + 15\Omega} \right) = 192.6mA$$

$$I = C \frac{dV}{dt}$$

$$192.6mA = C_1 \left( \frac{2V_{pp}}{1/60s} \right)$$

$$C_1 = 1605\mu F$$

Assume  $C_2 = 0$


$$V_2(AC) = \left( \frac{80\Omega}{(80\Omega) + (15 + j169.64)} \right) (2V_{pp})$$

$$|V_2(AC)| = 822.9mV_{pp}$$

For the ripple to be 250mVpp

$$\left| \frac{1}{j\omega C_2} \right| \approx \left( \frac{250mV}{822.9mV} \right) \cdot 80\Omega = 24.3037\Omega$$

$$C_2 = 109.1\mu F$$

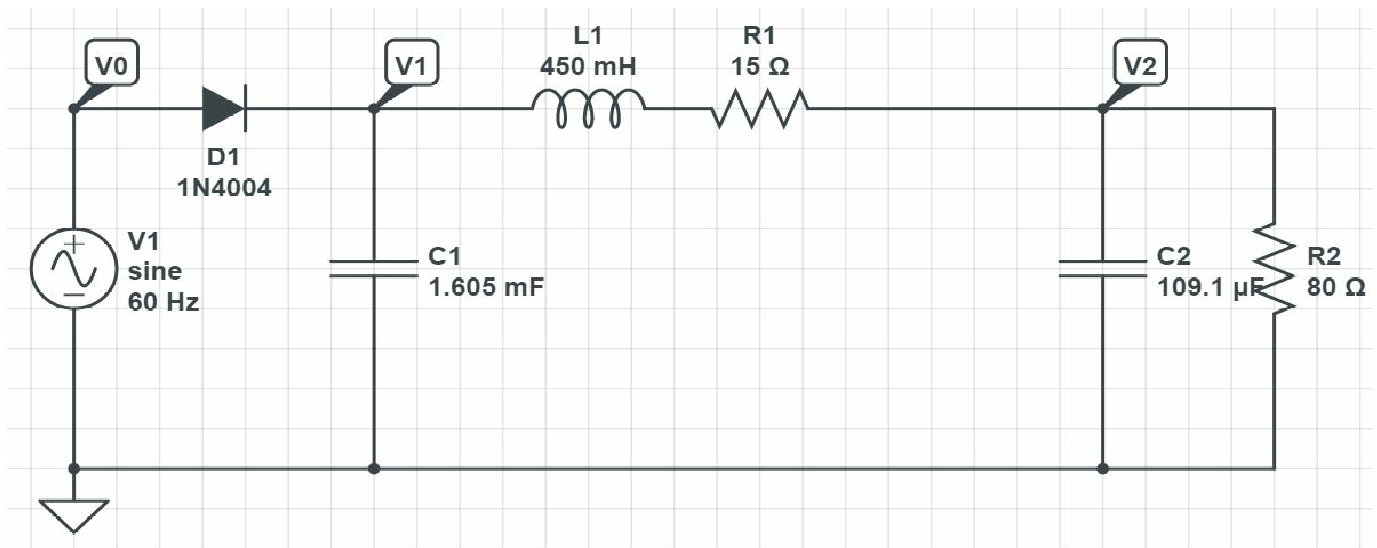

8) Build this circuit in CircuitLab (or similar program) and verify your calculations for problem #7

From CircuitLab

- $\max(V1) = 19.12V$
- $\min(V1) = 17.30V$
- $\max(V2) = 15.44V$
- $\min(V2) = 15.24V$

	V1		V2	
	DC	AC	DC	AC
Calculated	18.30V	2.000Vpp	15.41V	250mVpp
Simulated	18.21V	1.820Vpp	15.34V	200mVpp

