

# ECE 320 - Homework #5

555 Timers, Transistors used as a Switch, Schmitt Triggers. Due Monday, February 13th

Please submit as a hard copy or submit on BlackBoard

Assume a 3904 transistor (NPN) and 3906 (PNP) (\$0.04 each)

$$\beta = 100 \quad \min(|V_{ce}|) = 0.2V \quad \max(I_c) = 200mA$$

Assume a thermistor with


$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

## 555 Timers

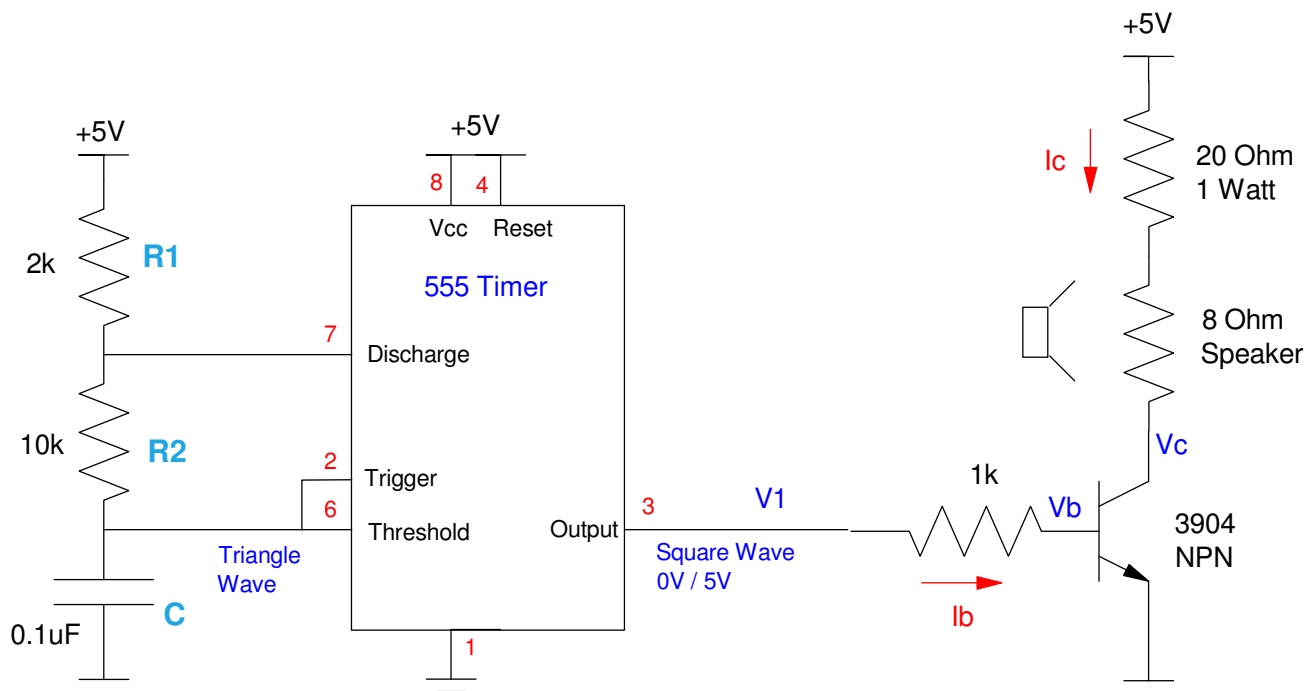1) Determine the on and off times for the voltage at V2 for following 555-timer circuit

$$T_{on} = (R_1 + R_2) \cdot C \cdot \ln(2) = 831.8\mu s$$

$$T_{off} = R_2 \cdot C \cdot \ln(2) = 693.1\mu s$$



2) Simulate this circuit in CircuitLab and verify the on and off times

From CircuitLab



- $t(\text{on}) = 11.30\text{ms}$
- $t(\text{off}) = 12.13\text{ms}$
- $t(\text{on}) = 12.84\text{ms}$

The on time is 830us

- 831.8us calculated

The off time is 710us

- 693.1us calculated

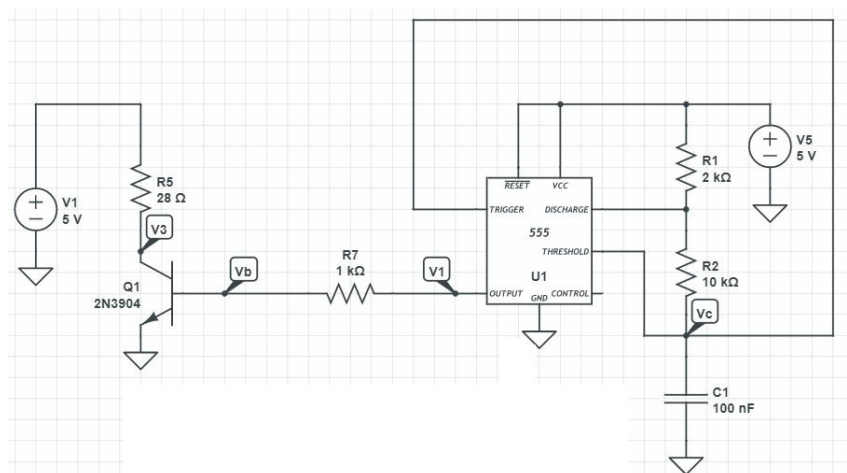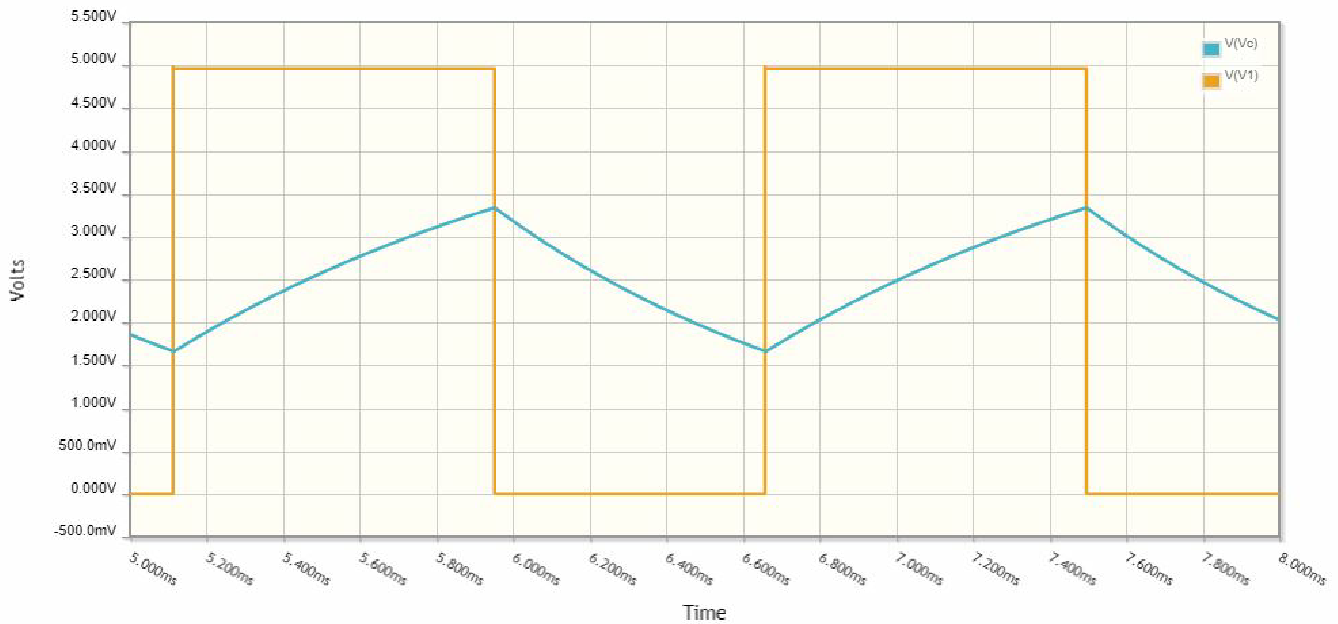

## Transistor Switch

3) Determine the voltages  $\{V_b, V_c\}$  and currents  $\{I_b, I_c\}$  when

**V1 = 0V**

- $V_b = 0V$
- $I_b = I_c = 0mA$
- $V_c = 5V$


**V1 = 5V**

$$V_b = 0.7V$$

$$V_c = 0.2V$$

$$I_b = \left( \frac{5V - 0.7V}{1k} \right) = 4.3mA$$
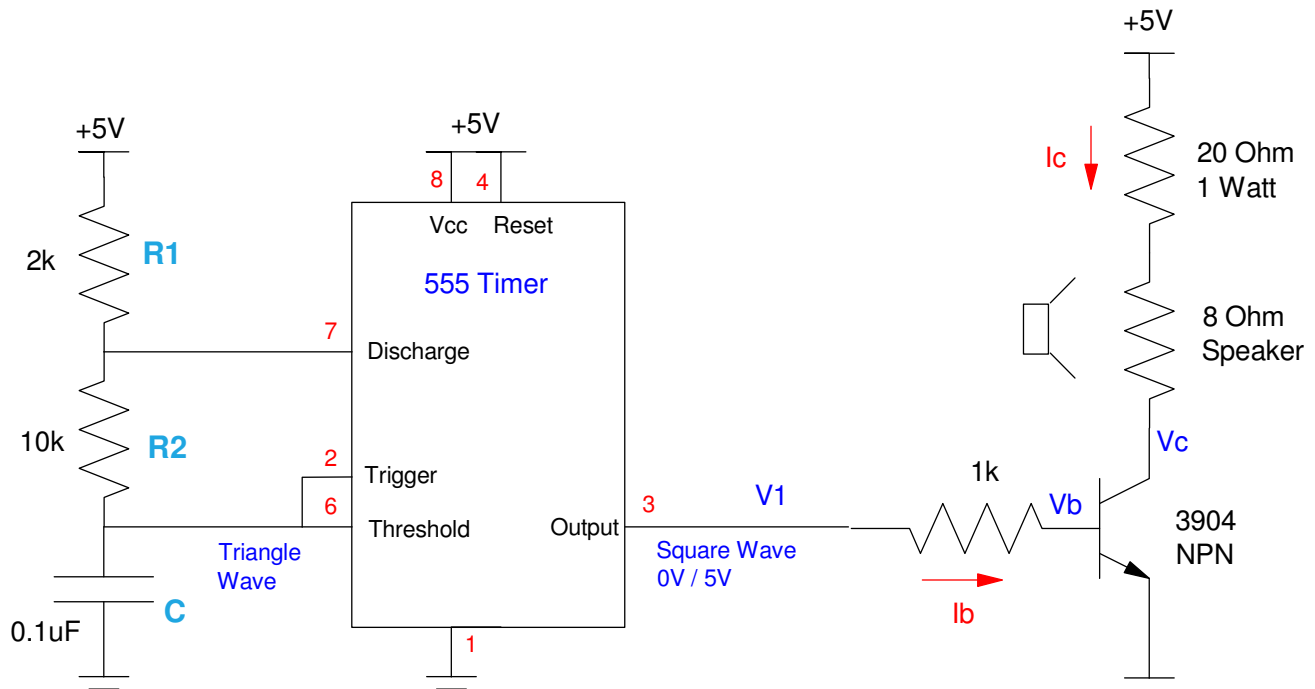
$$I_c = \left( \frac{5V - 0.2V}{28\Omega} \right) = 153.6mA$$



4) Verify your calculations using CircuitLab

### **Vout = 5V (on)**

$V_b = 836.1\text{mV}$

- vs. 700mV computed

$V_c = 241.7\text{mV}$

- vs. 200mV computed



### **Vout = 0V**

$V_b = 0.00\text{V}$

- vs. 0V

$V_c = 5.00\text{V}$

- vs 5.00V

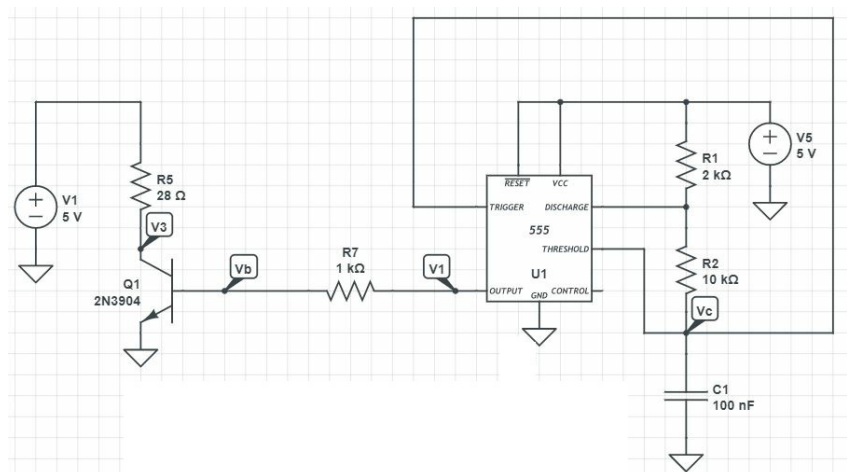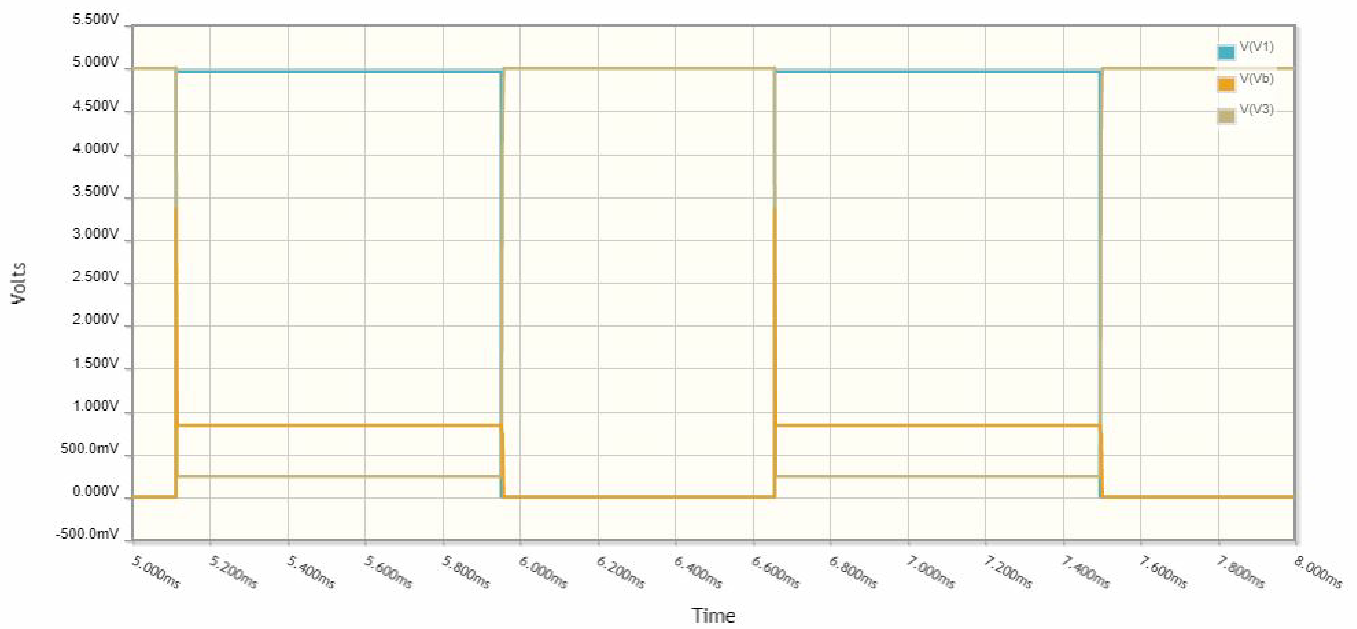

## Comparitor


## Add an electronic switch to turn the speaker on and off

5) Design a comparitor (shown in blue - don't add the red resistors (they are for a Schmitt trigger) ) to

- Turn on the speaker ( $V_3 = 5V$ ) when  $T > 50C$ , and
- Turn off the speaker ( $V_3 = 0V$ ) when  $T < 50C$

50C corresponds to 362.7 Ohms. Assuming a 330 Ohm resistor for the voltage divider
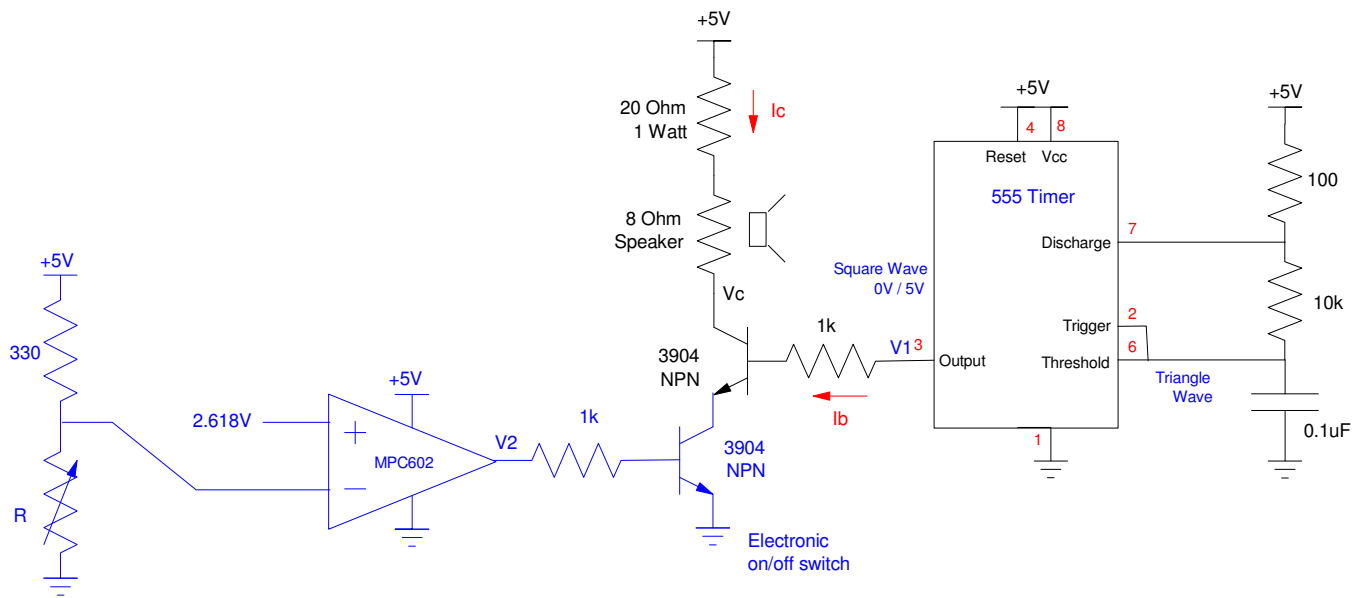
$$V = \left( \frac{362.7}{362.7 + 330} \right) 5V = 2.618V$$




6) Simulate the comparator in CircuitLab to verify the on / off temperature (or resistance or voltage)

- use a voltage source (V4) to simulate the voltage at the voltage divider)


From Circuitlab

$V(\text{off}) = 2.623\text{V}$  (vs.  $2.618\text{V}$  computed)

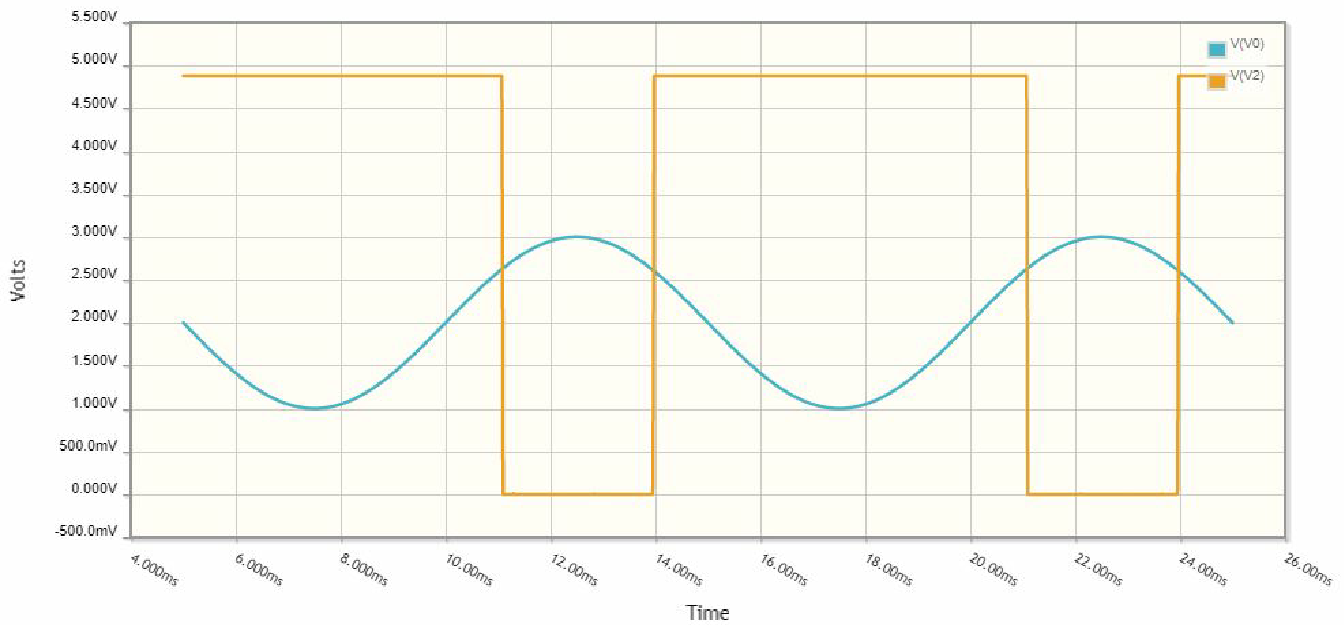$V(\text{on}) = 2.610\text{V}$  (vs.  $2.618\text{V}$  computed)



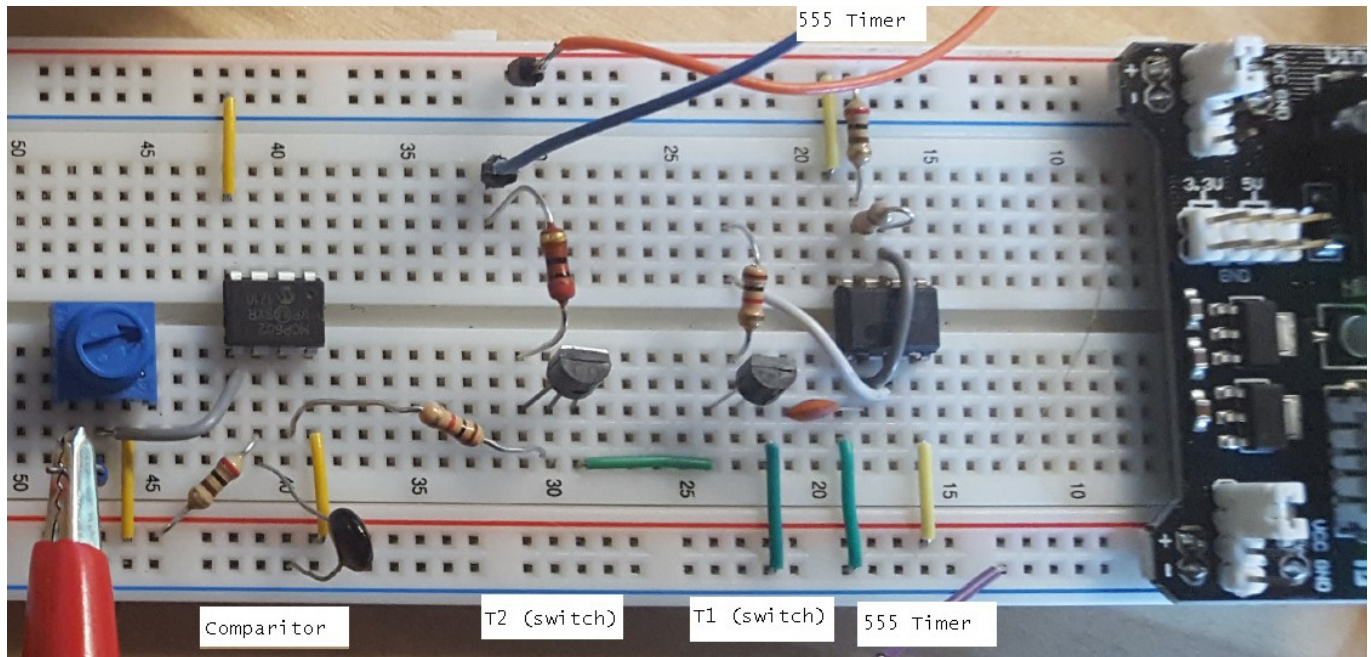7) Build this circuit and verify it's on and off temperature (or voltage or resistance. Replace R with a potentiometer for test purposes)



$V_p = 2.00V$  (set with a potentiometer)

- Turns on at 1.99V
- Turns off at 2.08V

Note that for a comparator,  $V(\text{on}) = V(\text{off})$  (approximately)

## Schmitt Trigger

Add an electronic switch to turn the speaker on and off

8) Design a Schmitt Trigger (modify section in blue) to

- Turn on the speaker (V3 = 5V) when T > 55C, and
- Turn off the speaker (V3 = 0V) when T < 45C

55C (on)

$$R = 301.6 \text{ Ohms}$$

$$V_a = 2.388V$$

45C (off)

$$R = 438.6 \text{ Ohms}$$

$$V_a = 2.853V$$

$V(\text{on}) < V(\text{off})$

connect to the minus input


$V(\text{on}) = 2.388V$

make the offset 2.388V

Gain:

$$\text{gain} = \left( \frac{5V - 0V}{2.853V - 2.388V} \right) = 10.74$$

Pick the resistors in a 10.74 : 1 ratio

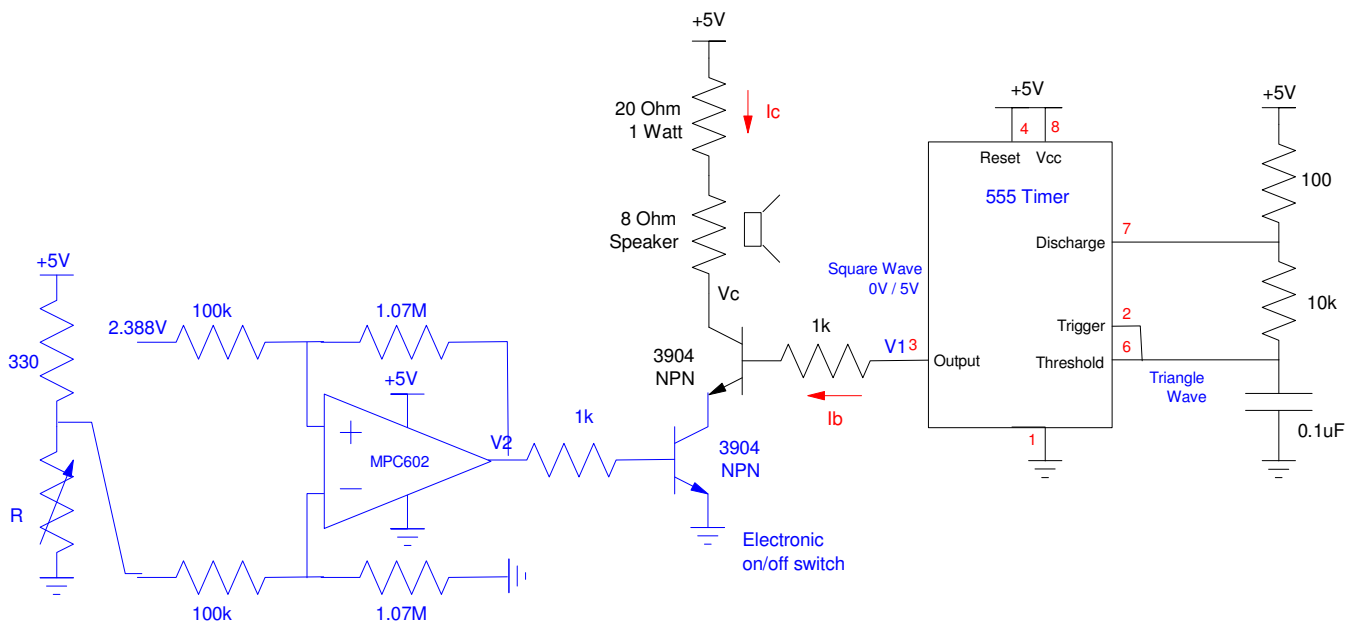



9) Simulate the comprior in CircuitLab to verify the on / off temperature (or ressitance or voltage)


- use a voltage source (V4) to simulate the voltage at the voltage divider)

$V(\text{off}) = 2.852\text{V}$


vs.  $2.853\text{V}$  computed

$V(\text{on}) = 2.349\text{V}$

vs.  $2.388\text{V}$  computed

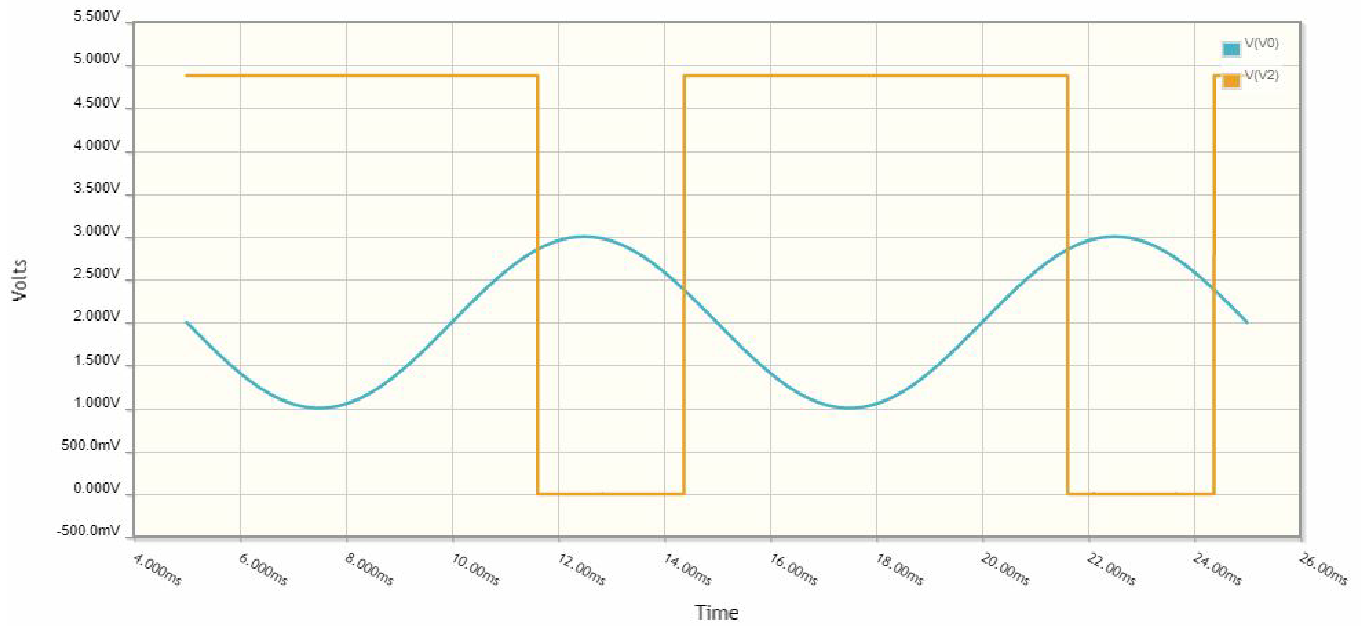

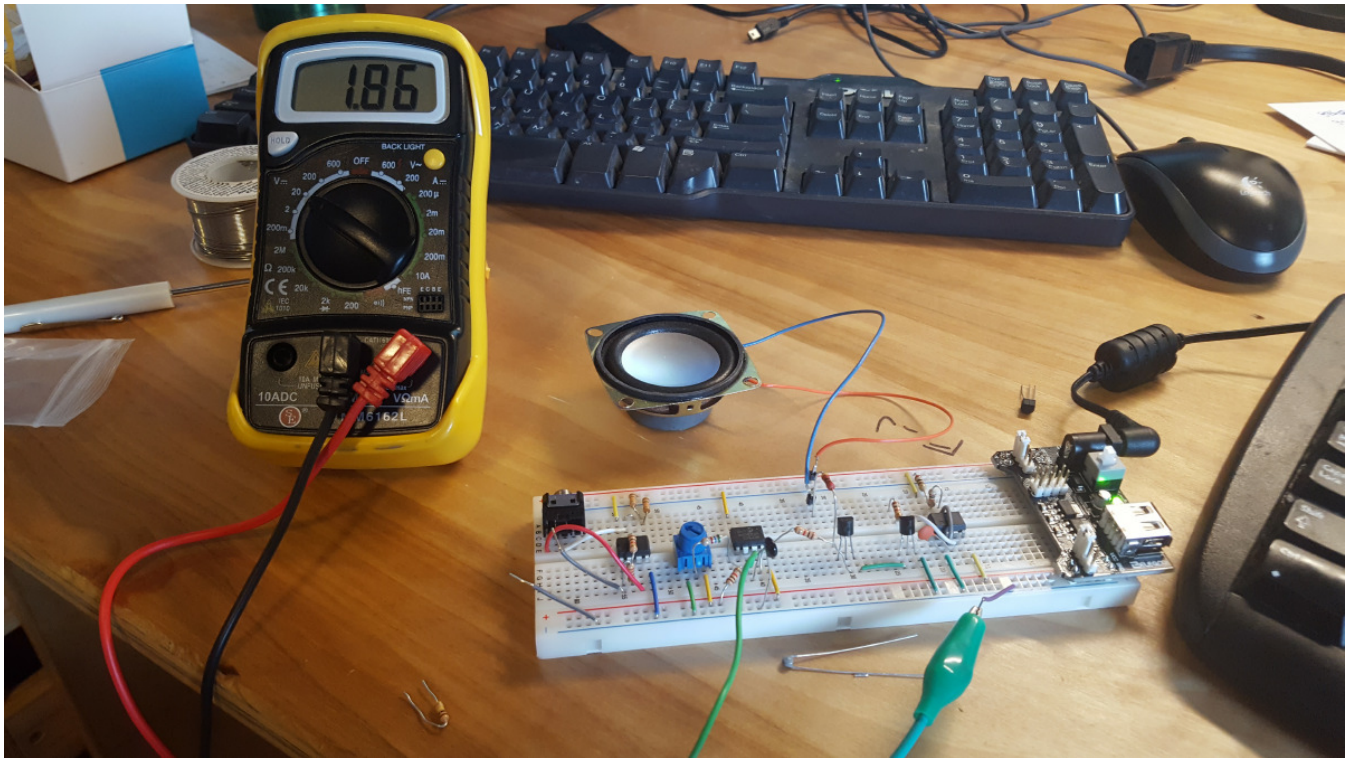10) Build this circuit and verify it's on and off temperature (or voltage or resistance. Replace R with a potentiometer for test purposes)



$V_p$  set to 2.00V with a potentiometer

- Turns on at 1.98V
- Turns off at 2.26V