ECE 320 - Homework #6

H-Bridge, DC to DC Converters

H-Bridges:

- 1) Determine the voltages and currents for the following 1/2 H-bridge for
 - V1 = 0V, V2 = 0V
 - V1 = 5V, V2 = 5V
 - V1 = 5V, V2 = 0V

Assume 3904/3906 transistors







5V:5V results in 0.2V



Voltages for 5V : 0V input

2) Check your results (votlages and currents) in CircuitLab



| | | Calculated | Simulated | Measured |
|--------------------|----|------------|-----------|----------|
| V1 = 5V V2 = 5V | V3 | 0.20V | 86.89mV | |
| | 13 | -46.0mA | -48.26mA | |
| V1 = 0V V2 = 0V | V3 | 4.80V | 4.884V | |
| | 13 | +46.0mA | +46.87mA | |
| V1 = 5V V2 = 0V | V3 | 2.50V | 2.500V | |
| | 13 | 0.0mA | 0.0mA | |

3) Lab: Build this circuit and measure the voltages and currents. (note: it's OK to compute the currents from the measured votlages).

| | | Calculated | Simulated | Measured |
|--------------------|----|------------|---------------|----------|
| V1 = 5V V2 = 5V | V3 | 0.20V | 86.89mV 0.09V | |
| | 12 | -46.0mA | -48.26mA | -48mA |
| V1 = 0V V2 = 0V | V3 | 4.80V | 4.884V | 4.96V |
| | 12 | +46.0mA | +46.87mA | +49mA |
| V1 = 5V V2 = 0V | V3 | 2.50V | 2.500V | 2.46V |
| | 12 | 0.0mA | 0.0mA | -1mA |





DC to DC Converters

4) Determine the voltages (both DC and AC) for V1 and V2.



DC:

 $V_1(DC) = 0.65 \cdot 20V + 0.35 \cdot (-0.7V)$ $V_1(DC) = 12.755V$ $V_2(DC) = \left(\frac{100}{100+5}\right) 12.755V$ $V_2(DC) = 12.148V$

AC:

$$V_1(AC) \approx 20.7 V_{pp}$$
$$V_2(AC) \approx \left(\frac{(9.2084 - j29.9145)}{(9.2084 - j29.9145) + (5 + j314)}\right) 20.7 V_{pp}$$
$$V_2(AC) \approx 2.2006 V_{pp}$$

5) Simulate the circuit in CircuitLab and determine V2 (DC and AC)

Use a PNP transistor as an electronic switch.

• Turn it on 65% of the time with PWM



The voltages at V1 and V2 are:

- V2(max) = 13.28V
- V2(min) = 10.83V

| | V1 | | V2 | |
|------------|---|----------|---------|----------|
| | Max | Min | DC | AC |
| Calculated | 20V ignores the 0.2V drop across the transistor | -0.7V | 12.148V | 2.200Vpp |
| Simulated | 19.84V | -0.7898V | 12.055V | 2.450Vpp |

6) Change the duty cycle and C so that

- The DC voltage at V2 = 5.00V
- The ripple at V2 is 1Vpp

DC Analysis:

$$V_2 = 5.00V = \left(\frac{100}{100+5}\right)V_1$$
$$V_1 = 5.25V$$

Duty Cycle

$$5.25V = 20V \cdot \alpha + (1 - \alpha)(-0.7V)$$
$$\alpha = \left(\frac{5.25V + 0.7V}{20V + 0.7V}\right) = 28.74\%$$

AC Analysis: (Method #1)

5uF produced 2.588Vpp ripple, so

$$C = \left(\frac{2.588V_{pp}}{1V_{pp}}\right)5\mu F = 12.94\mu F$$

AC Analysis (Method #2)

$$V_{2} = 1V_{pp} = \left(\frac{R||\frac{1}{j\omega C}}{R||\frac{1}{j\omega C} + (5+j314))}\right) 20.7V_{pp}$$

$$1V_{pp} \approx \left(\frac{\frac{1}{j\omega C}}{j314}\right) 20.7V_{pp}$$

$$\frac{1}{\omega C} \approx 15.17\Omega$$

$$C \approx 10.50\mu F$$



| | V2(DC) | V2(AC) |
|------------|--------|-----------|
| Calculated | 5V | 1Vpp |
| Simualted | 4.891V | 0.8500Vpp |

Fourier Transforms

8) Going back to problem #4, determine the Fourier Transform for V1 out to the 3rd harmonic (3kHz)

- 65% duty cycle square wave
- Going from -0.7V to +19.8V

Using the complex Fourier Transform

>> t = [0:0.0001:1]'; >> V0 = 19.8*(t<0.65) - 0.7*(t>=0.65); >> c0 = mean(V0) c0 = 12.6257 >> c1 = 2*mean(V0 .* exp(-j*2*pi*t)) c1 = -5.2779 -10.3582i >> c2 = 2*mean(V0 .* exp(-j*2*pi*t * 2)) c2 = 3.1040 - 4.2724i >> c3 = 2*mean(V0 .* exp(-j*2*pi*t * 3)) c3 = -0.6682 - 0.1058i

Translation: V1(t) is approximately

$$V_{1}(t) \approx 12.6357$$

-5.2779 cos($\omega_{0}t$) + 10.3582 sin ($\omega_{0}t$)
+3.1040 cos($2\omega_{0}t$) + 4.2724 sin ($2\omega_{0}t$)
-0.6682 cos($3\omega_{0}t$) + 0.1058 sin ($3\omega_{0}t$)

where ω_0 is 1000Hz (2000 pi)

9) Using the Fourier Transform approximation for V1, determine V2 out to the 3rd harmonic (3kHz)

```
% DC
>> R2 = 100;
>> R1 = 5;
>> Y0 = R2 / (R1+R2)*c0
Y0 = 12.0245
>> % 1kHz
>> w = 2*pi*1000;
>> Zc = 1/(j*w*5e-6);
>> R2 = 1/(1/2c + 1/100);
>> R1 = 5 + j*w*0.05;
>> Y1 = (R2) / (R2+R1) *c1
Y1 = 0.1396 + 1.2267i
>> % 2kHz
>> w = 2*pi*2000;
>> Zc = 1/(j*w*5e-6);
>> R2 = 1/(1/Zc + 1/100);
>> R1 = 5 + j*w*0.05;
>> Y2 = (R2) / (R2+R1) *c2
Y2 = -0.0970 + 0.0945i
>> % 3kHz
>> w = 2*pi*3000;
>> Zc = 1/(j*w*5e-6);
>> R2 = 1/(1/2c + 1/100);
>> R1 = 5 + j*w*0.05;
>> Y3 = (R2)/(R2+R1)*c2
Y3 = -0.0403 + 0.0441i
```

Pretty much, all that matters is the 1st harmonic (1kHz), resulting in the peak-to-peak voltage at V1 being

```
>> V1pp = 2*abs(Y1)
```

V1pp = 2.4692 vs. 2.4500Vpp from Circuitlab

>>>>>>>

Note: A better way to estimate the signal at V2 is to take the Fourier Transform of V1

DC term

• Tells you the DC term for V1

1st Harmonic

• Tells you the AC term for V1

The other harmonics have a minimal effect and can be ignored.