

ECE 320 - Homework #9

MOSFET Switches, CMOS logic. Due Monday, March 20th
Please email to jacob.glower@ndsu.com, or submit as a hard copy, or submit on BlackBoard

MOSFETs

1) The VI characteristics for an n-channel MOSFET are shown below.

- Label the off / ohmic / and saturated regions
- Determine the transconductance gain, k_n . Assume $V_{th} = 1.00V$

k_n Calculations: Point A (Ohmic Region)

$$I_{ds} = k_n \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$10mA = k_n \left(5V - 1V - \frac{2V}{2} \right) 2V$$


$$k_n = 1.667 \frac{mA}{V^2}$$

Point B (Saturated Region)

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$29mA = \frac{k_n}{2} (7V - 1V)^2$$

$$k_n = 1.611 \frac{mA}{V^2}$$

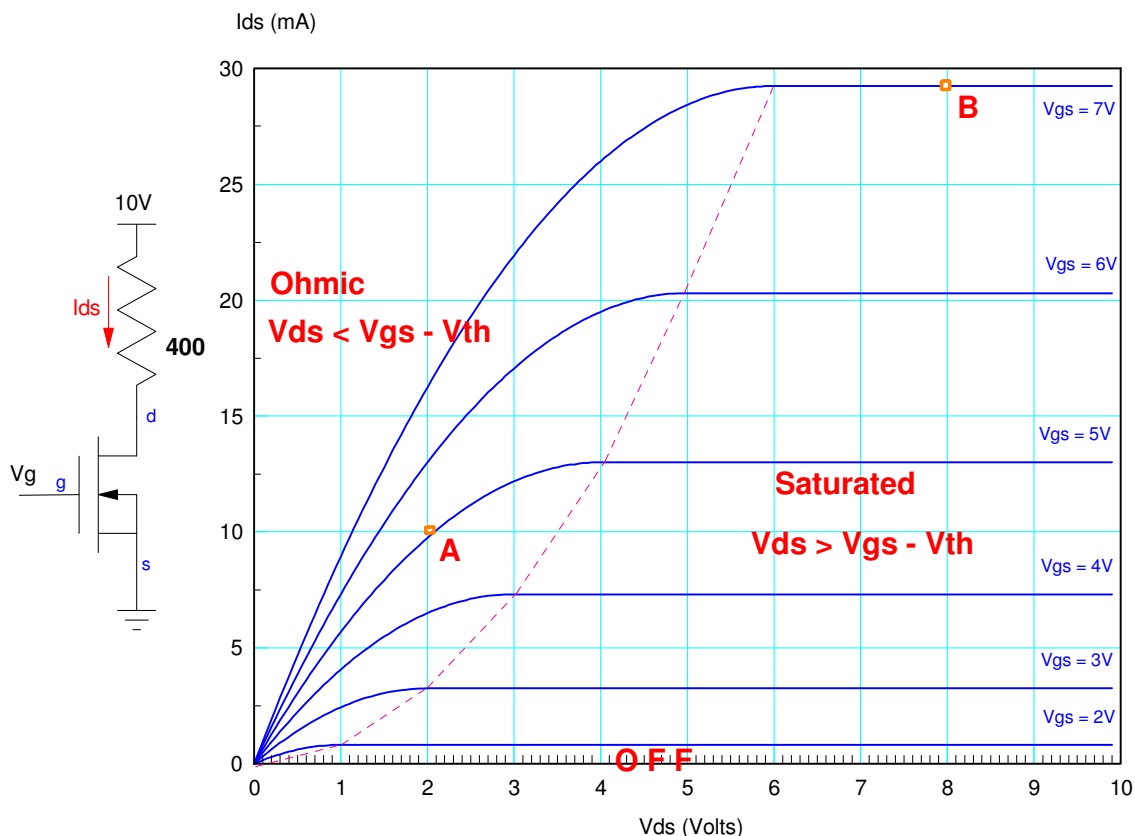

2) Draw the load-line for the circuit below. From the load line, determine the Q-point (V_{ds} , I_{ds}) when

A: $V_g = 0V$

$V_{ds} = 10V$, $I_{ds} = 0mA$

Off Region

$V_g = 4V$


$V_{ds} = 7V$, $I_{ds} = 7.5mA$

Saturated Region

$V_g = 7V$

$V_{ds} = 2.4V$, $I_{ds} = 18mA$

Ohmic Region

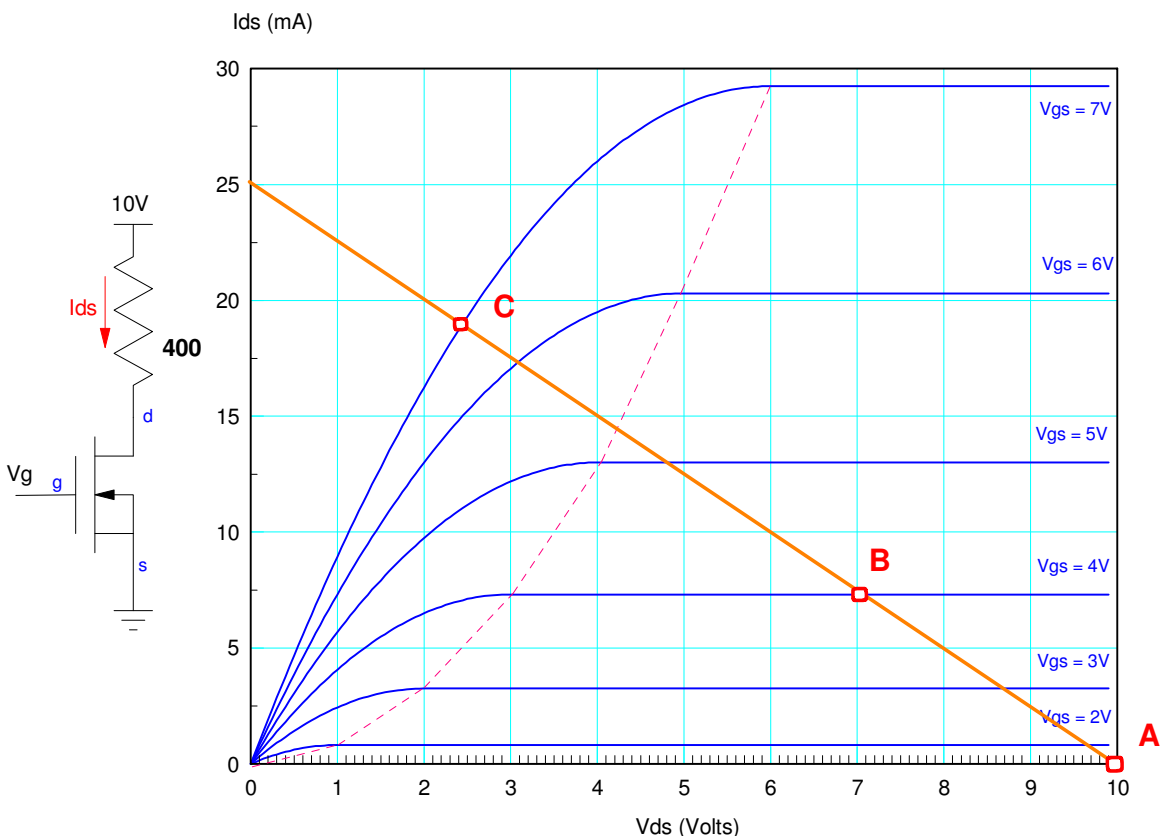

MOSFET Switch

The characteristics for a IRF3710 MOSFET are

- Max Current = 57A continuous (180A pulsed)
- $R_{ds} = 0.023 \Omega$ @ $V_{gs} = 10V$ @ $I_d = 28A$
- $2V < V_{th} < 4V$ assume $V_{th} = 3V$

3) Determine the transconductance gain, k_n

R_{ds} is given in the Ohmic region

$$I_{ds} = k_n \left(V_{ds} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} = 28A \cdot 0.023\Omega = 0.644V$$

$$28A = k_n \left(10V - 3V - \frac{0.644V}{2} \right) \cdot 0.644V$$

$$k_n = 5.663 \frac{A}{V^2} \quad V_{th} = 2V$$

$$k_n = 6.511 \frac{A}{V^2} \quad V_{th} = 3V$$

$$k_n = 7.657 \frac{A}{V^2} \quad V_{th} = 4V$$

4) The CircuitLab model for an IRF3710 MOSFET is

- $k = 48.1147 \frac{A}{V^2}$
- $V_{th} = 3.39715V$

Using the CircuitLab parameters, determine the voltages for the following circuit for

- $V_{in} = V_g = 0V$
- $V_{in} = V_g = 5V$
- $V_{in} = V_g = 10V$

$V_{in} = 0V$

Off region

$$V_{ds} = 10V$$

$$I_{ds} = 0mA$$

$V_{in} = 5V$

Assume saturated region

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$I_{ds} = \frac{48.1147 \frac{A}{V^2}}{2} (5V - 3.39715V)^2$$

$$I_{ds} = 61.806A$$

$$V_{ds} = 10 - 8I_{ds} = -484.45V$$

which is nonsense - meaning it's not in the saturated region. Assume Ohmic region. Write two equations for two unknowns.

$$I_{ds} = k_n \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$10 = 8I_{ds} + V_{ds}$$

Solving using numerical methods

$$V_{ds} = 0.0163V$$

$$I_{ds} = 1.2480A$$

Check:

$$V_{ds} < V_{gs} - V_{th}$$


$$0.0163V < 5V - 3.39715V$$

$V_{gs} = 10V$

Also Ohmic region

$$V_{ds} = 0.0039V$$





$$I_{ds} = 1.2495A$$

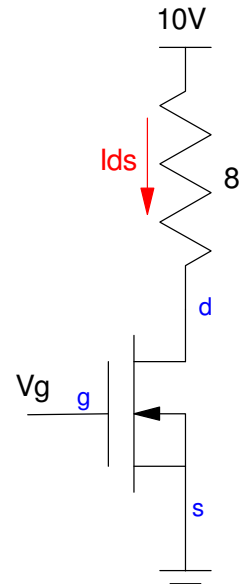

5) Simulate this circuit in CircuitLab using an IRF3710. Determine the voltages and currents when

- $V_{in} = V_g = 0V$
- $V_{in} = V_g = 5V$
- $V_{in} = V_g = 10V$

V_{gs}		V_{ds}	I_{ds}	R_{ds}
0V	Calculated	10V	0mA	n/a
	Simulated	10V	0mA	n/a
5V	Calculated	16.3mV	1.248A	13.1 mOhm
	Simulated	37.30mV	1.245A	30.0 mOhm
10V	Calculated	3.99mV	1.2495A	3.2 mOhm
	Simulated	24.95mV	1.247A	20.0 mOhm

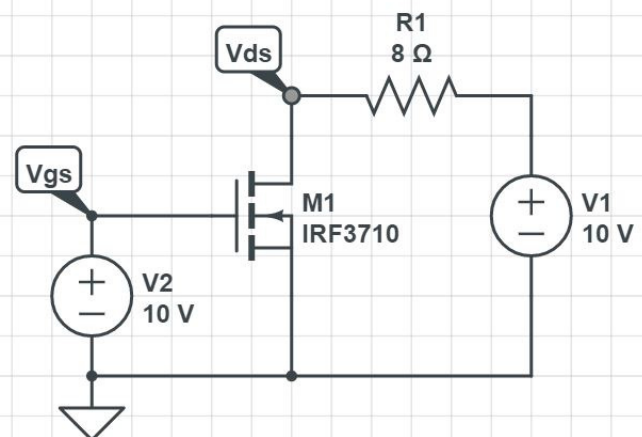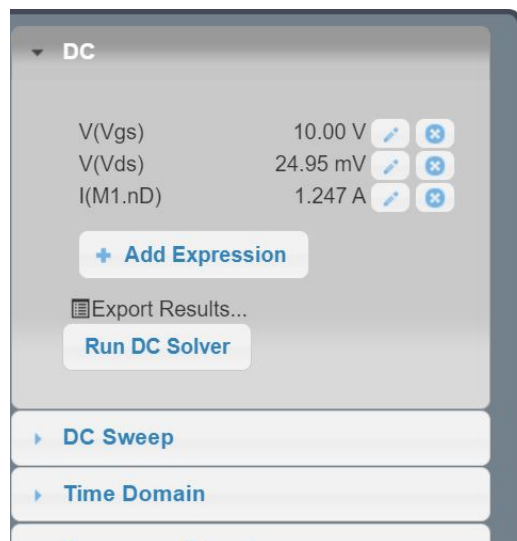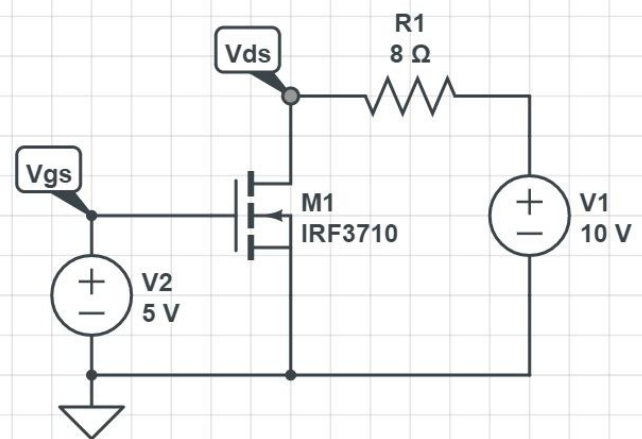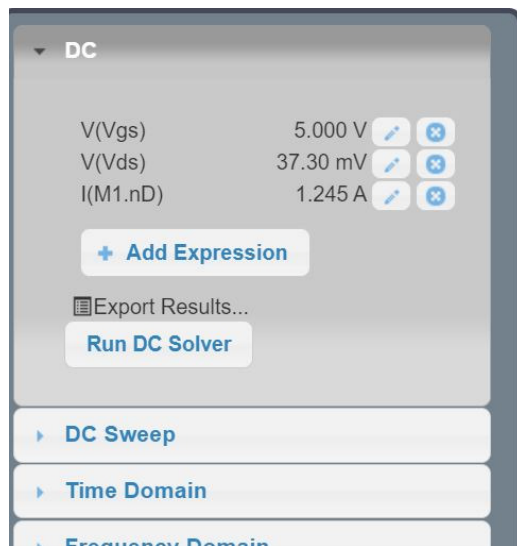

CMOS Logic

6) Design a CMOS gate to implement the function: $Y(A, B, C, D)$

Y(A,B,C,D)		CD			
		00	01	11	10
AB	00	1	0	0	x
	01	1	0	x	1
	11	1	x	1	0
	10	0	1	x	0

Start with circling the ones or zeros. I prefer zeros, but either one works

$$\bar{Y} = \bar{A}D + A\bar{B}\bar{D} + ACD$$

Use DeMorgan's law to get Y

$$Y = (A + \bar{D})(\bar{A} + B + D)(\bar{A} + \bar{C} + D)$$

Implement these using CMOS gates (series = and, parallel = or).

- Use $\sim Y$ for the n-channel MOSFETs (tied to ground)
- Use Y for the p-channel MOSFETs (tied to 5V)

