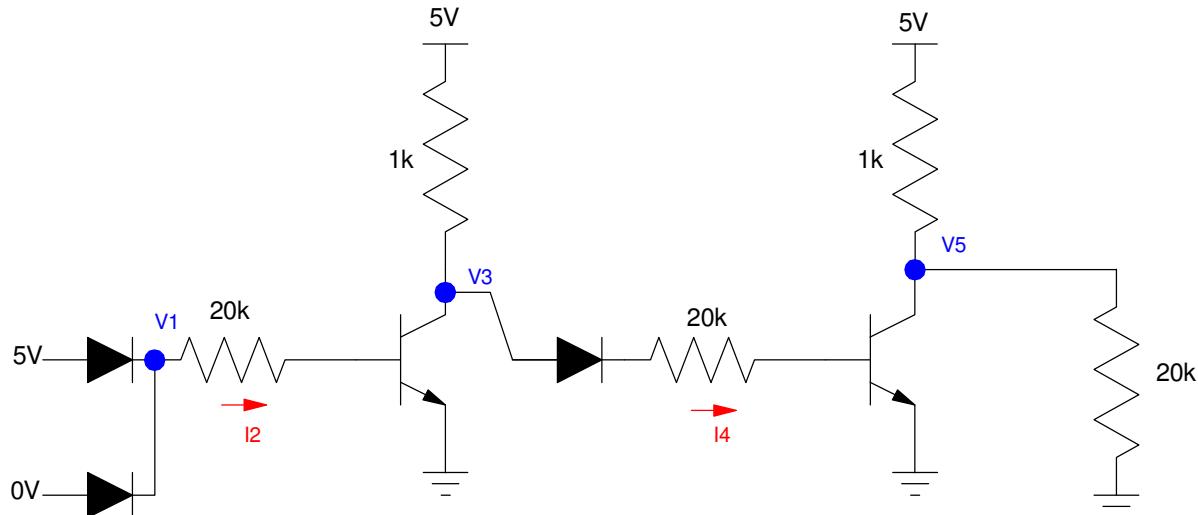


ECE 320 - Homework #8


DTL, TTL Logic

DTL Logic

- 1) Determine the voltages and currents for the following DTL OR gate. Assume 3904 NPN transistors
- 2) Simulate this circuit in CircuitLab to verify your answers





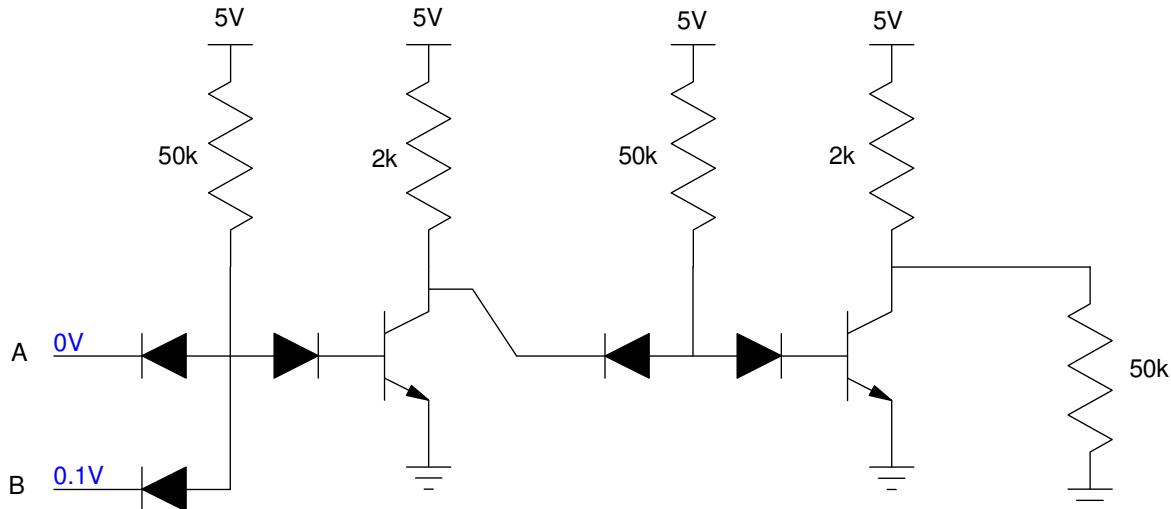- 3) Determine the voltages and currents for the following DTL AND gate. Assume 3904 NPN transistors
- 4) Simulate this circuit in CircuitLab to verify your answers



TTL Logic

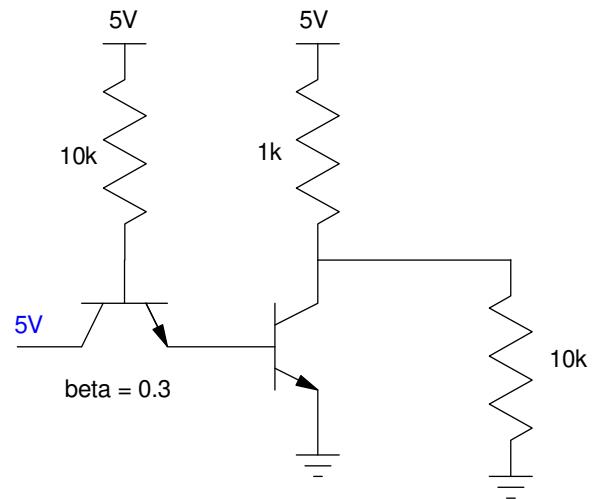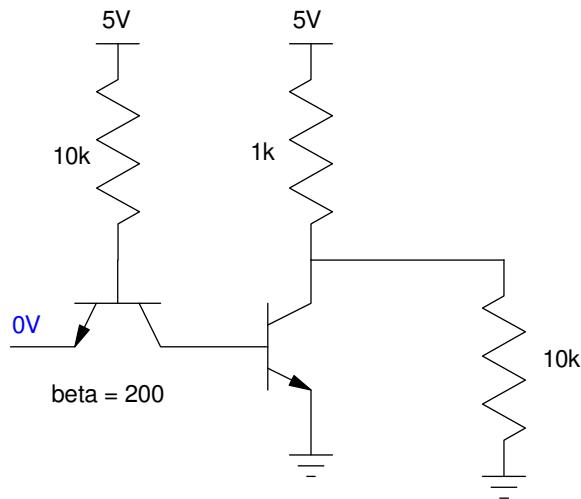- 5) Determine the voltages for the following TTL inverter. Assume 3904 transistors.
- 6) Simulate these circuits in CircuitLab to verify your answers



Temperature Alarm using DTL Logic

The circuit below uses a DTL NAND gate to drive the speaker when

- The 555 timer outputs 5V, and
- The comparitor outputs 5V.,

7) Determine the voltages when

- $V_1 = V_2 = 0V$
- $V_1 = V_2 = 5V$
- $V_1 = 0V, V_2 = 5V$

8) Verify your design using CircuitLab.

Lab: 9) (20pt): Verify your design in hardware (build and test the circuit with your lab kit).

- note: Use a potentiometer to simulate the temperature sensor.

