

# ECE 320 - Homework #9

MOSFET Switches, CMOS logic


## MOSFETs

1) The VI characteristics for an n-channel MOSFET are shown below.

- Label the off / ohmic / and saturated regions
- Determine the transconductance gain,  $k_n$ . Assume  $V_{th} = 1.00V$

2) Draw the load-line for the circuit below. From the load line, determine the Q-point ( $V_{ds}$ ,  $I_{ds}$ ) when

- $V_g = 0V$
- $V_g = 4V$
- $V_g = 7V$

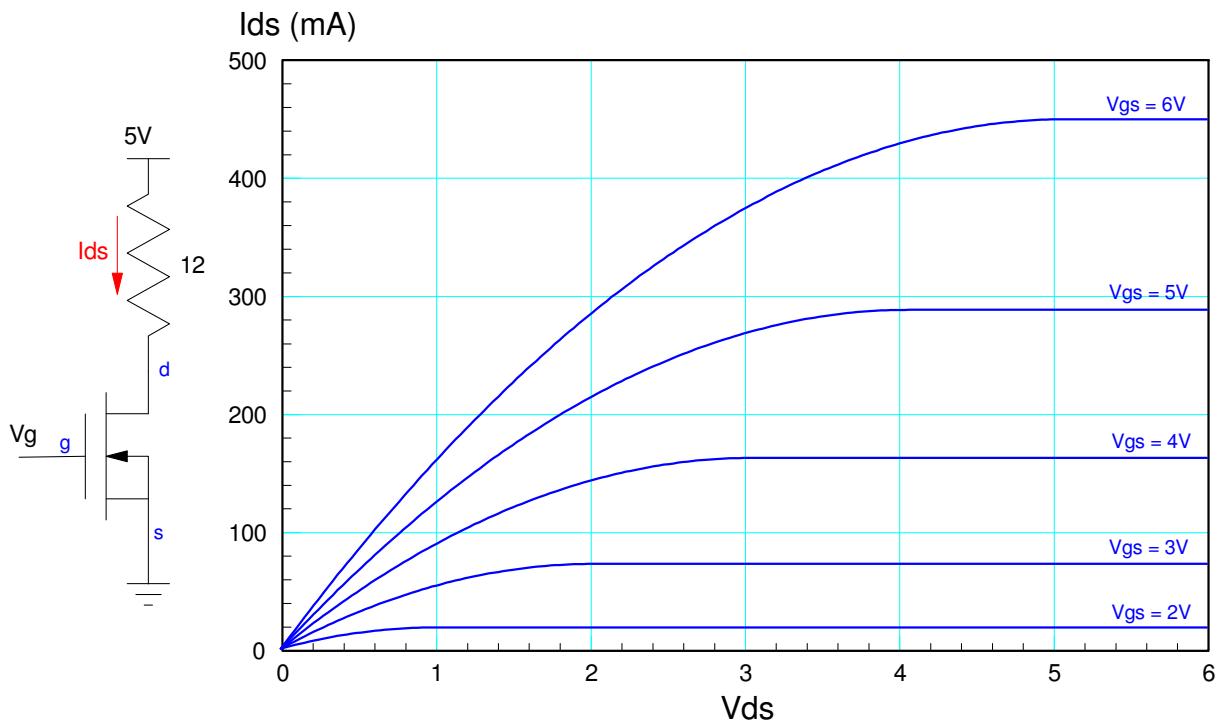

## MOSFET Switch

The characteristics for a IRF3205 MOSFET are

- Max Current = 110A continuous
- $R_{ds} = 0.008 \text{ Ohms}$  @  $V_{gs} = 10V$  @  $I_d = 62A$
- $V_{th} = 3V$  (range = 2V to 4V)


3) Determine the transconductance gain,  $k_n$

4) The CircuitLab model for an IRF3205 MOSFET is

- $k = 70.0 \frac{A}{V^2}$
- $V_{th} = 3.900V$

Using the CircuitLab parameters, determine the voltages for the following circuit for

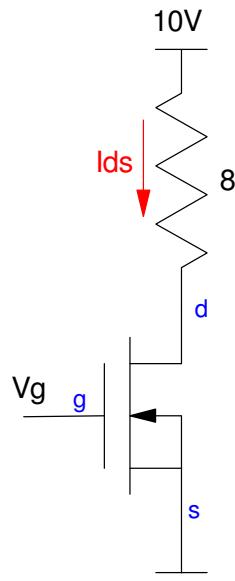- $V_{in} = V_g = 0V$
- $V_{in} = V_g = 5V$
- $V_{in} = V_g = 10V$



5) Simulate this circuit in CircuitLab using an IRF3710. Determine the voltages and currents when

- $V_{in} = V_g = 0V$
- $V_{in} = V_g = 5V$
- $V_{in} = V_g = 10V$
- 

## CMOS Logic

6) Design a CMOS gate to implement the function:  $Y(A, B, C, D)$

		CD			
		00	01	11	10
AB	00	0	1	1	x
	01	1	1	1	1
	11	0	x	0	0
	10	0	1	x	0