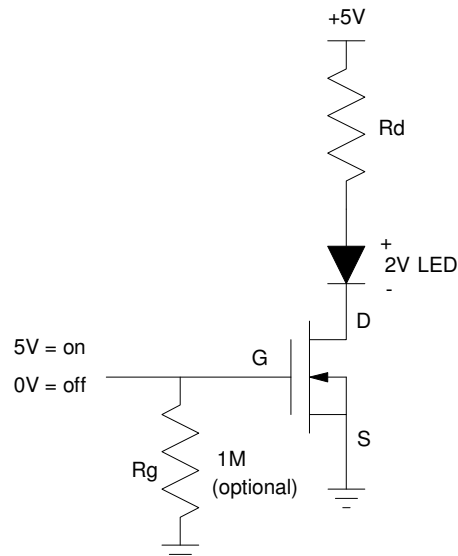


MOSFETs Used as a Switch

Problem: Use a MOSFET to turn on and off an LED. Assume the LED draws 20mA at 2V.

Solution: A MOSFET switch is very much like a BJT switch:



When $V_{GS} = 0V$, the MOSFET is off, as is the LED.

When $V_{GS} = 5V$, you want the LED to turn on with 20mA flowing. R_d serves to limit the current to 20mA (if needed). R_g is for safety: it discharges any static on the gate, making sure it's 0V when left floating.

First, pick out your favorite MOSFET. What we need is a MOSFET with an on-resistance less than 150 Ohms:

$$R_{on} = \frac{I_{DS}}{V_{DS}} = \frac{20mA}{5V-2V} = 150\Omega$$

Going to Digikey (www.digikey.com) and searching for MOSFET's results in 22,000 MOSFET's to choose from:

Discrete Semiconductor Products | MOSFETs, GaNFETs - Single

Series	Manufacturer	FET Type	FET Feature	Rds On (Max) @ Id, Vgs	Drain to Source Voltage (Vds)	Current - Continuous Drain (Id) @ 25° C	Vgs(th) (Max) @ Id	Gate Charge (Qg) @ Vgs
Alpha & Omega Semiconductor Inc Clare Diodes Inc Diodes/Zetex Diodes/Zetex Diodes/Zetex (VA) EPC Fairchild Optoelectronics Group Fairchild Semiconductor Honeywell Microelectronics & Precision Sensors	GalNFET N-Channel, Gallium Nitride MOSFET N-Channel, Metal Oxide MOSFET N-Channel, Schottky, Metal Oxide MOSFET P-Channel, Metal Oxide	Current Sensing Depletion Mode Diode (Isolated) Logic Level Gate Standard	0.7 mOhm @ 61A, 10V 0.95 mOhm @ 100A, 10V 1 mOhm @ 100A, 10V 1 mOhm @ 150A, 10V 1 mOhm @ 80A, 10V 1.1 mOhm @ 100A, 10V 1.15 mOhm @ 50A, 10V 1.17 mOhm @ 20A, 10V 1.2 mOhm @ 15A, 10V	6V 8V 12V 14V 15V 16V 20V 24V 25V	5mA 10mA 20mA 21mA 35mA 45mA 50mA 60mA 70mA	400mV @ 100uA 400mV @ 1mA 400mV @ 250uA 450mV @ 100uA 450mV @ 250uA 500mV @ 250uA 570mV @ 1mA 600mV @ 1.2mA 600mV @ 11uA	0.01nC @ 5V 0.31nC @ 4.5V 0.6nC @ 10V 0.6nC @ 2.5V 0.6nC @ 4.5V 0.6nC @ 5V 0.62nC @ 4.5V 0.62nC @ 4.5V 0.65nC @ 4.5V	

In stock
 Lead free
 RoHS Compliant

Reset Apply Filters

You have selected 22,839 items, spanning 916 pages.

View Page | 1

To narrow the search, select

- MOSFET, N Channel
- Through Hole
- In Stock
- 100mA < IDS < 200mA

This limits the number to something more manageable:


Image	Digi-Key Part Number	Manufacturer Part Number	Description	Series	Manufacturer	FET Type	FET Feature	Rds On (Max) @ Id, Vgs	Drain to Source Voltage (Vds)	Current - Continuous Drain (Id) @ 25° C	Vgs (th) (Max) @ Id	Gate Charge (Qg) @ Vgs	Input Capacitance (Ciss) @ Vds	Power-Max	Mounting Type	Package / Case	Packaging	Quantity Available	Minimum Quantity	Unit Price
	2N7000_D26ZTR-ND	2N7000_D26Z	MOSFET N-CH 60V 200mA TO-92	-	Fairchild Semiconductor	MOSFET N-Channel, Metal Oxide	Logic Level Gate	5 Ohm @ 500mA, 10V	60V	200mA	3V @ 1mA	-	50pF @ 25V	400mW	Through Hole	TO-92-3 (Standard Body), TO-226	Tape & Reel (TR)	38,000	2,000	Note Alternate Packaging 0.06400
	2N7000_D26ZCT-ND	2N7000_D26Z	MOSFET N-CH 60V 200mA TO-92	-	Fairchild Semiconductor	MOSFET N-Channel, Metal Oxide	Logic Level Gate	5 Ohm @ 500mA, 10V	60V	200mA	3V @ 1mA	-	50pF @ 25V	400mW	Through Hole	TO-92-3 (Standard Body), TO-226	Cut Tape (CT)	39,732	1	Note Alternate Packaging 0.68000
	2N7000FS-ND	2N7000	MOSFET N-CH 60V 200mA TO-92	-	Fairchild Semiconductor	MOSFET N-Channel, Metal Oxide	Logic Level Gate	5 Ohm @ 500mA, 10V	60V	200mA	3V @ 1mA	-	50pF @ 25V	400mW	Through Hole	TO-92-3 (Standard Body), TO-226	Bulk	176,258	1	0.42000
	ZVN0124A-ND	ZVN0124A	MOSFET N-CHAN 240V TO92-3	-	Diodes Zetex	MOSFET N-Channel, Metal Oxide	Logic Level Gate	16 Ohm @ 250mA, 10V	240V	160mA	3V @ 1mA	-	85pF @ 25V	700mW	Through Hole	TO-92-3 (Standard Body), TO-226	Bulk	4,000	1	0.72000

Selecting the third one (it's in stock, costs \$0.42 each, has an on resistance of 5 Ohms) gives you the pricing information:

All prices are in US dollars.

Digi-Key Part Number	2N7000FS-ND	Price Break	Unit Price	Extended Price
Quantity Available	176,258	1	0.42000	0.42
Manufacturer	Fairchild Semiconductor	10	0.30200	3.02
Manufacturer Part Number	2N7000	100	0.17810	17.81
Description	MOSFET N-CH 60V 200MA TO-92	250	0.12600	31.50
Lead Free Status / RoHS Status	Lead free / RoHS Compliant	500	0.10080	50.40
		750	0.08568	64.26
		1,000	0.07728	77.28
		2,000	0.06720	134.40
		4,800	0.06048	290.30

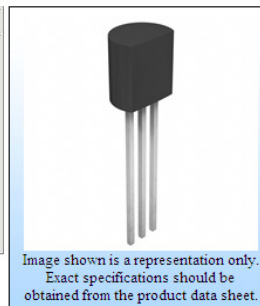Quantity [Item Number](#) Customer Reference



Click on the data sheet and you get the technical specs for this MOSFET:

Absolute Maximum Ratings $T_A = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	2N7000	2N7002	NDS7002A	Units
V_{DS}	Drain-Source Voltage		60		V
V_{DGR}	Drain-Gate Voltage ($R_{GS} \leq 1\text{ M}\Omega$)		60		V
V_{GS}	Gate-Source Voltage - Continuous		± 20		V
	- Non Repetitive ($t_p < 50\mu\text{s}$)		± 40		
I_D	Maximum Drain Current - Continuous	200	115	280	mA
	- Pulsed	500	800	1500	
P_D	Maximum Power Dissipation	400	200	300	mW
	Derated above 25°C	3.2	1.6	2.4	
T_J, T_{STG}	Operating and Storage Temperature Range	-55 to 150		-65 to 150	$^\circ\text{C}$
T_L	Maximum Lead Temperature for Soldering Purposes, 1/16" from Case for 10 Seconds	300			$^\circ\text{C}$
THERMAL CHARACTERISTICS					
$R_{\theta JA}$	Thermal Resistance, Junction-to-Ambient	312.5	625	417	$^\circ\text{C}/\text{W}$

We're operating at +5V and 20mA. This MOSFET can take +/- 20V and 115mA, so it will work.

To analyze this circuit, we need to know V_{TN} and K_n , however. On page 2 of the data sheets, the following is given:

$R_{DS(ON)}$	Static Drain-Source On-Resistance	Conditions	Device	V_{GS} (V)	I_D (mA)	T_J ($^\circ\text{C}$)	$R_{DS(ON)}$ (Ω)		
		$V_{GS} = 10\text{ V}, I_D = 500\text{ mA}$	2N7000	5	75	125	1.2		
						125	1.9		
		$V_{GS} = 4.5\text{ V}, I_D = 75\text{ mA}$	2N7000	5	75	125	1.8		
						125	5.3		
				$V_{GS} = 10\text{ V}, I_D = 500\text{ mA}$	2N7002	5	75	100	1.2
								100	7.5
$V_{GS} = 5.0\text{ V}, I_D = 50\text{ mA}$	100			1.7					
	100			13.5					

At

- $V_{GS} = 5.0\text{V}$
- $I_D = 50\text{mA}$
- $R_{DS} = 1.7\text{ Ohms (nominal)}$

This lets you solve for K_n :

$$\frac{1}{R_{DS}} = \frac{I_{DS}}{V_{DS}} = K_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right)$$

$$(1) \quad \frac{1}{1.7\Omega} = K_n \left(5\text{V} - 2 - \frac{(50\text{mA})(1.7\Omega)}{2} \right)$$

$K_n = 0.1989$

Assume $R_{ds} = 1.7$ Ohms. Then

$$R_{net} = \frac{5V-2V}{20mA} = 150\Omega$$

$$R_{net} = R_{DS} + R_d$$

$$R_d = 148.3\Omega$$

(plus or minus 5%. We have 5% tolerance resistors in lab.)

Assume you have a 148.3 Ohm resistor. Find the approximate (V_{ds} , I_{ds})

When ON, the MOSFET is approximately 1.7 Ohms

$$I_{ds} = \left(\frac{5V-2V}{148.3\Omega+1.7\Omega} \right)$$

$$I_{ds} = 20mA$$

Find the actual resistance using the MOSFET model with $K_n = 0.1989$ A/V²

The Mosfet gives us one equation for two unknowns:

$$I_{ds} = K_n \left(V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{ds} = 0.1989 \left(5 - 2 - \frac{V_{ds}}{2} \right) V_{ds}$$

The circuit gives the second equation

$$V_{ds} = 3 - 148.3I_{ds}$$

This is a quadratic with two solutions:

$$V_{ds} = \{ 0.0337V, 6.0341V \}$$

The one close to zero is the correct one:

- $V_{ds} = 33.7mV$
- $I_{ds} = 20.002mA$

Taking the ratio:

$$R_{ds} = V_{ds} / I_{ds} = 1.6854 \text{ Ohms}$$

The actual resistance when on isn't exactly 1.7 Ohms, but it's pretty close.

Note that you can power just about anything you like with this MOSFET, providing that

- 1.7 Ohms is small relative to the resistance of what you're driving (150 Ohms in this case),
- The net current flow is less than 115mA continuous, 800mA pulsed (from the data sheets),
- The power supply you're using is less than 60V. The maximum $V_{DS} = 60V$ for this MOSFET.

It also takes some time for the MOSFET to turn on. The capacitance is (from the data sheets)

$$C_{GS} = 20pF$$

$$C_{DS} = 11pF$$

Likewise, when you turn the MOSFET off, the capacitor charges up to +5V as

$$V_{DS} = 5V \cdot \left(1 - \exp\left(\frac{-t}{RC}\right)\right)$$

or

$$RC = (150\Omega)(11pF) = 1.6ns$$

In three time constants, you're at 95% of 5V:

$$e^{-3} \approx 0.05$$

$$\left(\frac{t}{RC}\right) = 3$$

$$t = 3RC = 4.95ns$$

It takes about 5 nanoseconds to turn the LED on, and 5 nanoseconds to turn it off with this MOSFET. The maximum frequency is likewise 100MHz (1 / 10ns).

MOSFETs are *fast* relative to BJT transistors.

If you need to power a bigger device, use a bigger MOSFET. For example, doing the same search in Digikey but looking for a MOSFET that takes 8A results in a slightly more expensive MOSFET (\$1.51 each):

All prices are in US dollars.				
Digi-Key Part Number	869-1043-ND	Price Break	Unit Price	Extended Price
Quantity Available	142	1	1.51000	1.51
Manufacturer	SANYO Semiconductor (U.S.A) Corporation	25	1.20400	30.10
Manufacturer Part Number	2SK4096LS	100	1.05350	105.35
Description	MOSFET N-CH 500V 8A TO-220FI	250	0.92452	231.13
Lead Free Status / RoHS Status	Lead free / RoHS Compliant	500	0.81700	408.50
		1,000	0.64500	645.00
		2,500	0.60200	1,505.00

Quantity	Item Number	Customer Reference	
<input type="text"/>	869-1043-ND	<input type="text"/>	<input type="button" value="Add to Order"/>




Image shown is a representation only. Exact specifications should be obtained from the product data sheet.

with one table from the data sheets:

Electrical Characteristics at $T_a=25^\circ\text{C}$

Parameter	Symbol	Conditions	Ratings			Unit
			min	typ	max	
Drain-to-Source Breakdown Voltage	$V_{(BR)DSS}$	$I_D=10\text{mA}, V_{GS}=0\text{V}$	500			V
Zero-Gate Voltage Drain Current	I_{DSS}	$V_{DS}=400\text{V}, V_{GS}=0\text{V}$			100	μA
Gate-to-Source Leakage Current	I_{GSS}	$V_{GS}=\pm 30\text{V}, V_{DS}=0\text{V}$			± 100	nA
Cutoff Voltage	$V_{GS(off)}$	$V_{DS}=10\text{V}, I_D=1\text{mA}$	3		5	V
Forward Transfer Admittance	$ y_{fs} $	$V_{DS}=10\text{V}, I_D=4\text{A}$	2.2	4.5		S
Static Drain-to-Source On-State Resistance	$R_{DS(on)}$	$I_D=4\text{A}, V_{GS}=10\text{V}$		0.65	0.85	Ω
Input Capacitance	C_{iss}	$V_{DS}=30\text{V}, f=1\text{MHz}$		600		pF
Output Capacitance	C_{oss}	$V_{DS}=30\text{V}, f=1\text{MHz}$		130		pF
Reverse Transfer Capacitance	C_{rss}	$V_{DS}=30\text{V}, f=1\text{MHz}$		28		pF
Turn-ON Delay Time	$t_d(on)$	See specified Test Circuit.		18.5		ns
Rise Time	t_r	See specified Test Circuit.		46		ns
Turn-OFF Delay Time	$t_d(off)$	See specified Test Circuit.		75		ns
Fall Time	t_f	See specified Test Circuit.		33		ns
Total Gate Charge	Q_g	$V_{DS}=200\text{V}, V_{GS}=10\text{V}, I_D=8\text{A}$		24		nC
Gate-to-Source Charge	Q_{gs}	$V_{DS}=200\text{V}, V_{GS}=10\text{V}, I_D=8\text{A}$		4.5		nC
Gate-to-Drain "Miller" Charge	Q_{gd}	$V_{DS}=200\text{V}, V_{GS}=10\text{V}, I_D=8\text{A}$		14		nC
Diode Forward Voltage	V_{SD}	$I_S=8\text{A}, V_{GS}=0\text{V}$		0.9	1.2	V

Note that this device

- Can turn on and off devices which take up to 8A and 500V
- Has an on-resistance of about 0.65 Ohms
- V_{GS} needs 10V to be on. The off voltage (V_{TN}) is between 3V and 5V.

It's also a bit slower: it takes 18ns (turn-on delay) or 75ns (turn off delay) to turn on and off. That's still really fast relative to a BJT.