
TTL Logic

Transistor Transistor Logic

ECE 320 Electronics I

Jake Glower - Lecture #21


Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions



TTL Logic


- Diodes are inherently capacitors
- This slows down DTL logic

TTL logic removes the diodes

 


TTL Inverter: Input = Logic 0 (0V)

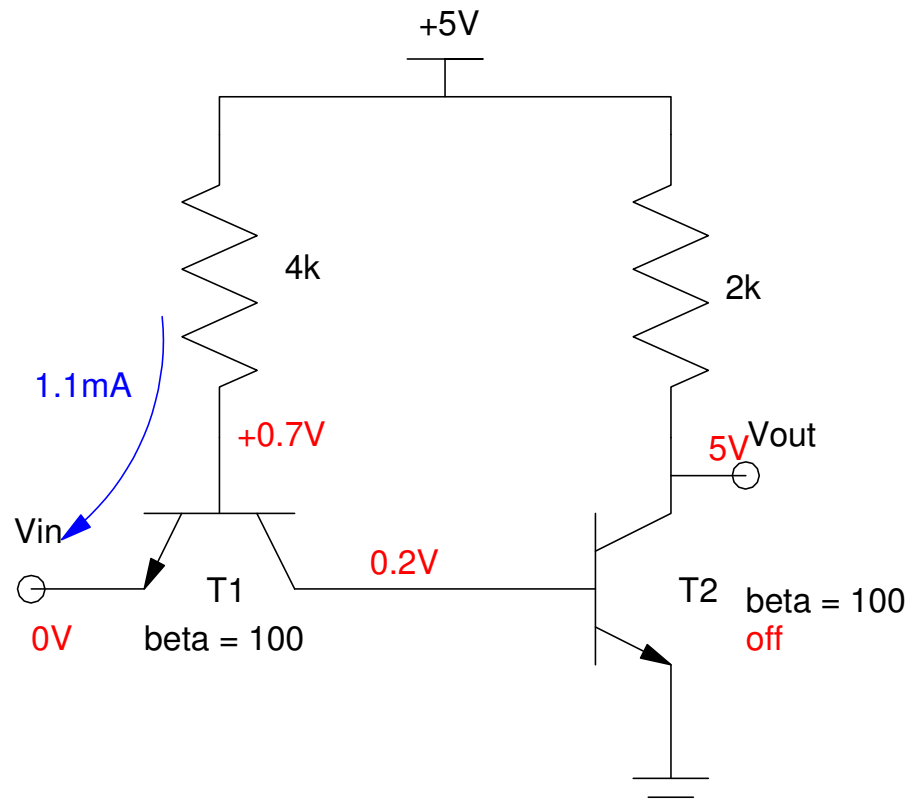- T1 saturates
- T2 is off
- $V_{out} = 5V$



TTL Inverter: Input = Logic 1 (5V)

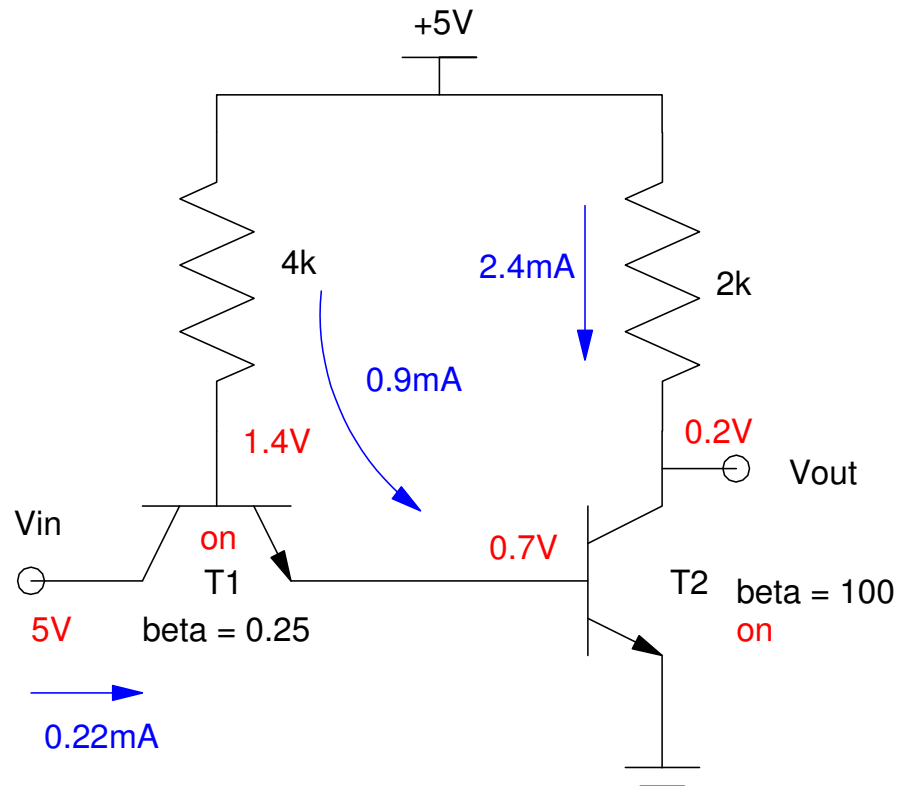- T1 flips (NPN becomes PNP, with lousy gain)
- T1 on (active mode)
- T2 saturates



Power: The power dissipated in this inverter is

$V_{in} = 0V$:


$$I = 1.1mA$$

$$P = VI = (5V)(1.1mA) = 5.5mW$$

$V_{in} = 5V$:


$$I = 0.9mA + 2.4mA = 3.3mA$$

$$P = VI = (5V)(3.3mA) = 16.5mW$$

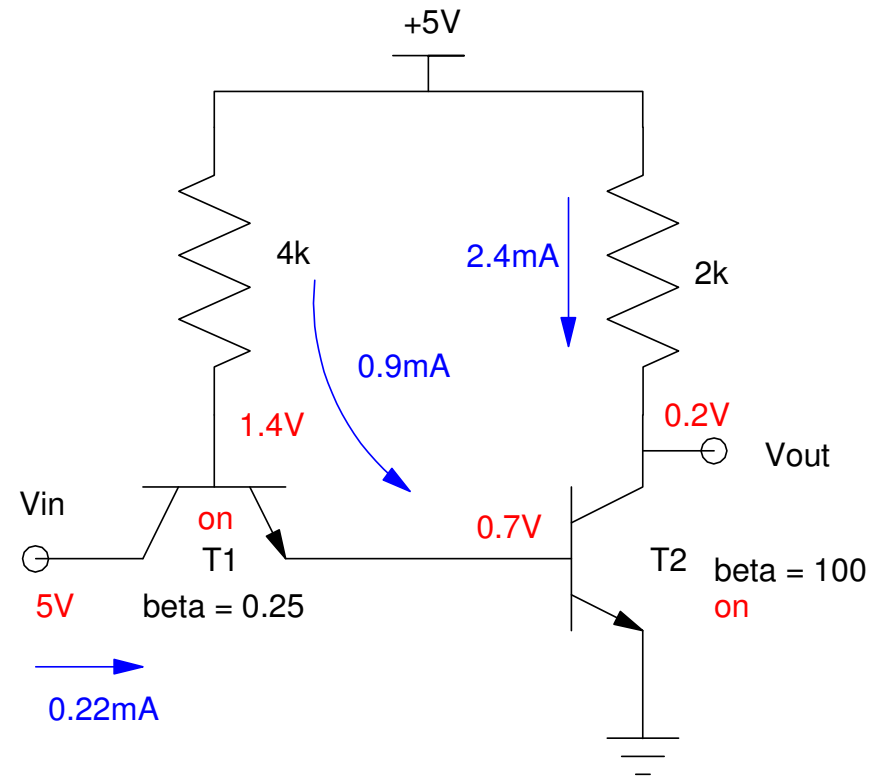


Logic Levels: To turn on T1, $V_{in} > 0.9V$: (V_b for T2 is $0.7V$. V_{ce} for T1 is about $0.2V$. V_{in} needs to be at least $0.7V + 0.2V$).

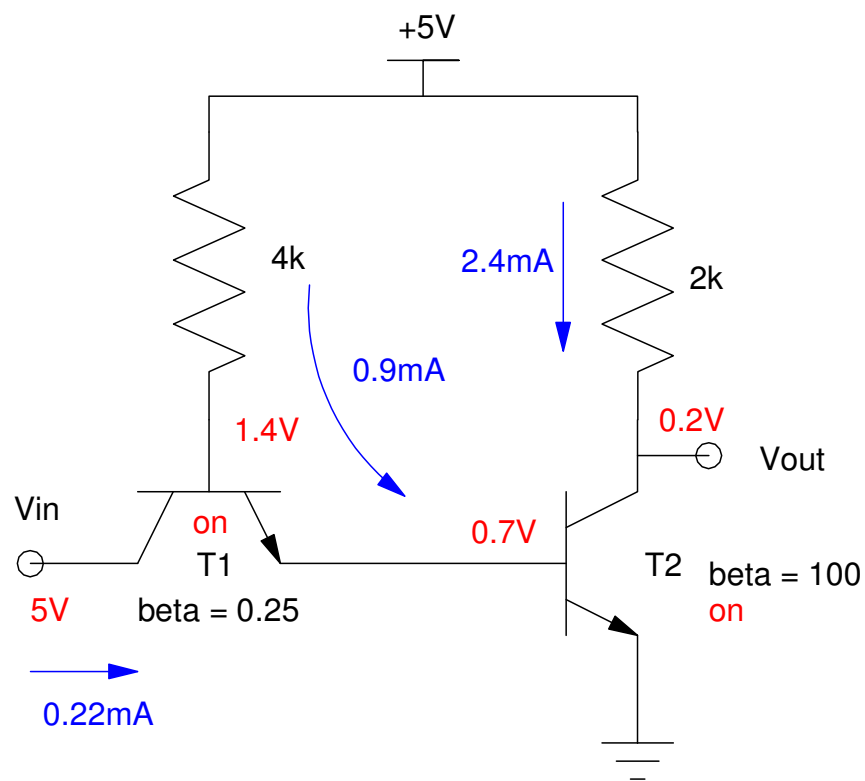- Logic Level 0 is a voltage less than $0.9V$.
- Logic level 1 is a voltage slightly higher than this.



In CircuitLab, you can test this by sweeping the input voltage and noting when the output is logic level 1 or 0.

 - $V_{in} > 700\text{mV}$ Transistor is saturated (Logic level 1 is more than 700mV)
- $V_{in} < 522\text{mV}$ Transistor is off (Logic level 0 is less than 522mV)




Fanout:

Each load


- Draws 0.22mA
- Drops V_{out} by 0.44V (2k resistor)
- For a 2V drop in V_{out} , you can have 4 gates
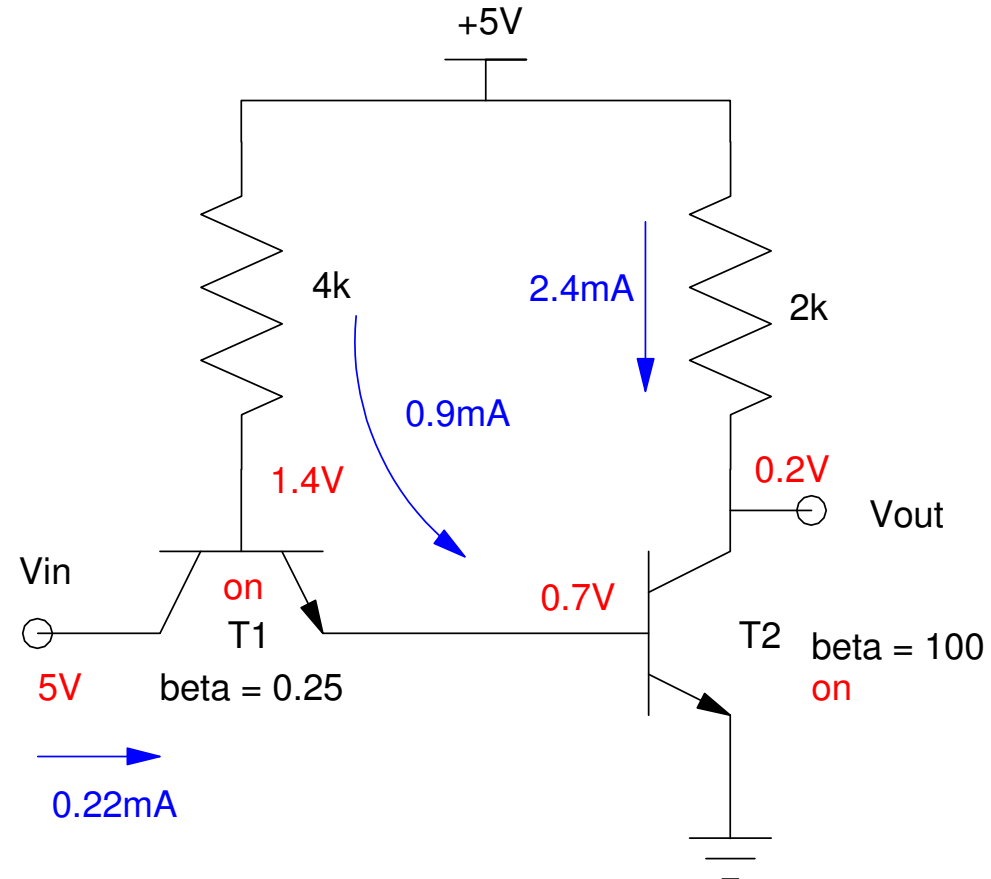
$$N = \frac{2V}{0.44V/gate} = 4.54 \text{ gates}$$



Max Clock Frequency

 It takes about 80ns for the output to go from logic level 0 to level 1. This limits the maximum clock frequency to about 10MHz.



CircuitLab simulation of a TTL inverter with 2MHz input.

7400 Series of TTL Inverters


The previous TTL inverter is the heart of the 7400 series inverters.

Assume $V_{in} = 0V$

- T1 is on
- T2 is off
- T3 is on
- $V_{out} = 5V$

Logic Level 0:

- $V_{in} < 1.6V$

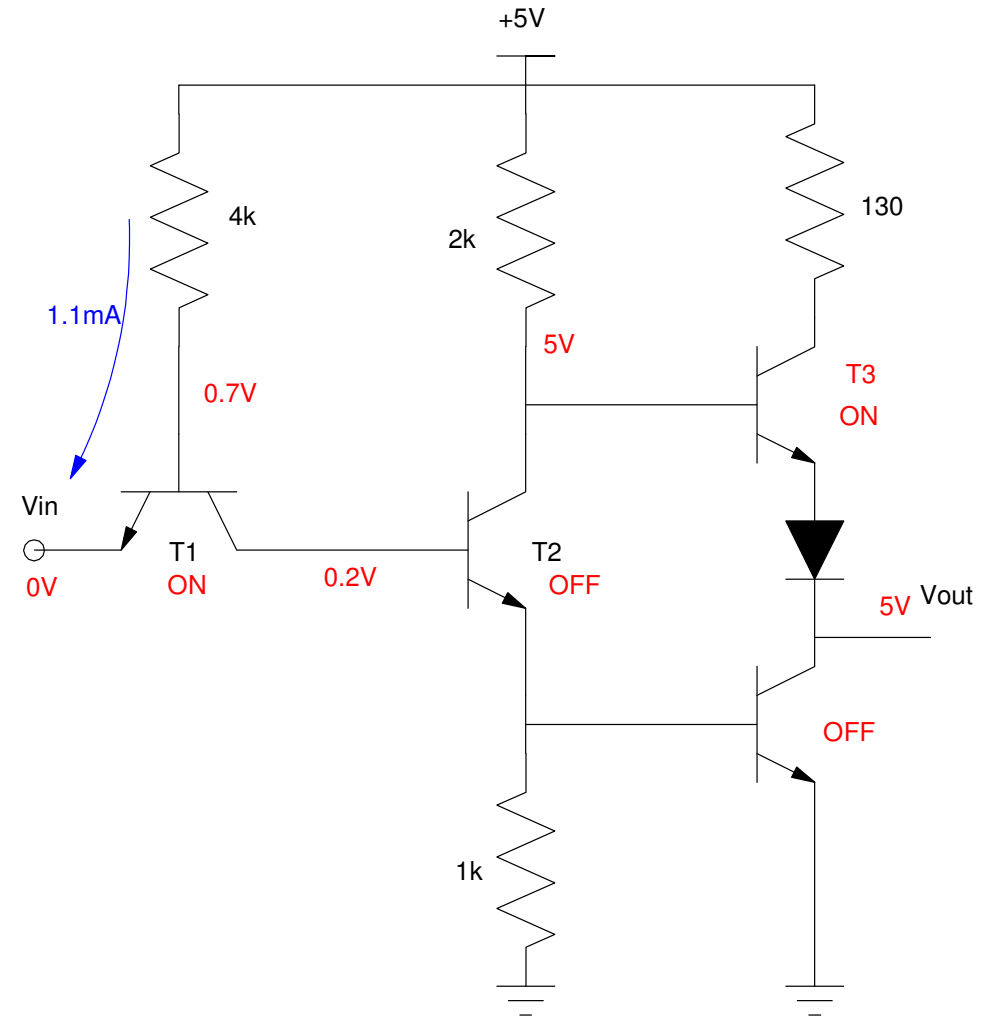


Assume $V_{in} = 5V$

- T1 is active
- T2 is saturated
- T4 is saturated

$V_{out} = 0.2V$

Logic Level 1:

- $V_{in} > 1.6V$

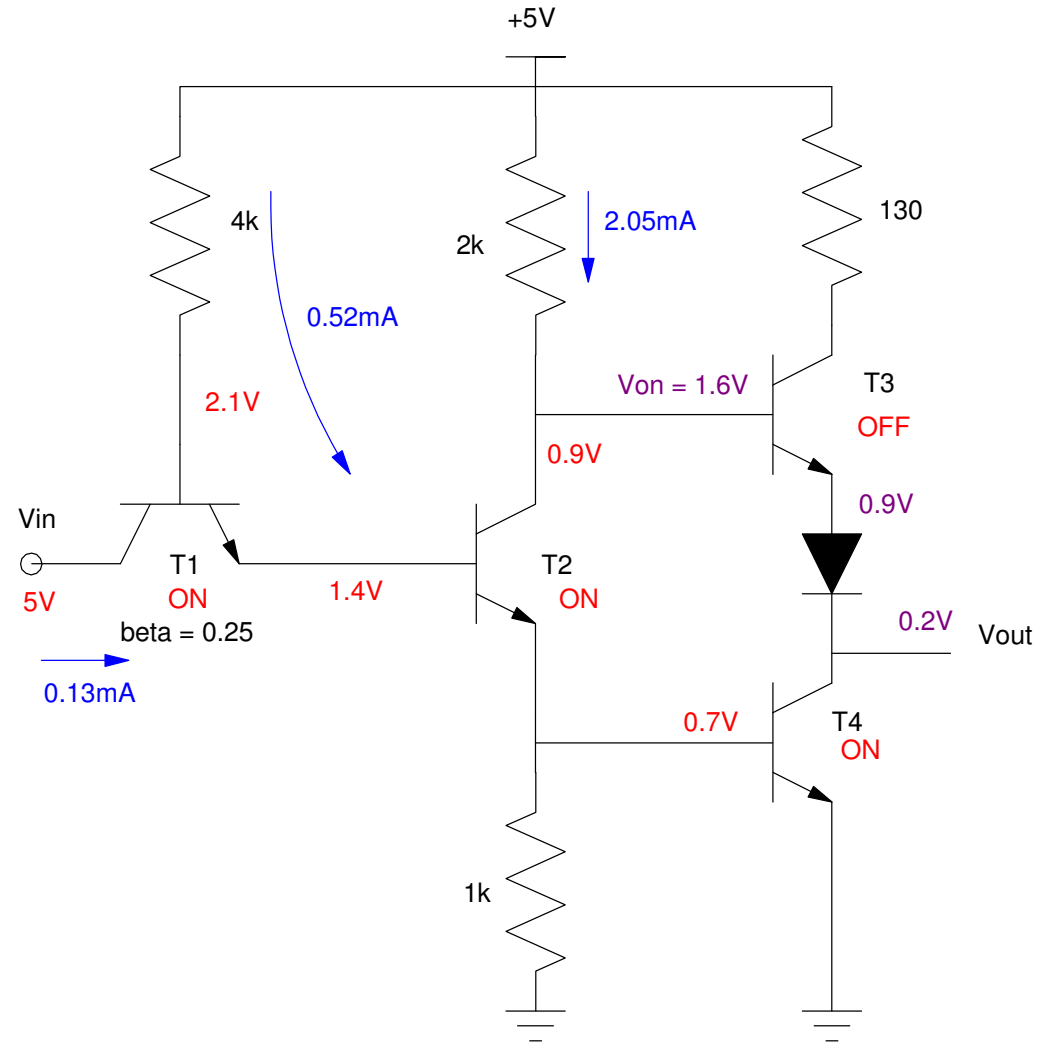

Fanout:

Logic Level 1: $V_{out} > 1.6V$


$$V_{out} = 5V - 130\Omega \cdot I - 0.7V > 1.6V$$

Each load draws $0.13mA$, so


$$5V - 130\Omega \cdot (N \cdot 0.13mA) - 0.7V > 1.6V$$

$$N \leq 159$$


Fanout = 159

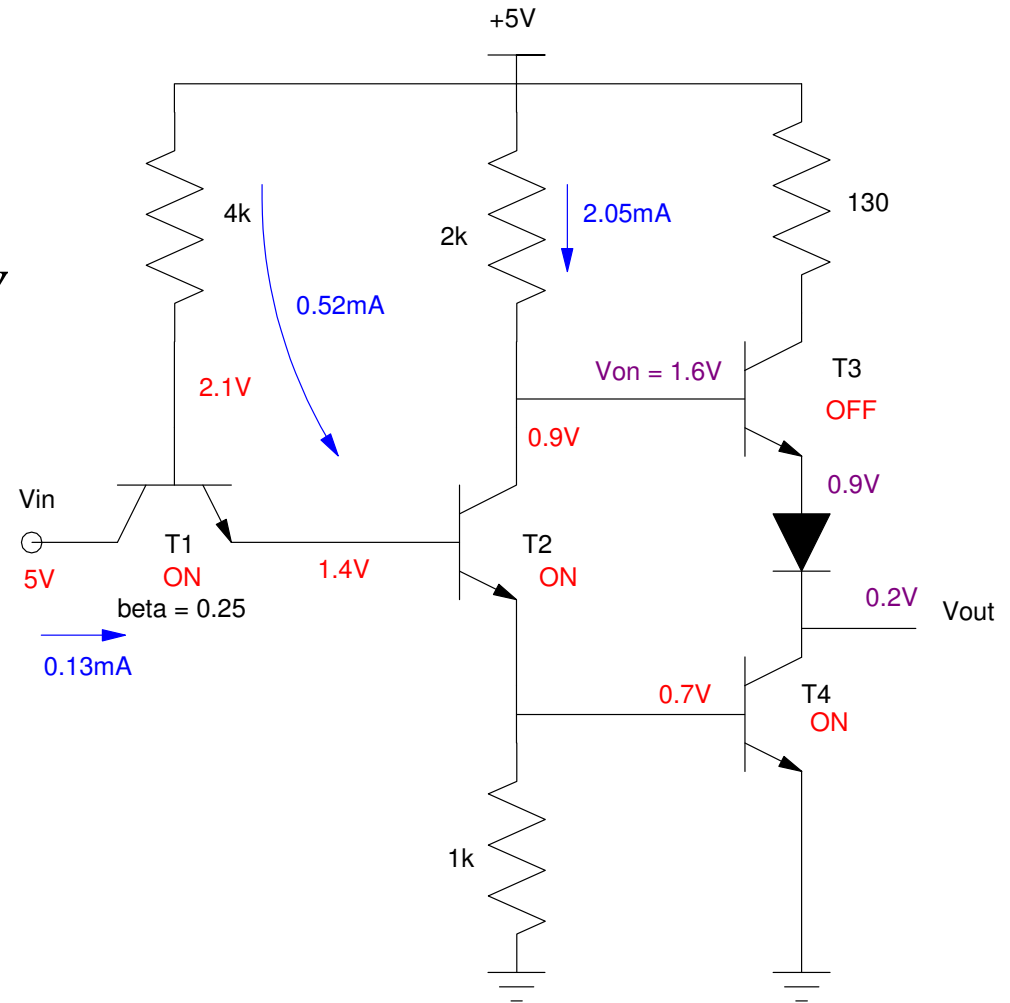


CircuitLab Simulation

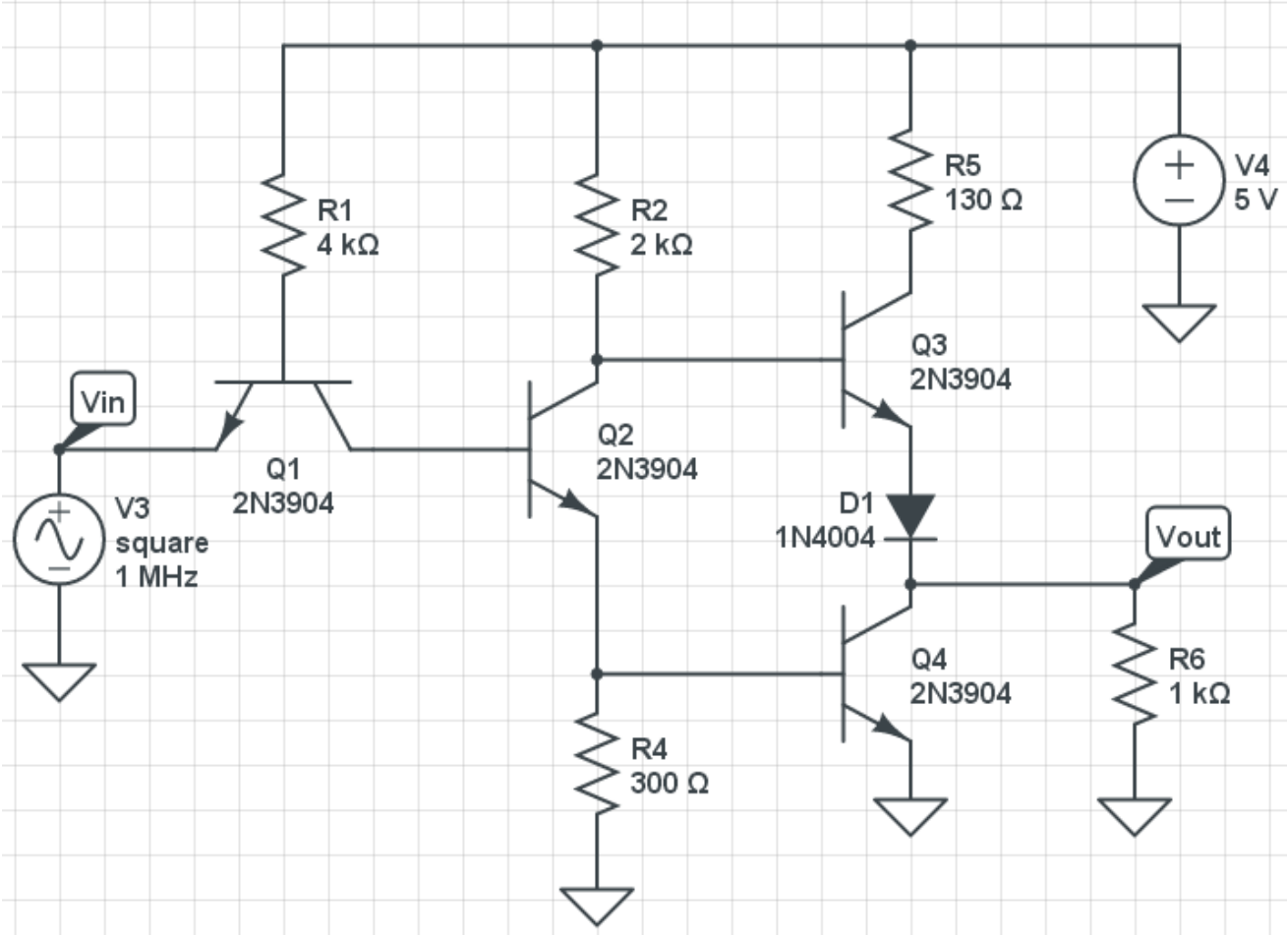

7400 TTL inverter for CircuitLab

 

 
It takes about 400ns to go from logic level 0 to level 1, limiting the clock speed to 2MHz



Current Consumption for TTL Logic. Spikes appear on the current line whenever you have a 1 / 0 transition

TTL NAND gate:

- Add more base pads to T1

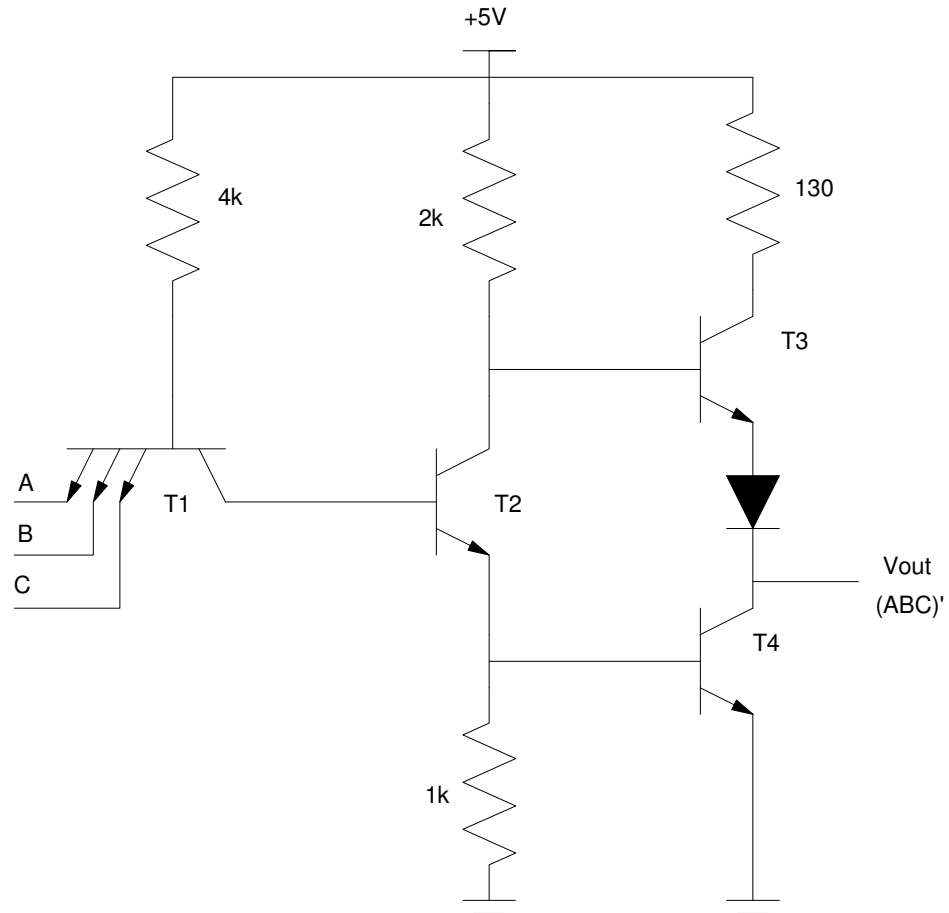

Open Collector Outputs:


Output is

- Floating (logic 1)
- Ground (logic 0)

Needs a pull-up resistor to see a voltage

Advantages:

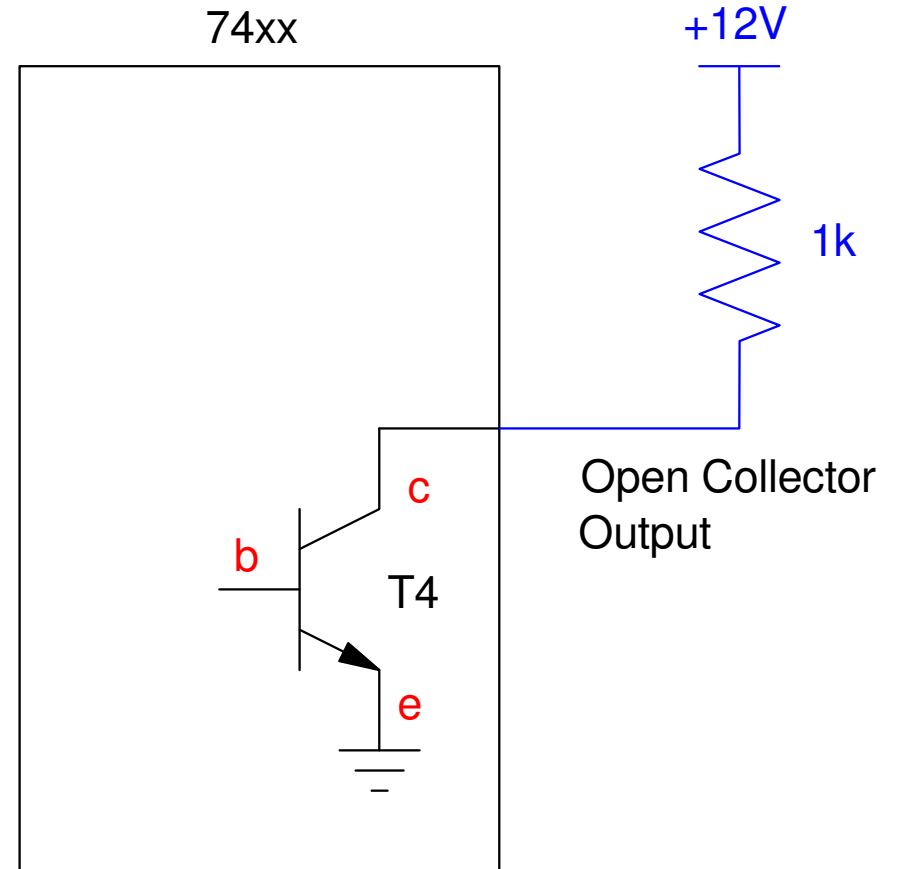- Allows any output voltage (12V)
- Can drive LEDs directly
- Allows for wire-OR logic



Wired-OR Logic

Used for CAN bus


- Zero-priority encoding
- If any driver outputs 0V (transistor saturated), output is 0V

Example:

A = 1 1 0 0 1 0 1 1 0
B = 1 1 0 1 1 1 0 1 1
C = 1 0 1 1 0 1 1 1 0

C goes first


- Then A
- Then B

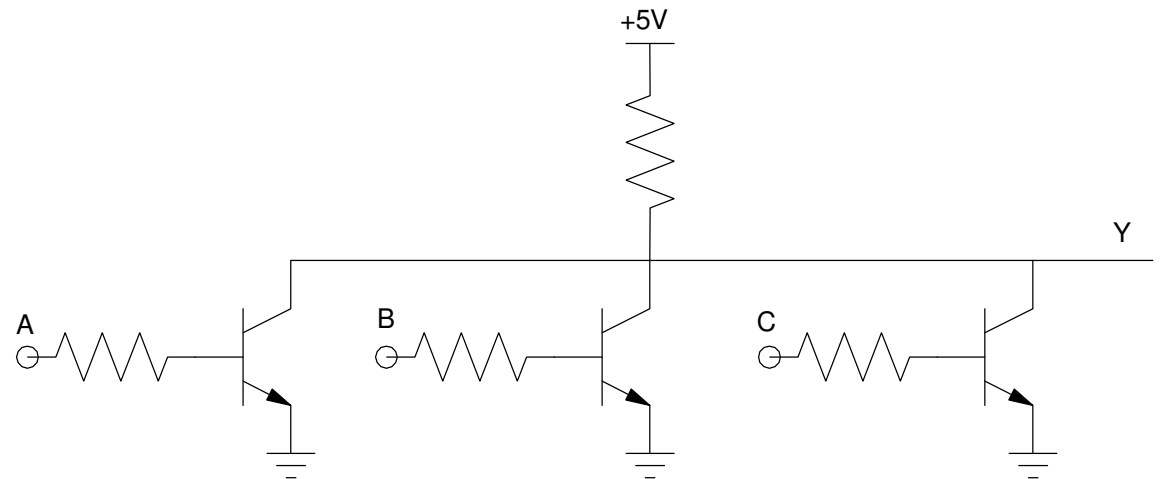

Wired-Or Example:

Determine the voltages and currents

- Assume 3904 transistors & $R = 1k$

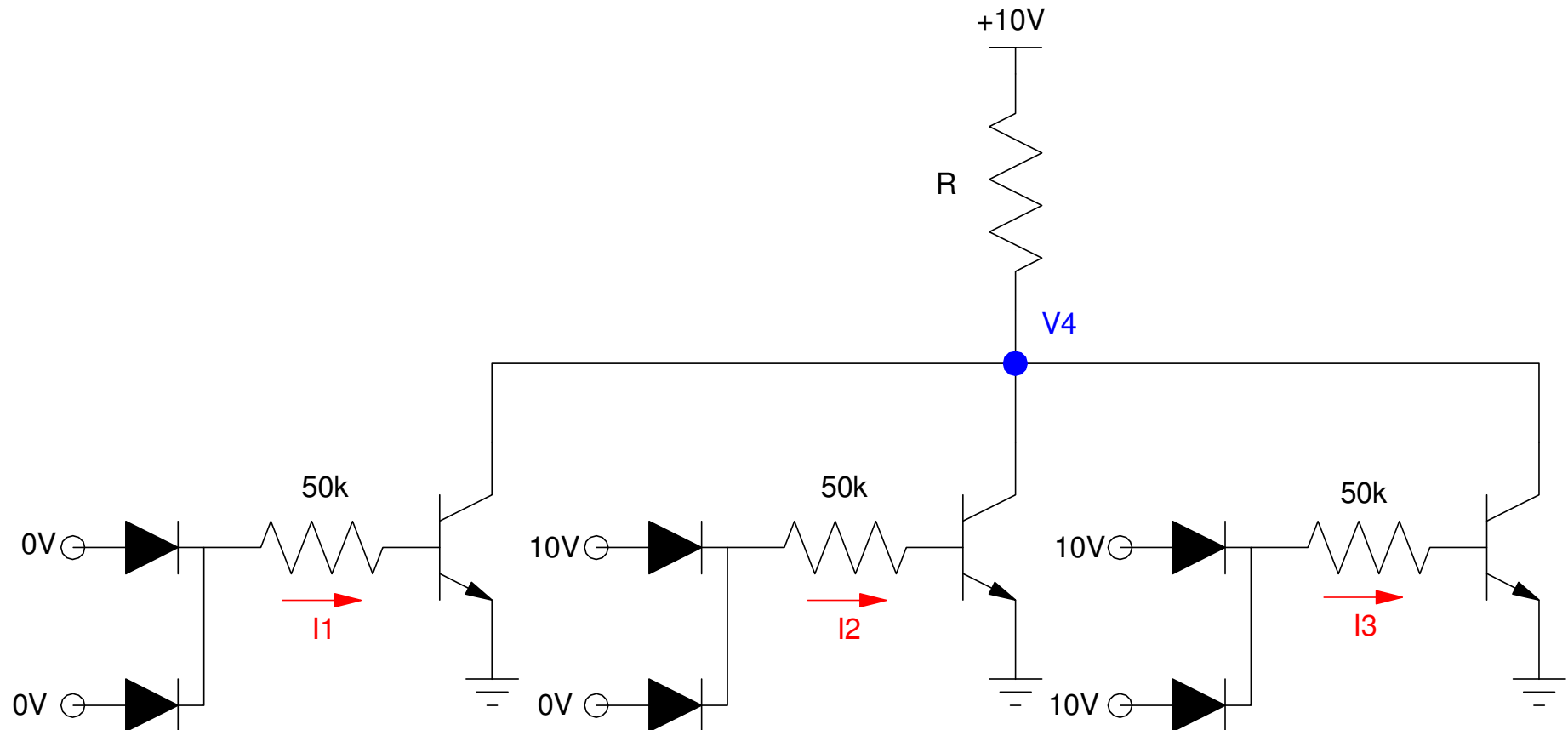

Summary

TTL Logic is faster than DTL

- Removing the diode removes a capacitor
- Results in faster switching

Wired-or logic allows

- You to shift logic levels (12V instead of 5V), and
- Multiple inputs without conflicts
 - ◆ 0V always wins
 - ◆ Zero-priority encoding