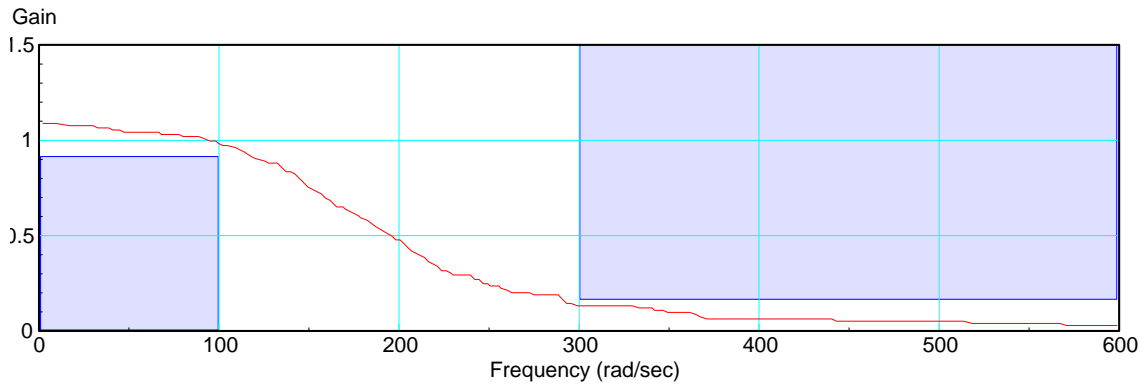


ECE 321 - Homework #3


Filters, 2-port models. Due Monday, November 23rd

- 1) Give the transfer function for a filter which meets the following requirements
 - $\omega < 100$ rad/sec Gain > 0.9
 - $\omega > 500$ rad/sec Gain < 0.1
- 2) Verify that your filter meets these requirements in MATLAB (or like program)
- 3) Design an op-amp circuit to implement your filter.




Problem 1-3

- 4) Give the transfer function for a filter which meets the following requirements
 - $90 < \omega < 110$ rad/sec Gain > 0.9
 - $\omega < 50$ rad/sec Gain < 0.1
 - $\omega > 150$ rad/sec Gain < 0.1
- 5) Verify that your filter meets these requirements in MATLAB (or like program)
- 6) Design an op-amp circuit to implement your filter.

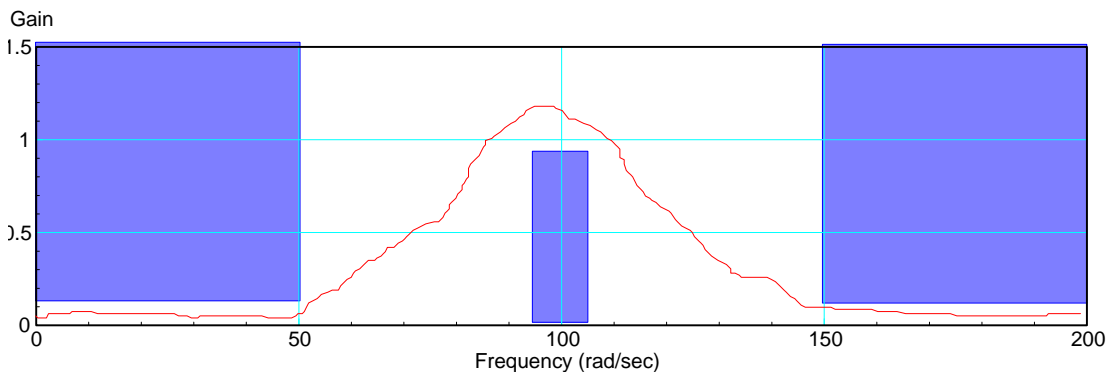

Problem 4-6

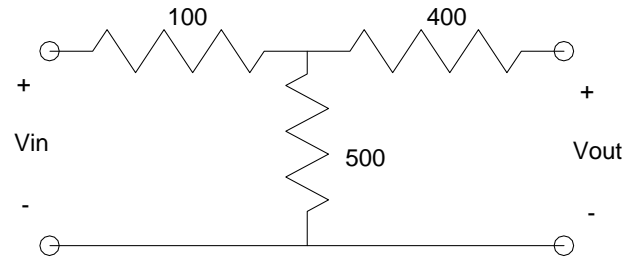7) Give a 2-port model for the following circuit



8) Give a 2-port model for the following circuit

