

ECE 321 - Quiz 4: Name _____

MOSFET Amplifiers - December 10, 2015


1) MOSFET DC Analysis: Find R_d , R_1 , and R_2 so that the Q-point for the following circuit is

- $V_{ds} = 5V$
- $I_{ds} = 1mA$

Assume

- $V_{th} = 2.0V$
- $k_n = 1mA/V^2$
- $I_{ds} = \frac{k_n}{2}(V_{gs} - V_{th})^2$ *saturated region*

R1	R2	Rd

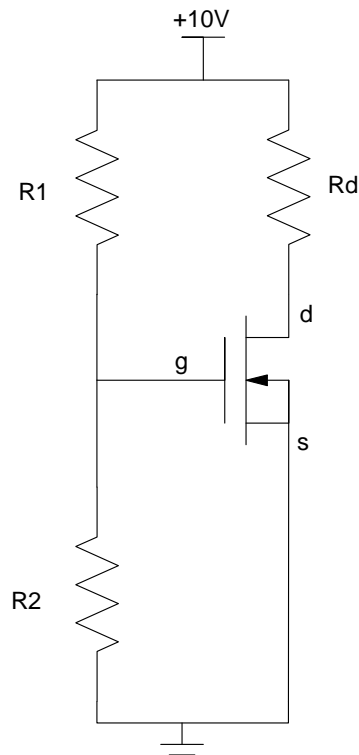


2) To stabilize the Q-point for variations in the turn-on voltage, R_s is added. Find R_1 and R_2 so that the Q-point is

- $V_{ds} = 5V$

Assume

- $V_{th} = 2.0V$
- $k_n = 1mA/V^2$
- $I_{ds} = \frac{k_n}{2}(V_{gs} - V_{th})^2$ *saturated model*


Ids	R1	R2

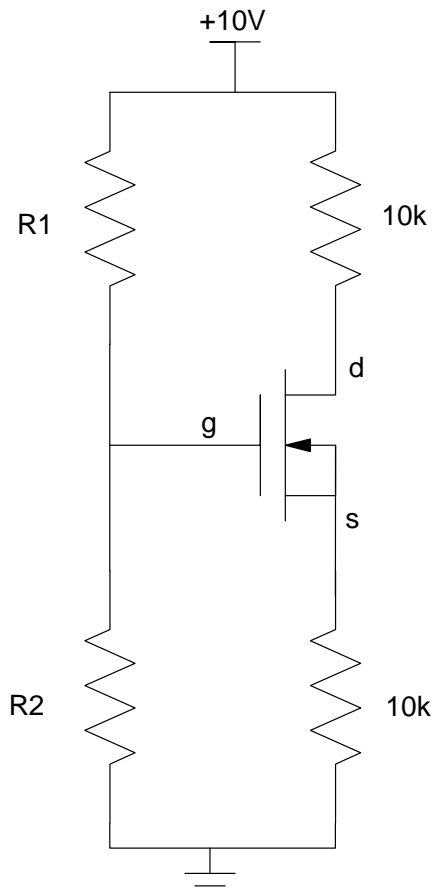


3) The V/I characteristics for a MOSFET are shown below along with a desired load-line.

- Find R_d to give this load line
- Find R_1 and R_2 so that the Q-point is ($V_{ds} = 5.5V$, $I_{ds} = 36\mu A$) and
- $R_1 \parallel R_2 = 100k$

Assume $V_{th} = 2V$


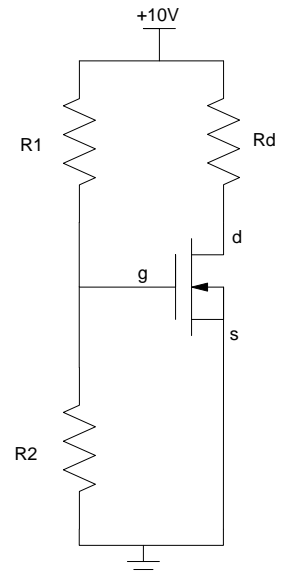


R_d	R_1	R_2

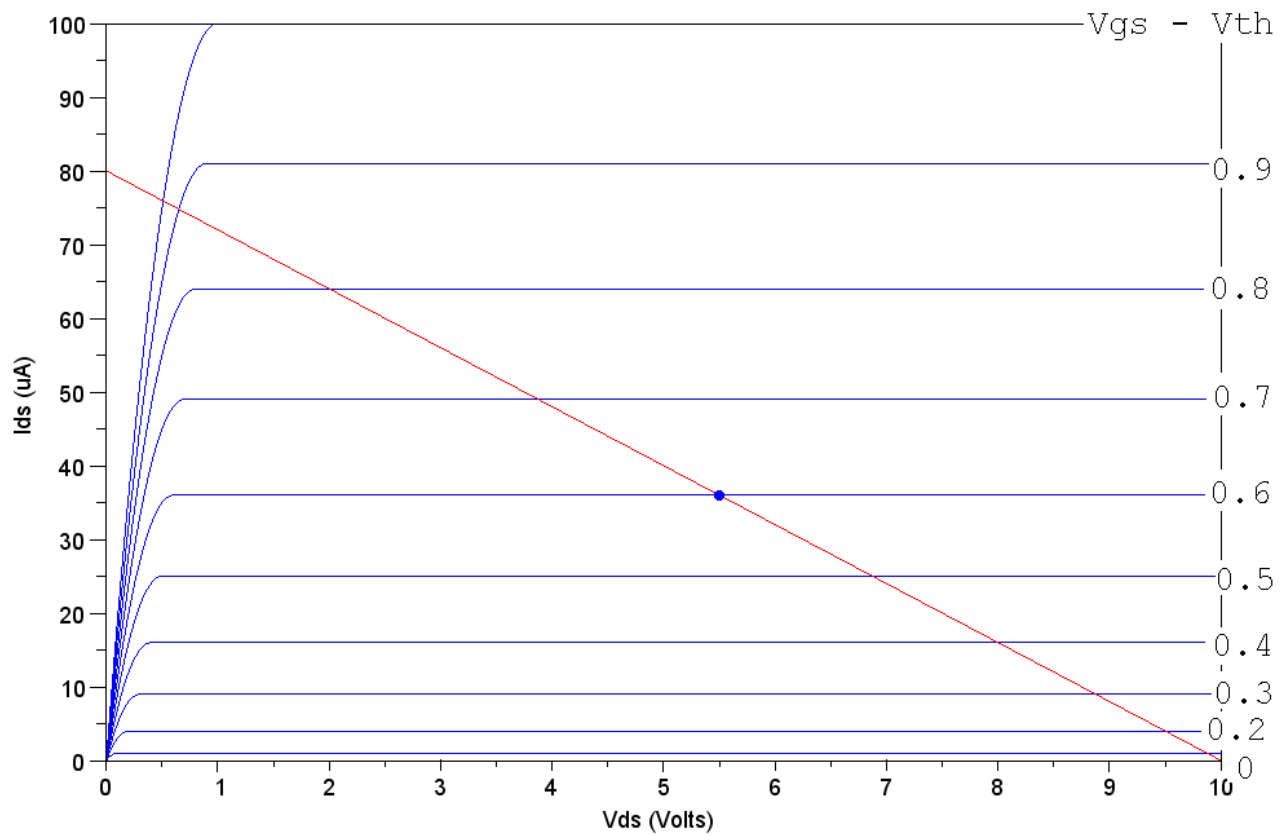

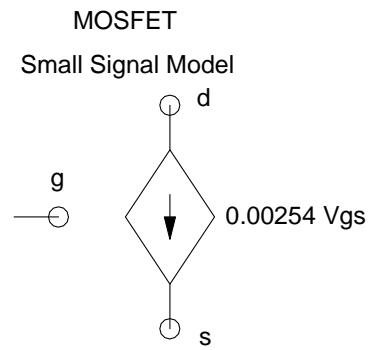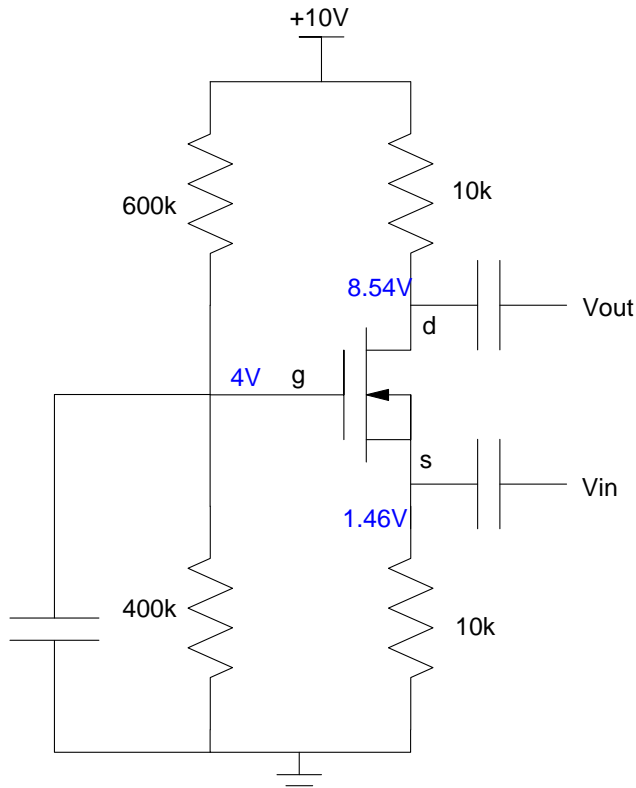4) Draw the small-signal model for the following amplifier. Assume the small-signal model for the MOSFET is

- $k_n = 1\text{mA/V}^2$
- $g_m = 0.00254\frac{\text{A}}{\text{V}^2}$



5) Find the 2-port model for the following MOSFET amplifier

Rin	Ai	Rout	Ao

