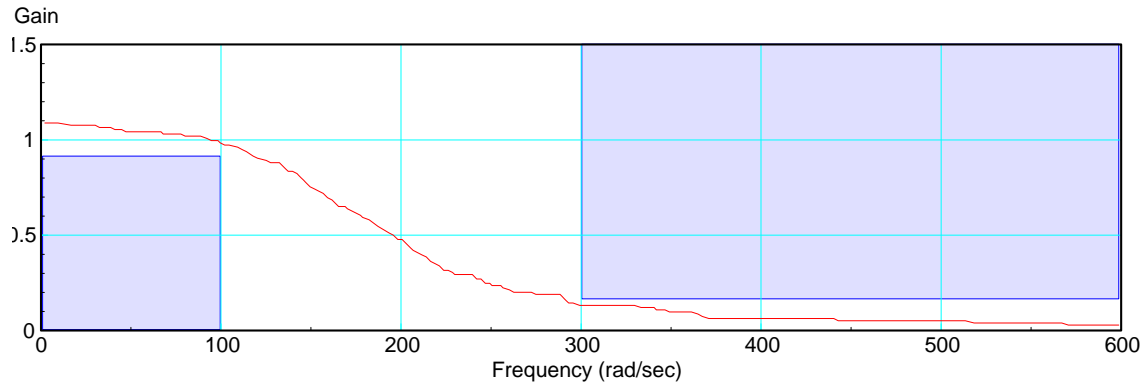


ECE 321 - Homework #3

Filters, 2-port models. Due Monday, November 23rd

1) Give the transfer function for a filter which meets the following requirements

- $\omega < 100$ rad/sec Gain > 0.9
- $\omega > 500$ rad/sec Gain < 0.1



There are multiple solutions. One that works:

Filter Order:

$$\left(\frac{100}{300}\right)^n < 0.1$$

$$n > 2.09$$

Assume a 3rd order filter.

Filter Type: Choose a Butterworth low pass filter (corner = 100 as a first guess)


$$G(s) = \left(\frac{100^3}{(s+100)(s+100\angle 60^\circ)(s+100\angle -60^\circ)} \right)$$

Filter Corner: Adjust in SciLab until it meets the specs

Corner	Gain at 100	Gain at 300
100	0.71	0.037
120	0.865	0.063
130	0.910	0.081

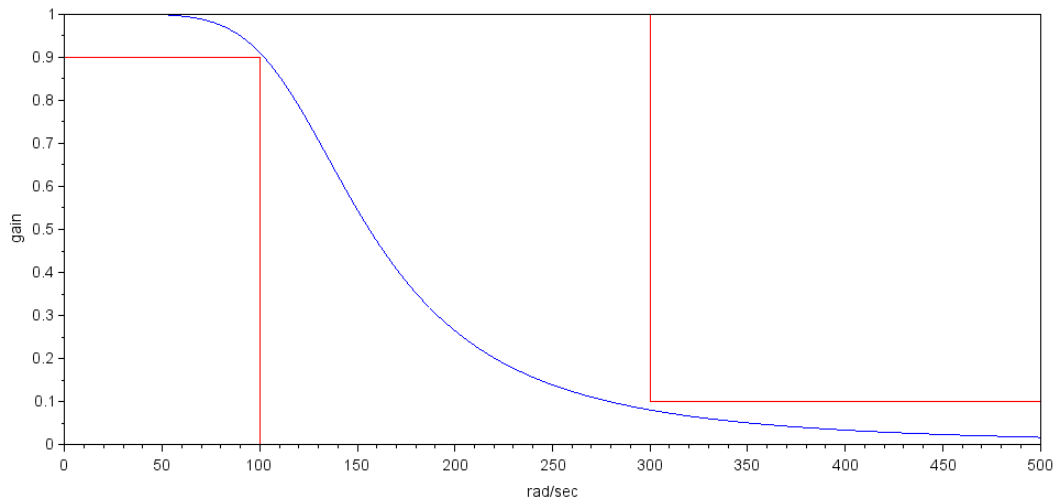2) Verify that your filter meets these requirements in MATLAB (or like program)

```
-->j = sqrt(-1);  
-->s1 = -130;  
-->s2 = -130*exp(j*60*pi/180)  
-->s3 = -130*exp(-j*60*pi/180)  
  
-->w = [0:500]';  
-->s = j*w;  
  
-->G = 130^3 ./ ( (s-s1) .* (s-s2) .* (s-s3) );  
-->plot(w,abs(G),'b');  
  
-->xlabel('rad/sec');  
-->ylabel('gain');  
  
-->plot([0,100,100],[0.9,0.9,0],'r');  
-->plot([300,300,500],[1,0.1,0.1],'r');
```



3) Design an op-amp circuit to impliment your filter.

$$\frac{1}{RC} = 130$$

Let


$$R = 100k, \quad C = 76.9nF$$

$$3 - k = 2 \cos(60^\circ)$$

$$k = 2 = 1 + R1/R2$$

Let

$$R1 = R2 = 100k$$

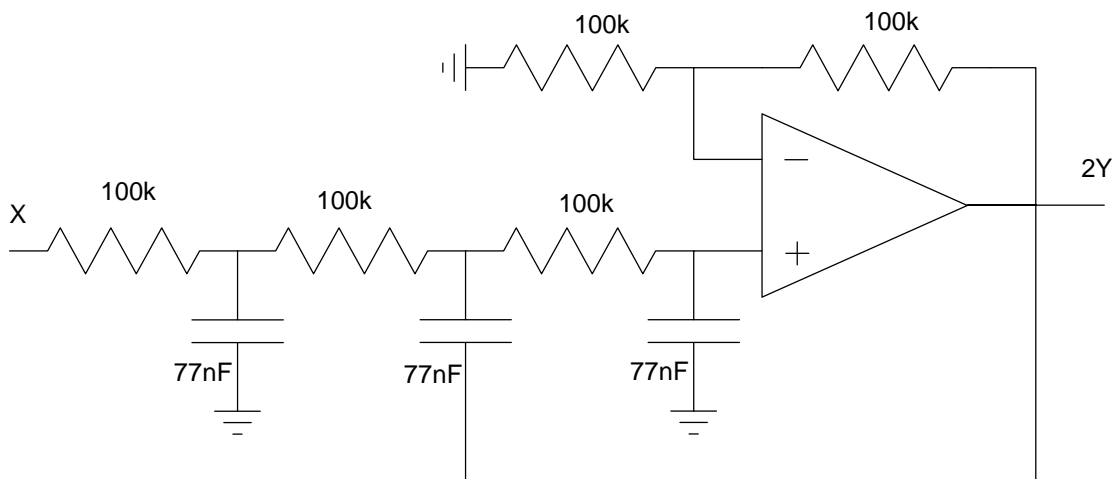

note: This filter has a DC gain of 2 (vs 1). You can reduce the gain with a voltage divider - or just incorporate that extra gain of 2 elsewhere.

4) Give the transfer function for a filter which meets the following requirements

- $90 < \omega < 110$ rad/sec Gain > 0.9
- $\omega < 50$ rad/sec Gain < 0.1
- $\omega > 150$ rad/sec Gain < 0.1

The center frequency = 100 rad/sec, meaning the complex part of the pole should be 100 rad/sec

The bandwidth is 10 rad/sec, so let the real part be 10

1st Attempt: Single Pole

Try a single pole at $-10 + j100$:

$$s = -10 + j100$$

$$G(s) = \left(\frac{20s}{(s+10+j100)(s+10-j100)} \right)$$

ω	50	90	110	150
$G(j\omega)$	0.13	0.67	0.74	0.23

A single pole won't work.

2st Attempt: Try two poles (plus their conjugate)

```
-->s1 = -10*exp(j*45*pi/180) + j*100
-->s2 = -10*exp(-j*45*pi/180) + j*100
-->s3 = conj(s1)
-->s4 = conj(s2)
```

```
-->w = [0:0.1:200]';
-->s = j*w;
```

```
-->G = s ./ ( (s-s1) .* (s-s2) .* (s-s3) .* (s-s4) );
-->max(abs(G))
```


```
0.0000250
```


```
-->k = 1/ans
```

```
40000.125
```

```
-->G = k*G;
```
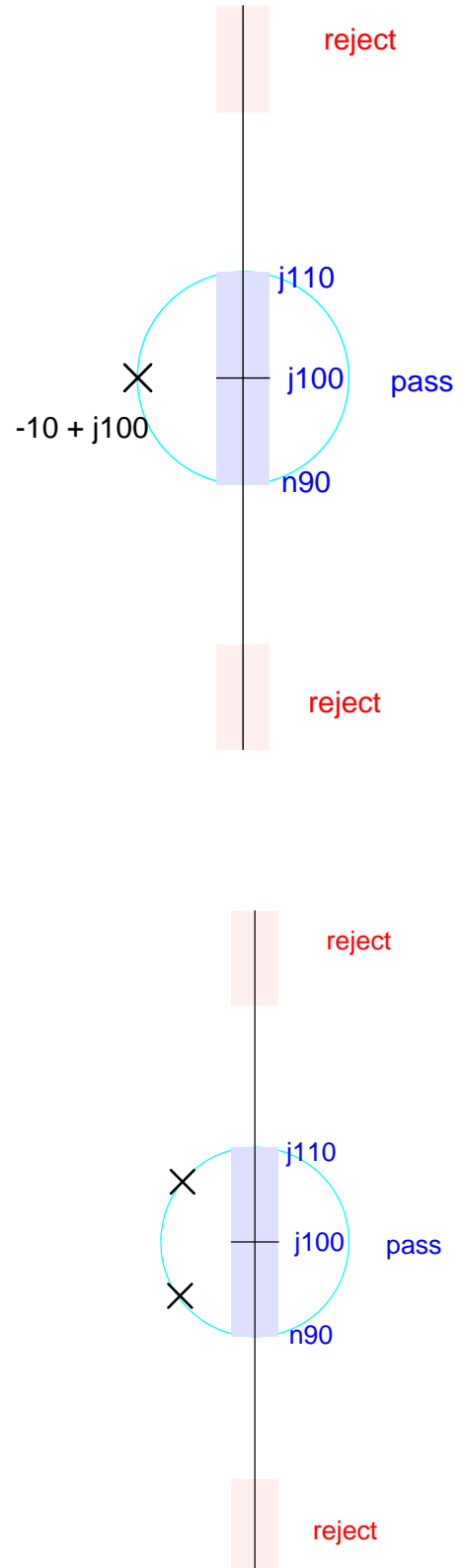
```
-->plot(w,abs(G))
-->plot([0,50,50],[0.1,0.1,1],'r');
-->plot([150,150,300],[1,0.1,0.1],'r');
-->plot([150,150,200],[1,0.1,0.1],'r');
-->plot([90,90,110,110],[0,0.9,0.9,0],'r');
```



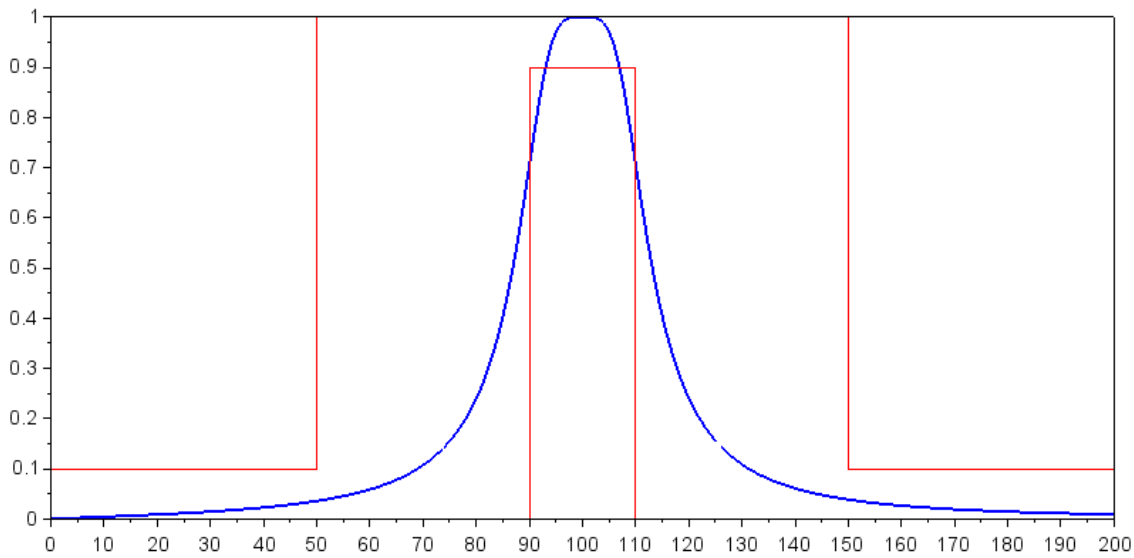

$$G(s) = \left(\frac{40,000s}{(s+10\angle 45^\circ + j100)(s+10\angle -45^\circ + j100)(s+10\angle 45^\circ - j100)(s+10\angle -45^\circ - j100)} \right)$$

3rd Attempt: Try a wider bandwidth with poles at 15


```
-->s1 = -15*exp(j*45*%pi/180) + j*100;
-->s2 = -15*exp(-j*45*%pi/180) + j*100;
-->s3 = conj(s1)
-->s4 = conj(s2);


-->G = s ./ ( (s-s1) .* (s-s2) .* (s-s3) .*
(s-s4) );

-->k = 1 / max(abs(G))

90001.424

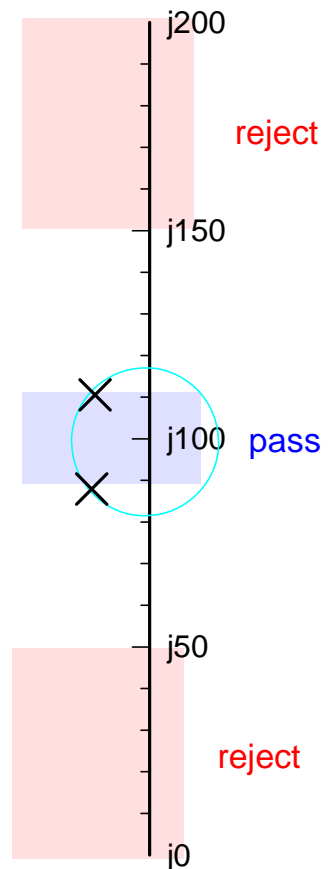-->G = G*k;
-->plot(w,abs(G))
-->plot([90,90,110,110],[0,0.9,0.9,0], 'r');
-->plot([150,150,200],[1,0.1,0.1], 'r');
-->plot([0,50,50],[0.1,0.1,1], 'r');
```



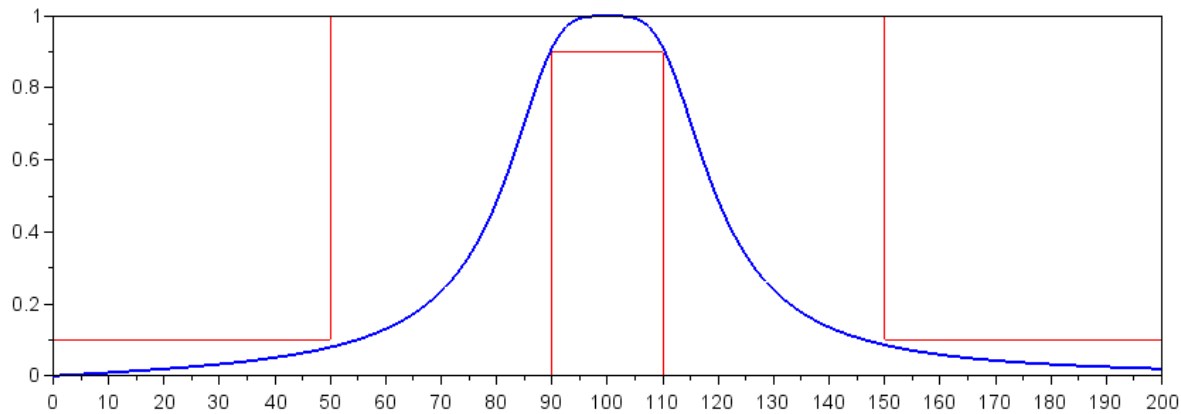

$$G(s) = \left(\frac{90,000s}{(s+15\angle 45^\circ + j100)(s+15\angle -45^\circ + j100)(s+15\angle 45^\circ - j100)(s+15\angle -45^\circ - j100)} \right)$$

5) Verify that your filter meets these requirements in MATLAB (or like program)

see above

6) Design an op-amp circuit to implement your filter.

$$G(s) = \left(\frac{90,000s}{(s+111.11\angle \pm 84.522^\circ)(s+90.02\angle \pm 83.23^\circ)} \right)$$

$$G(s) = \left(\frac{4.018s}{s+111.11\angle \pm 84.522^\circ} \right) \left(\frac{2.764 \cdot 90.02^2}{s+90.02\angle \pm 83.23^\circ} \right)$$

$$G(s) = \left(\frac{4.018s}{s^2+21.21s+12,345} \right) \left(\frac{2.764 \cdot 90.02^2}{s+90.02\angle \pm 83.23^\circ} \right)$$

Stage 1:

$$\left(\frac{1}{R_1 C} \right) = 4.018$$

$$C = 1\mu F \quad R_1 = 248k$$

$$\left(\frac{2}{R_3 C} \right) = 21.21$$

$$C = 1\mu F, \quad R_3 = 94.3k$$

$$\left(\frac{R_1 + R_2}{R_1 R_2} \right) \left(\frac{1}{R_3 C^2} \right) = 12,345$$

$$R_2 = 861$$


Stage 2:

$$\left(\frac{1}{RC} \right) = 90.02$$

$$R = 100k \quad C = 0.111\mu F$$


$$3 - k = 2 \cos(83.23^\circ)$$

$$k = 2.76 = 1 + R1/R2$$

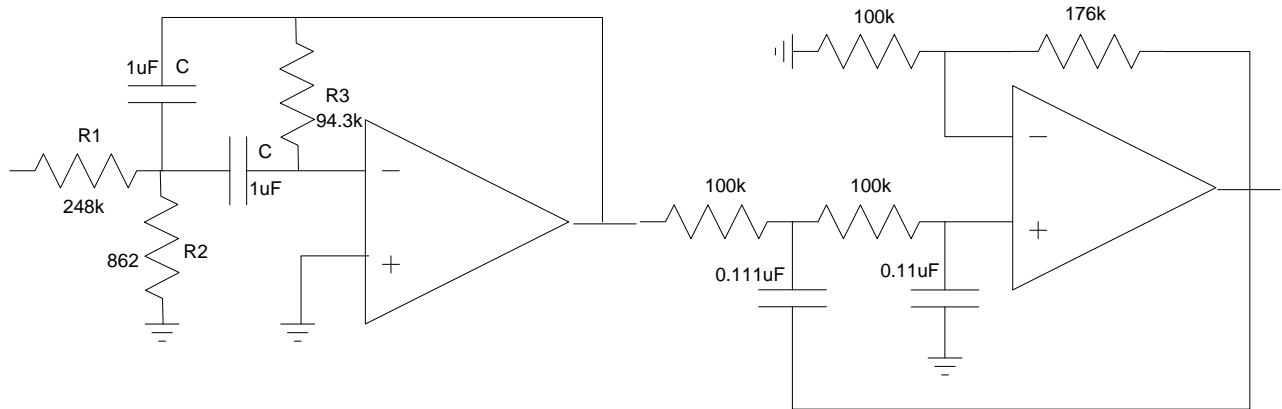

Problem 4-6

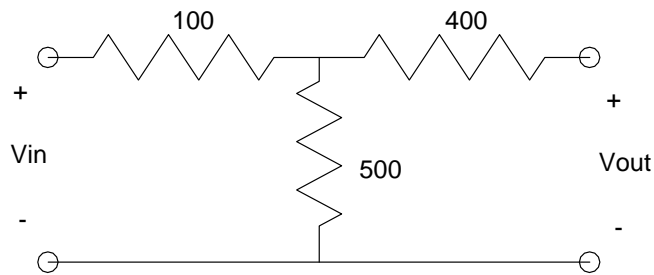7) Give a 2-port model for the following circuit



Rin: Short Vout, measure the resistance looking in

$$R_{in} = 100 + 400 || 500$$

$$R_{in} = 222$$

Ai Set Vout = 1V, measure Vin

$$A_i = \left(\frac{500}{500+400} \right) = 0.555$$


Rout: Short Vin, measure the resistance at the output

$$R_{out} = 400 + 100 || 500$$


$$R_{out} = 483$$

Ao: Set Vin = 1V, measure Vout
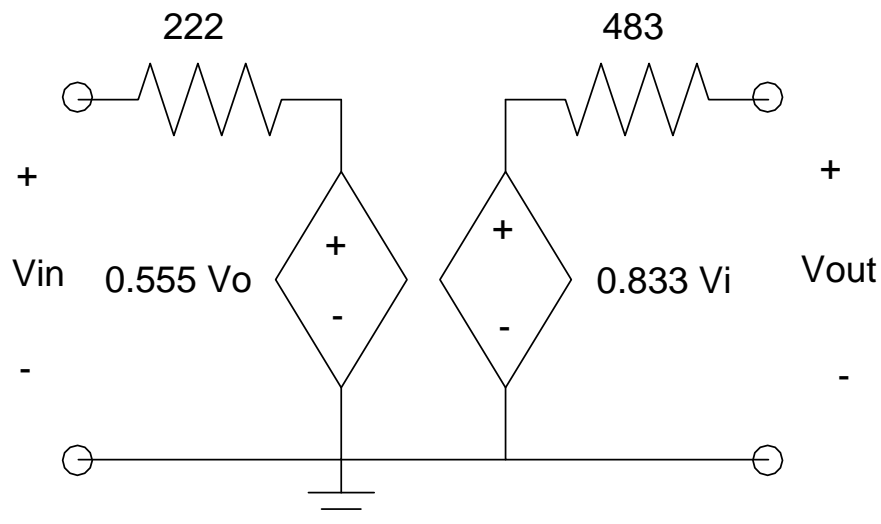
$$A_o = \left(\frac{500}{500+100} \right) = 0.833$$



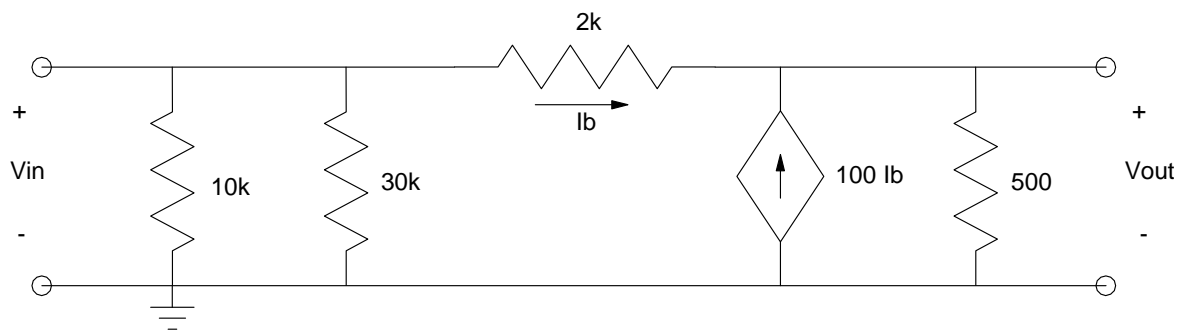8) Give a 2-port model for the following circuit



Rin: Set $V_{out} = 0V$, measure the resistance at the input

$$R_{in} = 10k || 30k || 2k$$

$$R_{in} = 1579\Omega$$

Ai: Set $V_{out} = 1V$, measure the voltage at the input

$$A_i = \left(\frac{10k || 30k}{10k || 30k + 2k} \right) = 0.7895$$

Rout: Set $V_{in} = 0V$, measure the resistance at the output. This isn't obvious, so apply a 1V test voltage and measure the current

$$I = \frac{1}{500} + \frac{1}{2k} + 100 \left(\frac{1}{2k} \right) = 52.5mA$$

$$R_{out} = \frac{V}{I} = \frac{1V}{52.5mA} = 19.04\Omega$$

Ao: Set $V_{in} = 1V$, measure V_{out} . This isn't obvious so use voltage nodes

$$\left(\frac{V_{out}-1}{2k} \right) - 100 \left(\frac{1-V_{out}}{2k} \right) + \left(\frac{V_{out}}{500} \right) = 0$$

$$V_{out} = A_o = 0.9619$$

