

ECE 321 - Homework #4



BJT Amplifiers, CE Amplifier. Due Monday, November 30th

Assume a BJT transistor with a gain of 100

DC Analysis

1) Determine the Q-point for the following circuit.

Redraw the circuit

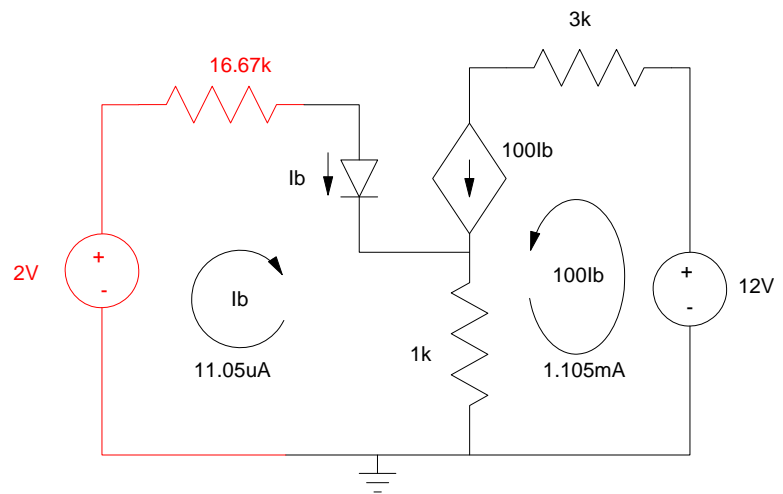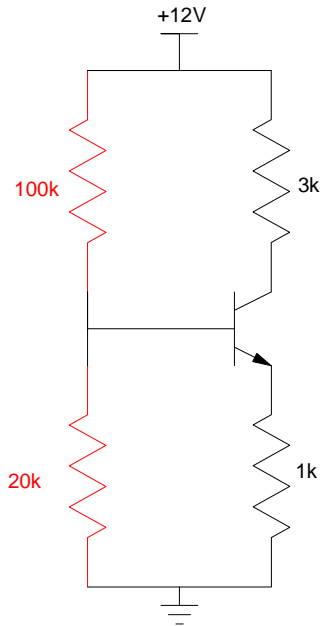

Write the loop equation around I_b :

$$-2 + 16667I_b + 0.7 + 1000(I_b + \beta I_b) = 0$$

$$I_b = 11.05\mu\text{A}$$

then

$$I_c = \beta I_b = 1.105\text{mA}$$

and the Q-point is

$$V_c = 12 - 3k \cdot I_c = 8.686\text{V}$$

$$V_e = (I_b + I_c)1k = 1.116\text{V}$$

$$V_{ce} = V_c - V_e = 7.57\text{V}$$

2) Change R1 and R2 so that

- The Q-point is stabilized for variations in β
- The Q point is $V_{ce} = 6V$

Going backwards, if $V_{ce} = 6V$

$$(12V - 6V) = 3k \cdot I_c + 1k \cdot (I_b + I_c)$$

$$I_c = \frac{6V}{3k + 1.01k} = 1.496mA$$

$$I_b = \frac{I_c}{\beta} = 14.96\mu A$$

To stabilize the Q-point

$$(1 + \beta)R_e \gg R_b$$

$$101k\Omega \gg R_b$$

Let

$$R_b = 10k$$

$$V_{bb} = 0.7V + R_b I_b + R_e (I_b + I_c)$$

$$V_{bb} = 2.361V$$



Converting back to R1 and R2

$$R_1 || R_2 = 10k$$

$$\left(\frac{R_2}{R_1 + R_2} \right) 12V = 2.361V$$

$$R_1 = \left(\frac{12V}{2.361V} \right) 10k = 50.83k$$

$$R_2 = 12.45k$$

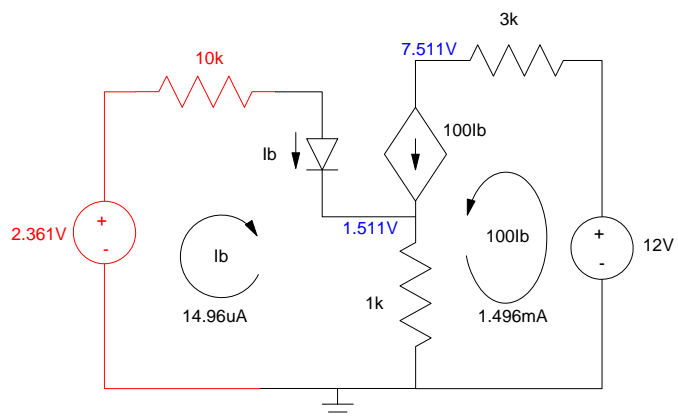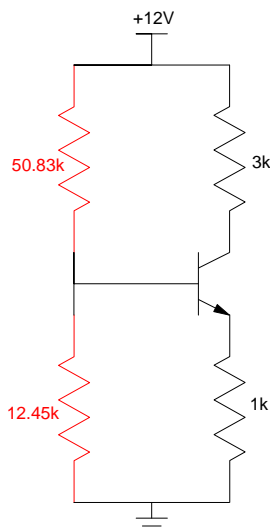


AC Analysis

3) Assume all capacitors are large ($\frac{1}{j\omega C} \ll 1k$). Determine the 2-port model for this circuit

$$r_f = \frac{0.052V}{I_{be}} = \frac{0.052V}{11.05\mu A} = 4706\Omega$$

Redraw the circuit (show on left)

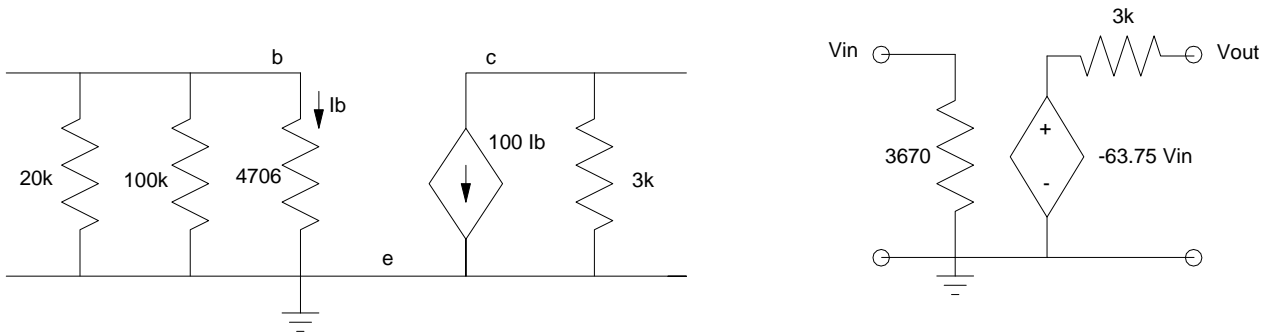

Rin:

$$R_{in} = 20k \parallel 100k \parallel 4706$$

$$R_{in} = 3670$$

Ai = 0 by inspection

Rout:

$$\text{Set } V_{in} = 0V$$

$$100I_b = 0$$

$$R_{out} = 3k$$

Aout:



$$\text{Set } V_{in} = 1V$$

$$I_b = \frac{1V}{4706\Omega} = 212\mu A$$

$$100I_b = 21.25mA$$

$$V_{out} = -3000 \cdot I_c = -63.75V$$

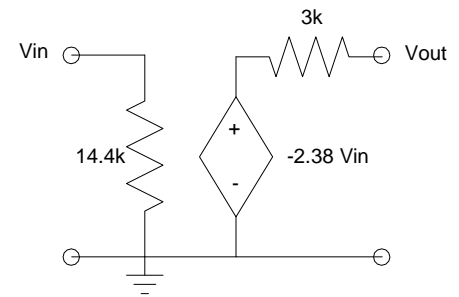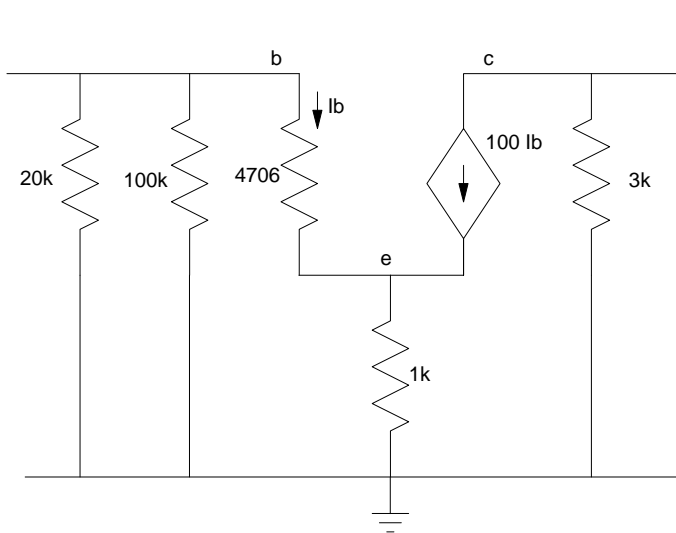4) Determine the 2-port model for this circuit when C_e is removed



R_{in} : Short V_{out} , apply 1V at V_{in} , determine the current

$$I_{in} = \frac{1}{20k} + \frac{1}{100k} + \frac{1}{4706+101k}$$

$$R_{in} = 20k \parallel 100k \parallel (4706 + 101k)$$

$$R_{in} = 14.4k$$

$A_i = 0$

R_{out} : Short V_{in}

$$V_b = 0$$

$$V_e = 0$$

$$I_b = 100I_b = 0$$

$$R_{out} = 3k$$

A_o : Apply 1V at V_{in}

$$I_b = \frac{1}{4706+101k} = 9.46\mu A$$

$$I_c = 100I_b = 946\mu A$$

$$V_o = -3000I_c = -2.38V$$

ECE 321 - Homework #5 & #6

Term project (part 1). Due Monday, December 7th

Term project (part 1). Due Monday, December 7th

Term Project Requirements

- Must have two sections
- Must have analog signals (can take on any value between V_{min} and V_{max})
- Must demonstrate knowledge of ECE 321 Electronics II

	HW 5: Section 1 Due Monday, December 7th	HW 6: sSection 2 Dut Monday December 14th
<p>1) Requirements (20pt)</p> <p>Specify the requirements for the first section of your device.</p> <ul style="list-style-type: none"> • Input Voltage range, current capability, frequency range • Output Voltage range, current capability • Relationship: What this section does (a picture is useful if it's a filter) 		
<p>2) Analysis (40pt)</p> <p>Computations for resistor and capacitor values.</p> <ul style="list-style-type: none"> • Calculate the voltages at a few points (frequencies, temperatures, light levels). This allows you to compare calculations to simulations to lab • Matlab plots if its a filter to show you meet the requirements. 		
<p>3) Test / Simulation Results (20pt)</p> <ul style="list-style-type: none"> • Simulate your circuit in PartSim or similar program • Check the gain at a few frequencies to compare to your calculations 		
<p>4) Validation (20pt)</p> <p>Lab Results Build your circuit in lab</p> <ul style="list-style-type: none"> • Take measurements at a few frequencies • Compare your lab data to simulation data to computations. • Does the circuit behave as expected? 		
<p>Total (100pt)</p>		