


ECE 321 - Homework #1

Op-Amp Amplifiers. Due Monday, November 9th

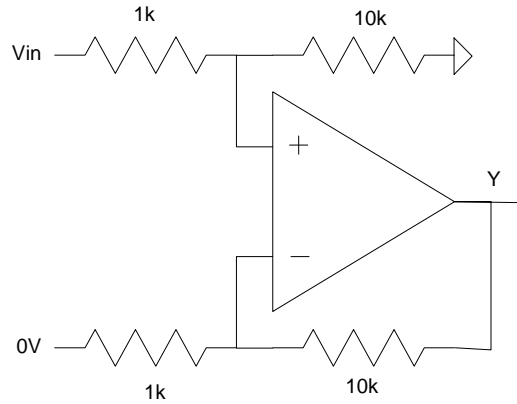1) Design an op-amp circuit to implement

$$Y = 10X$$


Multiple solutions. One that works uses an instrumentation amplifier



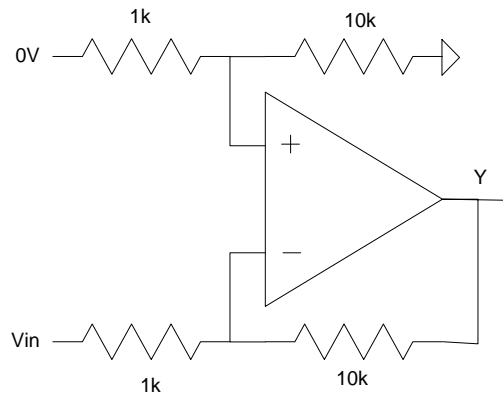2) Design an op-amp circuit to implement

$$Y = -10X$$

Multiple solutions. One that works uses an instrumentation amplifier




3) Design an op-amp circuit to implement

$$Y = 7X - 4$$

Rewrite as

$$Y = 7 (X - 4/7)$$

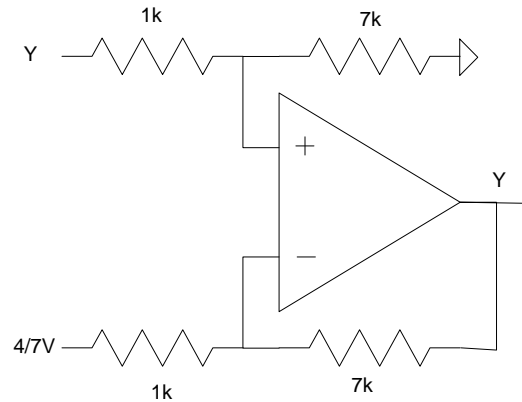

4) A thermistor has the temperature-voltage relationship of

$$R = 1000 \cdot e^{-0.0515(T-25)} \Omega$$

Design an op-amp circuit which output

- 0V at 0C,
- 10V at +40C,
- Proportional (0..10V) for temperatures between 0C and +40C

Assume a 1k resistor for a voltage divider

At 0C

$$R = 3623 \text{ Ohms}$$

$$V_a = 7.8372V$$

At +40C

$$R = 462 \text{ Ohms}$$


$$V_a = 3.1594V$$

The gain you need is

$$gain = \left(\frac{10V - 0V}{7.8372V - 3.1594V} \right) = 2.1377$$


The output increases as V_a decreases, so connect V_a to the - input

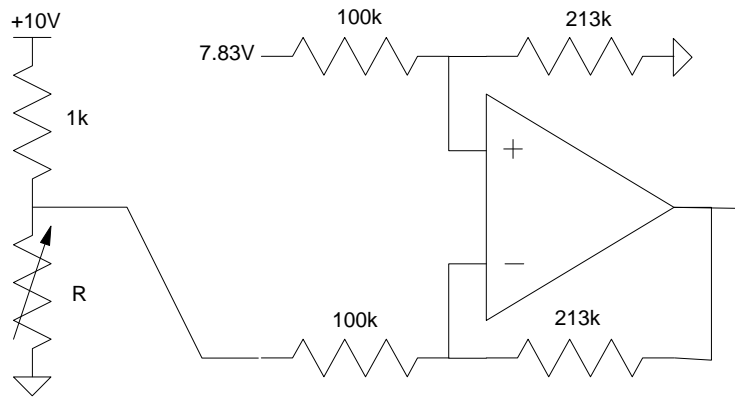The output should be 0V when $V_a = 7,83V$ (0C), so make the offset 7.83V




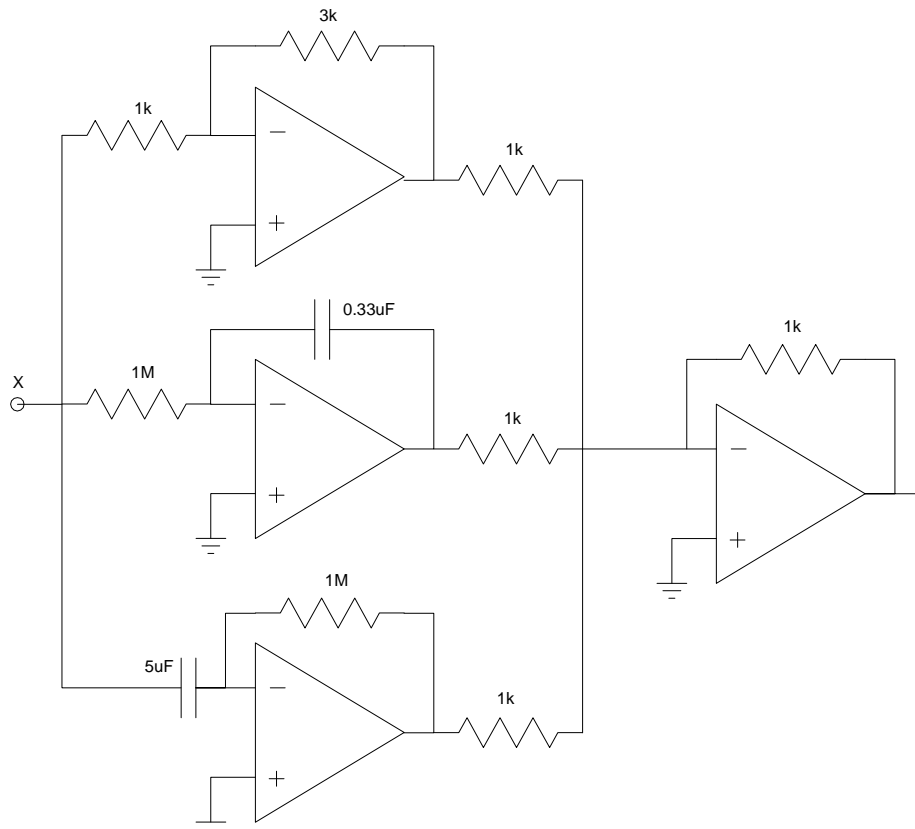5) Design an op-amp circuit to implement the following differential equation


$$Y = \left(3 + \frac{4}{s} + 5s \right) X$$



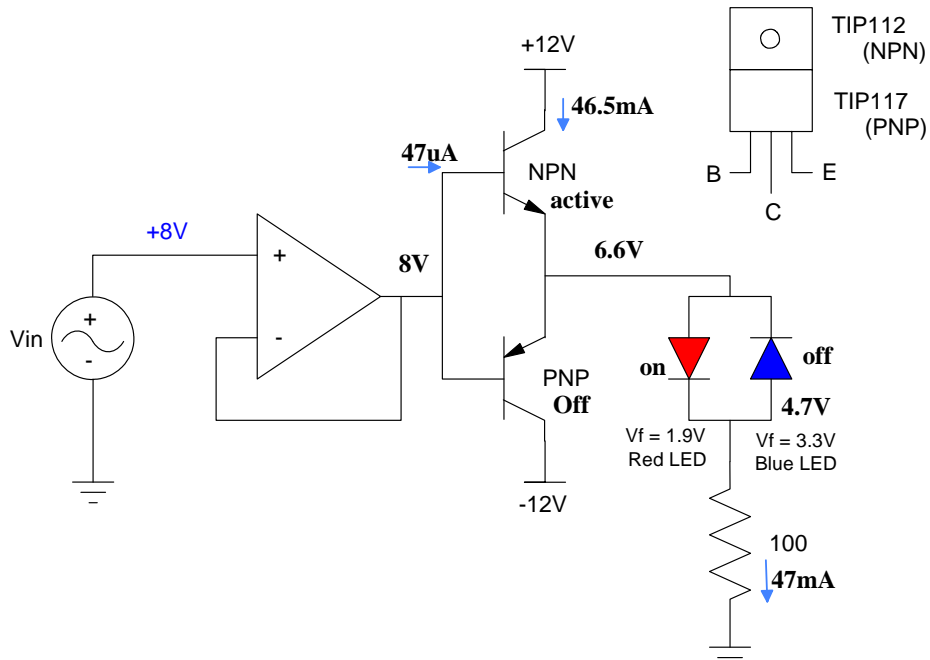6) Determine the node voltages for the following circuit when the input is +8VDC. Assume a TIP112 and TIP117 transistors. ($\beta = 1000$, $V_{be} = 1.4V$, $V_{ce:sat} = 0.9V$)




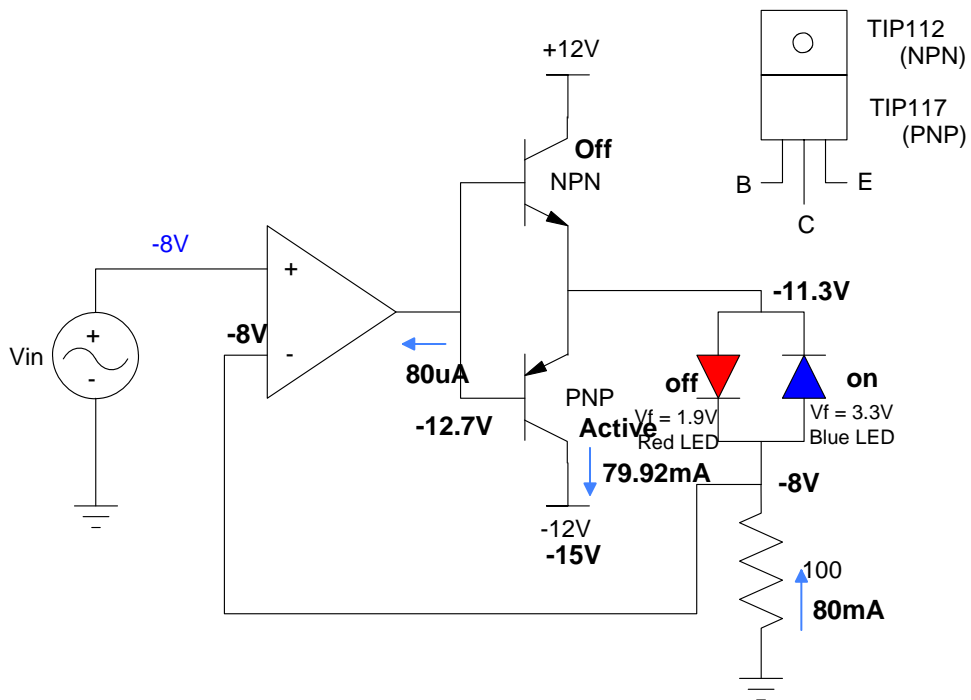7) Determine the node voltages for the following circuit when the input is -8VDC. Assume a TIP112 and TIP117 transistors.



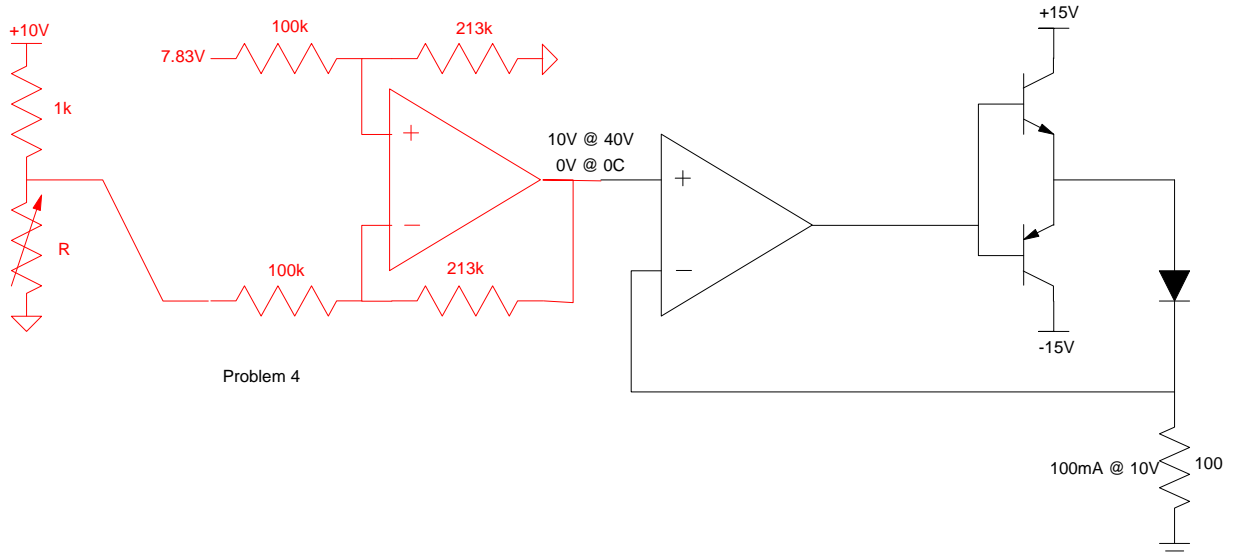
8) Design an op-amp circuit with a push-pull amplifier to drive a 100mA light

- 0mA at 0C
- 100mA at 40C
- Proportional (0..100mA) for temperatures between 0C and +40C.




(the PNP transistor in the push-pull amplifier can be deleted - current (and voltage) never goes negative)

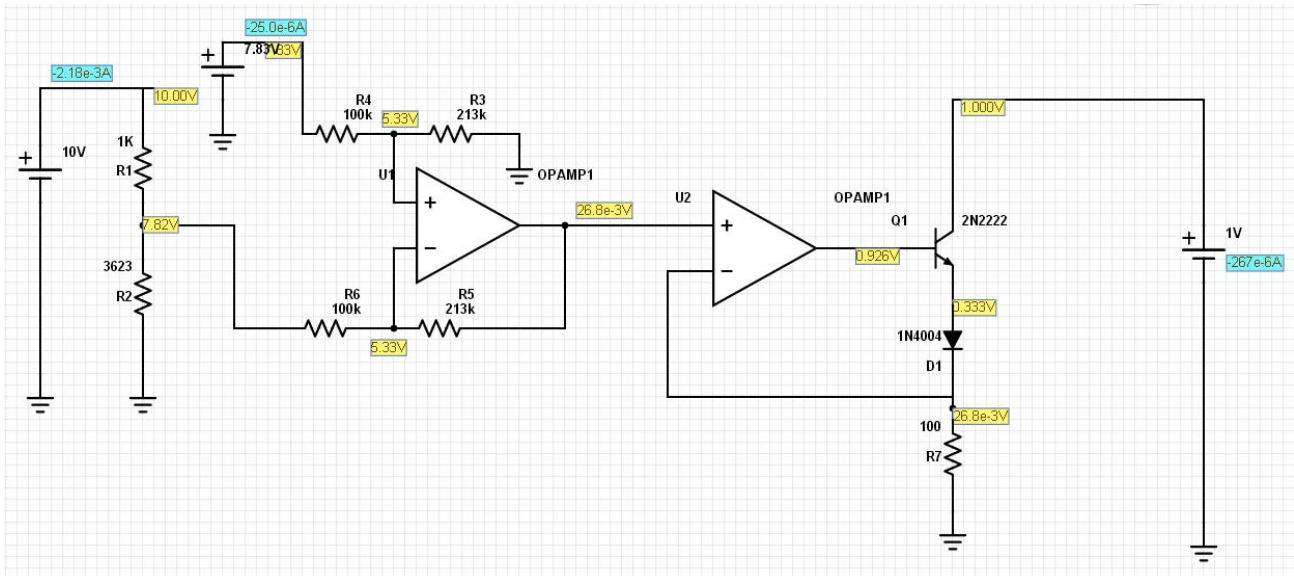
9) Simulate your circuit in problem 8 in PartSim (or similar software)



0C: Current to LED = 0mA

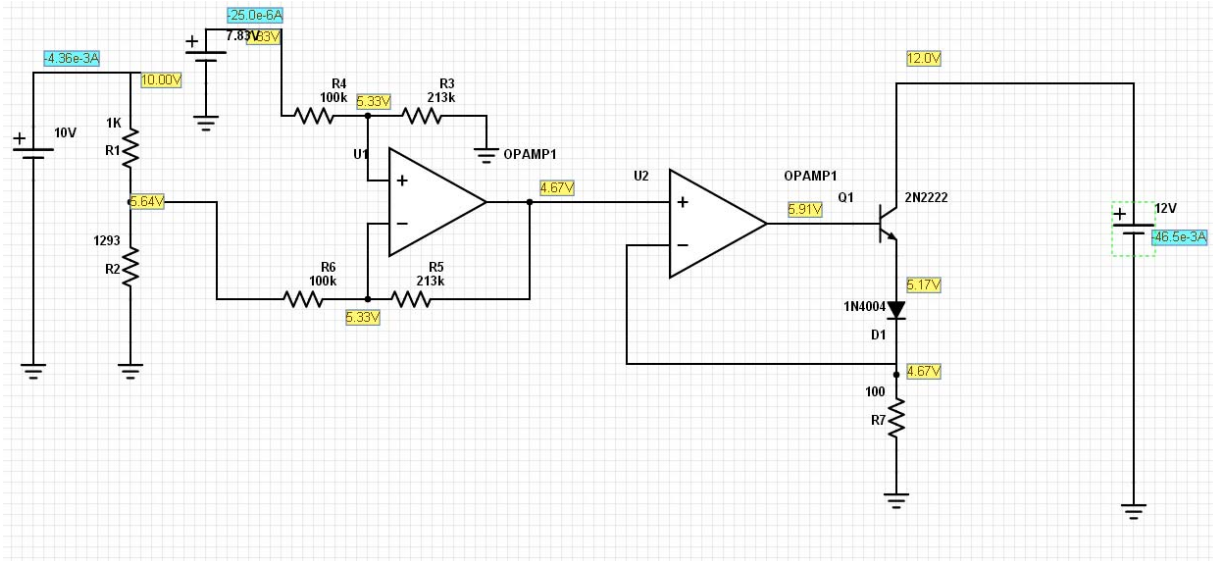

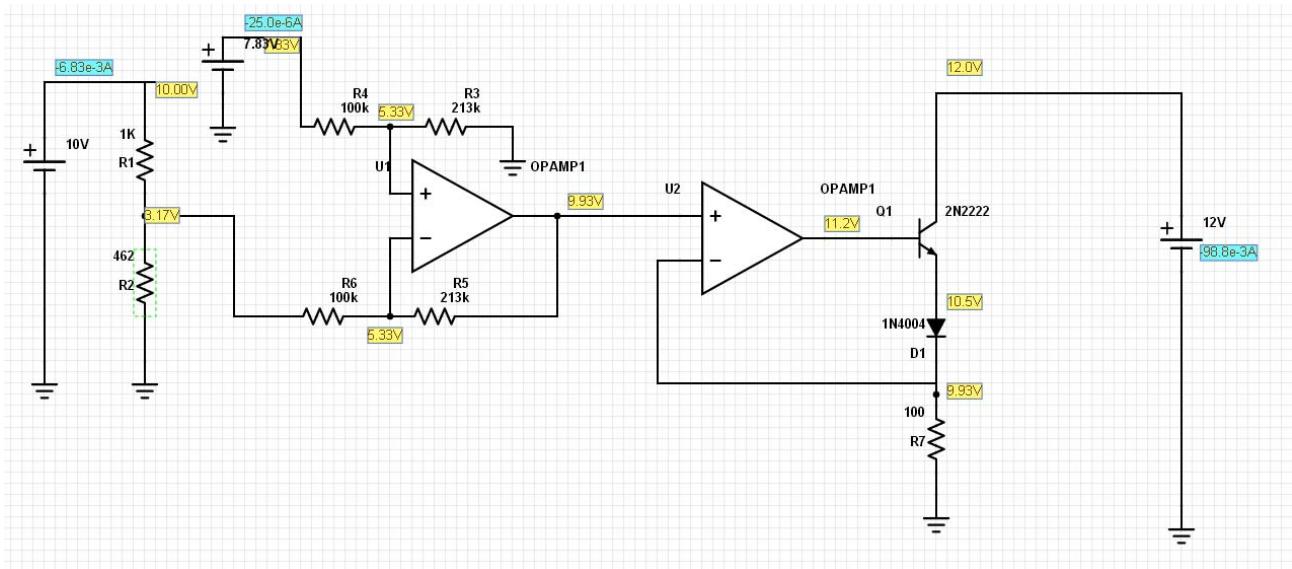+20C: Current to LED = 46.5mA (approx half way to 100mA)



+40C: Current to LED = 100mA

10) Lab: Build the circuit you designed in problem #8 in lab and verify its operation.