

ECE 321 - Homework #2

Phasors - Poles, Zeros, & Frequency Response. Due Monday, November 16th

Problem 1) For the following circuit,

- Determine the impedances of each component at 10 rad/sec
- Write the voltage node equations, and
- Determine the node voltages


Replace with impedances

$$R \rightarrow R = 100$$

$$C \rightarrow \frac{1}{j\omega C} = -j100$$

$$L \rightarrow j\omega L = j20$$

$$V_{in} = -j10$$

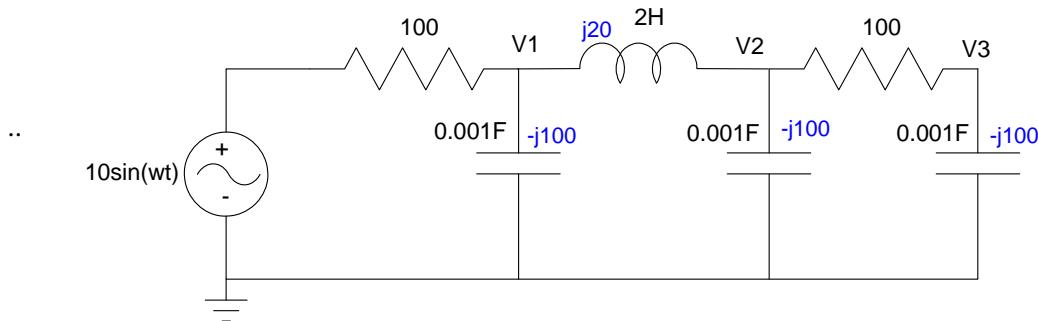

Write the voltage node equations:

$$\left(\frac{V_1 - V_{in}}{100}\right) + \left(\frac{V_1 - V_2}{j20}\right) + \left(\frac{V_1}{-j100}\right) = 0$$

$$\left(\frac{V_2 - V_1}{j20}\right) + \left(\frac{V_2 - V_3}{100}\right) + \left(\frac{V_2}{-j100}\right) = 0$$

$$\left(\frac{V_3 - V_2}{100}\right) + \left(\frac{V_3}{-j100}\right) = 0$$

Group terms

$$\left(\frac{1}{100} + \frac{1}{j20} + \frac{1}{-j100}\right)V_1 - \left(\frac{1}{j20}\right)V_2 = \left(\frac{1}{100}\right)V_{in}$$

$$\left(\frac{-1}{j20}\right)V_1 + \left(\frac{1}{j20} + \frac{1}{100} + \frac{1}{-j100}\right)V_2 + \left(\frac{-1}{100}\right)V_3 = 0$$

$$\left(\frac{-1}{100}\right)V_2 + \left(\frac{1}{100} + \frac{1}{-j100}\right)V_3 = 0$$

Put in matrix form

$$\begin{bmatrix} \left(\frac{1}{100} + \frac{1}{j20} + \frac{1}{-j100}\right) & \left(\frac{-1}{j20}\right) & 0 \\ \left(\frac{-1}{j20}\right) & \left(\frac{1}{j20} + \frac{1}{100} + \frac{1}{-j100}\right) & \left(\frac{-1}{100}\right) \\ 0 & \left(\frac{-1}{100}\right) & \left(\frac{1}{100} + \frac{1}{-j100}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \left(\frac{1}{100}\right) \\ 0 \\ 0 \end{bmatrix} V_{in}$$

Solve in MATLAB

```
-->w = 10;
-->R = 100;
-->L = j*w*2

20.i

-->C = 1/(j*w*0.001)

- 100.i

-->A = [1/R+1/L+1/C,-1/L,0;-1/L,1/R+1/L+1/C,-1/R;0,-1/R,1/R+1/C]

0.01 - 0.04i    0.05i      0
0.05i           0.01 - 0.04i   - 0.01
0               - 0.01       0.01 + 0.01i

-->B = [1/R;0;0]

0.01
0.
0.

-->V = inv(A)*B*Vin

- 2.3076923 - 1.5384615i
- 3.5384615 - 1.6923077i
- 2.6153846 + 0.9230769i
```

meaning

$$\mathbf{V1} = -2.3076 \cos(10t) + 1.5384 \sin(10t)$$

$$\mathbf{V2} = -3.5384 \cos(10t) + 1.6923 \sin(10t)$$

$$\mathbf{V3} = -2.6153 \cos(10t) - 0.9230 \sin(10t)$$

Problem 2) Repeat at 100 rad/sec

```
-->w = 100;
-->R = 100;
-->L = j*w*2           L → jωL
200.i
-->C = 1/(j*w*0.001)      C →  $\frac{1}{j\omega C}$ 
- 10.i
-->A = [1/R+1/L+1/C,-1/L,0;-1/L,1/R+1/L+1/C,-1/R;0,-1/R,1/R+1/C]
0.01 + 0.095i   0.005i       0
0.005i          0.01 + 0.095i - 0.01
0              - 0.01        0.01 + 0.1i
-->B = [1/R;0;0]
0.01
0.
0.
-->V = inv(A)*B*Vin
- 1.0438042 - 0.1104658i
0.0532108 + 0.0112425i
0.0016400 - 0.0051571i
```

Meaning

$$\mathbf{V1} = -1.0438 \cos(100t) + 0.1104 \sin(100t)$$


$$\mathbf{V2} = 0.0532 \cos(100t) - 0.0112 \sin(100t)$$

$$\mathbf{V3} = 0.0016 \cos(100t) + 0.0051 \sin(100t)$$

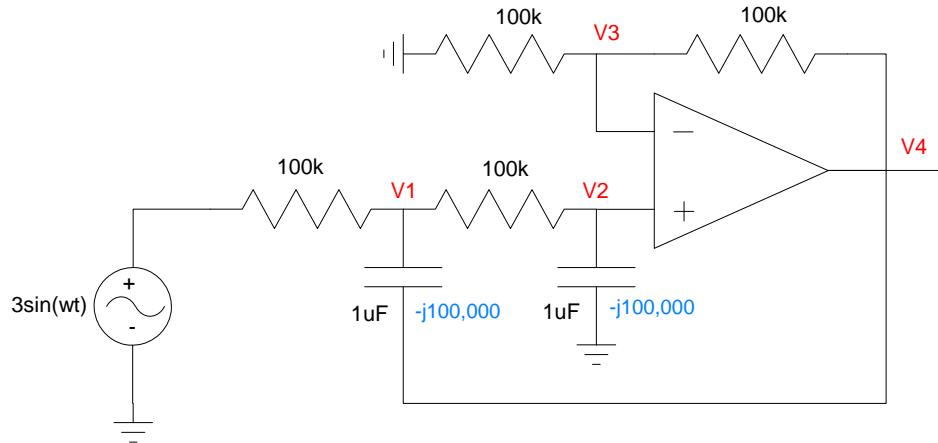Problem 3) For the following op-amp circuit

- Determine the impedances of each component at 10 rad/sec
- Write the voltage node equations, and
- Determine the node voltages

Replace R / L / C with their complex impedances



Write the node equations

$$V_2 = V_3$$

$$\left(\frac{V_1 - V_{in}}{100k} \right) + \left(\frac{V_1 - V_2}{100k} \right) + \left(\frac{V_1 - V_4}{-j100k} \right) = 0$$

$$\left(\frac{V_2 - V_1}{100k} \right) + \left(\frac{V_2}{-j100k} \right) = 0$$

$$\left(\frac{V_3}{100k} \right) + \left(\frac{V_3 - V_4}{100k} \right) = 0$$

Group terms and multiply each equation by 100k

$$(1)V_2 - (1)V_3 = 0$$

$$(2+j)V_1 + (-1)V_2 + (-j)V_4 = (1)V_{in}$$

$$(-1)V_1 + (1+j)V_2 = 0$$

$$(2)V_3 + (-1)V_4 = 0$$

Place in matrix form

$$\begin{bmatrix} 0 & 1 & -1 & 0 \\ 2+j & -1 & 0 & -j \\ -1 & 1+j & 0 & 0 \\ 0 & 0 & 2 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} V_{in}$$

Solve in MATLAB

```
-->A = [0,1,-1,0;2+j,-1,0,-j;-1,1+j,0,0;0,0,2,-1]

0.          1.          - 1.          0
2. + i      - 1.          0          - i
- 1.          1. + i      0          0
0.          0.          2.          - 1.

-->B = [0;1;0;0]

0.
1.
0.
0.

-->V = inv(A)*B*Vin

- 10. - 10.i
- 10.
- 10.
- 20.
```

meaning

$$\mathbf{V1} = -10 \cdot \cos(10t) + 10 \cdot \sin(10t)$$

$$\mathbf{V2} = -10 \cdot \cos(10t)$$

$$\mathbf{V3} = -10 \cdot \cos(10t)$$

$$\mathbf{V4} = -20 \cdot \cos(10t)$$

Problem 4) Releat at 100 rad/sec

R stays 100k

C becomes -j10,000

Scaling 1/R and 1/Zc by 100,000 results in

R => 1

C => j10

$$\begin{bmatrix} 0 & 1 & -1 & 0 \\ 2+j10 & -1 & 0 & -j10 \\ -1 & 1+j10 & 0 & 0 \\ 0 & 0 & 2 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} V_{in}$$

-->A = [0,1,-1,0;2+j10,-1,0,-j10;-1,1+j10,0,0;0,0,2,-1]

$$\begin{array}{rrrr} 0 & 1. & - 1. & 0 \\ 2. + 10.i & - 1. & 0 & - 10.i \\ - 1. & 1. + 10.i & 0 & 0 \\ 0 & 0 & 2. & - 1. \end{array}$$

-->V = inv(A)*B*Vin

$$\begin{array}{r} - 1.00999 - 0.0010100i \\ - 0.0101000 + 0.0999899i \\ - 0.0101000 + 0.0999899i \\ - 0.0202000 + 0.1999798i \end{array}$$

Meaning

$$V1 = -1.0099 \cos(100t) + 0.0010 \sin(100t)$$

$$V2 = -0.0101 \cos(100t) - 0.0999 \sin(100t)$$

$$V3 = -0.0101 \cos(100t) - 0.0999 \sin(100t)$$

$$V4 = -0.0202 \cos(100t) - 0.1999 \sin(100t)$$


Problem 5 - 7)

- Plot the gain vs. frequency for the following filter for $0 < w < 20$ rad/sec
- What kind of filter is it: low pass - band pass - high pass

$$5) Y = \left(\frac{4s}{s^2 + 4s + 50} \right) X$$

```
-->w = [0:0.01:20]';
-->s = j*w;
-->G5 = 4*s ./ (s.^2 + 4*s + 50);
-->plot(w,abs(G5));
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
-->title('Problem 5')
```

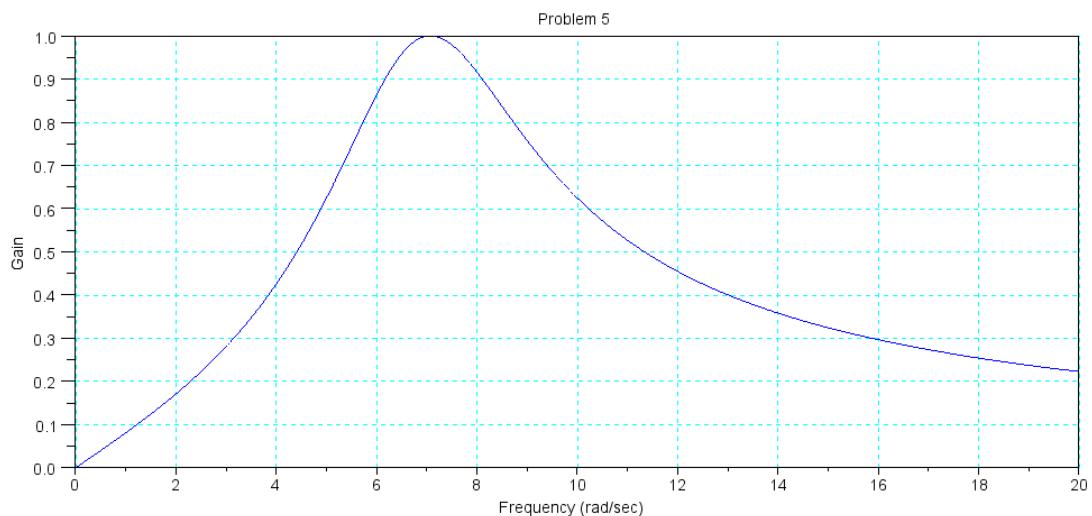
This is a band-pass filter, passing frequencies $\sqrt{50} \pm 2$ rad/sec



$$6) Y = \left(\frac{20,000}{(s^2 + 18s + 100)(s^2 + 8s + 100)} \right) X$$

```
-->w = [0:0.01:20]';
-->s = j*w;
-->G6 = 20000 ./ ( (s.^2 + 18*s + 100).* (s.^2 + 8*s+100) );
-->plot(w,abs(G6));
-->xgrid(4)
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
-->title('Problem 6');
```

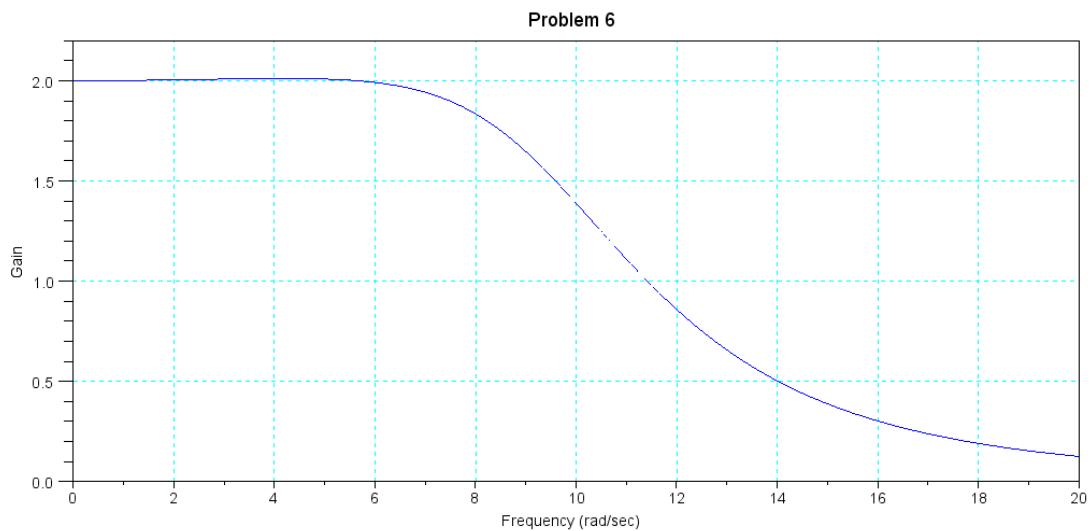
This is a low-pass filter. Frequencies below approximately 10 rad/sec are passed $(\sqrt{100})$



$$7) Y = \left(\frac{s^4}{(s^2 + 18s + 100)(s^2 + 8s + 100)} \right) X$$

```
-->w = [0:0.01:20]';
-->s = j*w;
-->G7 = s.^4 ./ ( (s.^2 + 18*s + 100).* (s.^2 + 8*s+100) );
-->plot(w,abs(G7));
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
-->xgrid(4)
-->title('Problem 7');
```

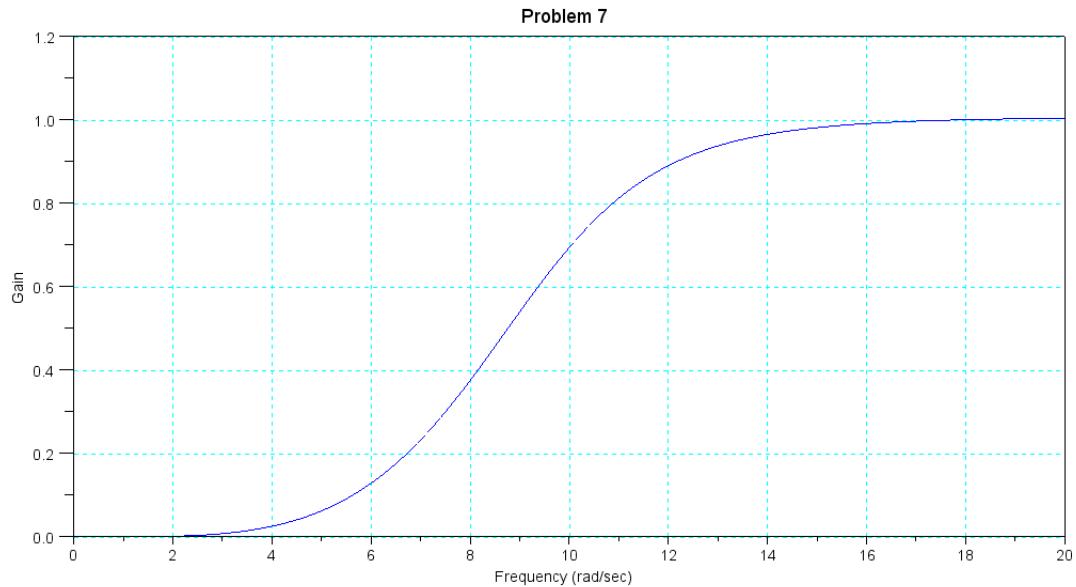This is a high-pass filter. It allows frequencies above 10 rad/sec to pass and blocks frequencies below 10.



- 8) Give the transfer function for a filter which passes frequencies between 0 and 100 rad/sec (16Hz). Plot the gain of your filter from 0 to 300 rad/sec to check your design.

This filter is centered at $j0$ rad/sec (DC). The complex part of the poles should be zero.


This filter passes 0 ± 100 rad/sec. The amplitude of the poles is 100

Pick a 2nd-order filter (order is arbitrary with these requirements)

Pick the numerator so that the DC gain is one (max gain = 1)

$$G_8(s) = \left(\frac{100}{s+100} \right)^2$$
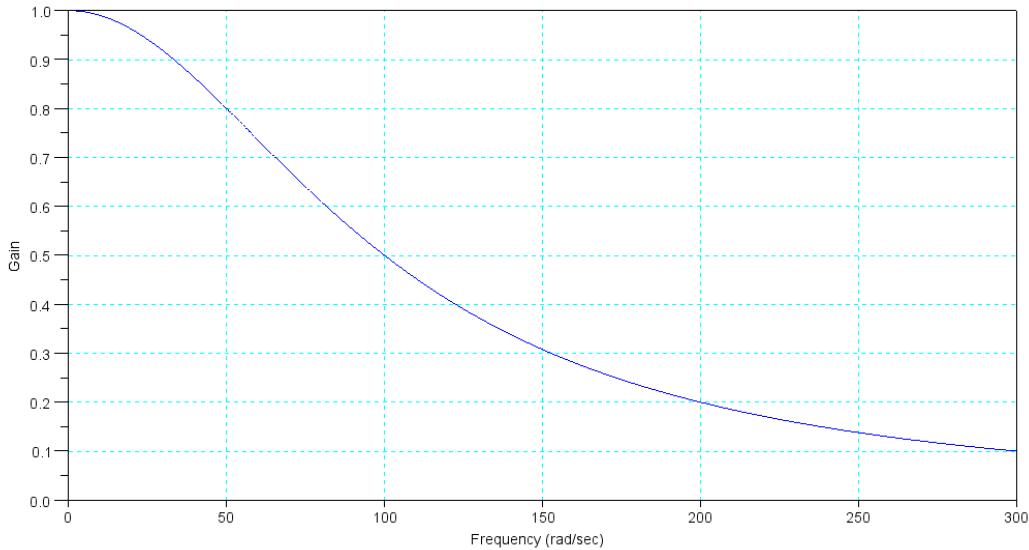
```
-->w = [0:0.1:300]';
-->s = j*w;
-->G8 = (100 ./ (s + 100)) .^ 2;
-->plot(w,abs(G8));
-->xgrid(4)
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
```



Note: This isn't a very good filter. We can do better, but that requires complex poles - which we'll get to next week.

- 9) Give the transfer function for a filter which passes frequencies between 25 and 33 rad/sec. Plot the gain of your filter from 15 to 40 rad/sec to check your design.

The center frequency = 29 rad/sec. The complex part of the pole is $j29$

The filter passes 29 rad/sec ± 4 rad/sec. The real part of the pole is 4

Add a zero at DC to make the gain here zero

Add a gain on top to make the max gain one

$$G_9 = \left(\frac{8s}{(s+4+j29)(s+4-j29)} \right)$$

```
-->w = [15:0.01:40]';
-->s = j*w;
-->G9 = s ./ ( (s+4+j*29).* (s+4-j*29) );
-->max(abs(G9))

0.1249975

-->k = 1/ans

8.0001616

-->G9 = k * s ./ ( (s+4+j*29).* (s+4-j*29) );
-->plot(w,abs(G9));
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
-->xgrid(4)
```

Again, it's not great and we can do better. We'll cover how next week with Butterworth and Chebychev filters.

