


ECE 321: Final Exam Name _____

December 13, 2016

- 1) Determine the voltages and currents for the following push-pull amplifier with a +2V input. Assume

- $\beta = 100$
- $V_{be} = 0.7V$

V1	V2	Ib	Ic
6.7V	6V	744.6mA	744.6mA

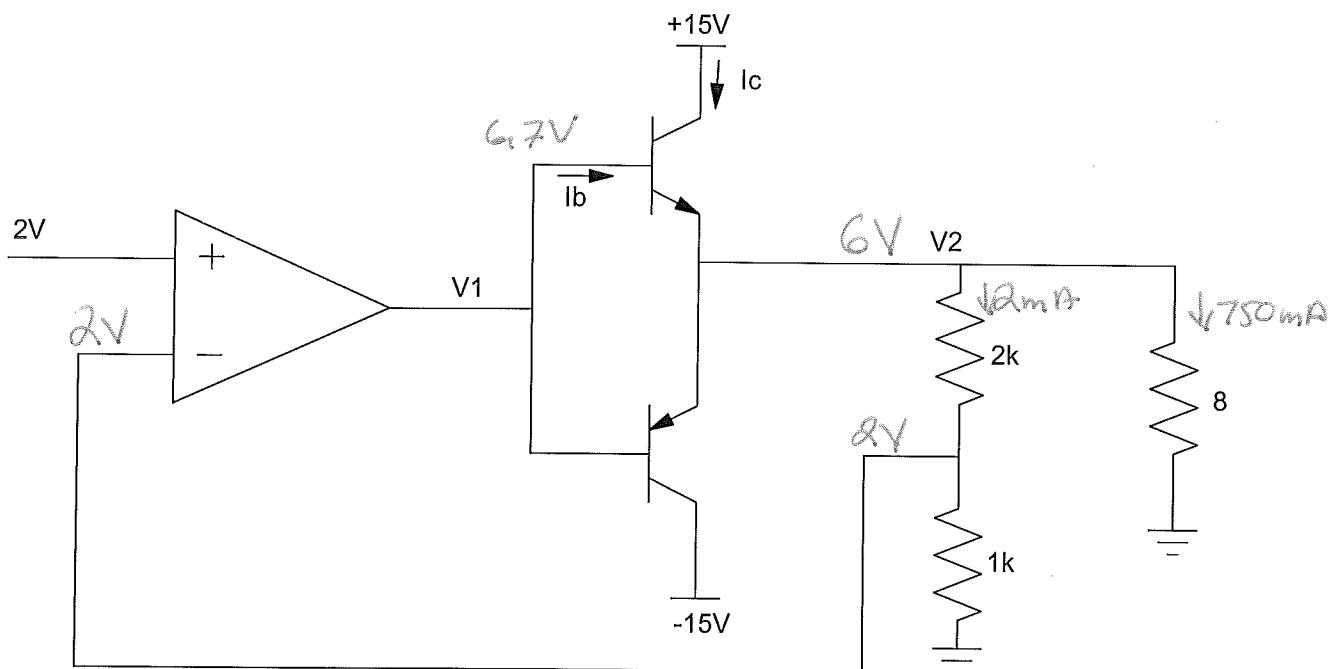


$$I_b + I_c = 752 \text{ mA}$$

$$I_b = \frac{752}{101} = 74.46 \text{ mA}$$

2) Determine the voltages and currents for the following circuit. Assume

- $\beta = 100$
- $V_{be} = 0.7V$
- $V_f = 3.0V$ (a white LED)

Ib	Ic	Vc	Ve
1.98mA	198mA	12V	2V

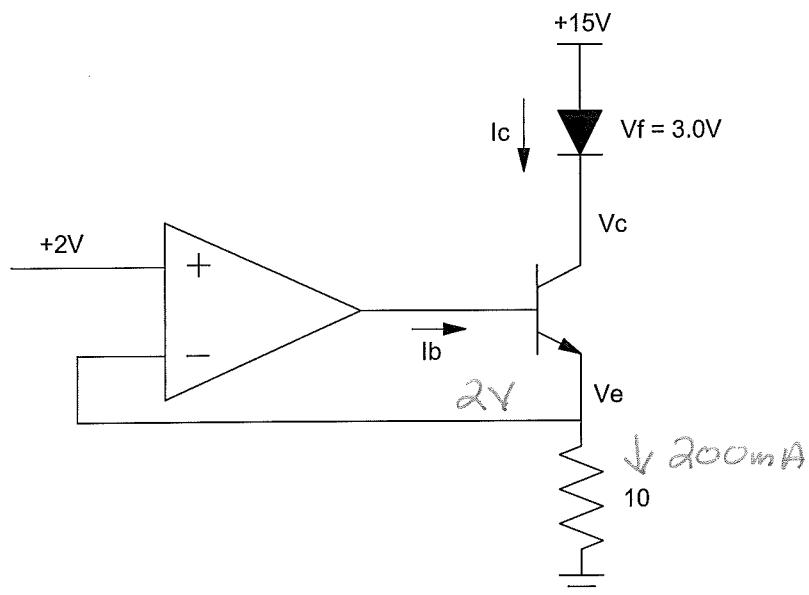

$$(1+\beta) I_b = 200mA$$

$$I_b = 1.98mA$$

3) Find R and C so the the following amplifier has the following transfer function


$$Y = \left(\frac{1000}{s^2 + 10s + 300} \right) X$$

R	C	R1	R2	R3	R4
100k	.577μF	100k	142k	376k	100k

$$V_{rc} = 17.32$$

$$\text{gain} = 2.423$$

$$.376$$

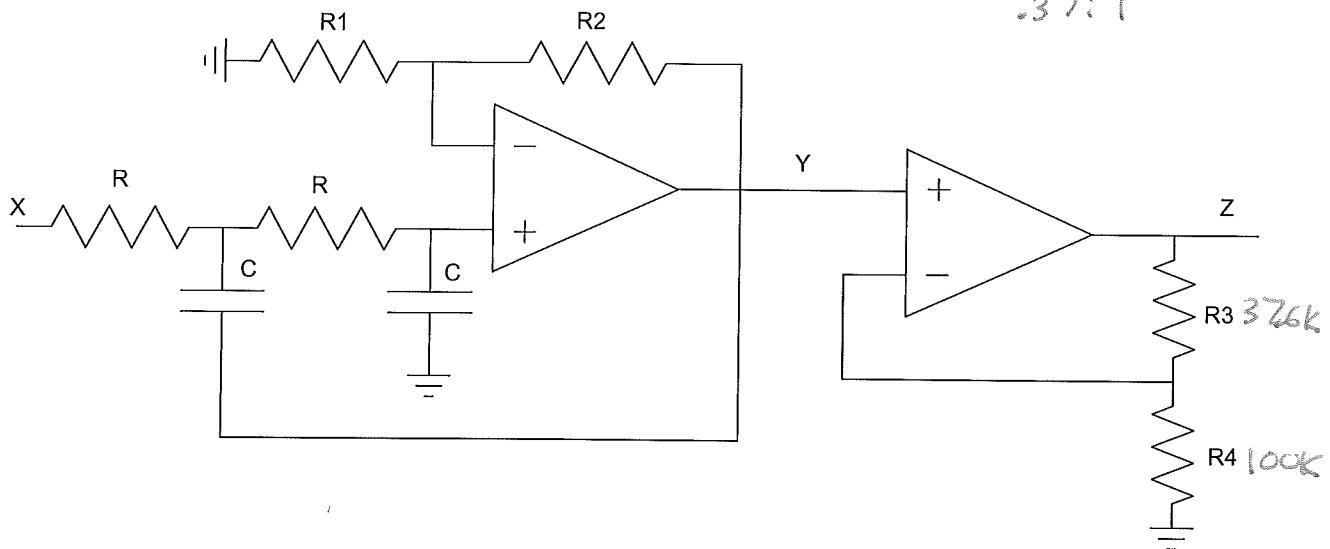

$$Y = \left(\frac{k \left(\frac{1}{RC} \right)^2}{s^2 + \left(\frac{3-k}{RC} \right)s + \left(\frac{1}{RC} \right)^2} \right) X$$

$$Z = \left(1 + \frac{R_3}{R_4} \right) Y$$

$$k = 1 + \frac{R_2}{R_1}$$

~~gain = 4.128~~

$$\left(\frac{3-k}{RC} \right) = 10$$

~~(4.128)(2.423) = 1~~

$$(3-k) = \frac{10}{\frac{1}{300}} = .577$$

$$\text{gain} = 1.376$$



$$(2.423)(1.376) = \frac{1000}{300}$$

$$k = 2.423$$

4) BJT and Load Lines: Determine the voltages and currents for the following circuit. Also draw the load line and show the Q-point on the load-line. Assume $\beta = 100$

I _b	I _c	V _c	V _e	Load Line & Q-Point
2.16mA	216mA	11.78V	2.18V	show on graph

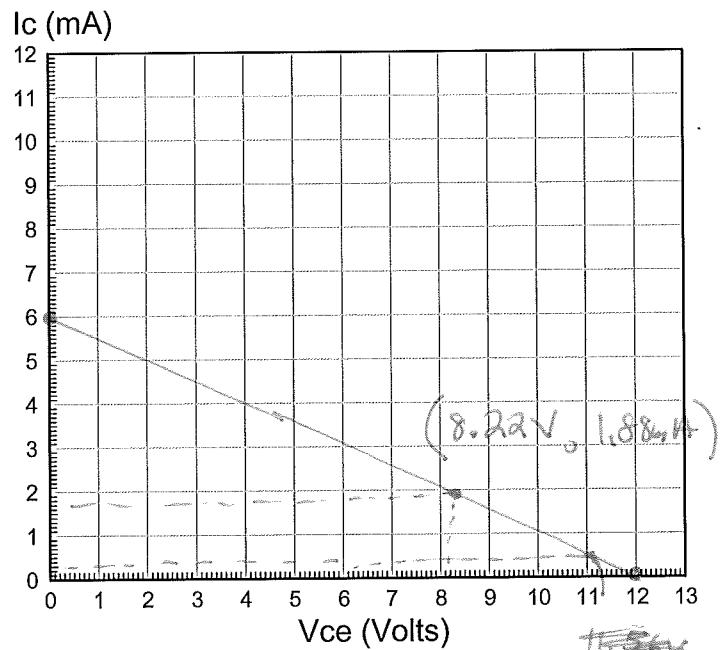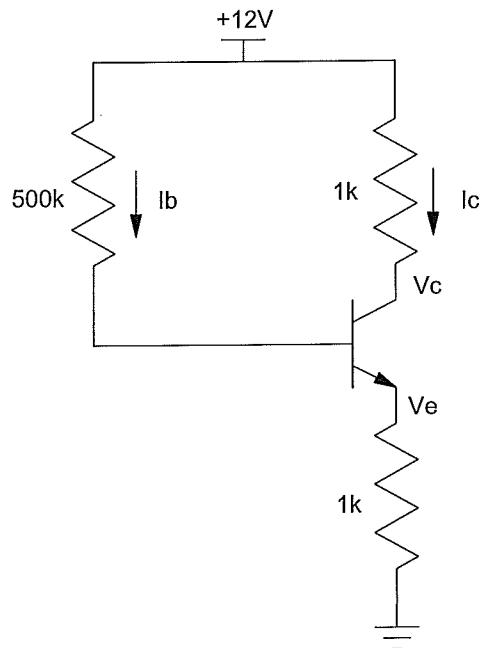~~1.8.8mA~~ ~~1.88mA~~ ~~10.12V~~ ~~1.9V~~




$$I_b = \frac{12 - 7}{500k + 10k} = 2.16mA$$

5) Find R₁ and R₂ so that

- The Q-point is stabilized for variations of β ($(1 + \beta)R_e \gg R_b$) and
- V_{ce} = 6.0V

Assume $\beta = 100$

R ₁	R ₂	V _b	R _b
22.95k	3451	6.569V	3k

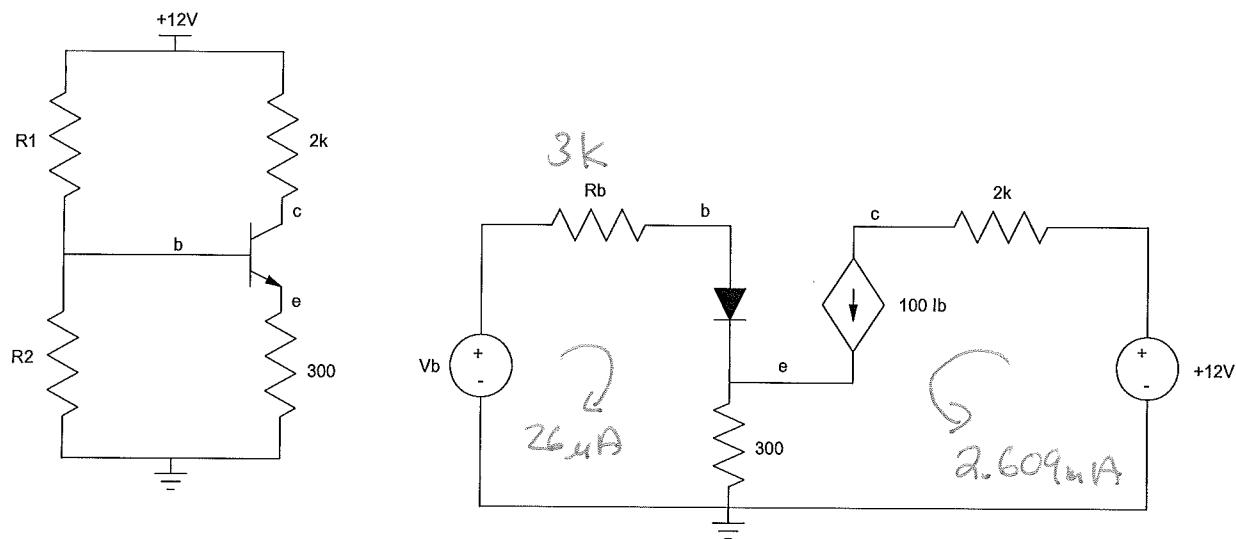

$$(101)300 \gg R_b$$

$$30k \gg R_b$$



$$\text{Let } R_b = 3k$$

$$V_b = 3k \cdot I_{st} + 3cv(I_{st} + I_c)$$

$$V_b = 6.569V$$


6) Draw the small-signal model for the following amplifier. Assume

- $\beta = 100$
- $r_f = 1500\Omega$

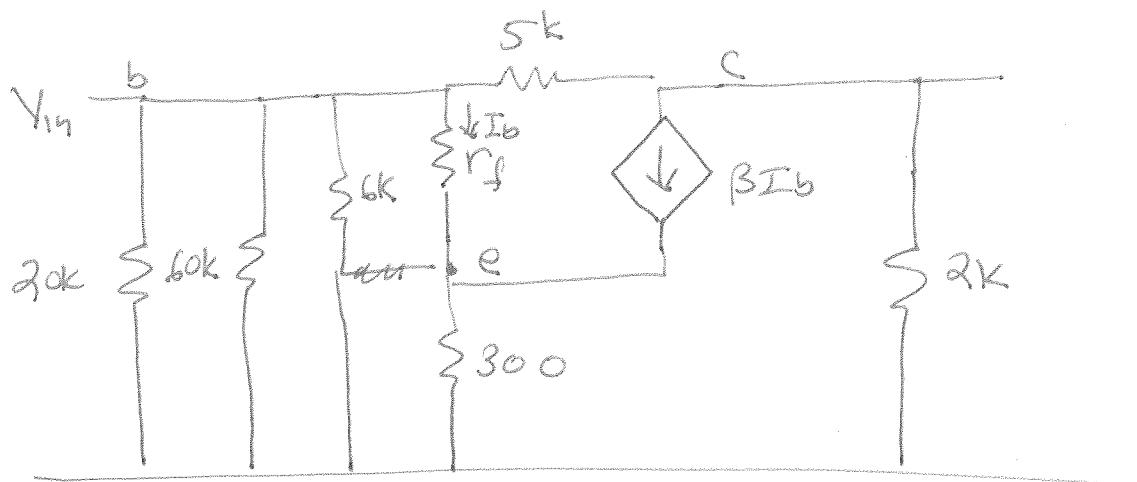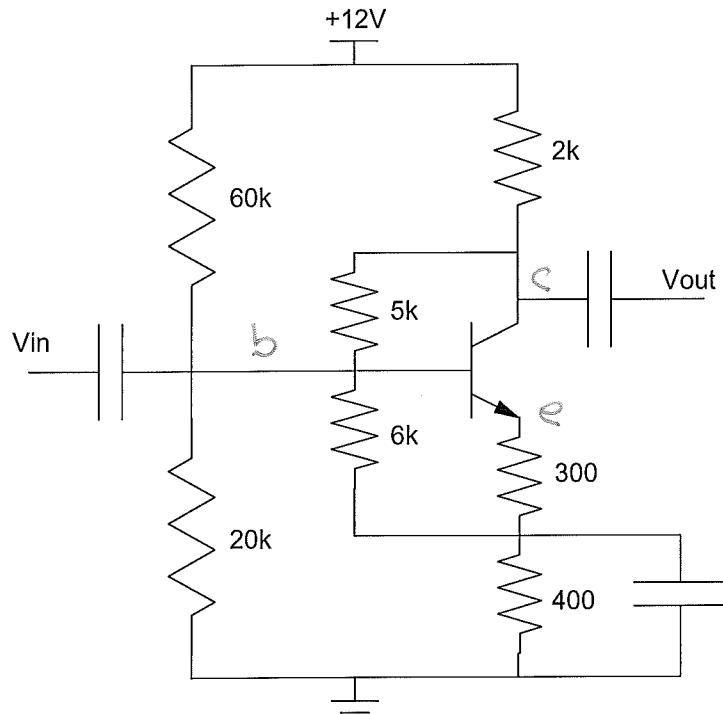

7) Determine the 2-port model for the following amplifier

Rin	Ai	Rout	Ao
3k	.75	36.7	.9266

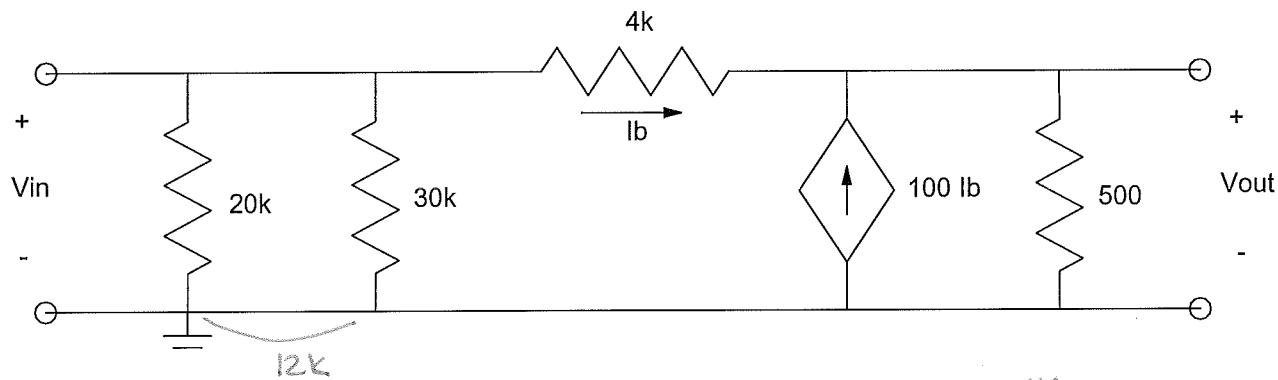

$$R_{in} = 20k \parallel 30k \parallel 4k \\ = 3k$$

$$R_{out} = 4k \parallel \frac{4k}{100} \parallel 500 \\ = 36.7 \Omega$$

$$A_i = \frac{12k}{12k + 4k} \\ = .75$$

$$A_{oi} = \frac{x-1}{4k} + 100 \left(\frac{x-1}{4k} \right) + \frac{x}{500} = 0$$

$$x = \frac{\frac{1}{4k} + \frac{100}{4k}}{\frac{1}{4k} + \frac{100}{4k} + \frac{1}{500}}$$

$$= .9266$$

Bonus! If the electoral college refuses to elect either Trump or Clinton, who determines who is our next President?

The house of representatives
Votes - 1 vote per state.