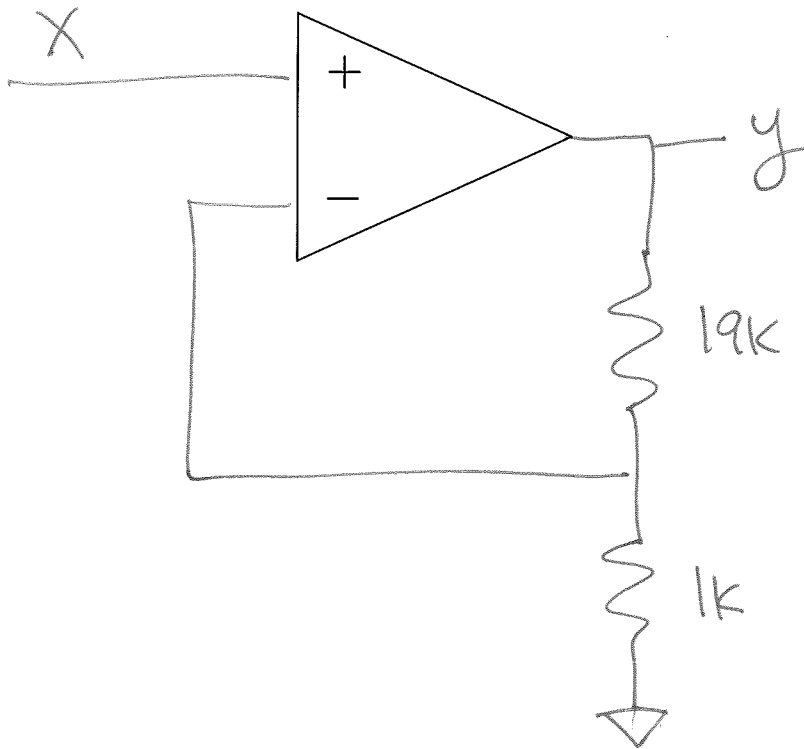


# ECE 321: Quiz #1 Name \_\_\_\_\_

Operational Amplifier Circuits - November 3, 2016


1) Design a circuit with a gain of +20

$$Y = 20X$$



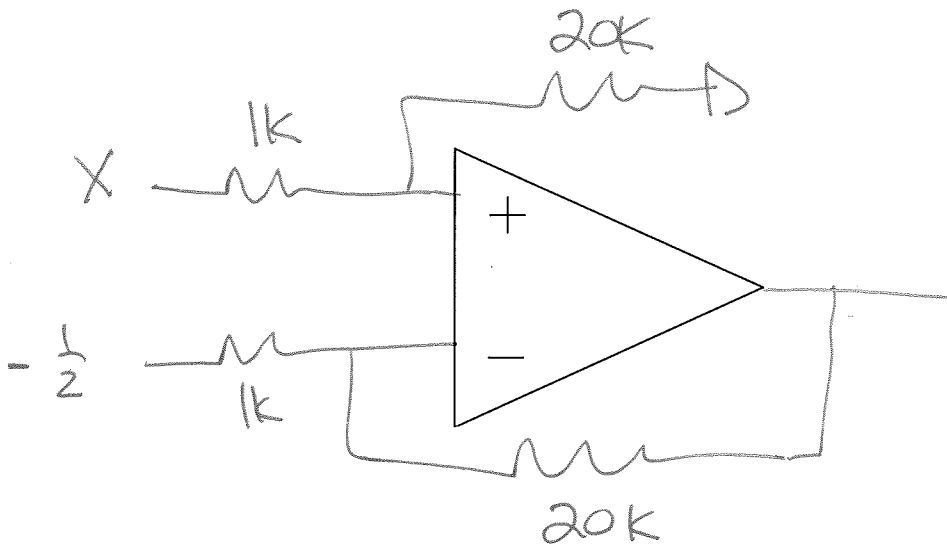
2) Design a circuit with a gain of +20 and an offset of +10V

$$Y = 20X + 10 = 20\left(X - \left(-\frac{1}{2}\right)\right)$$



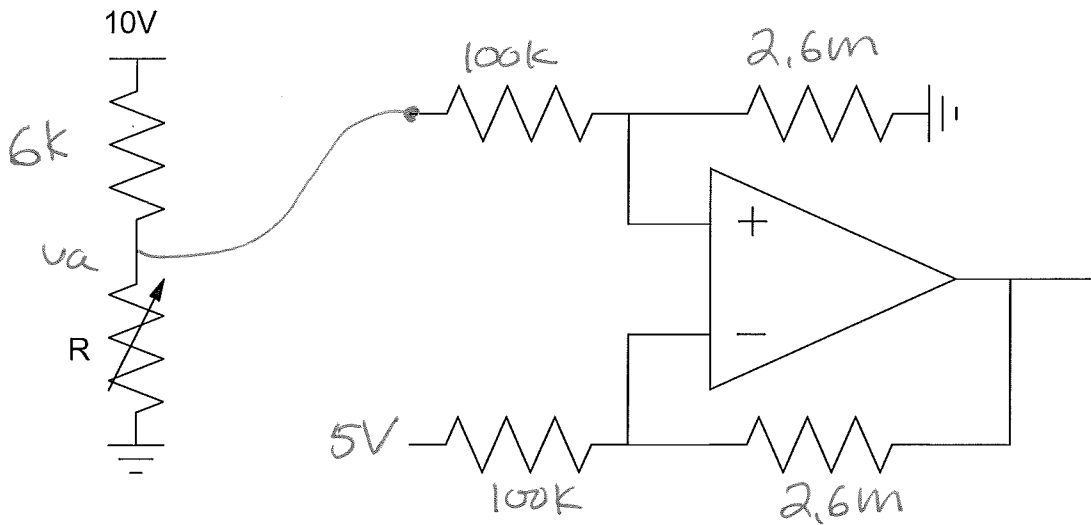3) Design an op-amp circuit where the output is

- 0V when  $R = 6k$  Ohms
- 10V when  $R = 7k$  Ohms



$$0V = 6k$$

$$7k \Rightarrow 10V$$


$$V_a = 5V$$

$$V_a = 5.38V$$

$$\text{gain} = 26$$

4) For the following circuit, determine

$X = f(A, B, C)$ $X$ as a function of $(A, B, C)$	$X = \frac{6A + 3B + 2C}{11}$
$Y = g(X)$ $Y$ as a function of $X$	$Y = 11X$
$Y = h(A, B, C)$ $Y$ as a function of $(A, B, C)$	$Y = 6A + 3B + 2C$

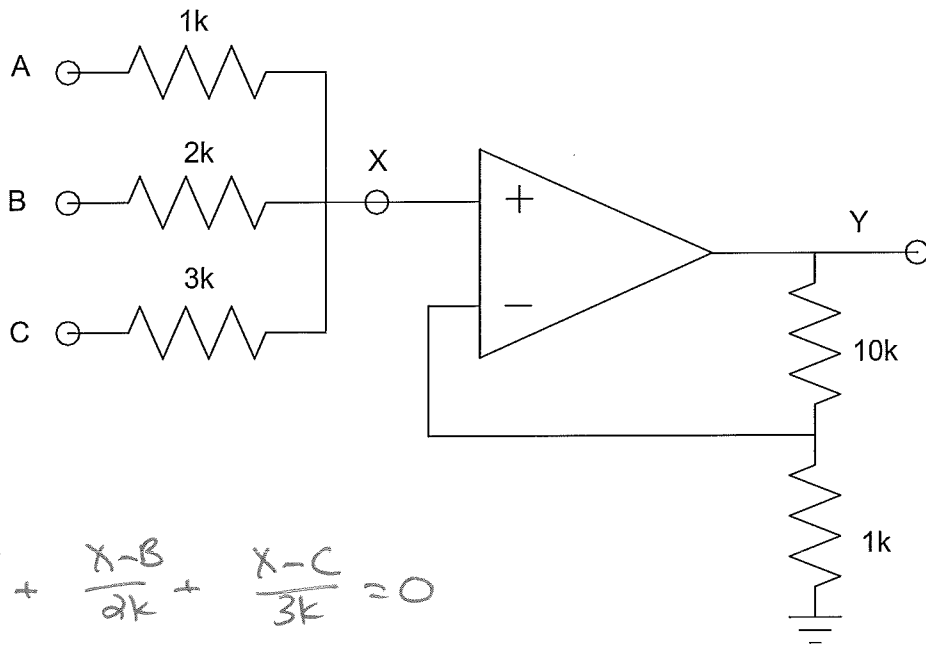

$$* \frac{6k}{6k} \frac{X-A}{1k} + \frac{X-B}{2k} + \frac{X-C}{3k} = 0$$

$$6(X-A) + 3(X-B) + 2(X-C) = 0$$

$$11X = 6A + 3B + 2C$$

5) For the following circuit, determine

$$X = f(A, B)$$

X as a function of (A, B)

$$X = -5A - 10B$$

$$Y = g(C, X)$$


Y as a function of (C, X)

$$Y = -2X - 3C$$

$$Y = h(A, B, C)$$

Y as a function of (A, B, C)

$$Y = 10A + 20B - 3C$$

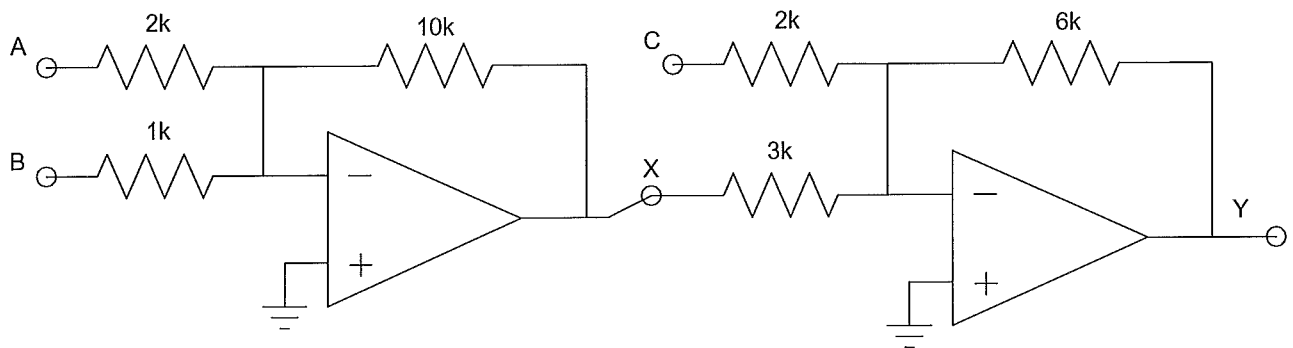

$$X = -5A - 10B$$

Bonus! Bernie Sanders (and other dinosaurs) Trivia!!! There have been six mass extinctions in Earth's history. What caused the K-T mass extinction which wiped out the dinosaurs, 65 million years ago?

meteor that hit in the Gulf of Mexico