



# ECE 321: Quiz #2 Name \_\_\_\_\_

Operational Amplifier Circuits - November 10, 2016

1) The VI characteristics for a white LED are given below. Draw the load-line and determine R so that 6mA flows through the LED.


Load Line	Vd	Id	R
show on graph	2.1V	6mA	1317Ω

$$R = \frac{7.9V}{6mA} = 1317\Omega$$

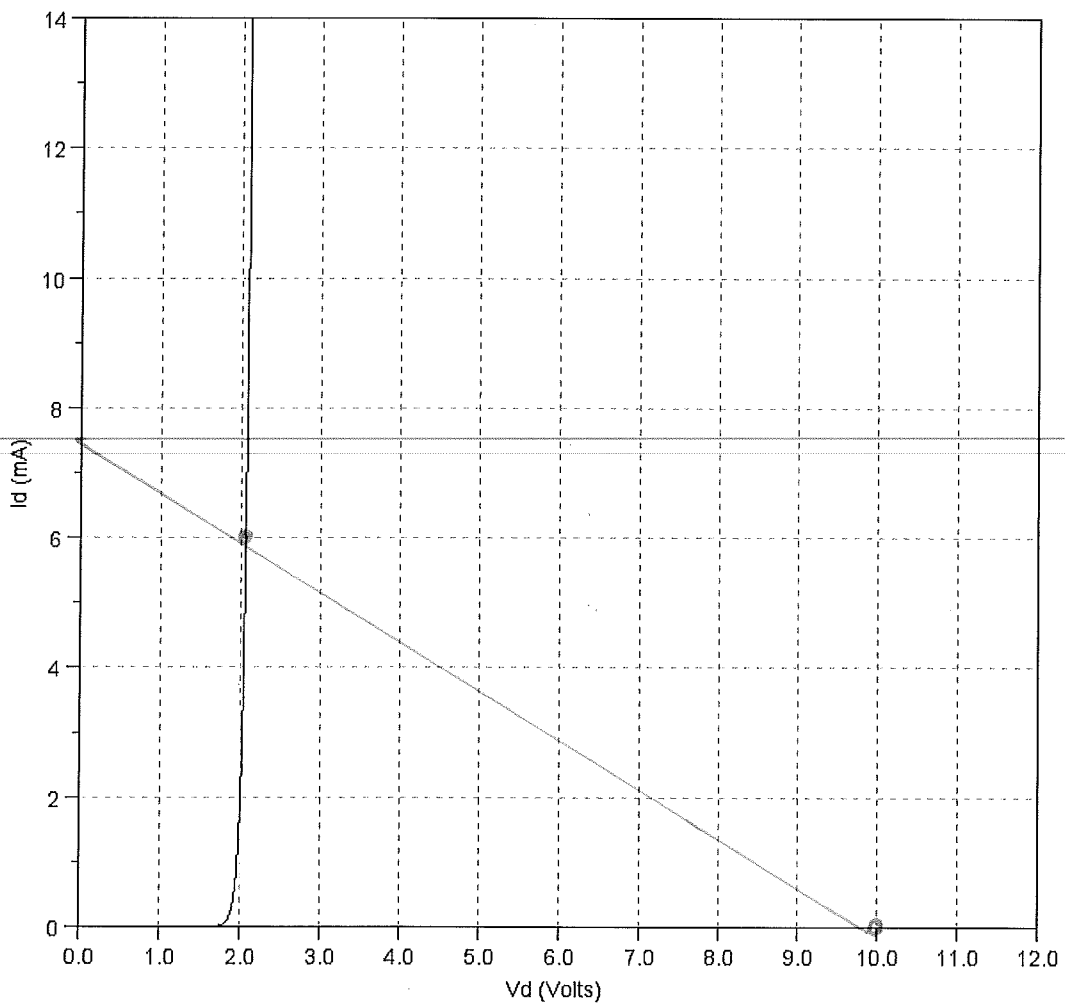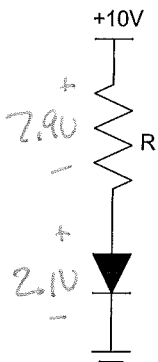


2) A 1kHz, 1Vp sine wave is added to the previous diode. Assume the Q-point is at  $I_d = 6\text{mA}$ . Determine the following:

$Z_c$ : Impedance of the capacitor at 1kHz (6280 rad/sec)	$I_{dpp}$ : The peak-to-peak current through the diode	$V_{dpp}$ : The peak-to-peak voltage across the diode
$-j530\Omega$	$1.88\text{mA}_{pp}$ $0.94\text{mA}_p$ $0.66\text{mA}_{rms}$	$35\text{mV}_{pp}$ $17\text{mV}_p$ $12\text{mV}_{rms}$

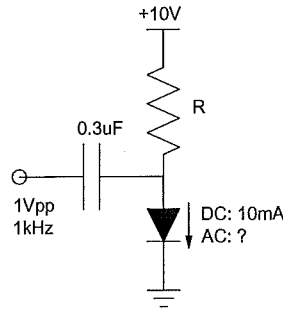

$$Z_c = \frac{1}{j\omega c} = -j530\Omega$$
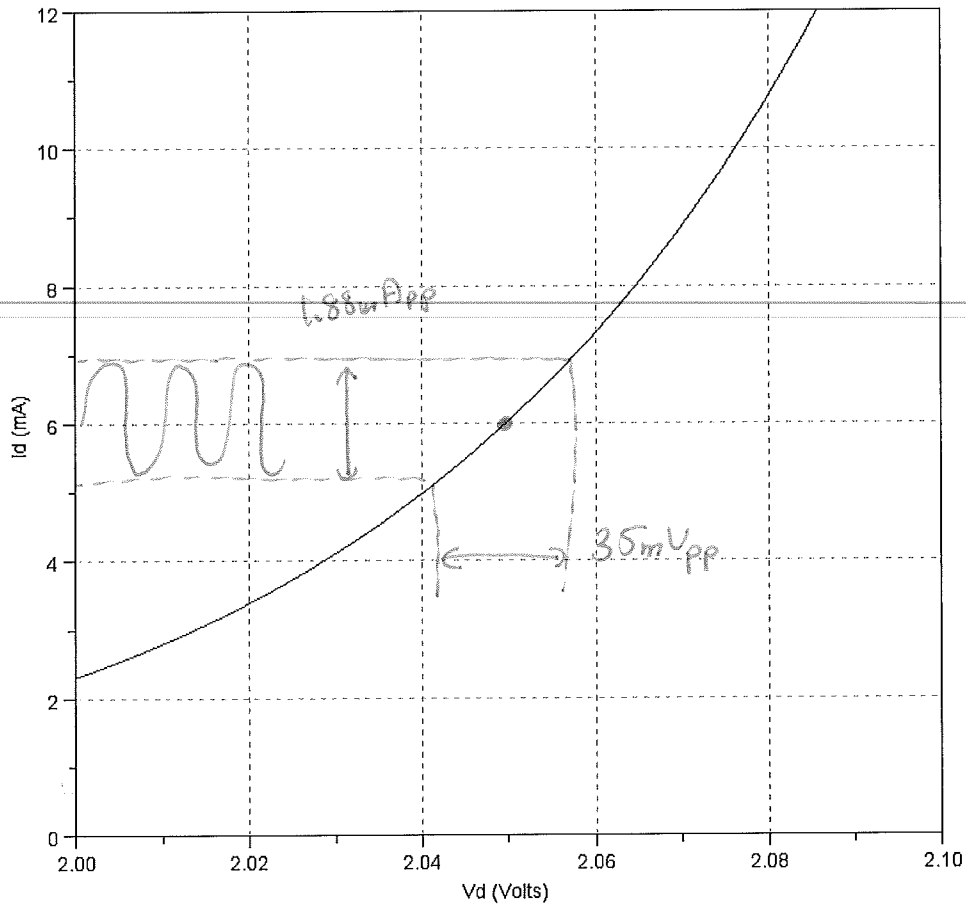
$$I_c = \frac{1V_{pp}}{530\Omega} = 1.88\mu A_{pp}$$




3) A light-sensitive resistor picks up the light and has a resistance of

$$R = 2000 + 10 \sin(6280t) \text{ Ohms}$$

Determine the DC and the AC voltage at  $V_c$ .

DC Value of $V_c$	AC Value of $V_c$ (1kHz term)
6.25V	19.5mV <sub>pp</sub> 9.76mV <sub>p</sub> 6.90mV <sub>rms</sub>

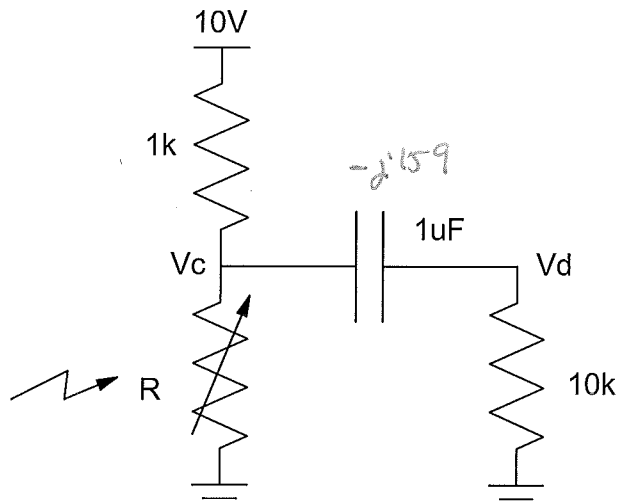

$$\frac{2010 \Omega}{2010 \parallel 10000 - j159} = 1673 \Omega$$

$$\left( \frac{1673}{1673 + 10000} \right) 10 = 6.2597V$$


$$\frac{2000 \Omega}{2000 \parallel 10k} = 1667 \Omega$$

$$\left( \frac{1667}{1667 + 10k} \right) 10 = 6.25V$$

DC value

$$\frac{1990 \Omega}{1990 \parallel 10k} = 1659 \Omega$$

$$6.24V$$

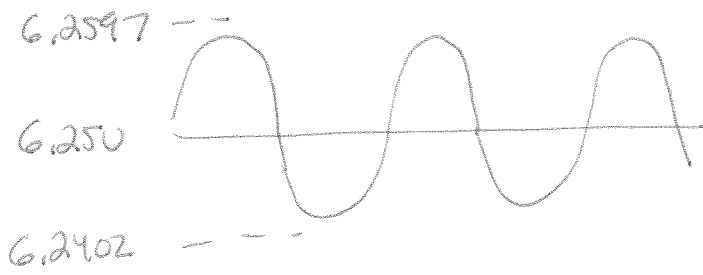


4) Assume

$$V_c(t) = 5 + 2 \cos(6280t)$$

Determine  $V_d(t)$

DC Value of $V_d$	AC value of $V_d$ (@ 100 rad/sec)
<del>5</del> 0V	$= 1.99997V_p$ $= 1.414V_{rms}$

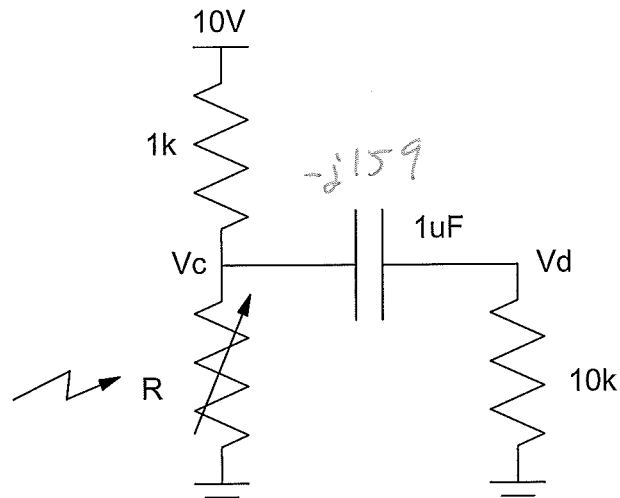

DC  
gain = 0


AC  
 $= \left( \frac{10k}{10k - j159} \right) \cdot 2V$   
 $= 1.99997V$

5) Assume  $V_d$  is

- 0V DC
- 0.1Vpp @ 1kHz

Design a circuit to amplify this signal to 2Vpp

gain = 20

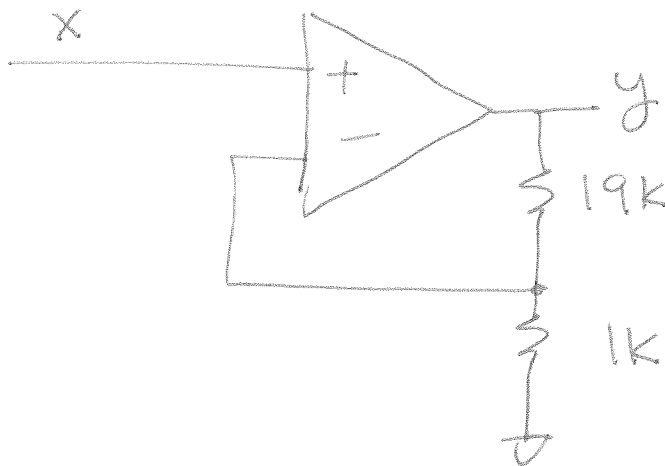

Bonus! The Permian extinction (251 million years ago) wiped out 97% of all life forms on Earth and left a planet that was nearly devoid of life for 10 million years. Scientists are pretty sure this mass extinction was triggered by climate change caused by CO<sub>2</sub> emissions from the Siberian Traps (a massive volcano).

How much was this temperature increase?

10°C