


ECE 321 - Homework #1

Op-Amps, Instrumentation Amplifiers. Due Monday, October 31st

Assume ideal op-amps.

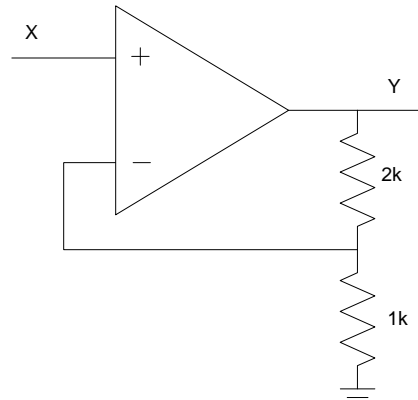
1) Design an op-amp circuit with a gain of +3.

There are many solutions. One that works is:



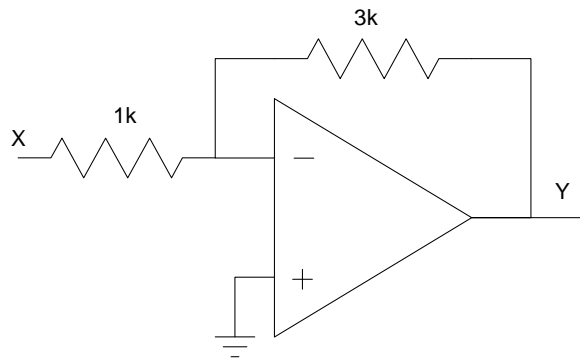2) Design an op-amp circuit with a gain of -3

There are many solutions. One that works is:




3) Design an op-amp circuit to implement the function

$$Y = 2X + 3$$

Rewrite as
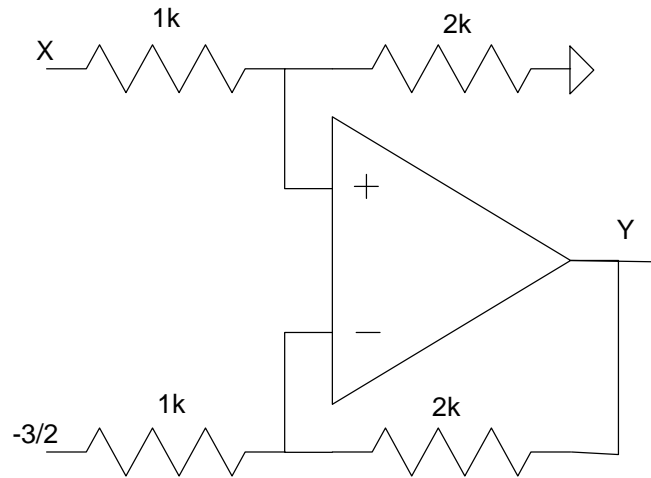
$$Y = 2\left(X - \left(-\frac{3}{2}\right)\right)$$



4) Design a circuit which meets the following requirements


Input: 3 voltages (A, B, C), each $\pm 5V$, 0-10kHz, capable of driving 10mA

Output: Y: $\pm 5V$, capable of driving 10mA


Relationship: $Y = 2A + 3B + 4C$

The input resistors need to be more than

$$R_{in} > \frac{5V}{10mA} = 500\Omega$$

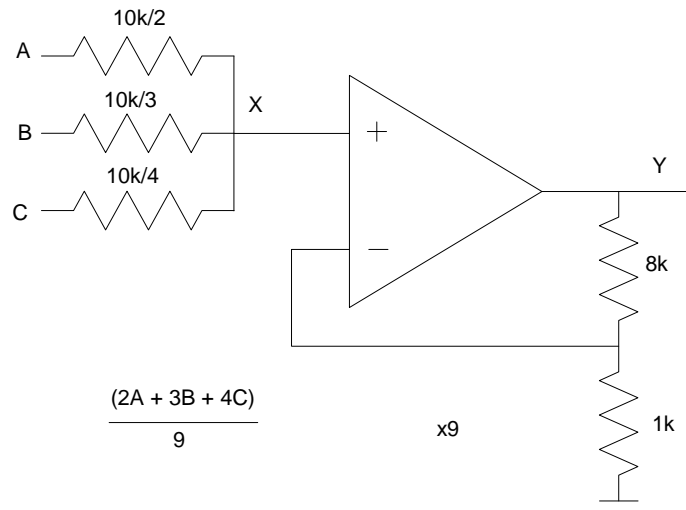

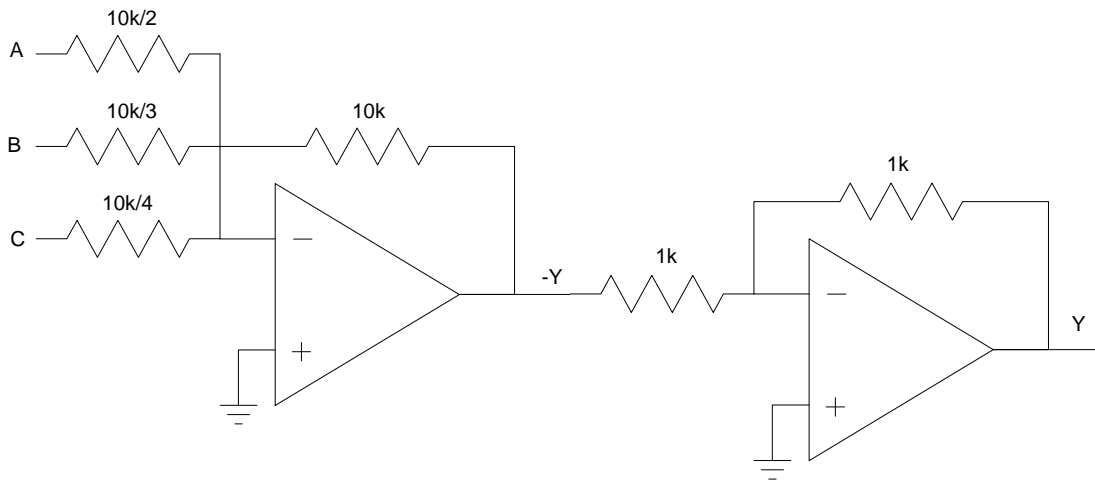Solution Based upon Non-Inverting Amplifiers:



Solution using inverting amplifiers.

5) Design a circuit which meets the following requirements:

Input: Thermistor

$$R = 1000 \cdot e^{-0.05(T-25)} \Omega$$

Output: Y, 0 .. 10V signal, capable of driving 10mA

Relationship:

- At 0C, Y = 0V
- At 10C, Y = 10V
- Y is proportional to temperature for 0C < T < 10C

At 0C

$$R = 3490 \text{ Ohms}$$

At 10C

$$R = 2117 \text{ Ohms}$$

Use a voltage divider with $R_{top} = 2700 \text{ Ohms}$ (the geometric mean of 0C and 10C).

$$R_{top} = \sqrt{3490 \cdot 2117} = 2718\Omega$$

Then, at 0C

$$V_a = \left(\frac{3490}{3490+2700} \right) 10V = 5.638V$$

At 10C


$$V_a = \left(\frac{2117}{2117+2700} \right) 10V = 4.3949V$$

For the output to have a spread of 10V, the gain needs to be

$$gain = \left(\frac{10V-0V}{4.3949V-5.638V} \right) = -8.04$$

The output increases when the input decreases (negative gain) so connect the divider to the - input.

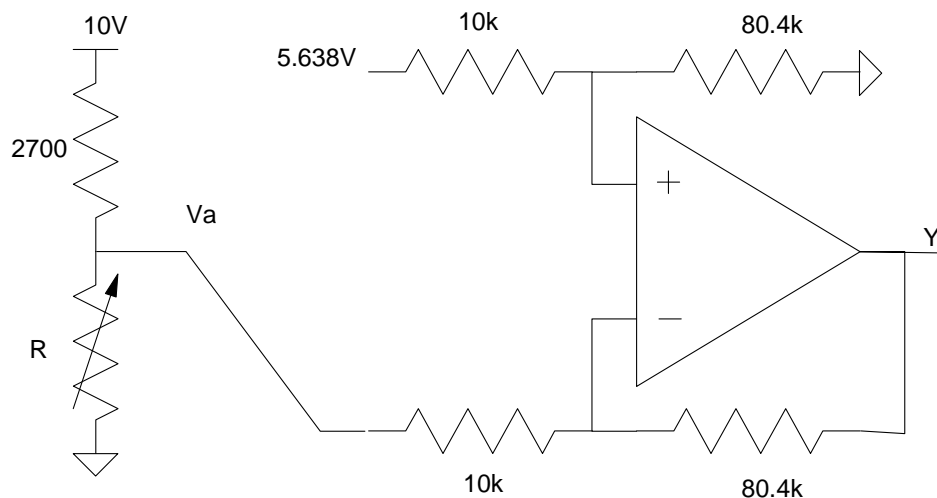The output is 0V when the input is 5.638V. Set the offset to 5.638V



In Matlab (not required)

```
-->T = [0:0.01:10]';  
-->R = 1000*exp(-0.05*(T - 25));  
-->Va = (R ./ (2700 + R))*10;  
-->gain = 8.04;  
-->Offset = 5.638;  
-->Y = gain*(Offset - Va);  
-->plot(T,Y)  
-->xlabel('Temperature (C)');  
-->ylabel('Y (Volts)');
```

