

# ECE 321 - Homework #4

Filters. Due Monday, November 21th

1) Assume you have a filter

$$Y = \left( \frac{2s+10}{s^2+20s+100} \right) X$$

a) What is the differential equation relating X and Y?

Cross Multiply

$$(s^2 + 20s + 100)Y = (2s + 10)X$$

which means

$$\frac{d^2y}{dt^2} + 20\frac{dy}{dt} + 100y = 2\frac{dx}{dt} + 10x$$

b) Determine y(t) assuming

$$x(t) = 2 + 3 \cos(4t)$$

Use superposition:

$$x(t) = 2$$

$$s = 0$$

$$\left( \frac{2s+10}{s^2+20s+100} \right)_{s=0} = 0.1$$

$$y = (0.1) \cdot 2$$

$$y = 0.2$$

$$x(t) = 3 \cos(4t)$$

$$s = j4$$

$$\left( \frac{2s+10}{s^2+20s+100} \right)_{s=j4} = 0.1104 \angle -4.94^\circ$$

$$y = (0.1104 \angle -4.94^\circ) \cdot 3 \cos(4t)$$

$$y = 0.3312 \cos(4t - 4.94^\circ)$$

Add the two inputs to get x(t)

Add the two outputs to get y(t)

$$y = 0.2 + 0.3312 \cos(4t - 4.94^\circ)$$

Design a filter for your light to sound circuit.

2) Requirements: Specify the requirements. For example,

Input: -10V to +10V analog, capable of 20mA, 0 to 10kHz

Output: -10V to +10V analog, capable of 20mA

Relationship: (Low-Pass Filter)

- $0.9 < \text{Gain} < 1.1$        $f < 250 \text{ Hz}$
- $\text{Gain} < 0.2$        $f > 750 \text{ Hz}$

3) Analysis: Design a filter (i.e. give the transfer function) for a filter which meets your design specs.

The number of poles you need are:

$$\left( \frac{250\text{Hz}}{750\text{Hz}} \right)^n = 0.2$$


$$n = 1.46$$

You need at least 1.46 poles to meet this requirement. Let  $n = 3$

Choosing a Chebychev filter with a corner at 250Hz:

```
-->p1 = 250*2*pi* 1.21*exp(j*69.5*pi/180)
      665.62641 + 1780.2987i
-->p2 = conj(p1)
      665.62641 - 1780.2987i
-->p3 = 250*2*pi * 0.85
      1335.1769
-->k = p1*p2*p3
      4.823D+09
-->Gs = k ./ ( (s + p1) .* (s + p2) .* (s + p3) );
-->plot(f,abs(Gs))
```
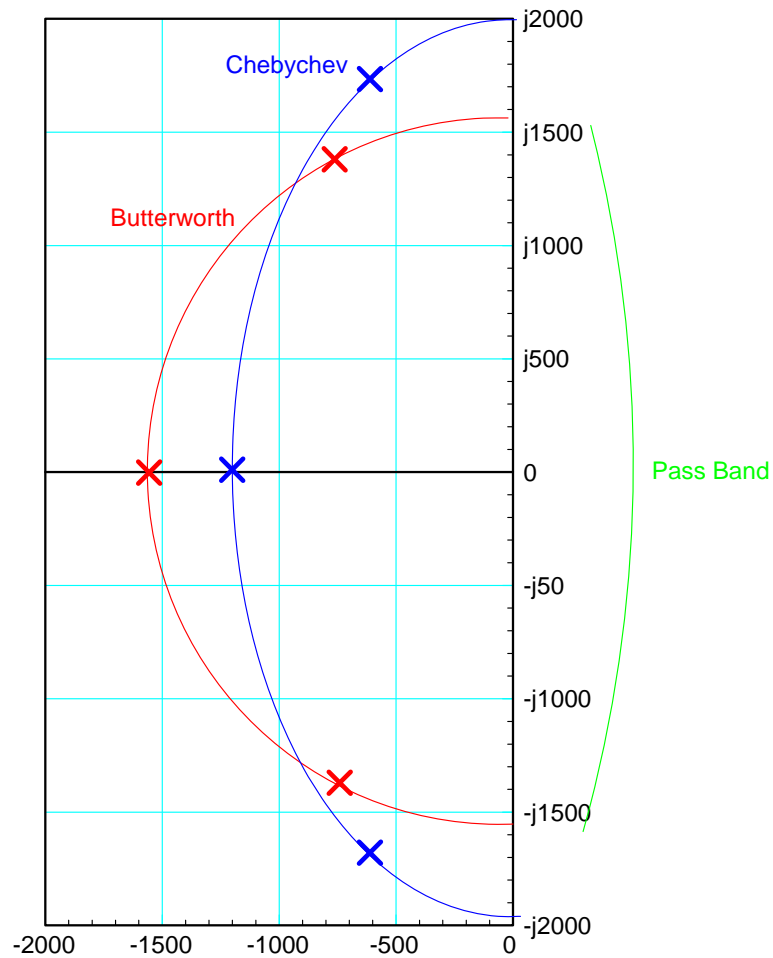
$$G(s) = \left( \frac{4.823 \cdot 10^9}{(s+1335)(s+1900\angle 69.5^\circ)(s+1900\angle -69.5^\circ)} \right)$$



Pole Location for the Chebychev filter: 250Hz Passband

a) Compute the gain of your filter at several points. For example, for the low-pass filter, compute the gain at  
{ 0Hz, 250Hz, 750Hz, 2kHz }

```
-->G = zpk([], [-p1, -p2, -p3], k)
-->evalfr(G, 0)
```

1.

```
-->abs(evalfr(G, j*250*pi*2))
```

0.9813375


```
-->abs(evalfr(G, j*750*pi*2))
```

0.0501830

```
-->abs(evalfr(G, j*1000*pi*2))
```

0.0203890

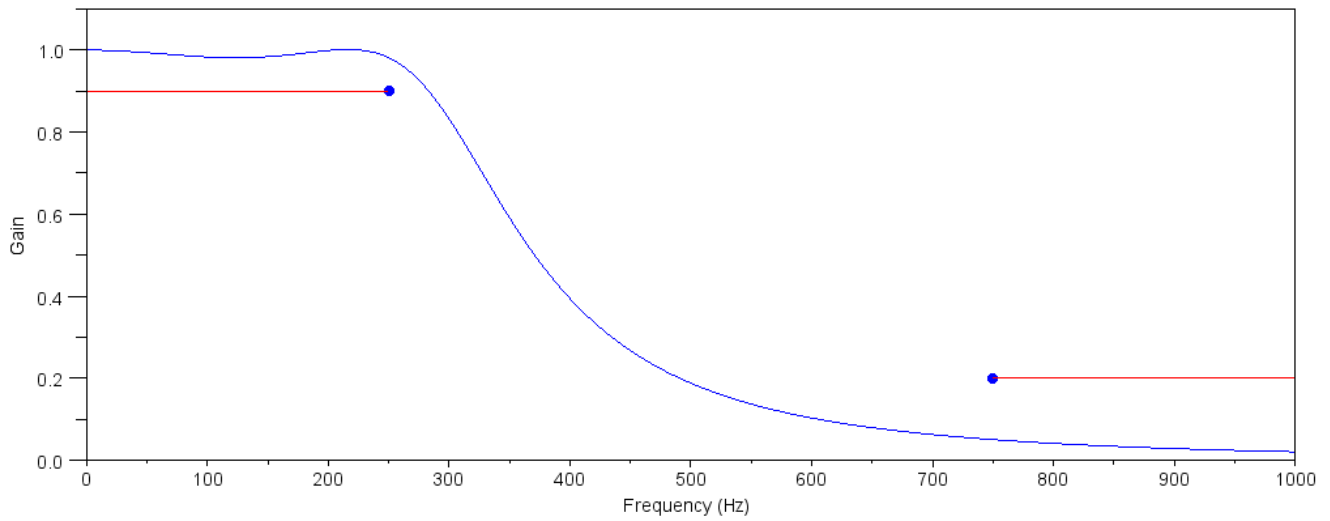b) Plot the gain of your filter from 0Hz to 1kHz (or so) to verify it meets your requirements.



4) Design an op-amp circuit to implement your filter. Let  $R = 100k$

$$\left(\frac{1}{RC}\right) = 1335$$

$$C = 0.0075\mu F$$

$$\left(\frac{1}{RC}\right) = 1900$$


$$C = 0.0053\mu F$$

$$3 - k = 2 \cos(69.5^\circ)$$

$$k = 2.23 = 1 + \frac{R_1}{R_2}$$


$$R_2 = 100k$$

$$R_1 = 123k$$

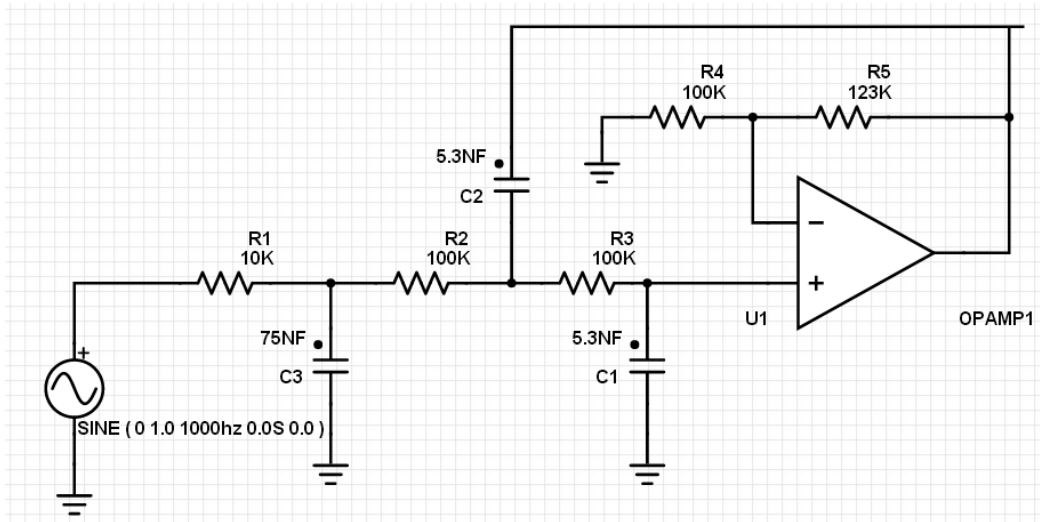

5) Simulation: Check your design in PartSim or similar programs at the same frequencies you computed in part 3.

	Calculated	Simulated	Measured
100 Hz	2.1924	2.209	-
250 Hz	2.1884	2.005	-
750 Hz	0.1119	0.106	-
1000 Hz	0.0455	0.044	-

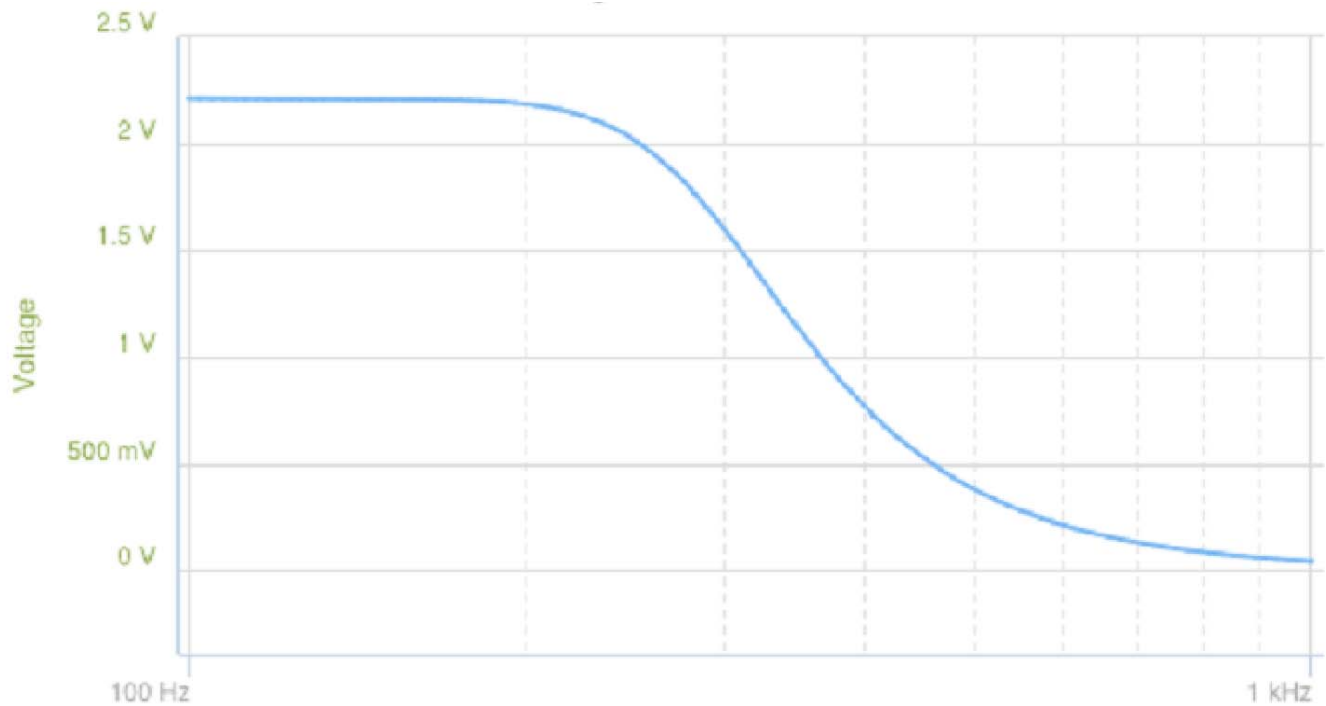

6) Validation: Build a the op-amp circuit and measure the gain at the frequencies computed in part 3.

