

# ECE 321 - Homework #1

Instrumentation Amplifiers, Push-Pull Amplifiers. Due Monday, November 6th, 2017

1) Design a circuit to implement the function

a)  $Y = 3X$

b)  $Y = -3X$

c)  $Y = 3X - 4$

2) An A/D converter on a microcontroller requires a 0..5V signal. Design a circuit which converts -10V..+10V to 0..5V.

3) The output of a D/A converter is 0..5V. Design a circuit to convert this to -10V..+10V

Requirements:

- Input: -10V .. +10V capable of 20mA
- Output: 8 Ohm speaker
- Relationship:  $Y = X$
- Tolerance:  $Y = X \pm 0.2V$

4) Analysis: Design a push-pull amplifier which meets the above requirements. Compute the voltages and currents at

- $V_{in} = -10V$  DC
- $V_{in} = +10V$  DC
- $V_{in} = +1V$  DC

(check the two endpoints and one or two points inbetween)

5) Simulation: Check your analysis using PartSim. Verify its operation at

- $V_{in} = -10V$  DC
- $V_{in} = +10V$  DC
- $V_{in} = +1V$  DC

6) Validation: Build the push-pull amplifier and verify its operation at

- $V_{in} = -10V$  DC
- $V_{in} = +10V$  DC
- $V_{in} = +1V$  DC

Note: Save your circuits. We'll be using them in the following weeks.