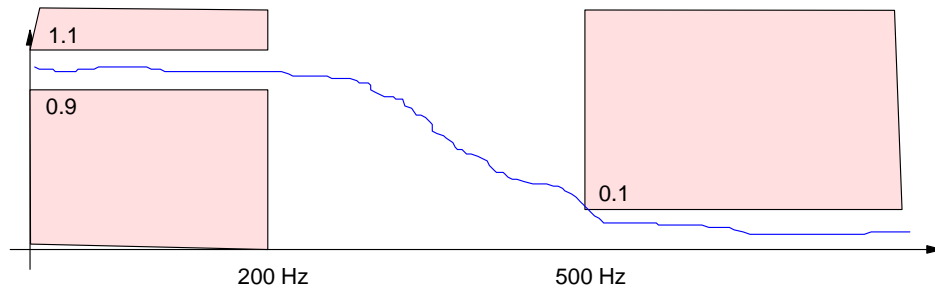


# ECE 321 - Homework #3

Filter Design, Analog Computers. Due Monday, November 20th, 2017

Problem 1-3) Design a low-pass filter to meet the following requirements:


- Input: +/- 10V, capable of 20mA
- Output: +/- 10V capable of 20mA
- Relationship:
  - $1.1 < \text{Gain} < 0.9$        $f < 200$  Hz
  - $\text{Gain} < 0.1$                $f > 600$  Hz



- 1) Give a filter,  $G(s)$ , which meets these requirements. Plot the gain vs. frequency for your  $G(s)$  in Matlab.
- 2) Design a circuit to implement this circuit
- 3) Test your design in PartSim

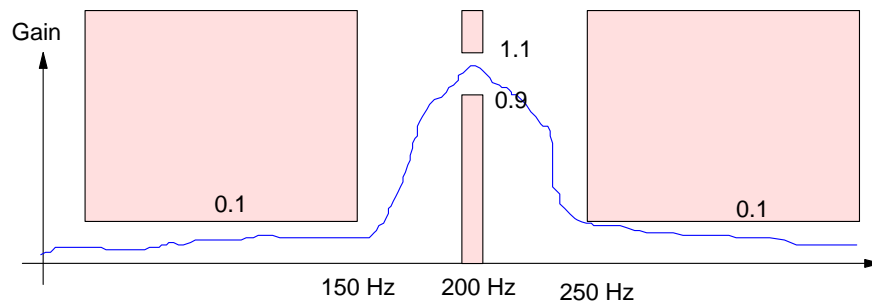2) Design a band-pass filter to meet the following requirements:

- Input: +/- 10V, capable of 20mA
- Output: +/- 10V capable of 20mA
- Relationship:
  - $1.1 < \text{Gain} < 0.9$        $f = 200$  Hz
  - $\text{Gain} < 0.1$                $f > 250$  Hz
  - $\text{Gain} < 0.1$                $f < 150$  Hz



- a) Give a filter,  $G(s)$ , which meets these requirements. Plot the gain vs. frequency for your  $G(s)$  in Matlab.
  - b) Design a circuit to implement this circuit
  - c) Test your design in PartSim
- 3) Build one of these circuits and check that it meets the requirements