

ECE 321 - Homework #5

2-port models, CE, CB, CC Amplifiers. Due Monday, December 4th, 2017

- 1) Determine the Q-point for the following circuit. Assume a 3904 transistor ($\beta = 200$)
- 2) Modify this circuit so that the Q-point is $V_{ce} = 6.0V$

- 3a) Draw the small-signal model for your circuit of problem #2 when set up as a common emitter (CE) configuration
- 3b) Determine the 2-port model for this amplifier in a CE configuration.

- 4a) Draw the small-signal model for your circuit of problem #2 when set up as a common base (CB) configuration
- 4b) Determine the 2-port model for this amplifier in a CB configuration.

- 5a) Draw the small-signal model for your circuit of problem #2 when set up as a common collector (CC) configuration
- 5b) Determine the 2-port model for this amplifier in a CC configuration.

- 6) Determine the 2-port model for a 4-stage amplifier:
CB : CE : CE : CC

