

ECE 321 - Quiz #3 - Name _____

2-Port Models, DC Analysis of Transistor Circuits. November 30, 2017

1) The transfer function for a 6th-order Butterworth filter with a corner at 1 rad/sec is

$$G(s) = \left(\frac{1}{(s+1\angle\pm 15^\circ)(s+1\angle\pm 45^\circ)(s+1\angle\pm 75^\circ)} \right)$$

What is the transfer function for a 6th-order Butterworth low-pass filter with

- A corner at 100 Hz and
- A DC gain of 1.00



$$G(s) = \frac{(200\pi)^6}{(s + 200\pi\angle\pm 15^\circ)(s + 200\pi\angle\pm 45^\circ)(s + 200\pi\angle\pm 75^\circ)}$$

$$100\text{Hz} = 200\pi \text{ rad/sec}$$

$$G(s) = \frac{1}{\left(\frac{s}{200\pi} + 1\angle\pm 15^\circ\right)\left(\frac{s}{200\pi} + 1\angle\pm 45^\circ\right)\left(\frac{s}{200\pi} + 1\angle\pm 75^\circ\right)}$$

2) Determine the 2-port model for the following circuit

Rin	Ai	Ao	Rout
667	2/3	1/4	250

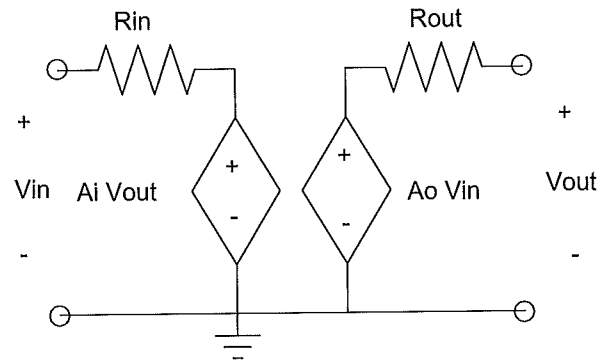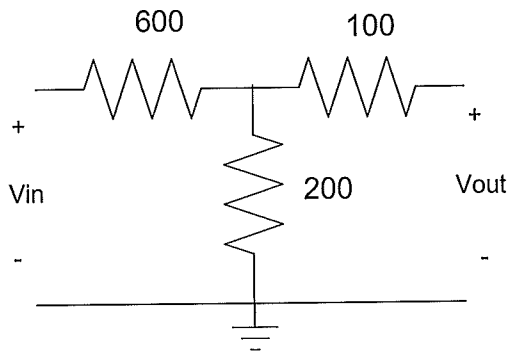

$$R_{in} = 600 + 100 \parallel 200 = 667$$



$$A_i = \left(\frac{200}{200 + 100} \right) = \frac{2}{3}$$

$$A_o = \left(\frac{200}{200 + 600} \right) = \frac{1}{4}$$

$$R_{out} = 100 + 600 \parallel 200 = 250$$

3) Determine the 2-port model for the following circuit

Rin	Ai	Ao	Rout
105Ω	.53	.75	19.67

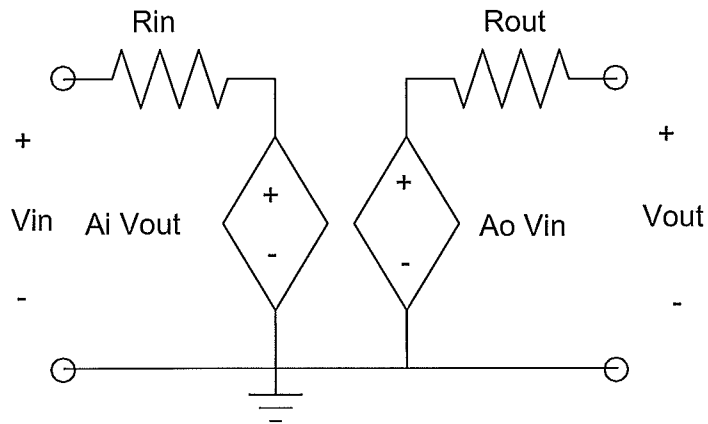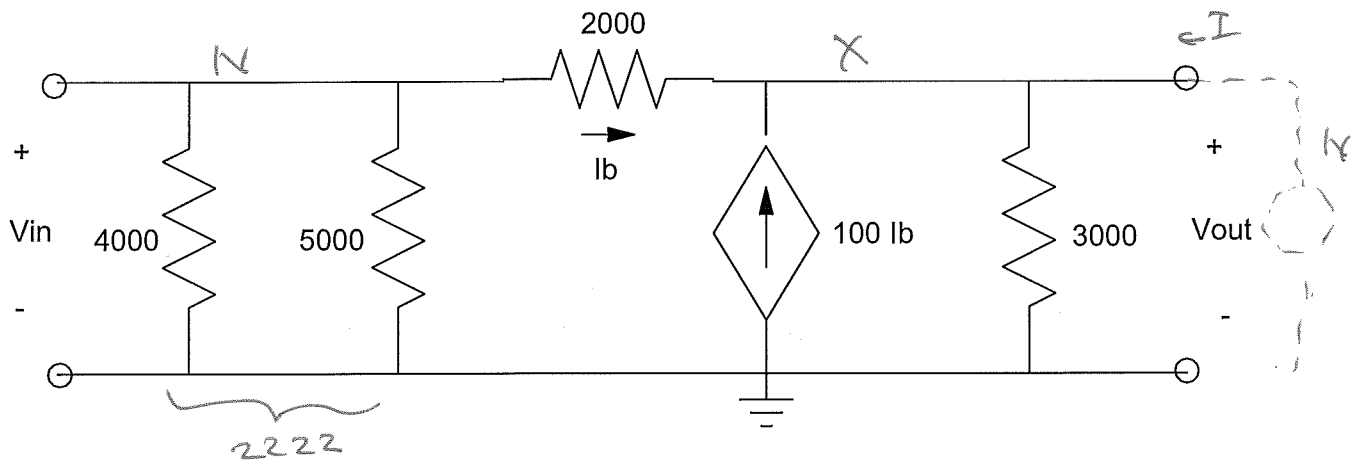

$$R_{in}: 4k \parallel 5k \parallel 2k = 105\Omega$$

$$A_i: \left(\frac{2222}{2000 + 2222} \right) = .53$$

$$A_o: \frac{X-1}{2k} + 100 \frac{X-1}{2k} + \frac{X}{3k} = 0$$

$$X = \frac{1/2k + 1/2k}{1/2k + 1/2k + 1/3k} = .75$$

$$R_{out}: I = \frac{1}{3k} + \frac{1}{2k} + \frac{100}{2k}$$



$$I = 50 \mu A$$

$$R = 1/I = 19.67\Omega$$

4) Determine the Thevenin equivalent for R1 and R2 as well as the Q-point for the following transistor amplifier. Assume ideal silicon transistors with

- $V_{be} = 0.7V$
- $\beta = 200$

Thevenin Equivalent of R1 and R2		Q-Point	
Vb	Rb	Vce	Ic
4V	66.7k	4.944V	1.408mA

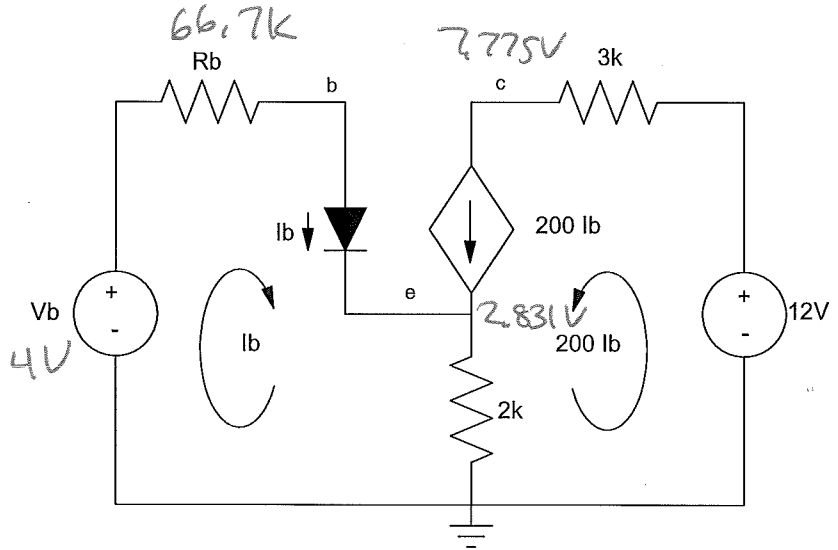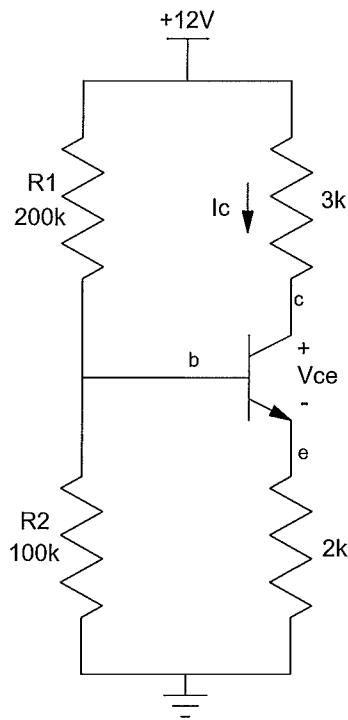


$$I_b = \frac{4 - 0.7}{66.7k + 2k(1 + 200)} = 7.04 \mu A$$

$$I_c = \beta I_b = 1.408 mA$$

5) Design a transistor amplifier so that the Q-point is


- $V_{ce} = 6.0V$

R1 and R2		Thevenin Equivalent of R1 and R2	
R1	R2	V_b	R_b
143k	55.47k	3.347V	40k

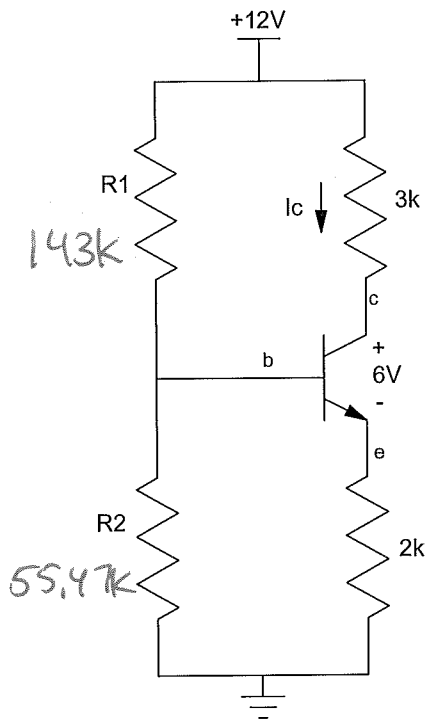

$$\frac{R_1 R_2}{R_1 + R_2} = 40k$$
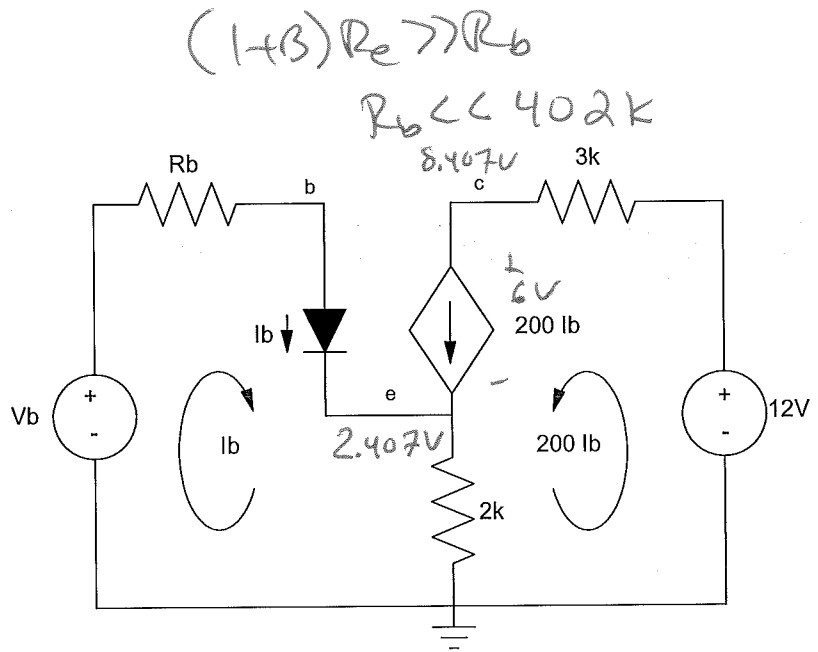
$$R_{th} \left(\frac{R_2}{R_1 + R_2} \right) 12V = 3.347V$$



$$\sum 2000 \cdot 200 I_b + 3000 \cdot 200 I_b = 6V$$

$$I_b = 5.988 \mu A$$

$$V_b = 3.347V$$

Bonus! How close is solar to being competitive? In industry, a 7-year payback is considered the break-even point: if an investment pays for itself in less than 7 years, you do it. If it takes more than 7 years, you don't.

What is the present payback time (in years) for solar energy in Fargo, ND at 10 cents / kWh with no government subsidies?

12 years

