

## ECE 321 - Homework #2

Active Filters. Poles, Zeros, Frequency Response. Due Monday, November 13th, 2017

1) For the following filter

$$Y = \left( \frac{100}{(s+5)(s+10)} \right) X$$

a) What is the differential equation relating X and Y?

Cross multiply

$$(s+5)(s+10)Y = (100)X$$

$$(s^2 + 15s + 50)Y = 100X$$

$sY$  means *the derivative of Y*

$$\frac{d^2y}{dt^2} + 15\frac{dy}{dt} + 50y = 100x$$

b) Determine  $y(t)$  assuming

$$x(t) = 2 + 3 \sin(5t) + 4 \sin(100t)$$

Use superposition

$$x(t) = 2$$

$$s = 0$$

$$\left( \frac{100}{(s+5)(s+10)} \right)_{s=0} = 2$$

$$y = (2) \cdot 2$$

$$y = 4$$

$$x(t) = 3 \sin(5t)$$

$$s = j5$$

$$\left( \frac{100}{(s+5)(s+10)} \right)_{s=j5} = 1.26 \angle -71^\circ$$

$$y = (1.26 \angle -71^\circ) \cdot 3 \sin(5t)$$

$$y = 3.79 \sin(5t - 71^\circ)$$

$$x(t) = 4 \sin(100t)$$

$$s = j100$$

$$\left( \frac{100}{(s+5)(s+10)} \right)_{s=j100} = 0.01 \angle -171^\circ$$

$$y = (0.01 \angle -171^\circ) \cdot 4 \sin(100t)$$

$$y = 0.04 \sin(100t - 171^\circ)$$


Add up the three inputs to get the total input.

Add up the three outputs to get the total output.

$$y(t) = 4 + 3.79 \sin(5t - 71^\circ) + 0.04 \sin(100t - 171^\circ)$$

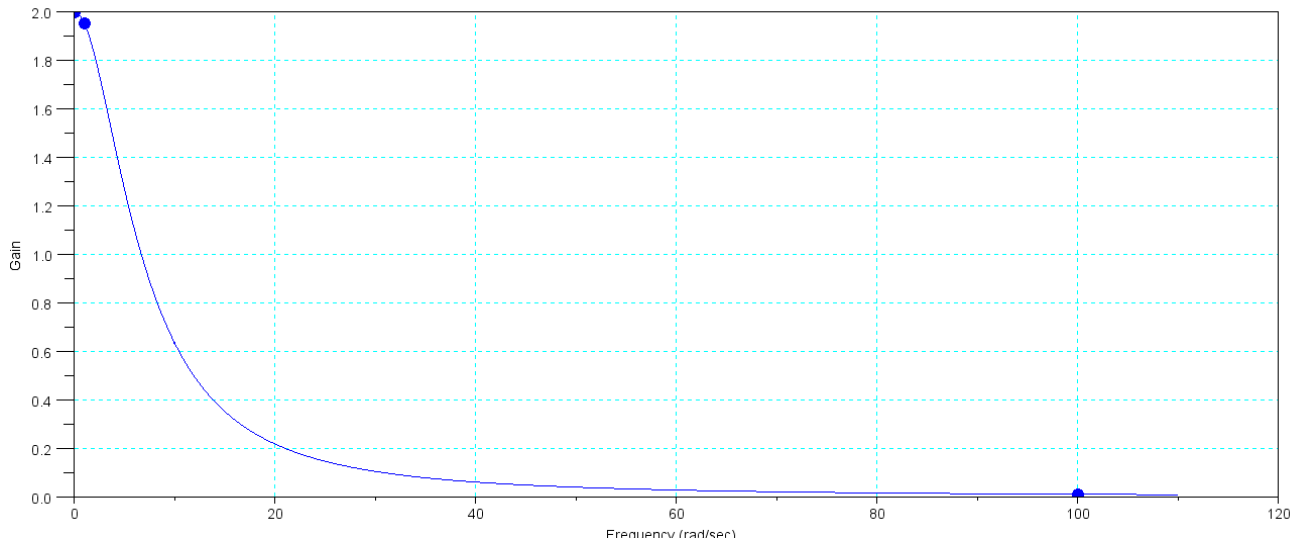c) Plot the gain vs. frequency for this filter from 0 to 20 rad/sec

```
-->w = [0:0.01:20]';
-->j = sqrt(-1);
-->s = j*w;
-->G = 100 ./ ((s+5).*(s+10));
-->plot(w,abs(G))
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
```



Gain vs. frequency with the gain at {0, 5, 100} shown. Note that this is a low-pass filter:

- Low frequencies are passed (0, 5)
- High frequencies are rejected (100)


d) Design a circuit to implement this filter.

Since you have real poles, use a 2-stage RC filter

$$\frac{1}{R_1 C_1} = 5 \quad R_1 = 100k \quad C_1 = 2\mu F$$

$$\frac{1}{R_2 C_2} = 100 \quad R_2 = 1M \quad C_2 = 0.01\mu F$$

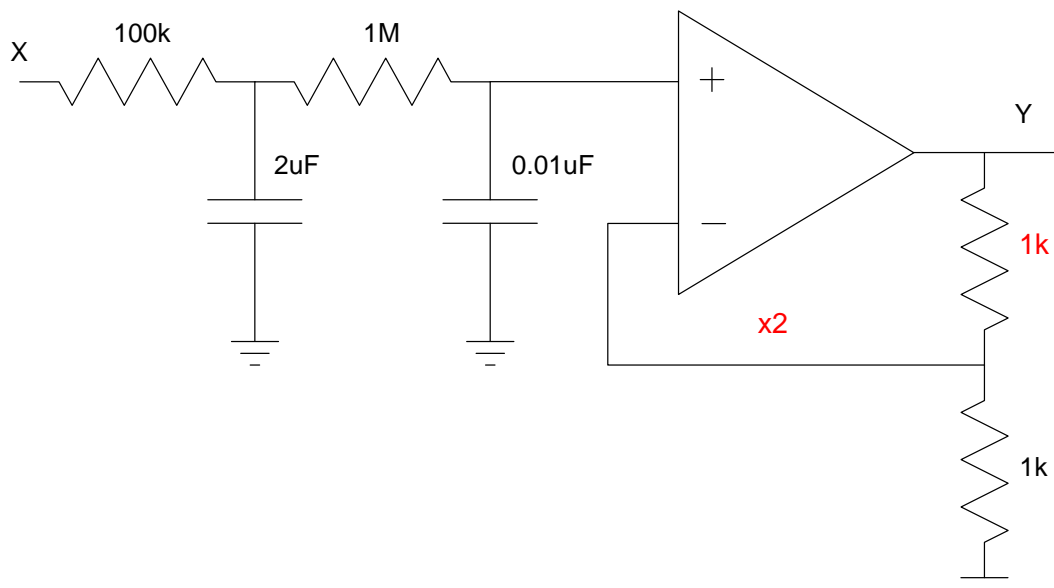To add a gain of 4 (DC gain is 4), add a x4 amplifier at the end:



2) For the following filter:

$$Y = \left( \frac{200}{s^2 + 4s + 25} \right) X$$

a) What is the differential equation relating X and Y?

Cross multiply

$$(s^2 + 4s + 25)Y = (200)X$$

$sY$  means *the derivative of Y*

$$\frac{d^2y}{dt^2} + 4\frac{dy}{dt} + 25y = 200x$$

b) Determine  $y(t)$  assuming

$$x(t) = 2 + 3 \sin(5t) + 4 \sin(100t)$$

$$x(t) = 2$$

$$s = 0$$

$$\left( \frac{200}{s^2 + 4s + 25} \right)_{s=0} = 8$$

$$y = (8) \cdot 2$$

$$y = 16$$

$$x(t) = 3 \sin(5t)$$

$$s = j5$$

$$\left( \frac{200}{s^2 + 4s + 25} \right)_{s=j5} = 10 \angle -90^\circ$$

$$y = (10 \angle -90^\circ) \cdot 3 \sin(5t)$$

$$y = 30 \sin(5t - 90^\circ)$$

$$x(t) = 4 \sin(100t)$$

$$s = j100$$

$$\left( \frac{200}{s^2 + 4s + 25} \right)_{s=j100} = 0.02 \angle -178^\circ$$

$$y = (0.02 \angle -178^\circ) \cdot 4 \sin(100t)$$


$$y = 0.08 \sin(100t - 178^\circ)$$

Putting it all together:

$$y(t) = 16 + 30 \sin(5t - 90^\circ) + 0.08 \sin(100t - 178^\circ)$$

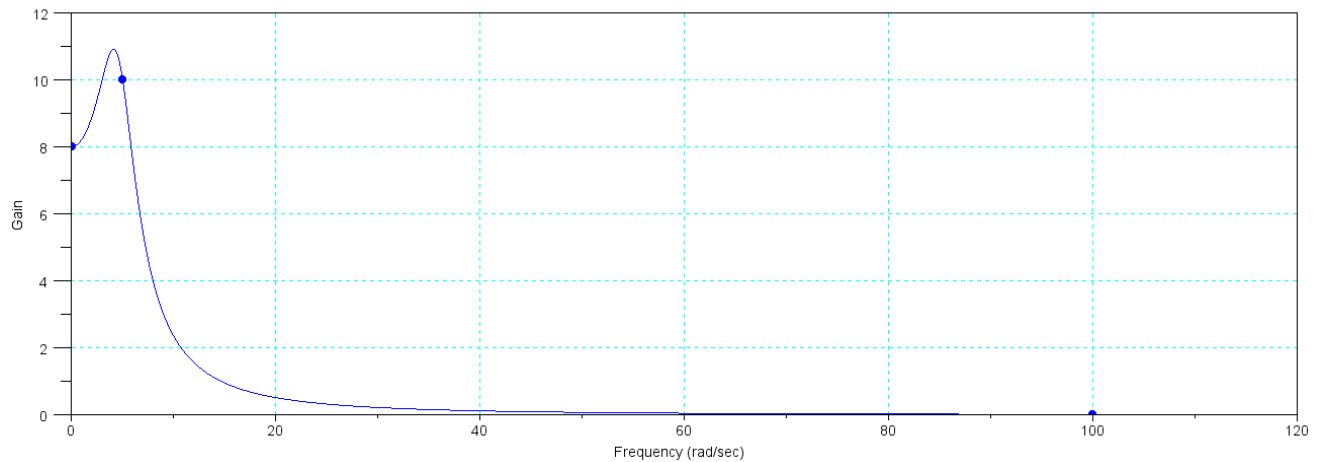c) Plot the gain vs. frequency for this filter from 0 to 20 rad/sec

```
-->w = [0:0.01:110]';  
-->s = j*w;  
-->G = 200 ./ (s.^2 + 4*s + 25);  
-->plot(w,abs(G))  
-->xlabel('Frequency (rad/sec)');  
-->ylabel('Gain');
```



d) Design a circuit to implement this filter.

$$\left( \frac{200}{s^2 + 4s + 25} \right) = \left( \frac{k \left( \frac{1}{RC} \right)^2}{s^2 + \left( \frac{3-k}{RC} \right) s + \left( \frac{1}{RC} \right)^2} \right)$$

This filter has poles at

$$s = -2 \pm j4.58 = -5 \angle \pm 66.42^\circ$$

$1/RC$  is the amplitude of the poles

$$\left( \frac{1}{RC} \right)^2 = 25$$

$$\left( \frac{1}{RC} \right) = 5$$

Let  $R = 100k$ ,  $C = 2\mu F$

$k$  sets the angle of the pole


$$\left( \frac{3-k}{RC} \right) = 4$$

$$3 - k = 2 \cos(66.42^\circ)$$

$$k = 2.2$$

Let  $R_1 = 100k$ ,  $R_2 = 120k$

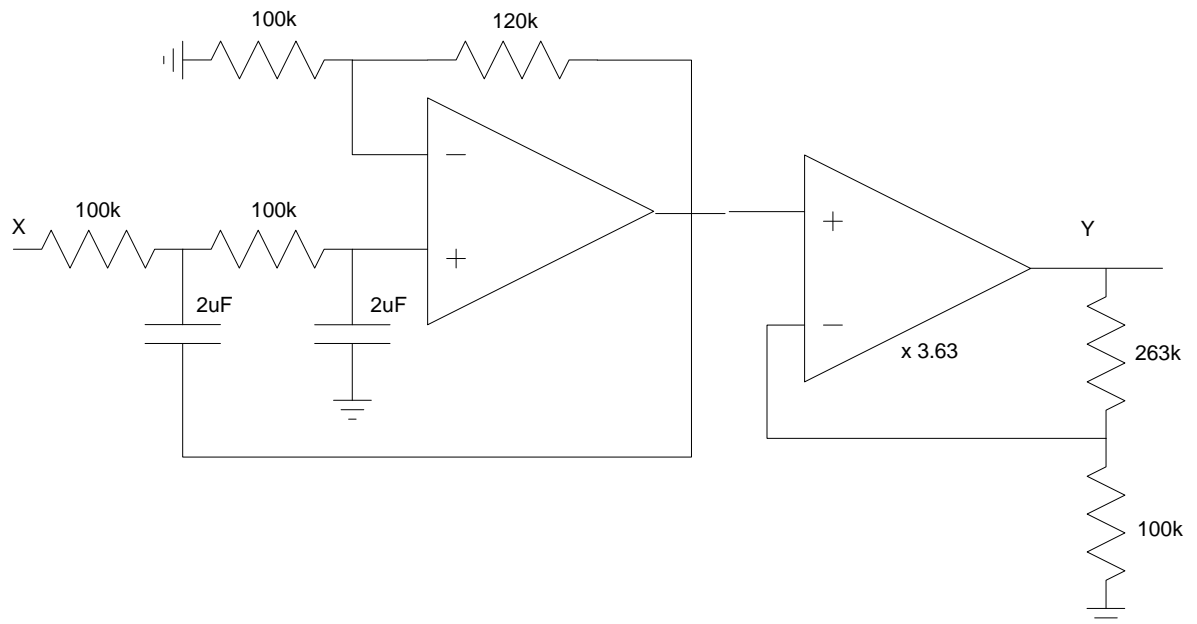This gives a DC gain of 2.2. For a DC gain of 8, add another gain of 3.63



3) For the following filter:

$$Y = \left( \frac{2s}{s^2 + 2s + 25} \right) X$$

a) What is the differential equation relating X and Y?

Cross multiply

$$(s^2 + 2s + 25)Y = (2s)X$$

$sY$  means *the derivative of Y*

$$\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + 25y = 2\frac{dx}{dt}$$

b) Determine  $y(t)$  assuming

$$x(t) = 2 + 3 \sin(5t) + 4 \sin(100t)$$

$$x(t) = 2$$

$$s = 0$$

$$\left( \frac{2s}{s^2 + 2s + 25} \right)_{s=0} = 0$$

$$y = (0) \cdot 2$$

$$y = 0$$

$$x(t) = 3 \sin(5t)$$

$$s = j5$$

$$\left( \frac{2s}{s^2 + 2s + 25} \right)_{s=j5} = 1$$

$$y = (1) \cdot 3 \sin(5t)$$

$$y = 3 \sin(5t)$$

$$x(t) = 4 \sin(100t)$$

$$s = j100$$

$$\left( \frac{2s}{s^2 + 2s + 25} \right)_{s=j100} = 0.02 \angle -88^\circ$$

$$y = (0.02 \angle -88^\circ) \cdot 4 \sin(100t)$$


$$y = 0.08 \sin(100t - 88^\circ)$$

Putting it all together:

$$y(t) = 0 + 3 \sin(5t) + 0.08 \sin(100t - 88^\circ)$$

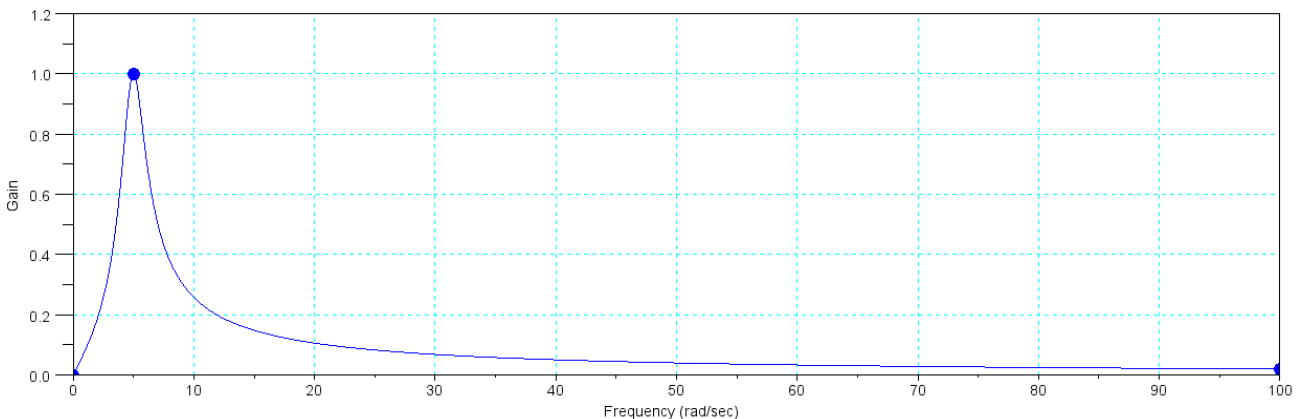c) Plot the gain vs. frequency for this filter from 0 to 20 rad/sec

```
-->w = [0:0.01:100]';
-->s = j*w;
-->G = 2*s ./ (s.^2 + 2*s + 25);
-->plot(w,abs(G))
-->xlabel('Frequency (rad/sec)');
-->ylabel('Gain');
```




This is a band-pass filter: frequencies over the band of 3 to 7 rad/sec are passed.

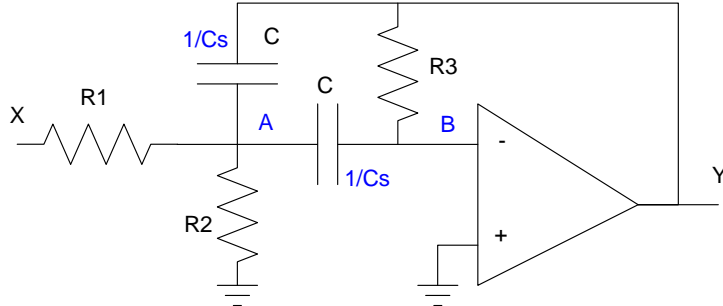d) Design a circuit to implement this filter.

$$Y = \left( \frac{2s}{s^2 + 2s + 25} \right) X$$

From the lecture notes, this form has the following circuit:



$$Y = \left( \frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2}\right)\left(\frac{1}{R_3 C^2}\right)} \right) X$$

Matching terms: Let  $C = 1\mu\text{F}$

$$\left( \frac{1}{R_1 C} \right) = 2 \quad R_1 = 500\text{k}$$

$$\left( \frac{2}{R_3 C} \right) = 2 \quad R_3 = 1\text{M}$$

$$\left( \frac{R_1 + R_2}{R_1 R_2} \right) \left( \frac{1}{R_3 C^2} \right) = 25 \quad R_2 = 43.5\text{k}$$