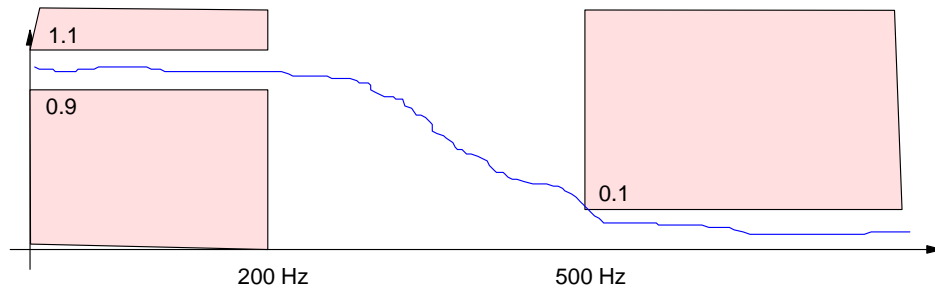


ECE 321 - Homework #3

Filter Design, Analog Computers. Due Monday, November 20th, 2017

Problem 1-3) Design a low-pass filter to meet the following requirements:

- Input: +/- 10V, capable of 20mA
- Output: +/- 10V capable of 20mA
- Relationship:
 - $1.1 < \text{Gain} < 0.9$ $f < 200 \text{ Hz}$
 - $\text{Gain} < 0.1$ $f > 500 \text{ Hz}$



1) Give a filter, $G(s)$, which meets these requirements. Plot the gain vs. frequency for your $G(s)$ in Matlab.

First, determine the number of poles you need:

$$\left(\frac{200\text{Hz}}{500\text{Hz}}\right)^n = 0.1$$

$$n = \frac{\ln(0.1)}{\ln(0.4)} = 2.51$$

Let $n = 3$

Second, pick a type of filter. Let's use a Chebychev filter. From Bison Academy, a 3rd-order Chebychev filter with a corner at 1 rad/sec is

$$G(s) = \left(\frac{k}{(s+0.85)(s+1.21\angle\pm 69.5^\circ)} \right)$$

Scale this so the corner is at 200Hz (400π)

$$G(s) = \left(\frac{k}{(s+1068)(s+1520\angle\pm 69.5^\circ)} \right)$$

Plot the gain vs. frequency in Matlab


```
-->f = [0:1000]';
-->w = 2*pi*f;
-->s = j*w;
-->p1 = 1068;
-->p2 = 1520*exp(j*69.5*pi/180);
-->p3 = conj(p2);
-->G = 1 ./ ((s+p1) .* (s+p2) .* (s+p3));
-->k = 1/abs(G(1))
```

2.468D+09

```

-->G = k ./ ( (s+p1) .* (s+p2) .* (s+p3) );
-->plot(f,abs(G))
-->plot([0,200,200],[0.9,0.9,0], 'r')
-->plot([500,500,1000],[1,0.1,0.1], 'r')
-->xlabel('Hz');

```

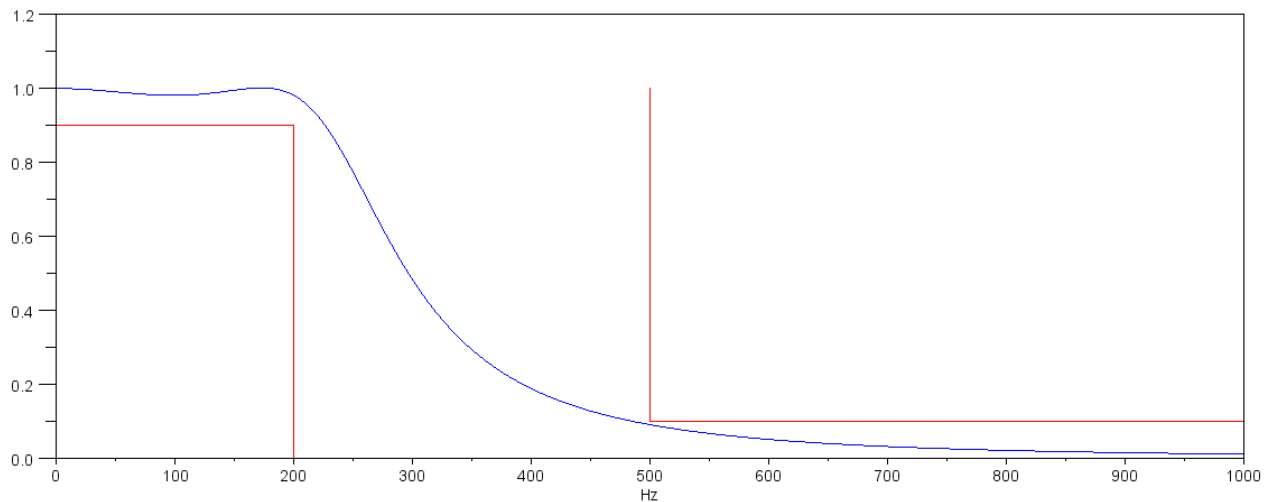

Pretty lucky: this meets the requirements.

answer:

$$G(s) = \left(\frac{2.468 \cdot 10^9}{(s+1068)(s+1520 \angle \pm 69.5^\circ)} \right)$$

2) Design a circuit to implement this circuit

Let $R_1 = 10k$

$$\frac{1}{R_1 C_1} = 1068$$

$$C_1 = 94nF$$

Let $R_2 = 100k$

$$\frac{1}{R_2 C_2} = 1520$$

$$C_2 = 6.58nF$$

For the gain:


$$(3 - k) = 2 \cos(69.5^\circ)$$

$$k = 2.3$$

Let $R_3 = 100k$, $R_4 = 130k$

This results in the circuit having a gain of 2.3. Either

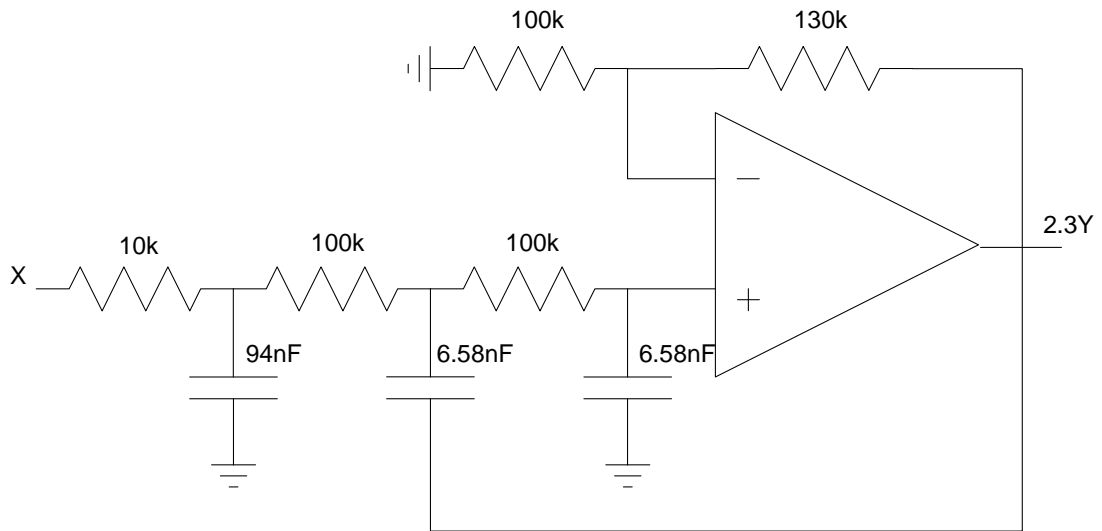- Live with it. Call the output 2.3Y and adjust later stages, or
- Drop the gain by a factor of 2.3




Using the latter and Thevenin equivalents.


$$R_a || R_b = R_{th} = 10k$$


$$\left(\frac{R_b}{R_a + R_b} \right) X = \frac{X}{2.3}$$

which gives $R_a = 23k$, $R_b = 17.7k$

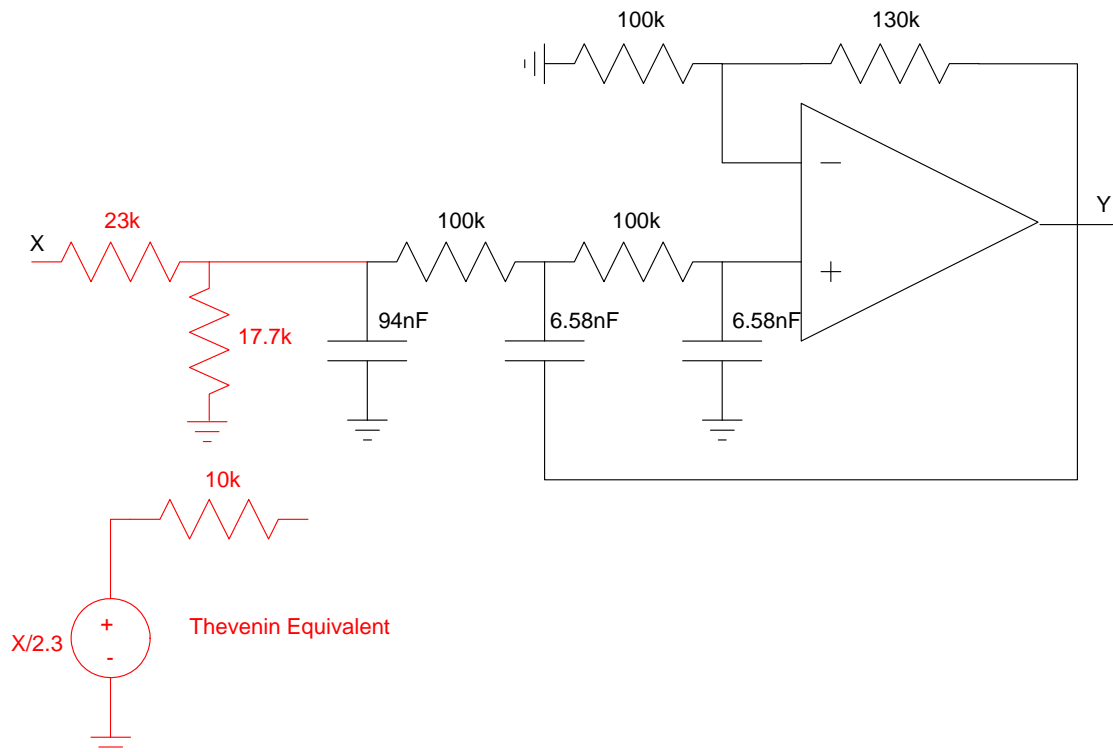


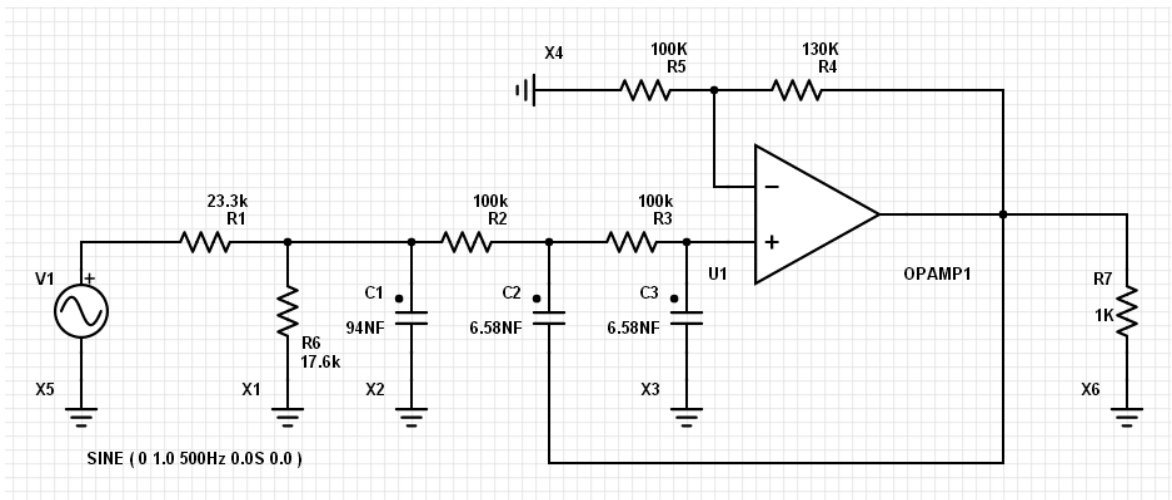3) Test your design in PartSim: Assume a load of 1k Ohms is added (should be part of the requirements: capable of driving a 1k Ohm load)



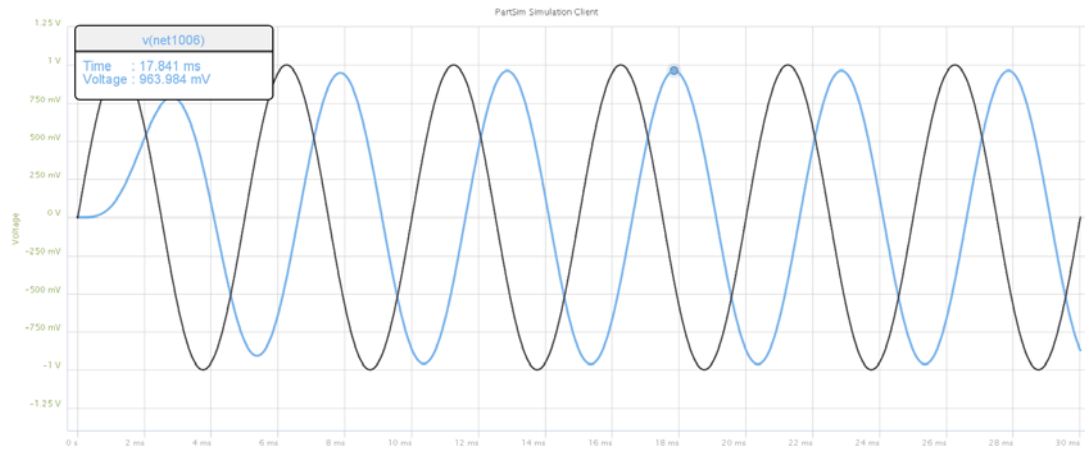

200Hz: Gain = 0.963

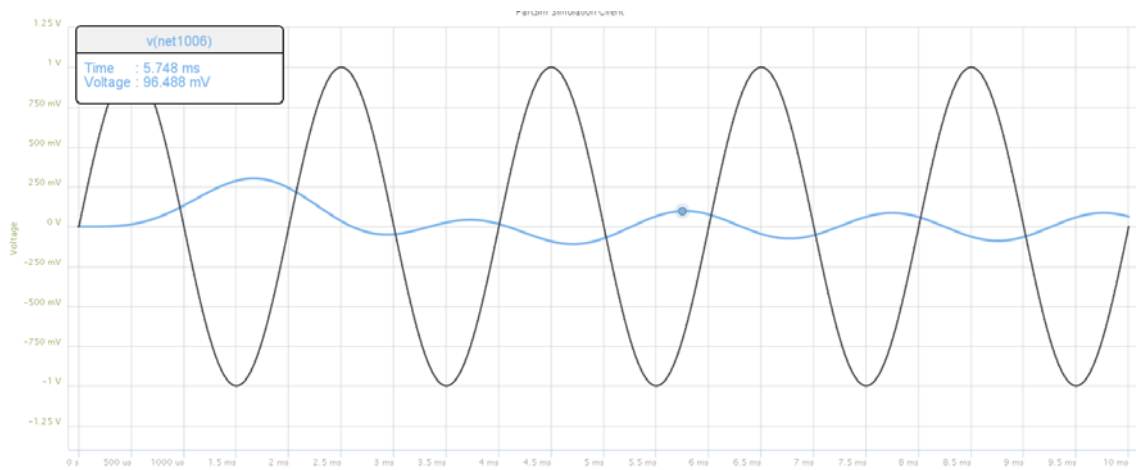


500Hz: Gain = 0.09648

	200 Hz	500 Hz
Gain (calc)	0.9815	0.0899
Gain (sim)	0.963	0.09648
Spec	$0.9 < G < 1.1$	< 0.1
Meet Spec?	yes	yes

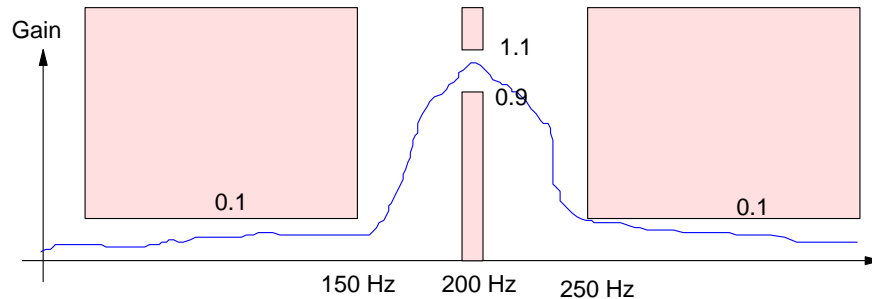2) Design a band-pass filter to meet the following requirements:

- Input: +/- 10V, capable of 20mA
- Output: +/- 10V capable of 20mA
- Relationship:
 - $1.1 < \text{Gain} < 0.9$ $f = 200 \text{ Hz}$
 - $\text{Gain} < 0.1$ $f > 250 \text{ Hz}$
 - $\text{Gain} < 0.1$ $f < 150 \text{ Hz}$



a) Give a filter, $G(s)$, which meets these requirements. Plot the gain vs. frequency for your $G(s)$ in Matlab.

- The pass frequency is 200Hz: the complex part of the pole is 200Hz (1257 rad/sec)
- Assume the band width is +/- 10Hz: the real part of the pole is 10Hz away from the resonance (62.8 rad/sec)

Pick a filter with poles at

$$G(s) = \left(\frac{ks}{(s+62.8+j1255)(s+62.8-j1255)} \right) = \left(\frac{125s}{s^2+125s+1257^2} \right)$$

Check this in Matlab:

```
-->G = tf([125,0],[1,125,1257^2])

      125s
-----
s^2 + 125s + 11580000
```

Check the gain at 150Hz, 200Hz, 250Hz:

```
-->abs(evalfr(G,j*150*2*pi))

0.1678813

-->abs(evalfr(G,j*200*2*pi))

0.9999831

-->abs(evalfr(G,j*250*2*pi))

0.2160498
```

The gain is 2.1x too large at 250Hz. To fix this, make the real part of the pole smaller (make the 's' term smaller). A little trian and error results in

$$G(s) = \left(\frac{ks}{(s+28+j1257)(s+28-j1257)} \right) = \left(\frac{56s}{s^2+56s+1257^2} \right)$$

```
-->G = tf2ss2([56,0],[1,56,1257^2]);

-->abs(evalfr(G,j*150*2*pi))

0.0760725
```

```
-->abs(evalfr(G,j*200*2*pi))
```

```
0.9999160
```

```
-->abs(evalfr(G,j*250*2*pi))
```

```
0.0986480
```

Plotting the graph:

```
-->f = [100:0.1:300]';
```

```
-->w = 2*pi*f;
```

```
-->s = j*w;
```

```
-->G = 56*s ./ (s.^2 + 56*s + 1257^2);
```

```
-->plot(f,abs(G))
```

```
-->hold on
```

```
-->plot([200,200],[0,0.9], 'r')
```


```
-->plot([100,150,150],[0.1,0.1,1], 'r');
```

```
-->plot([250,250,300],[1,0.1,0.1], 'r');
```

```
-->xlabel('Hz');
```

ull the real part of the pole in by a factor of 2.1

$$real(s) = \frac{62.5}{2.1} = 29.76$$

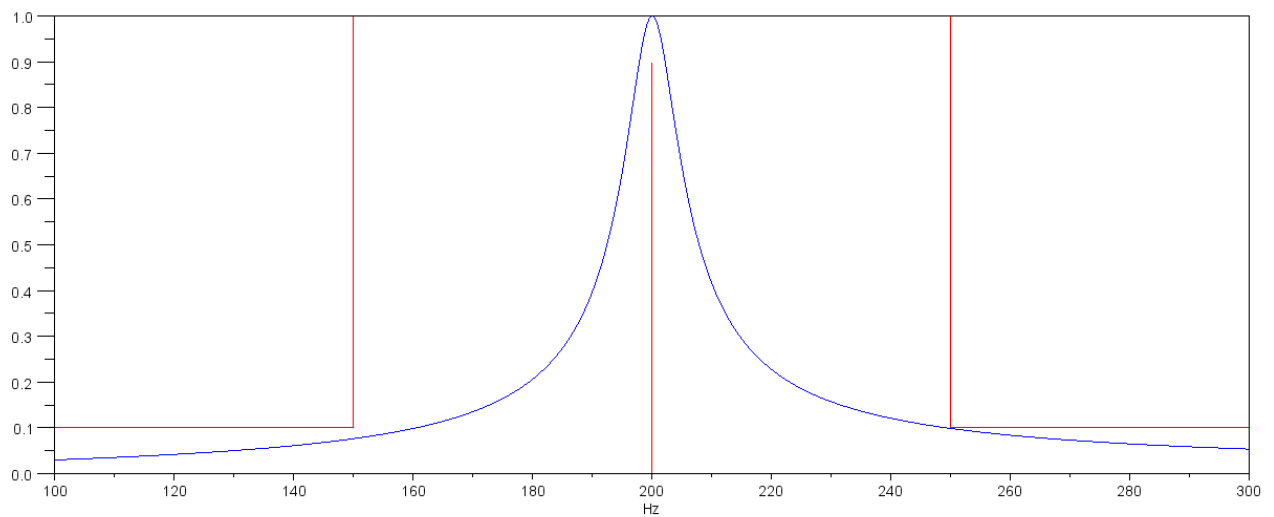

b) Design a circuit to implement this circuit

$$\left(\frac{56s}{s^2 + 56s + 1257^2} \right) = \left(\frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2}\right)\left(\frac{1}{R_3 C^2}\right)} \right)$$

Let C = 1uF


$$\left(\frac{1}{R_1 C} \right) = 56 \quad R_1 = 17.8k$$

$$\left(\frac{2}{R_3 C} \right) = 56 \quad R_3 = 35.7k$$


$$\left(\frac{R_1 + R_2}{R_1 R_2} \right) \left(\frac{1}{R_3 C^2} \right) = 1257^2 \quad R_2 = 17.74$$

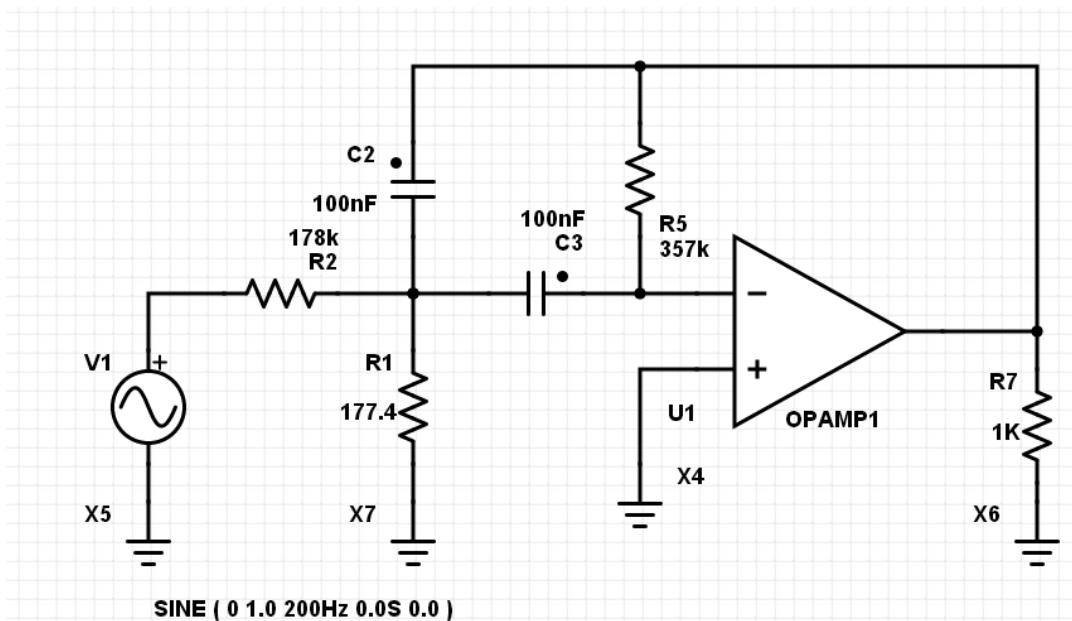17.74 Ohms is a little small, so make


- All resistors 10x larger
- All capacitors 10x smaller




c) Test your design in PartSim

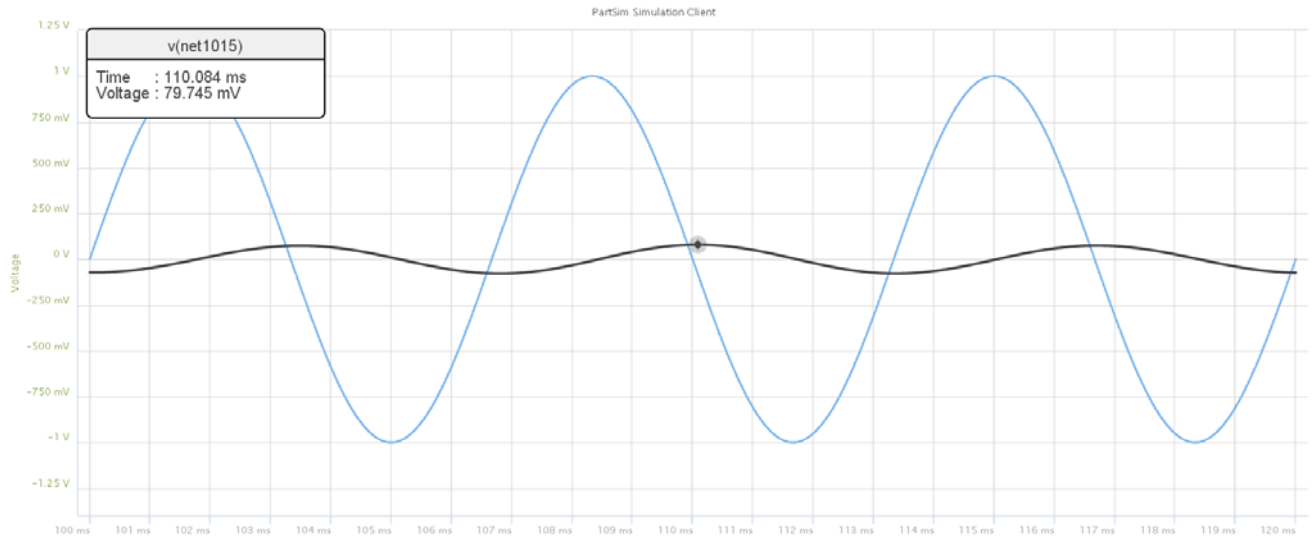

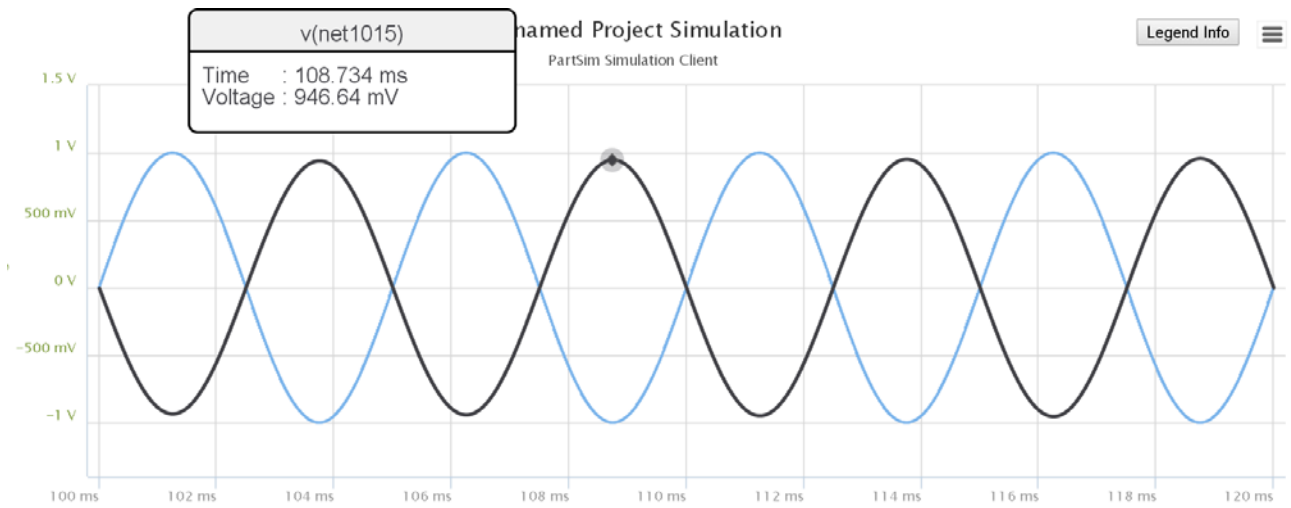150Hz: Gain = 0.0797 (0.076 computed in Matlab)



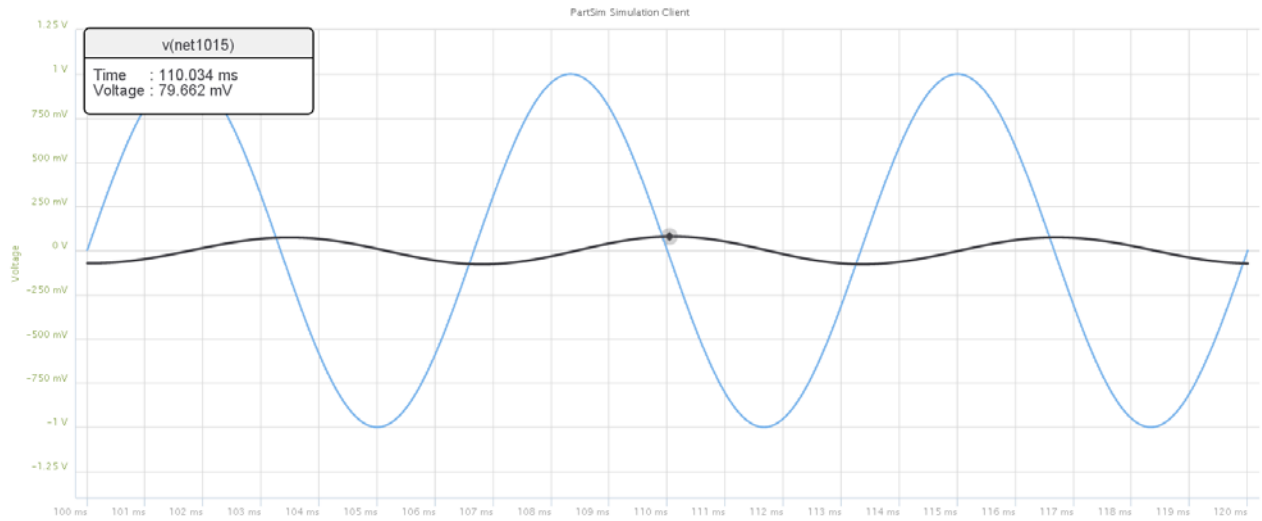200Hz: Gain = 0.9466 (1.00 computed in Matlab)



250Hz: Gain = 0.0796 (0.098 computed in Matlab)

	200 Hz	200 Hz	250 Hz
Gain (calc)	0.076	1.000	0.098
Gain (sim)	0.0797	0.9466	0.0796
Spec	< 0.1	0.9 < g < 1.1	< 0.1
Meet Spec?	yes	yes	yes

3) Build one of these circuits and check that it meets the requirements