

# ECE 321 - Homework #5

2-port models, CE, CB, CC Amplifiers. Due Monday, December 4th, 2017


- 1) Determine the Q-point for the following circuit. Assume a 3904 transistor ( $\beta = 200$ )

Redraw using the Thevenin equivalent at the base

$$R_{th} = 400k \parallel 800k = 266.7k$$

$$V_{th} = \left( \frac{400k}{400k+800k} \right) 12V = 4V$$

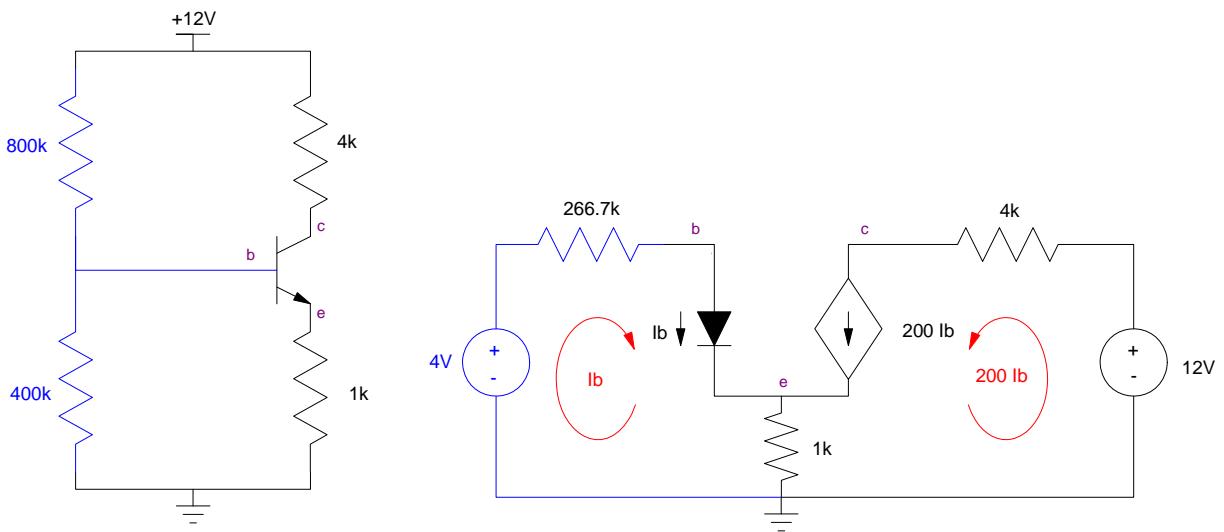Replace the transistor with its model in the active region



Write the loop equation for  $I_b$

$$-4 + 266.7kI_b + 0.7 + 1k \cdot (I_b + 200I_b) = 0$$

$$I_b = \left( \frac{4-0.7}{266.7k+201 \cdot 1k} \right) = 7.0563\mu A$$

$$I_c = \beta I_b = 1.411mA$$

Solve for the Q-point

$$V_c = 12 - 4k \cdot I_c = 6.355V$$

$$V_e = 1k \cdot (I_b + I_c) = 1.418V$$

$$V_{ce} = V_c - V_e = 4.937V$$

**The Q-Point is**

**V<sub>ce</sub> = 4.937V**

**I<sub>c</sub> = 1.411mA**

2) Modify this circuit so that

- The Q-point is  $V_{ce} = 6.0V$
- The Q-point is stabilized for variations in  $\beta$

First, redraw the circuit using the Thevenin equivalent for  $R_1$  and  $R_2$ . Next, from the specs, determine the current  $I_c$

$$V_{ce} = V_c - V_e$$

$$6V = (12 - 4000I_c) - 1000(I_b + I_c)$$

$$I_c = 200I_b$$

$$I_c = \left( \frac{12V - 6V}{4000 + 1000 \left( 1 + \frac{1}{200} \right)} \right) = 1.199mA$$

This means

$$I_b = \frac{I_c}{\beta} = 5.994\mu A$$

To stabilize the Q-point

$$R_b \ll (1 + \beta)R_e = 20, 100\Omega$$

Let  $R_b = 2k$

$$V_b = V_{th} = 2k \cdot I_b + 0.7 + 1k \cdot (I_b + I_c) = 1.917V$$

Convert back to  $R_1$  and  $R_2$


$$\left( \frac{R_1 R_2}{R_1 + R_2} \right) = 2k$$

$$\left( \frac{R_2}{R_1 + R_2} \right) 12V = 1.917V$$

Solving

$$R_1 = \left( \frac{12V}{1.917V} \right) 2k = 12.52k$$


$$R_2 = 2.38k$$

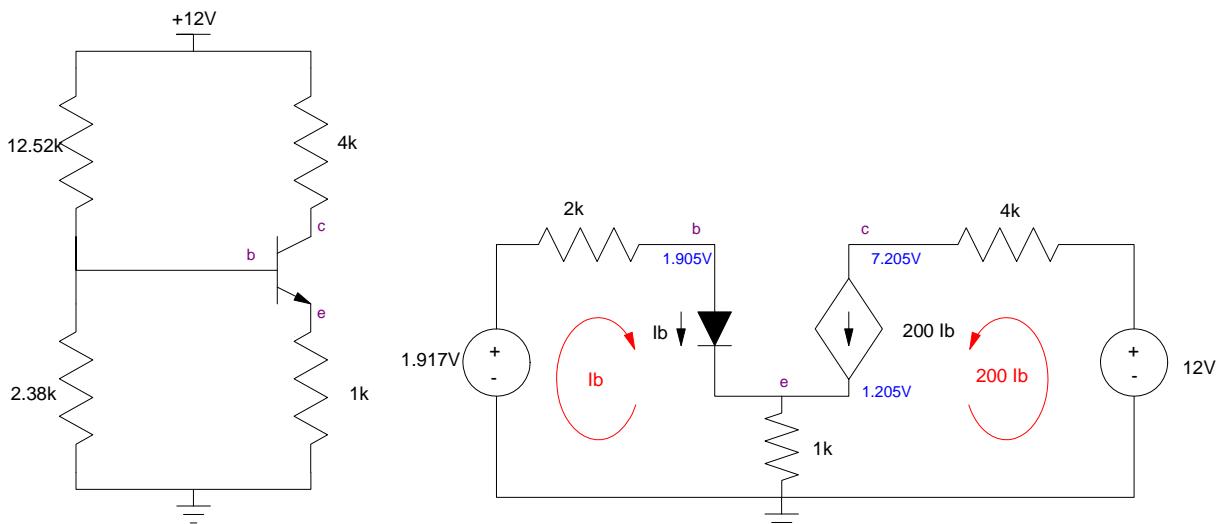

3a) Draw the small-signal model for your circuit of problem #2 when set up as a common emitter (CE) configuration

$$I_b = 5.994 \mu A$$
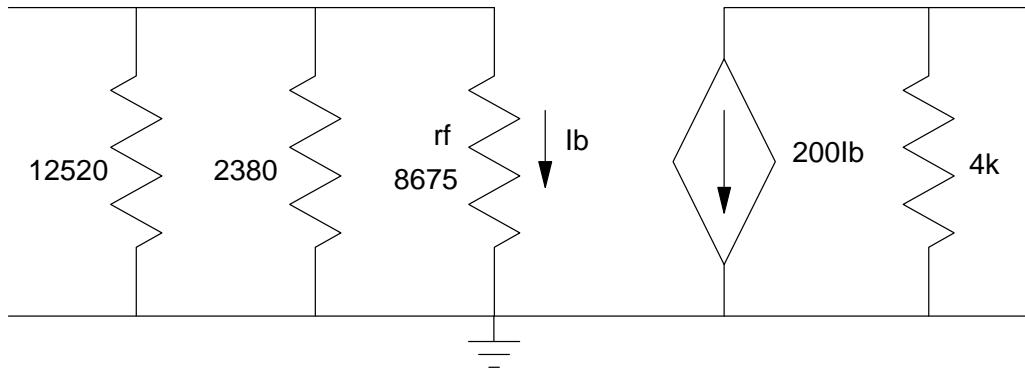
$$r_f = \frac{0.052}{I_b} = 8675 \Omega$$




3b) Determine the 2-port model for this amplifier in a CE configuration.

$$R_{in} = 12520 \parallel 2380 \parallel 8675 = 1625 \Omega$$


$$A_{in} = 0$$

$$R_{out} = 4k$$
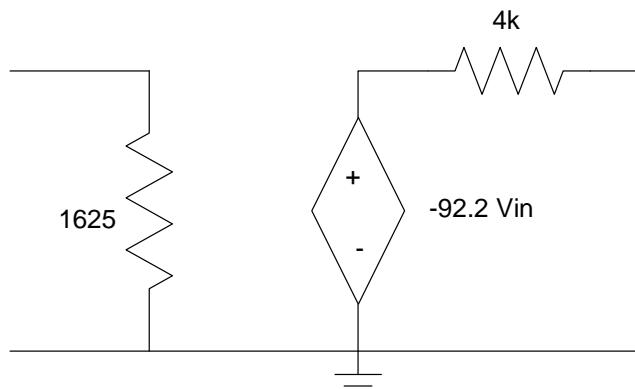
$$A_{out} = -\frac{200 \cdot 4k}{8675} = -92.2$$



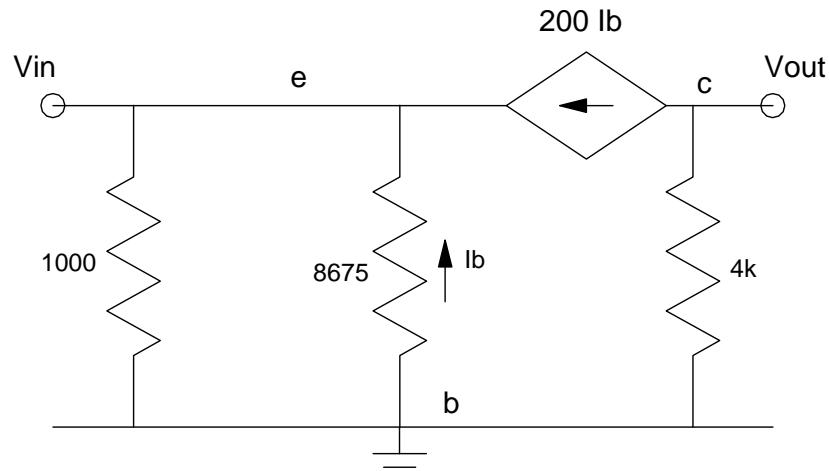4a) Draw the small-signal model for your circuit of problem #2 when set up as a common base (CB) configuration




4b) Determine the 2-port model for this amplifier in a CB configuration.

$$R_{in} = 1000 \parallel 8675 \parallel \frac{8675}{\beta} = 41.4 \Omega$$


$$A_{in} = 0$$

$$R_{out} = 4k$$
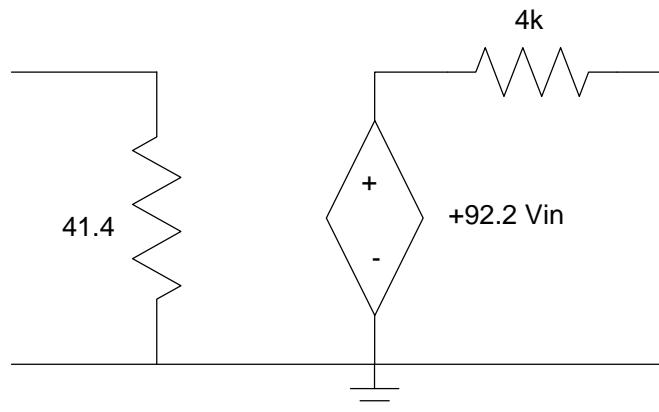
$$A_{out} = +\frac{200 \cdot 4k}{8675} = +92.2$$



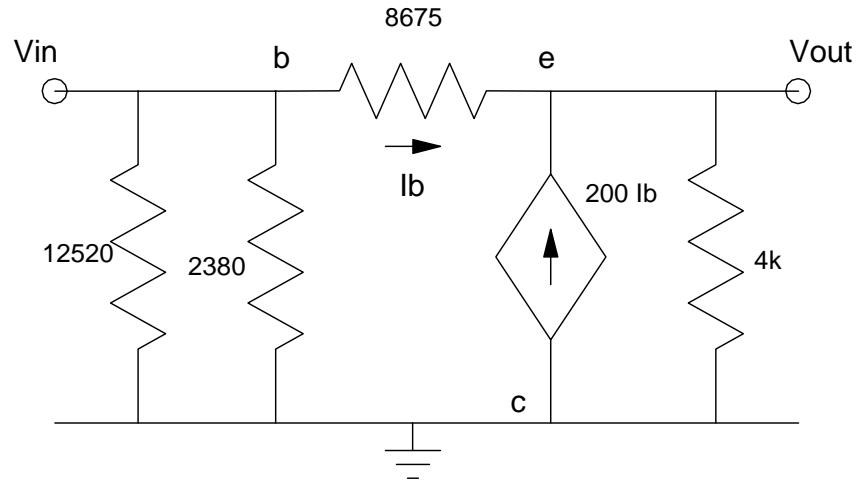5a) Draw the small-signal model for your circuit of problem #2 when set up as a common collector (CC) configuration



5b) Determine the 2-port model for this amplifier in a CC configuration.

$$R_{in} = 12520 \parallel 2380 \parallel 8675 = 1625\Omega$$


$$A_{in} = \left( \frac{12520 \parallel 2380}{12520 \parallel 2380 + 8675} \right) = 0.1873$$

$$R_{out} = 4k \parallel 8675 \parallel \frac{8675}{\beta} = 42.7\Omega$$

Aout: Apply 1V at the input, vind Vout (X)

$$\left( \frac{X-1}{8675} \right) + 200 \left( \frac{X-1}{8675} \right) + \left( \frac{X}{4000} \right) = 0$$


$$A_{out} = 0.9893$$

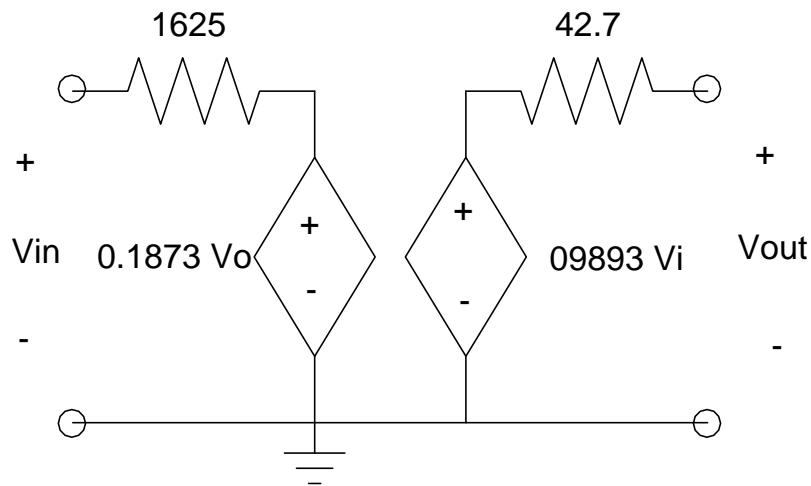

6) Determine the 2-port model for a 4-stage amplifier:

CB : CE : CE : CC

Draw the circuit using 2-port models

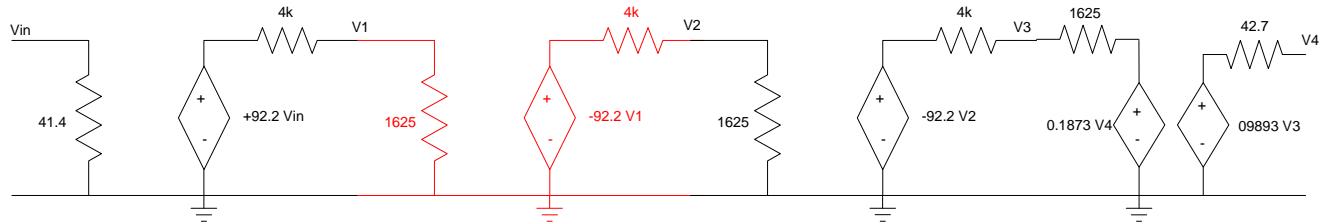


By inspection

$$R_{in} = 41.4$$

$$A_{in} = 0$$

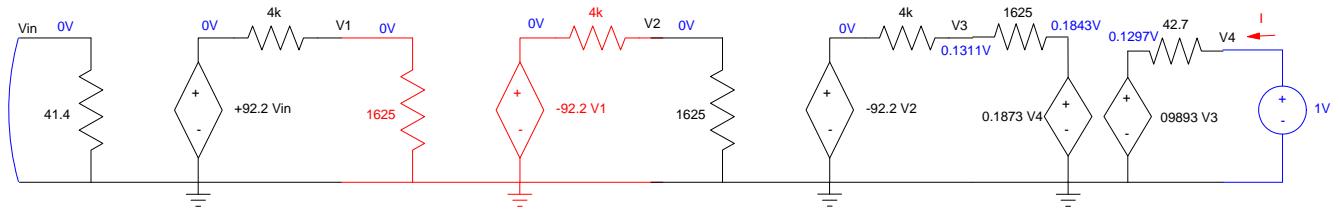Rout: Short Vin. Apply 1V to V4. Calculate the current draw



$$V_4 = 1V$$

$$0.1873 V_4 = 0.1873 V$$


$$V_3 = \left( \frac{4k}{4k+1625} \right) \cdot 0.1873 V = 0.1311 V$$

$$0.9893 V_3 = 0.1297 V$$

$$I = \left( \frac{1-0.1297 V}{42.7 \Omega} \right) = 20.38 mA$$

$$R_{out} = \frac{1V}{20.38mA} = 49.1 \Omega$$

Aout: Apply 1V at Vin. Compute V4

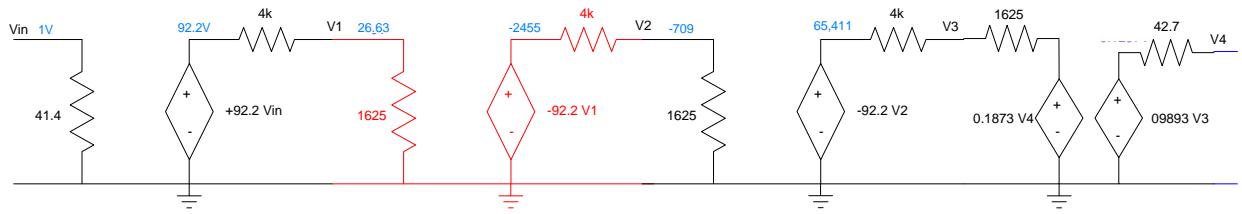

$$V_3 = \left( \frac{1625}{1625+4000} \right) 65411 + \left( \frac{4000}{4000+1625} \right) \cdot 0.1873 V_4$$

$$V_4 = 0.9893 V_3$$

Solving

$$V_3 = \left( \frac{18,896}{1-0.7111 \cdot 0.1873 \cdot 0.9893} \right) = 21,764$$

$$V_4 = 0.9893 V_3 = 21,531$$

$$A_o = 21,531$$

