

ECE 321 - Homework #1

Push-Pull Amplifiers, Op-Amp Amplifiers. Due Monday, November 5th, 2018

ECE 321 Project:


- 1) Pick a project for ECE 321 (see page 2 for suggestions)
 - Give the name of the people in your group
 - Specify the requirements for the overall project

For the following sections, assume TIP112 (NPN) and TIP117 (PNP) transistors:

- $\beta = 1000$
- $|V_{be}| = 1.4V$
- $\min(|V_{ce}|) = 0.9V$
- $\max(|I_c|) = 3A$


Push-Pull Amplifiers

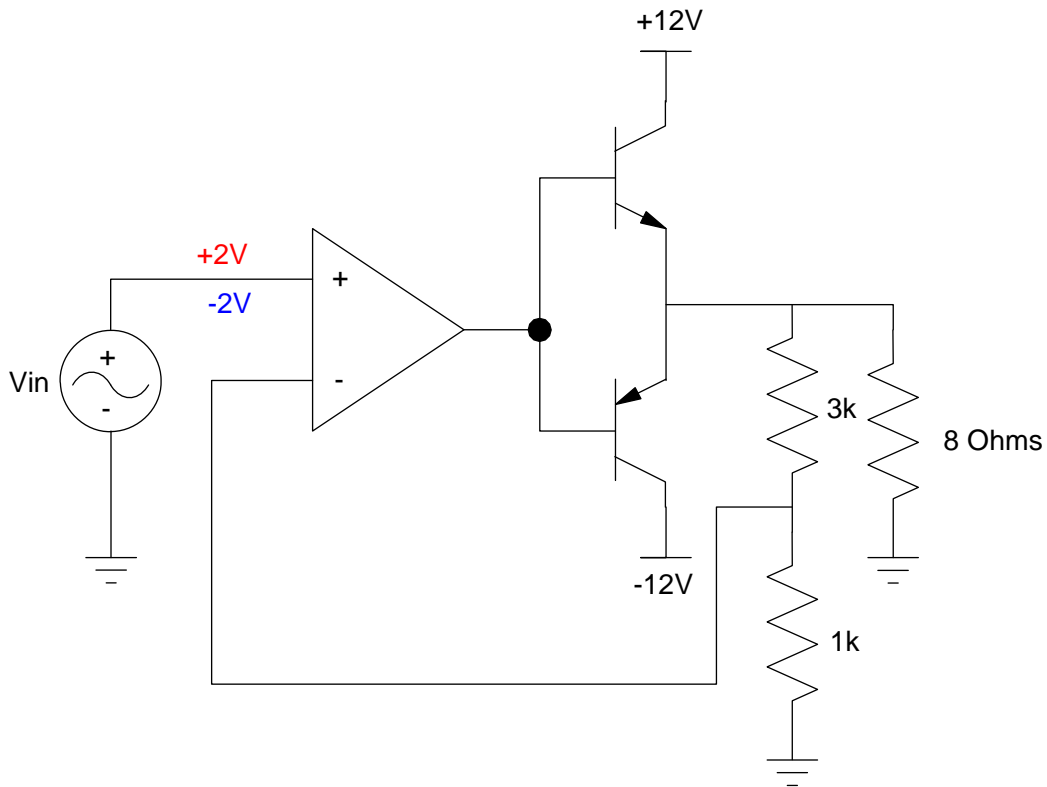- 2) Specify the voltages and currents for the following voltage amplifier for
 - $V_{in} = +2V$
 - $V_{in} = -2V$



3) Specify the voltages and currents for the following current amplifier for

- $V_{in} = +5V$

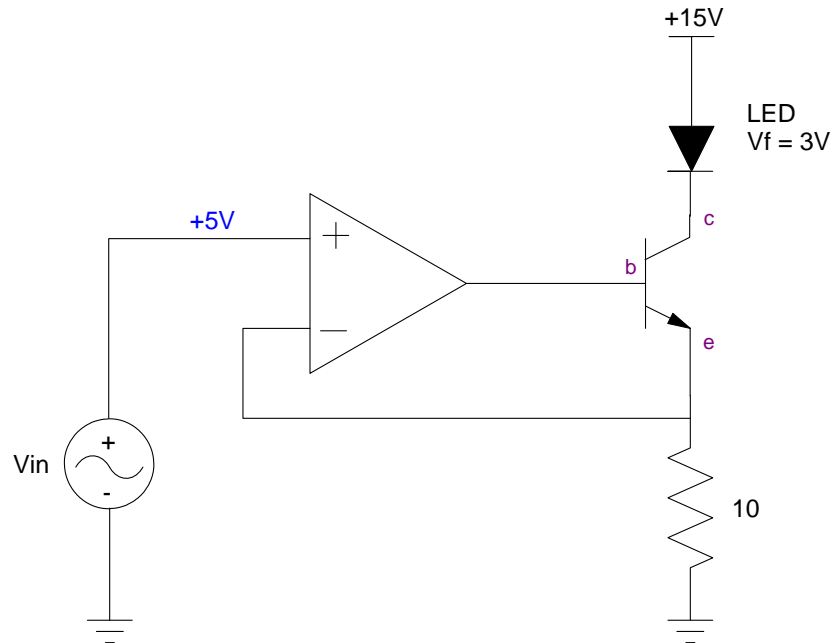

Op-Amp Amplifiers

4) Design a circuit which implements the function

$$Y = 4X$$

5) Design a circuit which implements the function


$$Y = -4X$$

6) Design a circuit which implements the function

$$Y = 4X + 6$$


Suggestions for ECE 321 Projects:

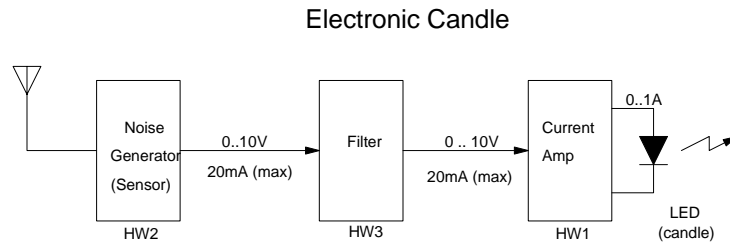a) Electronic Candle: Build a circuit which drives an LED at 0 .. 50 lumens (1A). Have the electronic candle flicker like a real candle.




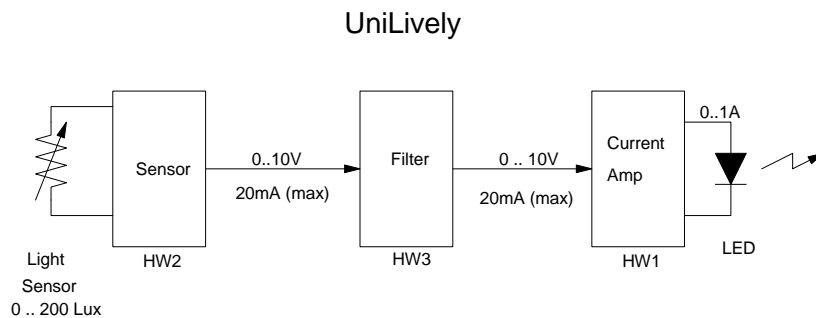b) UniLively: Build a single pixel of an OctoLively.


- If there is no filter, the LED output marches the light from the sensor.
- With the filter, the LED will bounce up and down (get brighter and dimmer) and then settle out after 4 sec



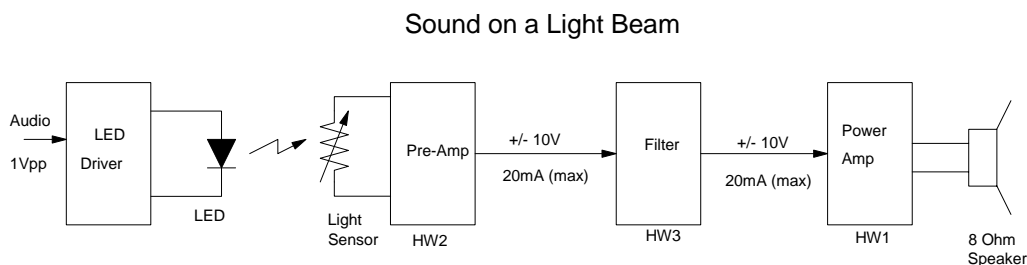c) Sound on a Light Beam: Build a circuit which transmits sound over a light beam



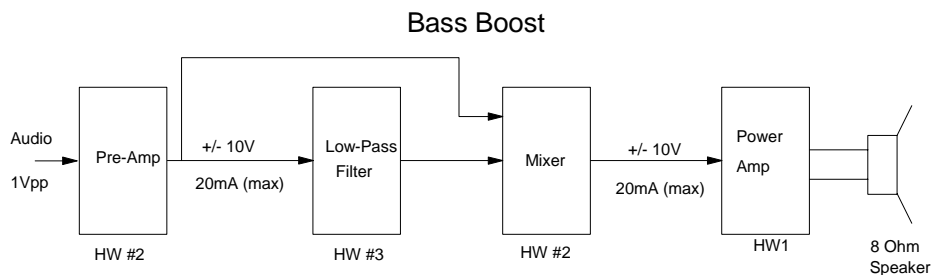d) Bass Boost: Build a circuit to amplify bass ($f < 250\text{Hz}$) and mix it with the original (or different) audio signal



e) Other: Design your own system which includes a power amp (push-pull or current), filter, and amplifier