

# ECE 321 - Homework #5


Project part (c). Due Monday, December 3rd, 2018

## Project (part c):

**Problem 1: Requirements** Specify the requirements for the filter. You can use the following or change them if you like.

Bass Boost:

- Input: +/- 5V AC signal from 0 to 1000Hz capable of driving 10mA
- Output: +/- 5V AC signal capable of driving 10mA
- Relationship:
  - Pass-band (ex:  $0.9 < \text{gain} < 1.1$  for frequencies from 0 to 300Hz)
  - Reject band (ex:  $\text{gain} < 0.1$  for frequencies above 400Hz)

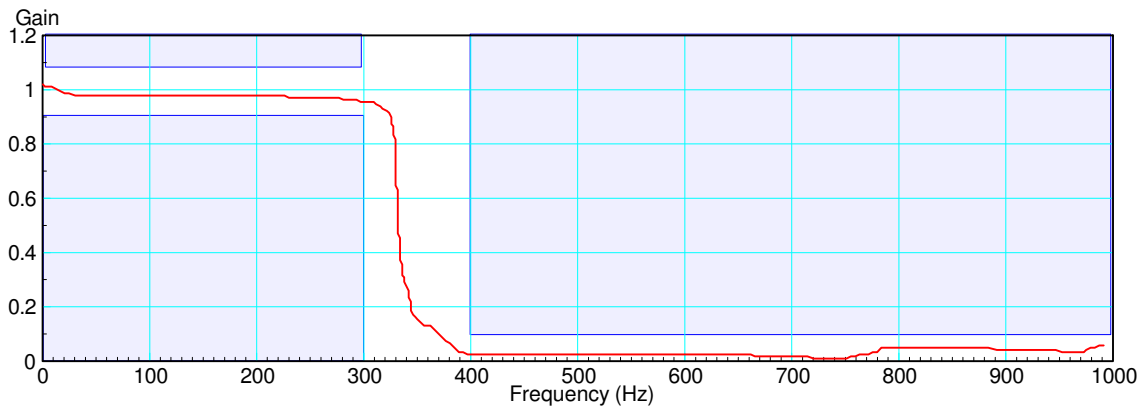

**Problem 2: Analysis:** Design filter to meet these requirements. Give

- The resulting transfer function
- A plot of the theoretical gain vs. frequency
- A circuit to implement this transfer function

**Problem 3: Simulation** Check your circuit design by simulating your circuit. Include

- The gain at the edge of the pass-band (500Hz?)
- The gain at the edge of the reject band (500Hz?)
- Compare the simulated results vs. theoretical results from problem 2

**Problem 4: Hardware** Build your circuit in lab and verify it operates correctly. Check

- The gain at the edge of the pass-band (500Hz?)
- The gain at the edge of the reject band (500Hz?)
- Compare the simulated results vs. theoretical and simulation results from problem 2 and 3

**Problem 5) Demo.** Demonstrate your filter works with part (a) and part (b) (video or in person).