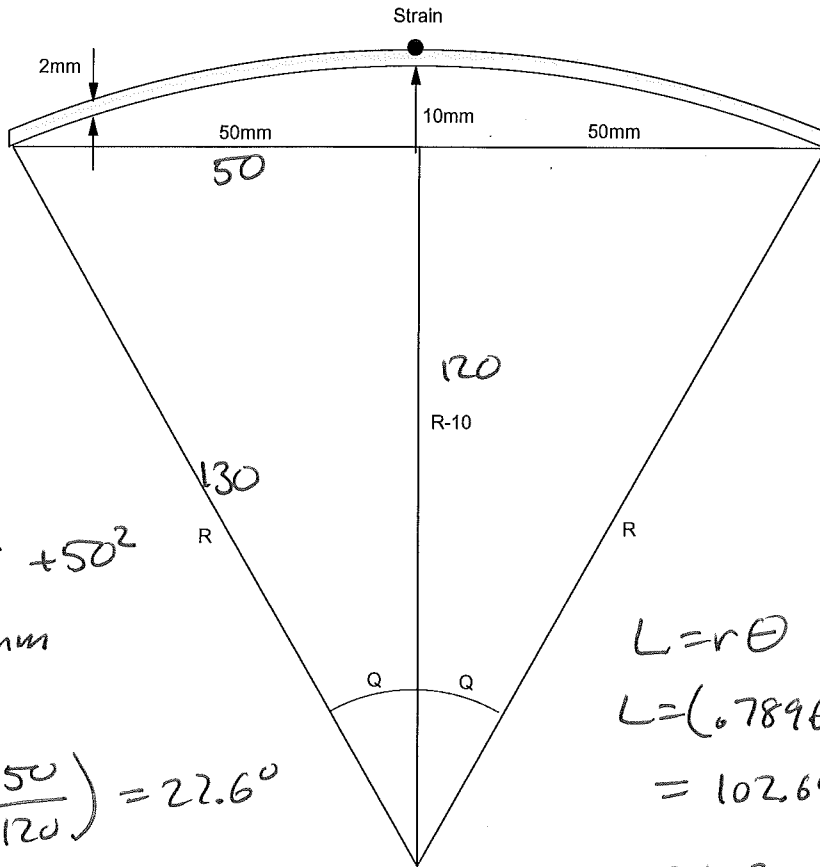


# ECE 321 - Quiz #2 - Name \_\_\_\_\_

Push-Pull Amplifiers, Op-Amp Amplifiers, November 8, 2018

1) An accelerometer uses the deflection of a beam to measure acceleration. Calculate the strain on the beam when the deflection is 10mm. Assume the beam is 100mm long and 2mm thick.

Radius R	Arc Length 2Q	Length of Deflected Beam (L)	Strain dL/L
130mm	45.23° 0.7896 rad	L = rθ 103.43mm outer 102.64mm center	+0.0077 free end +0.0343 fixed end



$$R^2 = (R-10)^2 + 50^2$$

$$R = 130\text{mm}$$

$$Q = \arctan\left(\frac{50}{120}\right) = 22.6^\circ$$

$$2Q = 45.23^\circ$$

$$L = r\theta$$

$$L = (0.7896)(130\text{mm})$$

$$= 102.64\text{mm center}$$

$$= 103.43 \text{ outer}$$

$$\epsilon = \frac{103.43 - 102.64}{102.64}$$

$$= +0.0077$$

$$= \frac{1}{130}$$

2) Assume the strain goes from 0 .. 0.03. Design a circuit which has an output of


- $Y = 10V$  for  $\epsilon = 0.03$
- $Y = 0V$  for  $\epsilon = 0$

Assume the strain sensor has a resistance of

$$R = 120 \cdot (1 + 2.14\epsilon) \Omega$$

$$= 127.70 \Omega \quad (\epsilon = 0.03)$$

$$= 120 \Omega \quad (\epsilon = 0)$$

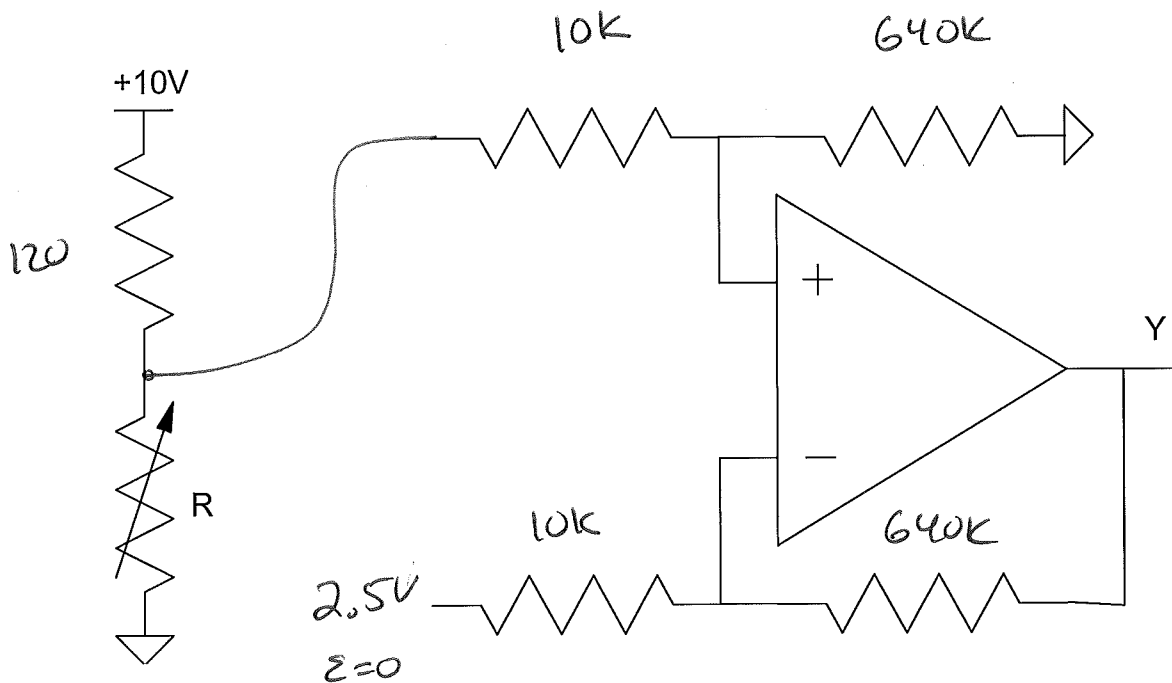


$$V(127.7) = 2.5778V$$

$$\text{gain} = \frac{10}{2.5778 - 2.5} = 64$$

3) Linearizing Circuit: The following circuit is intended to linearize the resistance between 0C and +40C. Determine the net impedance at 0C, 20C, and 40C as well as the "error" in this linearizing circuit

$$R = 1000 \cdot \exp\left(\frac{3905}{K} - \frac{3905}{298}\right)$$

Z(0C) (273K) (R = 3320 Ohms)	Z(20C) (293K) (R = 1250 Ohms)	Z(40C) (313K) (R = 534 Ohms)	Sum Squared Error $E = \left(Z_{20C} - \frac{Z_{0C} + Z_{40C}}{2}\right)^2$
440.75	383.72	325.66	.2607

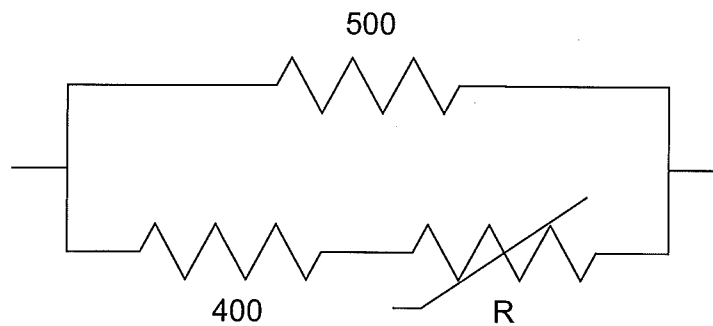


$$Z = \left( \frac{1}{R + 400} + \frac{1}{500} \right)^{-1}$$

4) Assume an RTD has a resistance vs. temperature relationship of

$$R = 1000 \cdot (1 + 0.0043T) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

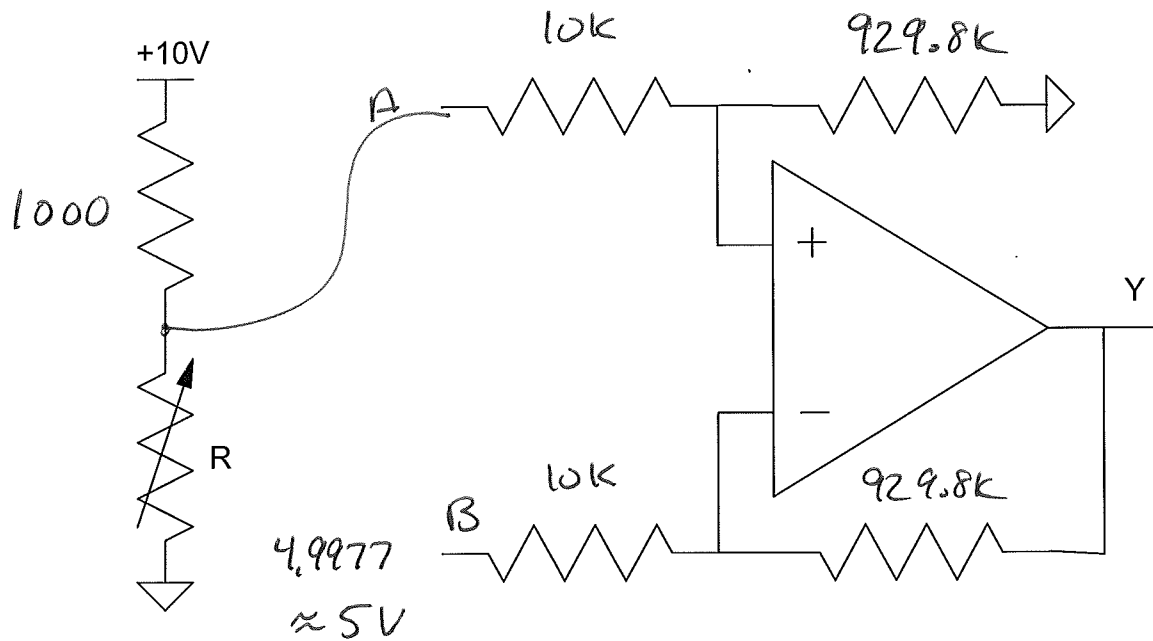- Y = -10V at T = -10C and
- Y = +10V at T = +10C



$$\begin{aligned} \frac{-10^\circ}{R=957} \\ V=4.89 \end{aligned}$$

$$\begin{aligned} \frac{+10^\circ}{R=1043} \\ V=5.1052 \end{aligned}$$

$$\text{gain} = \frac{20V}{5.1052 - 4.89} = 92.98$$

$$y = 92.98(A - B)$$


$$10 = 92.98(5.1052 - B)$$

$$B = 5V$$

5) For the following amplifier, determine the gains {a, b, c}

$$Y = aA + bB + cC$$

a	b	c
-10	+10	+1

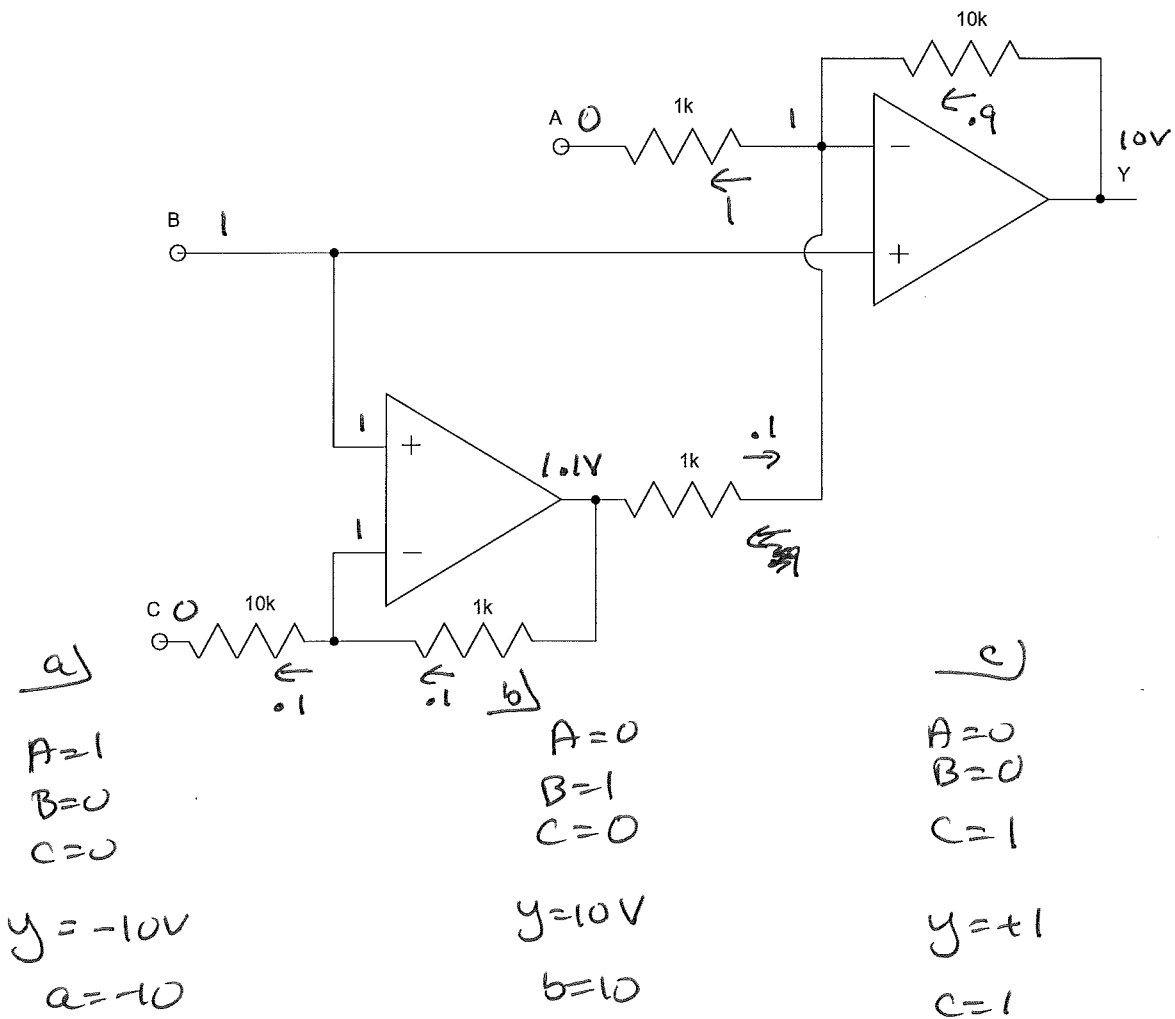

Industrial Help Bonus! Hemp-based plastics take 3-6 months to decompose. How long do petroleum-based plastics to decompose?

≈ 450 years (plastic bottle)

1000+ years plastic bags