

# ECE 321 - Homework #4

Filters. Project part (b). Due Monday, November 26th, 2018

## Filters:

**Problem 1)** Assume  $x(t)$  and  $y(t)$  are related by the following transfer function:

$$Y = \left( \frac{10}{(s+2)(s+3)} \right) X$$

Find  $y(t)$  assuming

$$x(t) = 2 + 3 \cos(4t)$$

Use superposition

$$x(t) = 2$$

$$s = 0$$

$$\left( \frac{10}{(s+2)(s+3)} \right)_{s=0} = 1.6667$$

$$Y = \left( \frac{10}{(s+2)(s+3)} \right) X$$

$$Y = (1.6667)(2)$$

$$Y = 3.3333$$

$$y(t) = 3.3333$$

$$x(t) = 3 \cos(4t) \quad X = 3 + j0 \text{ (phasor form)}$$

$$s = j4$$

$$\left( \frac{10}{(s+2)(s+3)} \right)_{s=j4} = 0.4472 \angle -116^\circ$$

$$Y = \left( \frac{10}{(s+2)(s+3)} \right) X$$

$$Y = (0.4472 \angle -116^\circ)(3 + j0)$$

$$Y = 1.3416 \angle -116^\circ$$

$$y(t) = 1.3416 \cos(4t - 116^\circ)$$

The total answer is the DC term and the AC term

$$y(t) = 3.3333 + 1.3416 \cos(4t - 116^\circ)$$


**Problem 2)** Assume  $x(t)$  and  $y(t)$  are related by the following transfer function:

$$Y = \left( \frac{5s+2}{s^2+5s+300} \right) X$$

2a) Plot the gain from X to Y vs. frequency from 0 rad/sec to 30 rad/sec.

```
w = [0:0.01:30]';
s = j*w;
G = (5*s+2) ./ (s.^2 + 5*s + 300);
```
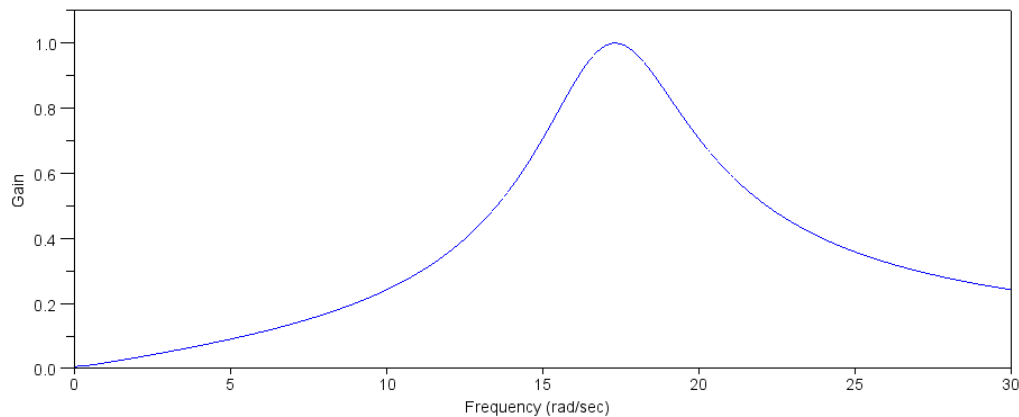
```
plot(w, abs(G))
xlabel('Frequency (rad/sec)');
ylabel('Gain');
```



2b) Find the frequency,  $w$ , which results in the gain being a maximum (resonance):

$$x(t) = 2 \cos(\omega t)$$

Find  $y(t)$  for this  $x(t)$ .

The maximum is at  $w = 17.32 \left( \sqrt{300} \right)$

$$\left( \frac{5s+2}{s^2+5s+300} \right)_{s=j17.32} = 1.0003 \angle -1.3^\circ$$

$$Y = (1.0003 \angle -1.3^\circ) \cdot 2 \cos(17.32t)$$

$$y(t) = 2.0005 \cos(17.32t - 1.3^\circ)$$

## Project (part b):

### Amplifier and Mixer

#### Problem 3) Requirements

Input: Two cell phones.

- A: 1Vpp analog signal, capable of driving 10mA
- B: 1Vpp analog signal, capable of driving 10mA

Output

- Y: -10V to +10V analog signal, capable of driving 10mA


Relationship

$$Y = 10(\alpha A + (1 - \alpha)B)$$

#### Problem 4) Analysis

1V at 10mA = 100 Ohms. The impedance at the input must be at least 100 Ohms. Use a 10k potentiometer


To model the 10mA @ 10V load, use a 1k resistor at the load

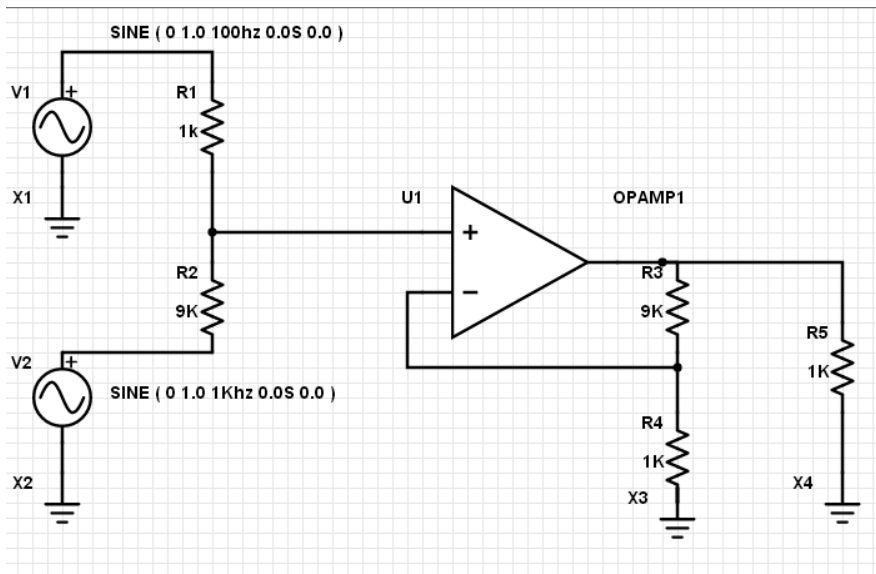

**Problem 5)** Simulate your circuit to verify it operates correctly. Check the voltages at

- At the endpoints
- One or two points in between

to see if they match your computations.

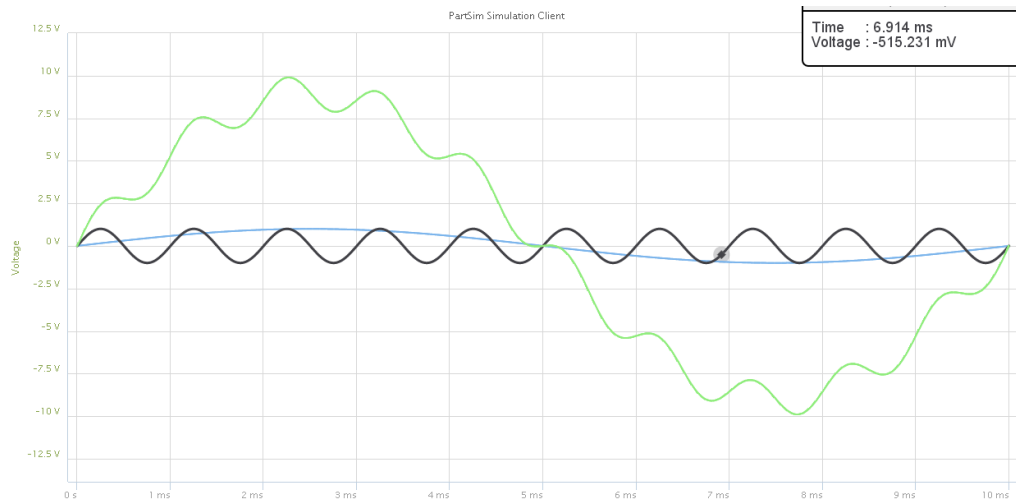

The output is

- 90% of a 10Vp 100Hz sine wave (10x the input), mixed with
- 10% of a 10Vp 1kHz sine wave (10x the input)

The result has a peak of 10V and a 1kHz component which is 1Vpp

**Problem 6)** Build your circuit in lab and verify it operates correctly. Check the voltages at

- At the endpoints
- One or two points in between

to see if they match your computations and simulation results.

**Problem 7) Demo.** Demonstrate your amplifier with the power amp from homework #1 (video or in person).