


ECE 321 - Final - Name _____

Fall 2019

1) Push-Pull: Determine the voltages and currents for the following push-pull amplifier. Assume TIP transistors

- $|V_{be}| = 1.4V$
- $\beta = 1000$


V1	V2	V3	Ib	Ic

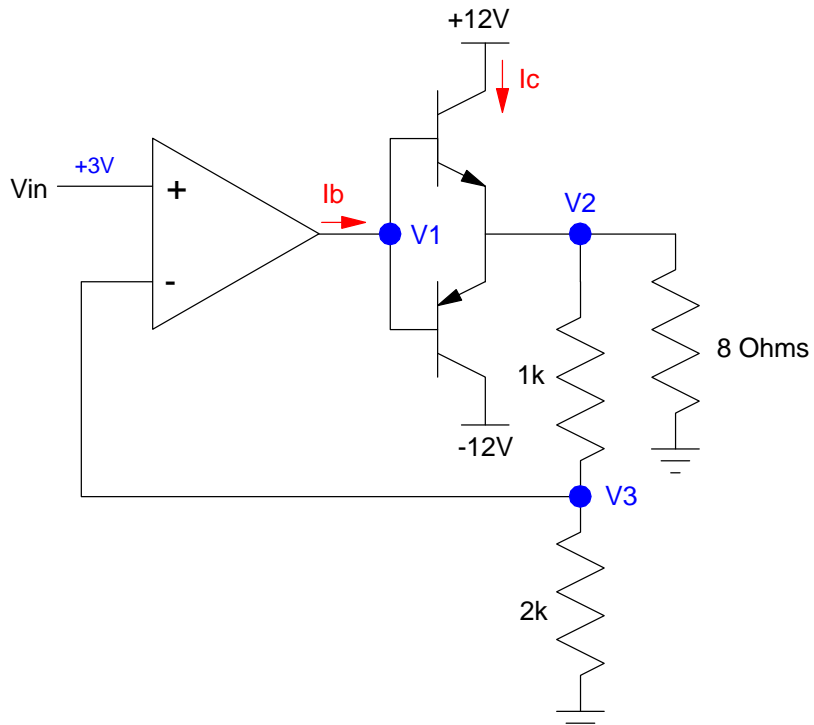

2) Determine the voltages, current, and power dissipated by the transistor for the following push-pull amplifier. Assume TIP transistors



- $|V_{be}| = 1.4V$
- $\beta = 1000$

V1	I2	V3	I4	Power dissipated by the transistor

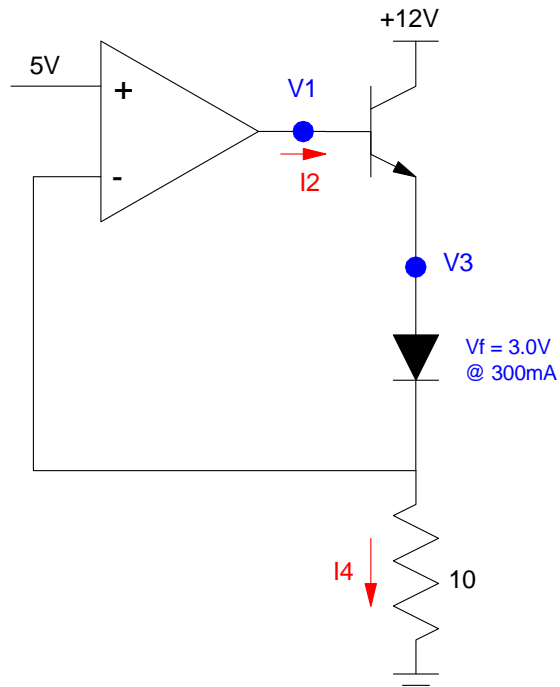

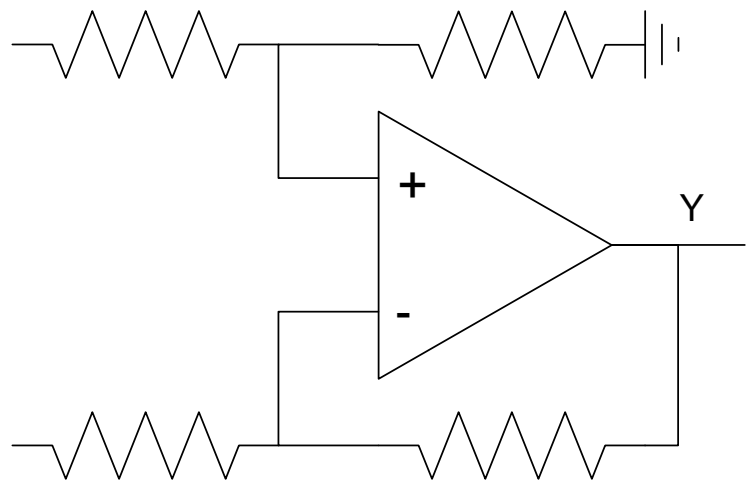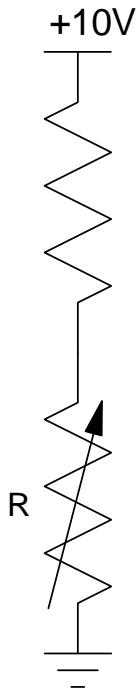
3) Design an instrumentation amplifier so that

- $Y = -10V$ when $R = 2k$
- $Y = +10V$ when $R = 3k$



4) Determine the voltages for the following amplifier. Assume ideal op-amps.

V1	V2	V3	V4

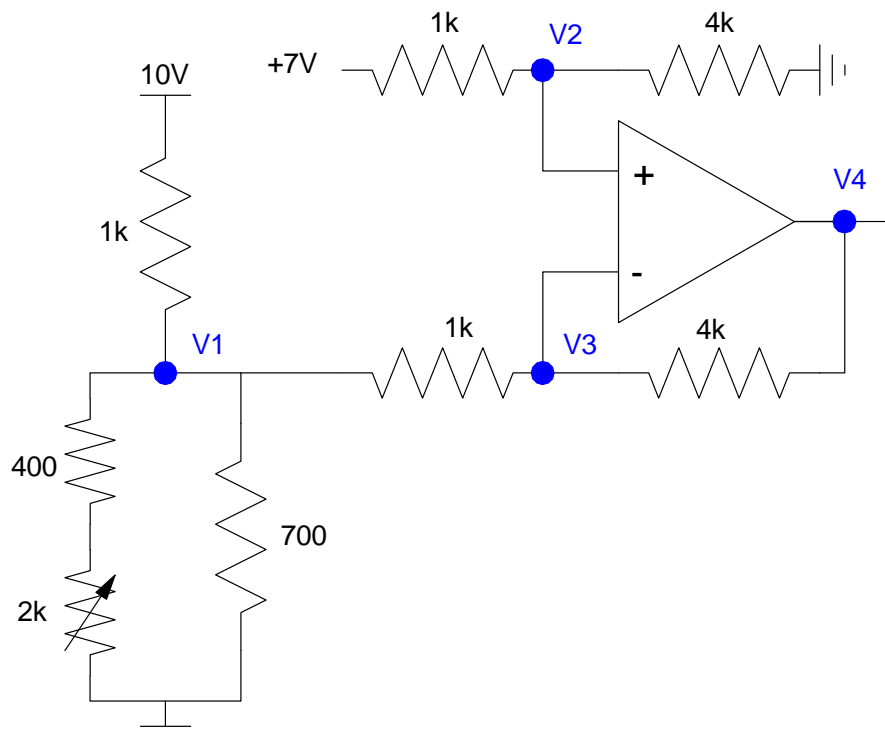

5) Filter Analysis: Assume X and Y are related by the following transfer function

$$Y = \left(\frac{200}{(s+3)(s+6)(s+12)} \right) X = \left(\frac{200}{s^3 + 21s^2 + 126s + 216} \right) X$$

What is the differential equation relating X and Y?

Determine y(t) assuming

$$x(t) = 5 + 6 \cos(10t) + 7 \sin(10t)$$

6) Design a filter to meet the following specs (approximately):

- $0.9 < \text{gain} < 1.1$ for frequencies below 400 rad/sec
- $0.1 < \text{gain}$ for frequencies above 700 rad/sec



Determine the number of poles required and give the transfer function for a Butterworth filter which meets these specs (they may require some fine tuning in Matlab). The poles for a Butterworth filter with a corner at 1 rad/sec are:

	N=2	N=3	N=4	N=5	N=6
zeros	none	none	none	none	none
poles	$-1 \angle \pm 45^\circ$	-1 $-1 \angle \pm 60^\circ$	$-1 \angle \pm 22.5^\circ$ $-1 \angle \pm 67.5^\circ$	-1 $-1 \angle \pm 36^\circ$ $-1 \angle \pm 72^\circ$	$-1 \angle \pm 15^\circ$ $-1 \angle \pm 45^\circ$ $-1 \angle \pm 75^\circ$

7) CE Amplifier: Determine the operating point for the following transistor circuit. Assume LM833 transistors:



- $\beta = 200$
- $|V_{be}| = 0.7V$

Vce	Ic	Vb	Rb

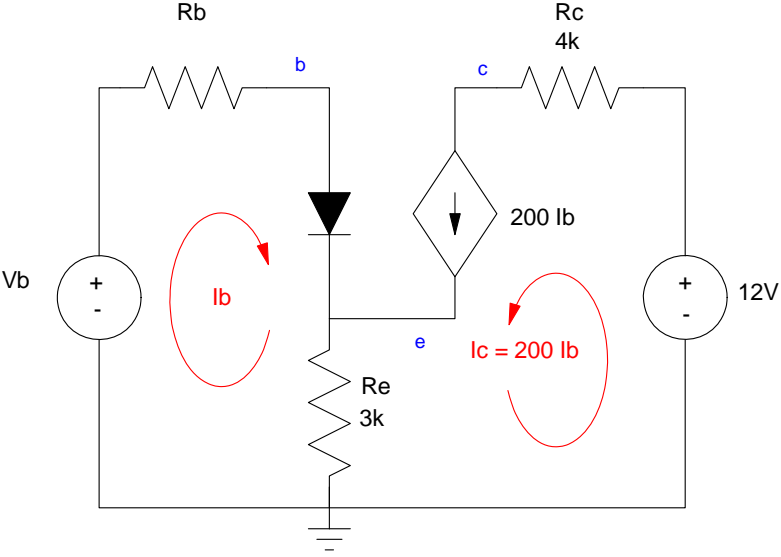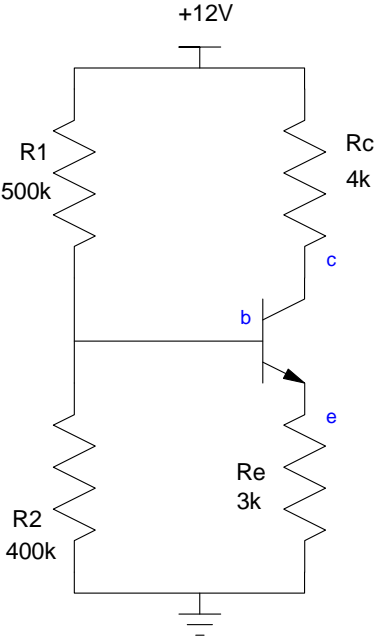

8) Determine the 2-port model for the following amplifier

R_{in}	A_i	R_{out}	A_o

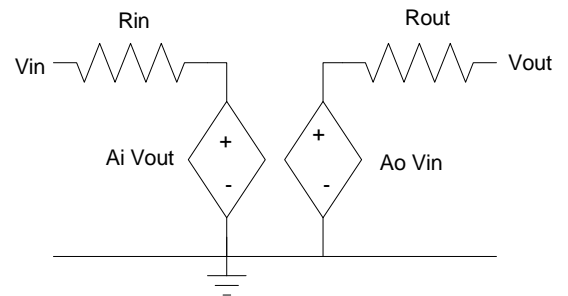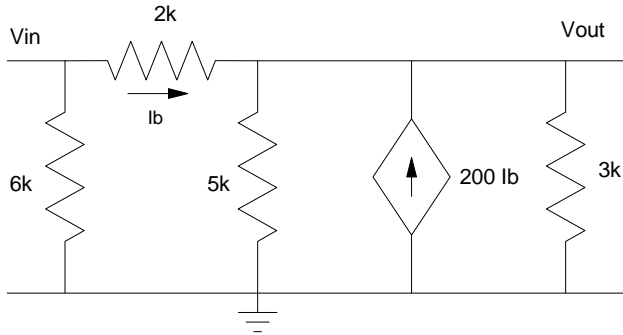

Bonus! What is the purpose of the Age-Inator?

- Make kids grow up faster to get rid of that annoying day care that was put up next door
- Turn puppies into dogs because Dr. Doofenschmirtz hates puppies.
- Turn Dr. Doofenschmirtz's younger brother's hair white for calling Dr. Doofenschmirtz "old man"
- Make cheese age faster because Dr. Doofenschmirtz is hungry now.