
ECE 321 - Quiz #2 - Name

Strain Gages, Audio Sensors, Calibration. Fall 2019

1) A beam that is 150mm long deflects 5mm when a force is applied in the middle. Determine the radius of curvature and the strain on the inside and outside edge. Assume the center line has zero strain.

Radius, R	Strain on inside edge	Strain at center line	Strain on outside edge
565.01	-0.0018	0.0000	+0.0018

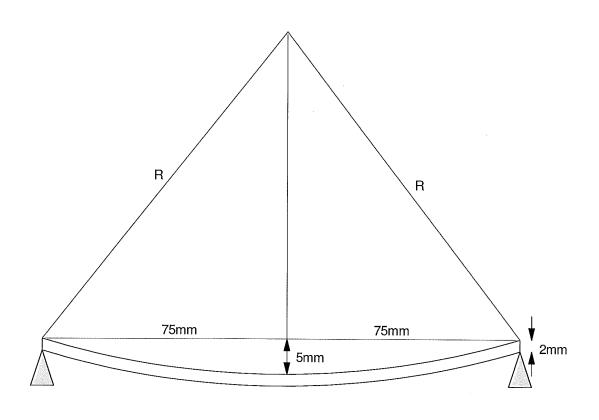

$$\mathbb{R}^{2} = (5R-5)^{2} + 75^{2}$$

$$\mathbb{R} = 565.01$$

$$\mathbb{E}_{\text{MW}} = \frac{1}{565} = 0.0018$$


$$\mathbb{E}_{\text{OR}} = \frac{1}{565} = 0.0018$$

2) A strain sensor has a strain - resistance relationship of

$$R = 120(1 + 2.14\epsilon) \Omega$$

Design a circuit which outputs

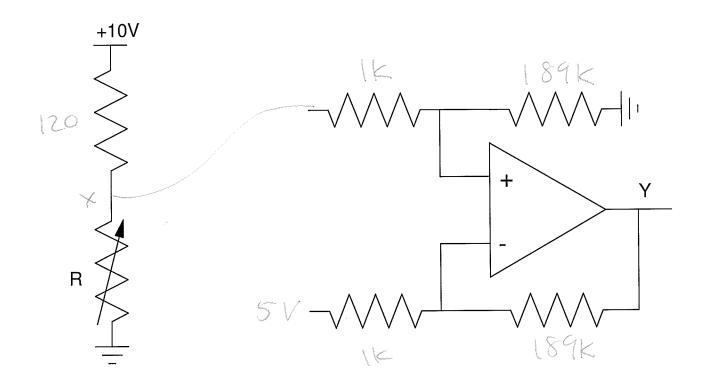- 0V when the strain is 0.000
- +10V when the strain is +0.01



$$E = 0.01$$

$$R = 128.568$$

$$V_{X} = \left(\frac{122.568}{122.568}\right) 10$$

$$= 5.0529$$

$$999 = \frac{10-0}{5.0529-5}$$


$$= 188.9$$

3) The voltage at a microphone is

$$Vx = 2.00 + 0.1 \sin(wt)$$


Design a circuit so that the output is

$$Vy = 0.00 + 10.0 \sin(wt)$$

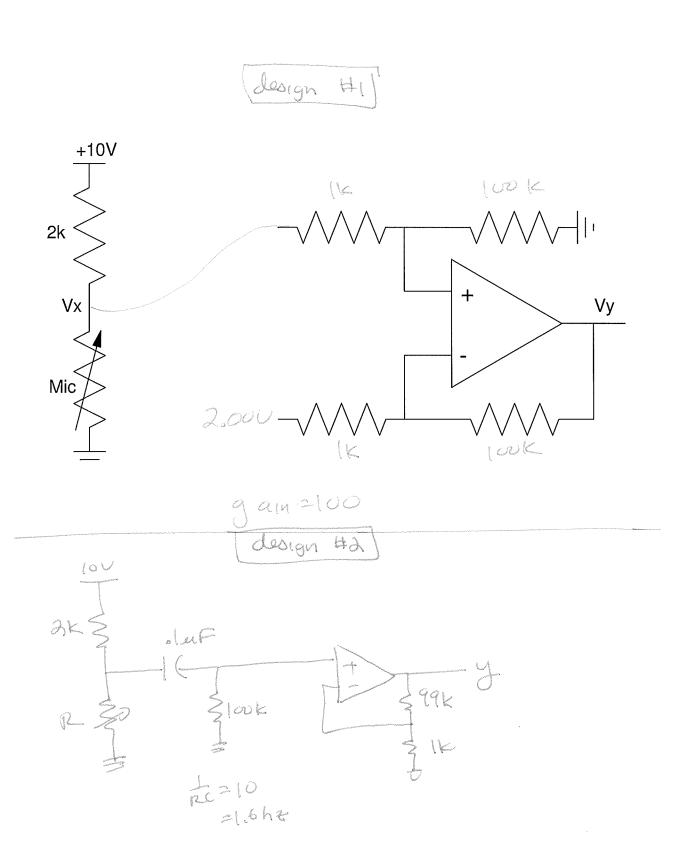

4) Determine the voltages V1..V5 for the following op-amp circuit. Assume ideal op-amps.

V1	V2	V3	V4	V5
2.0V	8.0V	_40.0V	06894 6.85V	288V
44 -54		<i>う</i>	6(V2-V3)	

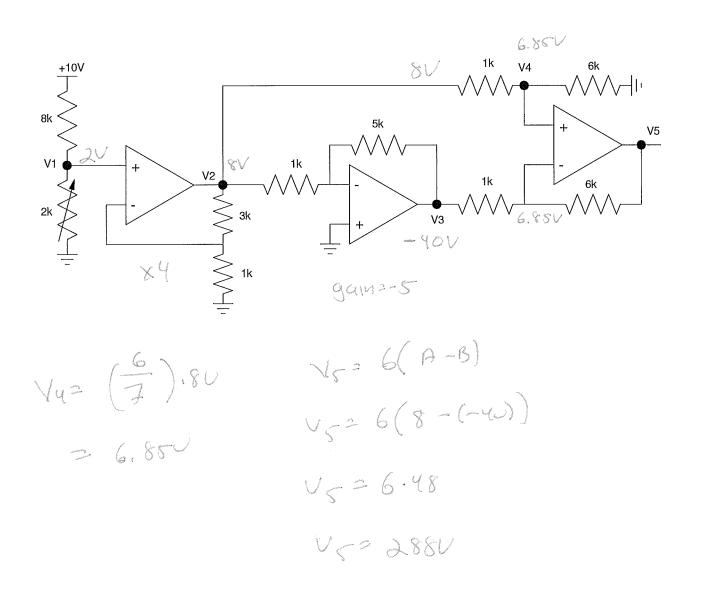


5) The voltage across a votlage divider is shown below. Determine a calibration function

$$R = aV + b$$

to approximate this curve for 0 < R < 1000 Ohms

Straight-Line Approximation	Linear Curve Fit R = aV + b	
show on plot	R ≈ 330V - 13Z	

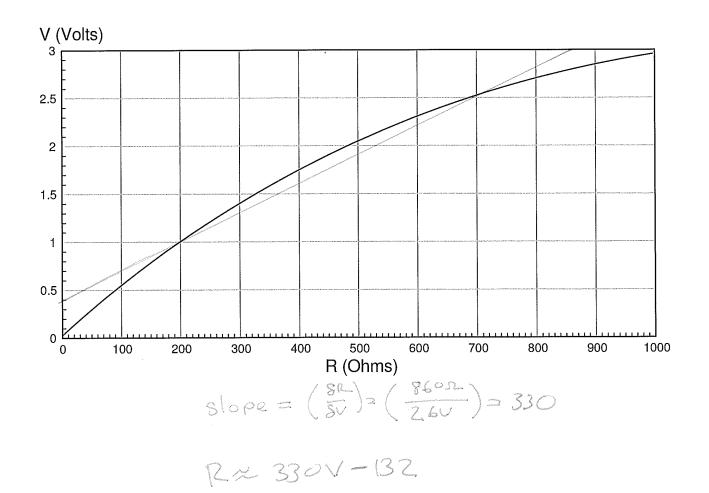

Phinneas and Ferb Bonus! What was the purpose of the Go-Away-Inator?

- Make door-to-door salesmen go away
- · Make Dr. Doofenschmirtz invisable to avoid having to take his girlfriend shopping
- · Make the green beans on his plate dissapear so Dr. Doofenschmirtz can get to dessert faster
- Keep those pesky neighbor kids off of Dr. Doofenschmirtz's front lawn