



# ECE 321 - Quiz #4 - Name \_\_\_\_\_

Transistor Amplifiers. Fall 2019

1) Determine the Thevenin equivalent of R1, R2, +12V and the Q-point. Assume

- $V_{be} = 0.7V$
- $\beta = 200$

$V_{th}$ ( $V_b$ )	$R_{th}$ ( $R_b$ )	$V_{ce}$	$I_c$

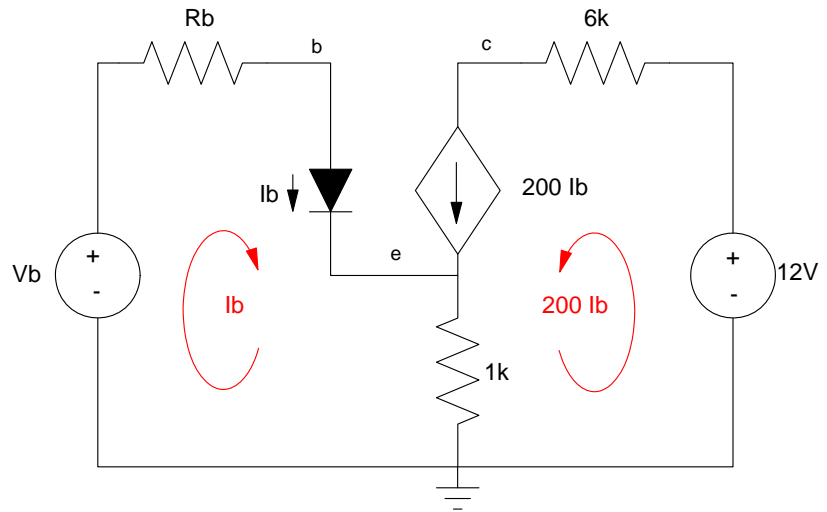
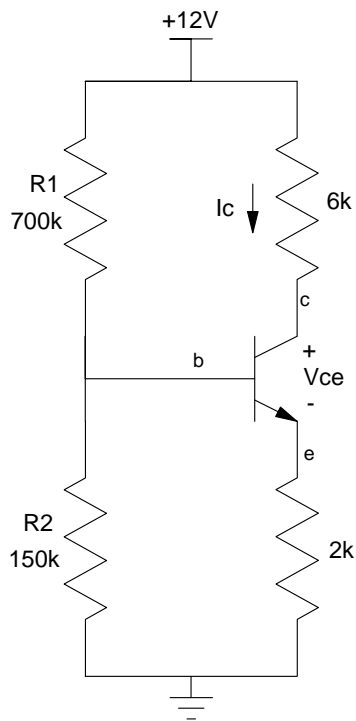


2) Determine R1 and R2 so that

- The Q-point is stabilized for variations in  $\beta$  ( i.e.  $(1 + \beta)R_e \gg R_b$  )
- The Q-point is  $V_{ce} = 4.0V$


Assume  $V_{be} = 0.7V$  and  $\beta=200$

Vth (Vb)	Rth (Rb)	Vce	Ic

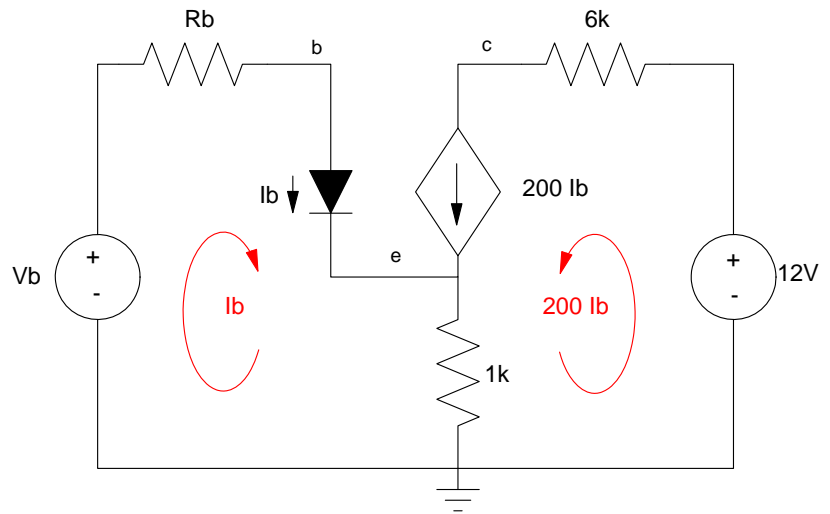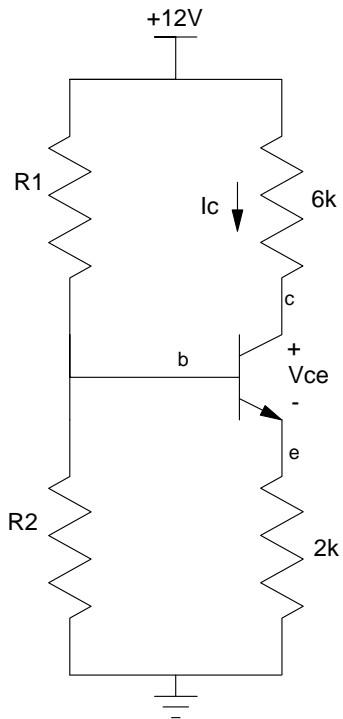

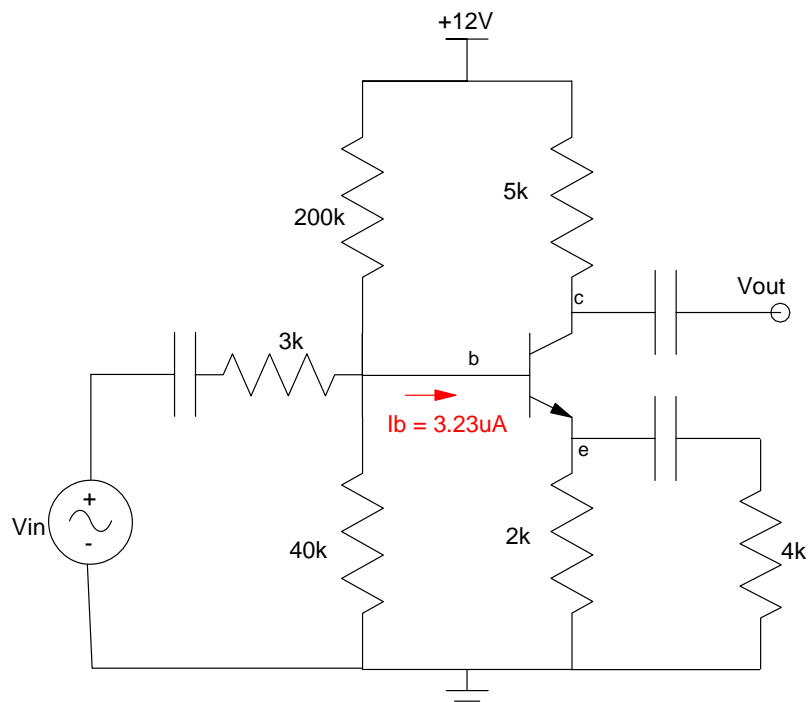
3) Small Signal Model. Draw the small signal model for the following amplifier. Assume

- $\beta = 200$
- $r_f = 16k\Omega$  ( $I_b = 3.23 \mu A$ )





4) Determine the 2-port model for the following circuit

Rin	Ai	Rout	Ao

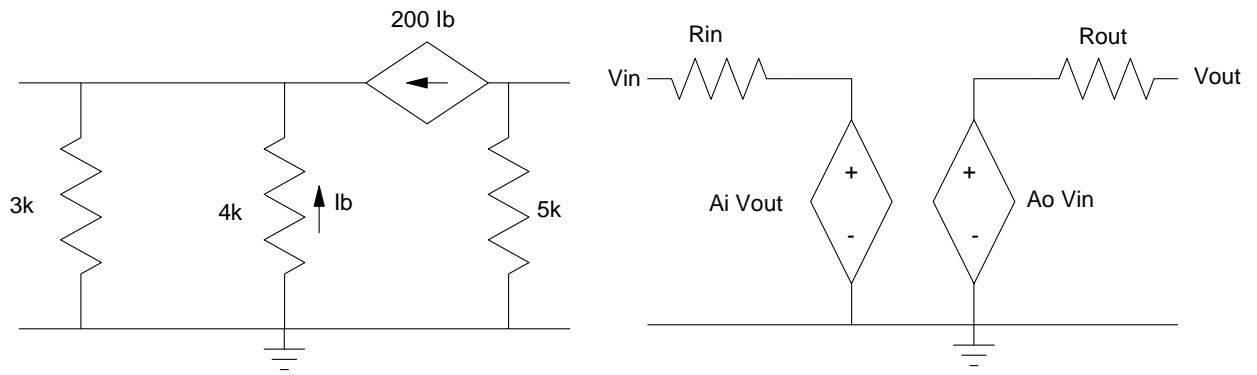

5) Determine the 2-port model for the following circuit

$R_{in}$	$A_i$	$R_{out}$	$A_o$

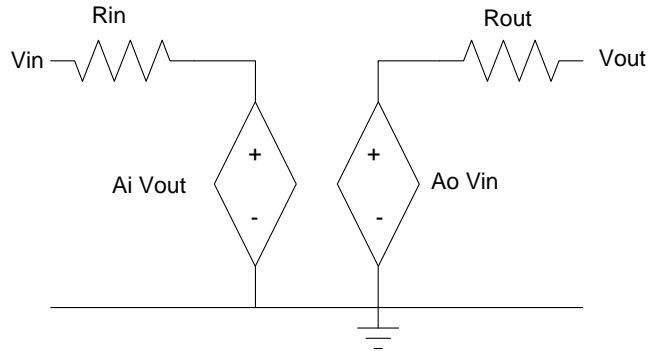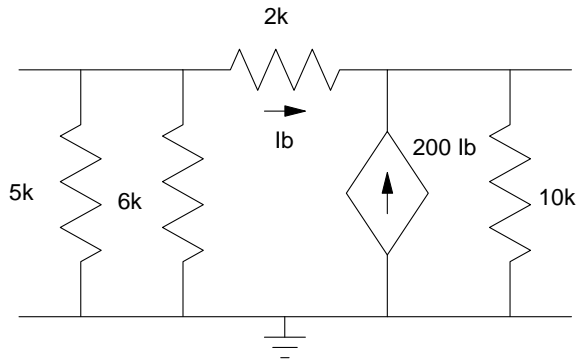

Bonus!!! What was the purpose of the Reconstitute-Inator?

- Turn dinosaur bones back into dinosaurs because Dr. Doofenschmirtz always wanted a pet T-rex
- Restore the dried out courage that Dr. Doofenschmirtz's girlfriend gave him back in high-school
- Turn raisins back into grapes.
- Turn orange-juice back into orange trees to fill Dr. Doofenschmirtz's new green house