

# ECE 321 - Homework #1

Push-Pull Amplifiers, Instrumentation Amplifiers, Temperature Sensors. Due Wednesday, November 13th

## ECE 321 Project:

0) Pick a project for ECE 321 (see page 2 for suggestions)

- Give the name of the people in your group
- Specify the requirements for the overall project

For the following sections, assume TIP112 (NPN) and TIP117 (PNP) transistors:


- $\beta = 1000$
- $V_{be} = 1.4V$
- $\min(V_{ce}) = 0.9V$
- $\max(I_c) = 3A$

## Push-Pull Amplifiers

1) Determine the voltages and currents for a the push-pull amplifier with a voltage outout for


- $X = -3V$
- $X = +3V$
- $X = 0V$

At 0V, everything is zero

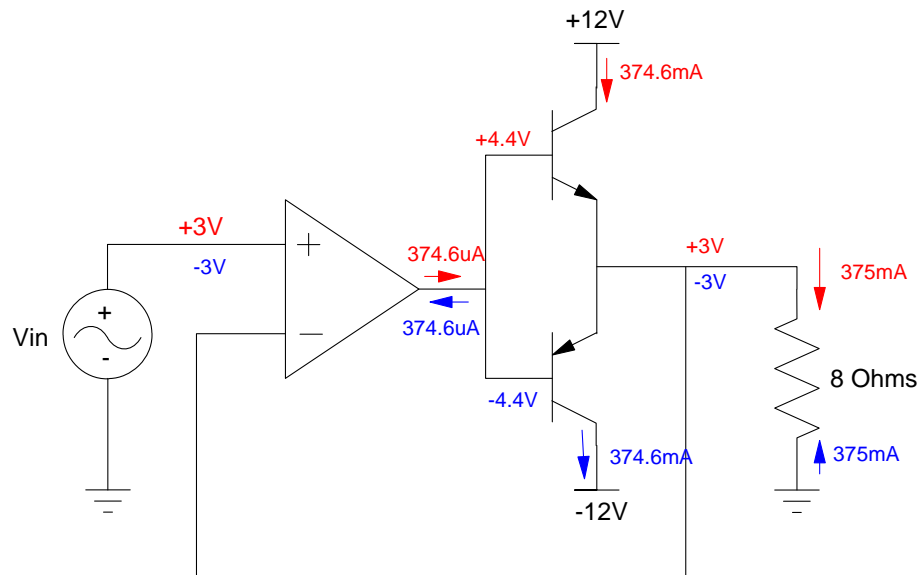



2) Determine the voltages and currents for a the push-pull amplifier with a current out for

- $X = -3V$
- $X = +3V$
- $X = 0V$

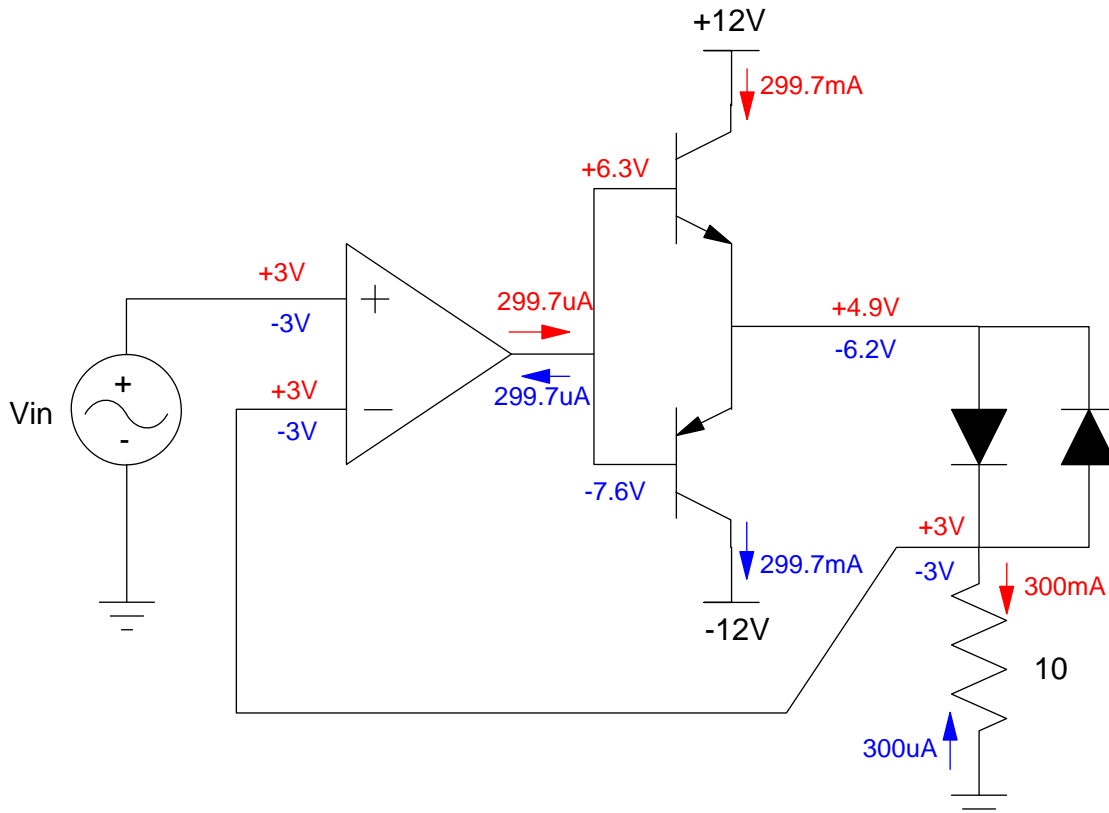

Pick one of these two push-pull amplifiers (your choice) for your term project.

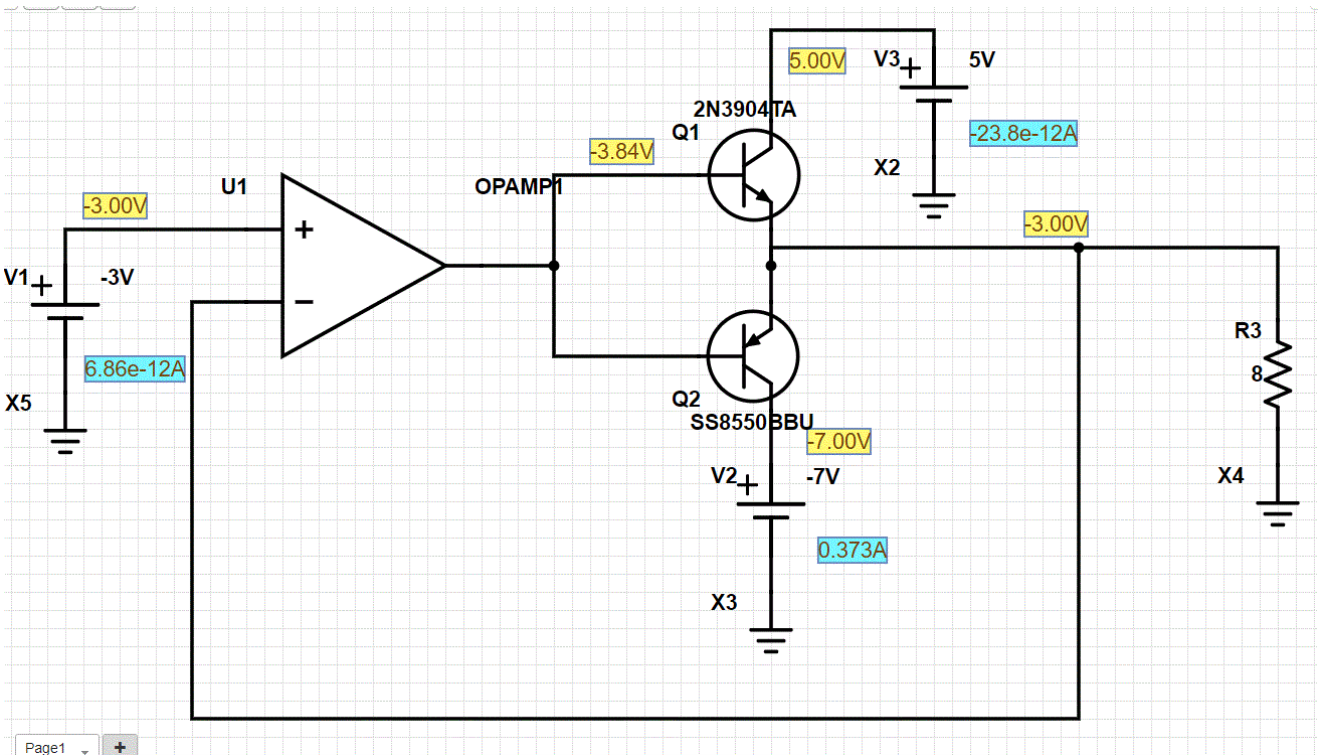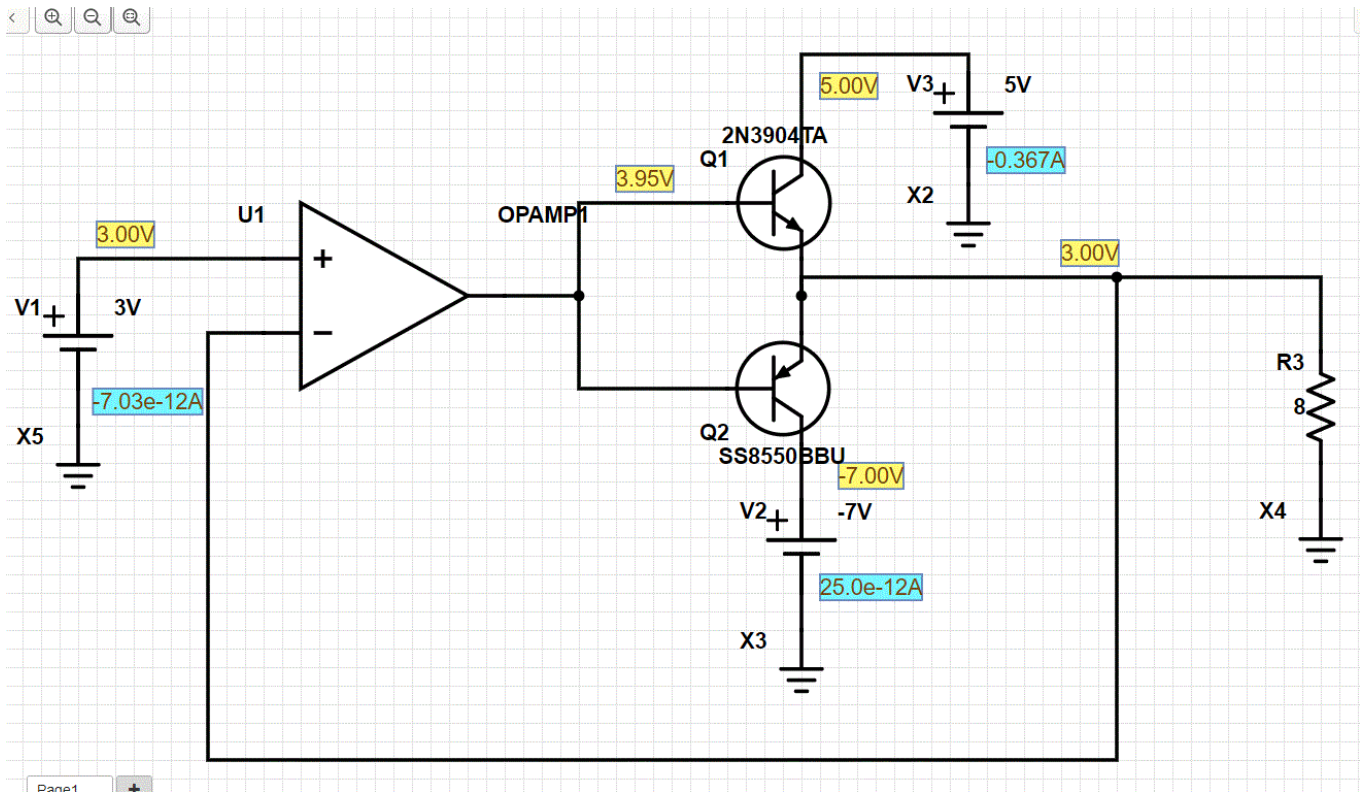
3) Check your computations using PartSim for the amplifier you picked (voltage or current output)




4) Build this amplifier in lab. Verify that it is operating correctly at -3V, 0V, and +3V.

### Instrumentation Amplifiers

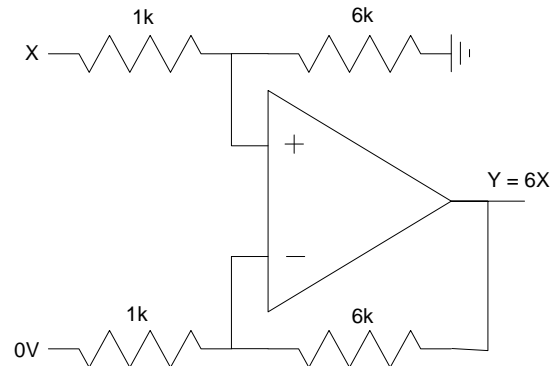
5) Design an op-amp circuit to implement the following functions



$$Y = 6X$$

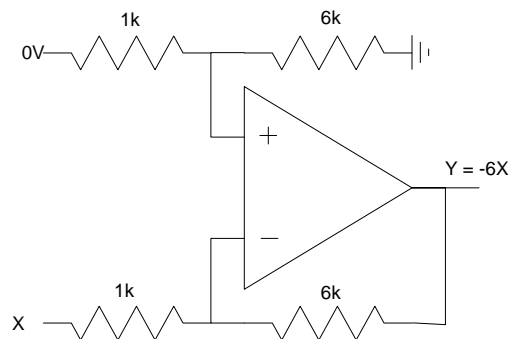

$$Y = -6X$$

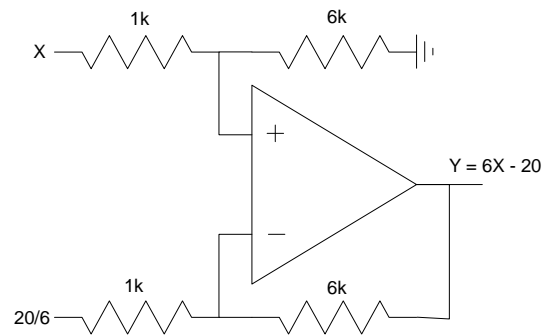

$$Y = 6X - 20$$


## Temperature Sensors

Assume a thermistor has a temperature - resistance relationship of

$$R = 1000 \cdot \exp\left(\frac{3905}{T} - \frac{3905}{298}\right) \Omega$$

6) Design a circuit so that the resistance is linear between 0C and +20C

Assume the following circuit

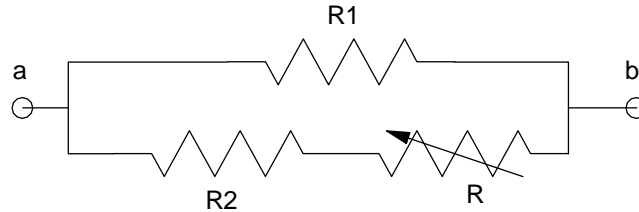

0C:

$$R = 3320.12 \text{ Ohms}$$

20C:

$$R = 1250.59 \text{ Ohms}$$

The total resistance is

$$R_{ab} = \left( \frac{R_1(R_2+R)}{R_1+R_2+R} \right)$$

Find R1 and R2 so that the resistance at 10C is the midpoint between 0C and 20C

$$R_{ab}(10C) = \left( \frac{R_{ab}(20C)+R_{ab}(0C)}{2} \right)$$

After some trial and error, a cost function that works is

```
function J = costR(Z)
// linearizing resistance

R1 = Z(1);
R2 = Z(2);

R0 = 3320.12;
R10 = 2002.83;
R20 = 1250.59;

Rab0 = (R1*(R2+R0)) / (R1 + R2 + R0);
Rab10 = (R1*(R2+R10)) / (R1 + R2 + R10);
Rab20 = (R1*(R2+R20)) / (R1 + R2 + R20);

E1 = 2*Rab10 - Rab0 - Rab20;
E2 = (R1 - 1000)/1000;


J = E1^2 + E2^2;

end
```


```
[E, Z] = leastsq(costR, [1000,2000])
      R1      R2
Z = 1000.0003  504.52357
E = 2.991D-16
```

Plotting Rab from 0C to 20C
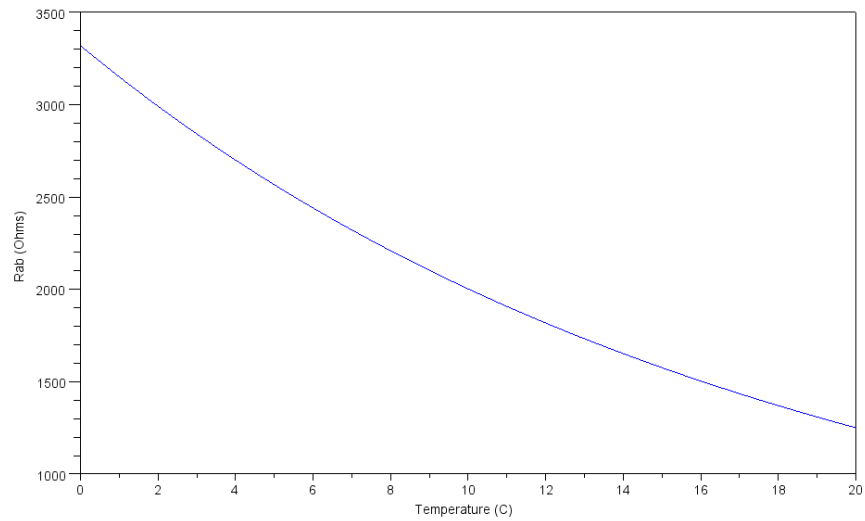
```
-->T = [0:0.01:20]';
-->K = T + 273;
-->R = 1000*exp( 3905 ./ K - 3905/298 )
-->plot(T,R)
```



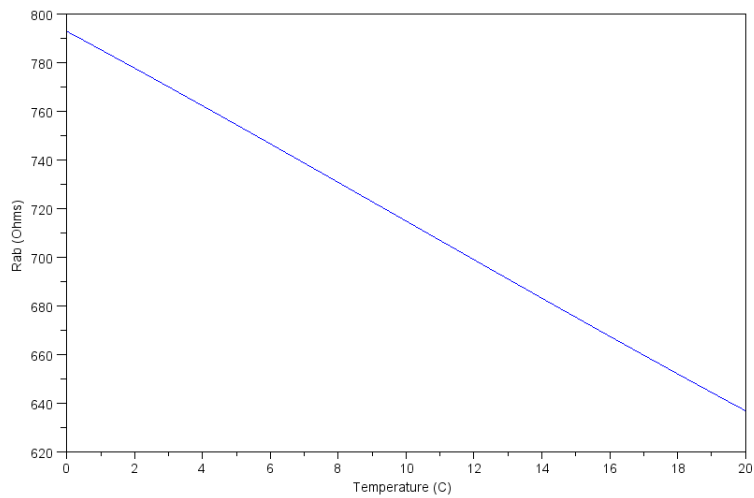
```
-->Rab = R1*(R2+R) ./ (R1 + R2 + R);
-->plot(T,Rab)
```



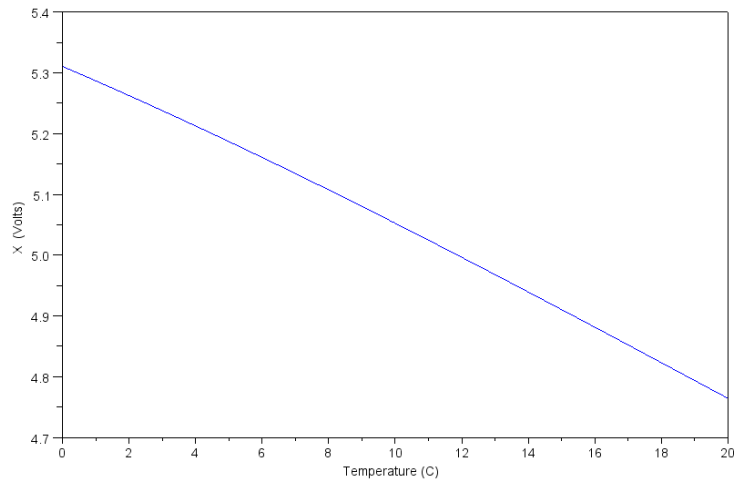7) Design a circuit which outputs

- 0V at 0C,
- 10V at 20C, and
- Proportional inbtween 0C and 20C


```
-->X = Rab ./ (700 + Rab) * 10;  
-->plot(T,X)  
-->xlabel('Temperature (C)');  
-->ylabel('X (Volts)')
```




```
gain = (10 - 0) / (max(V1) - min(V1))  
gain = 18.31307
```

```
offset = V1(1)  
offset = 5.3106093
```
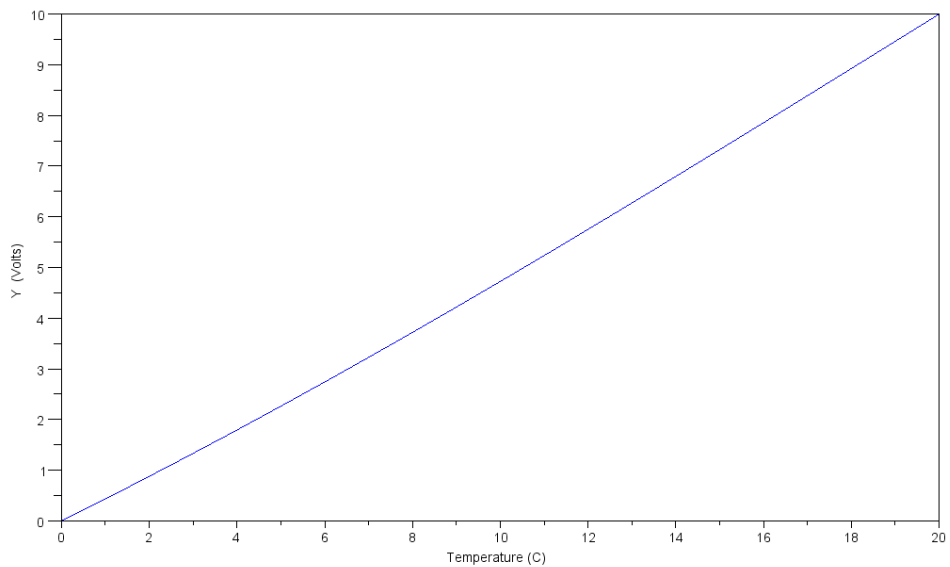
```
Y = gain*(offset - X);  
plot(T,Y)  
xlabel('Temperature (C)');  
ylabel('Y (Volts)')
```



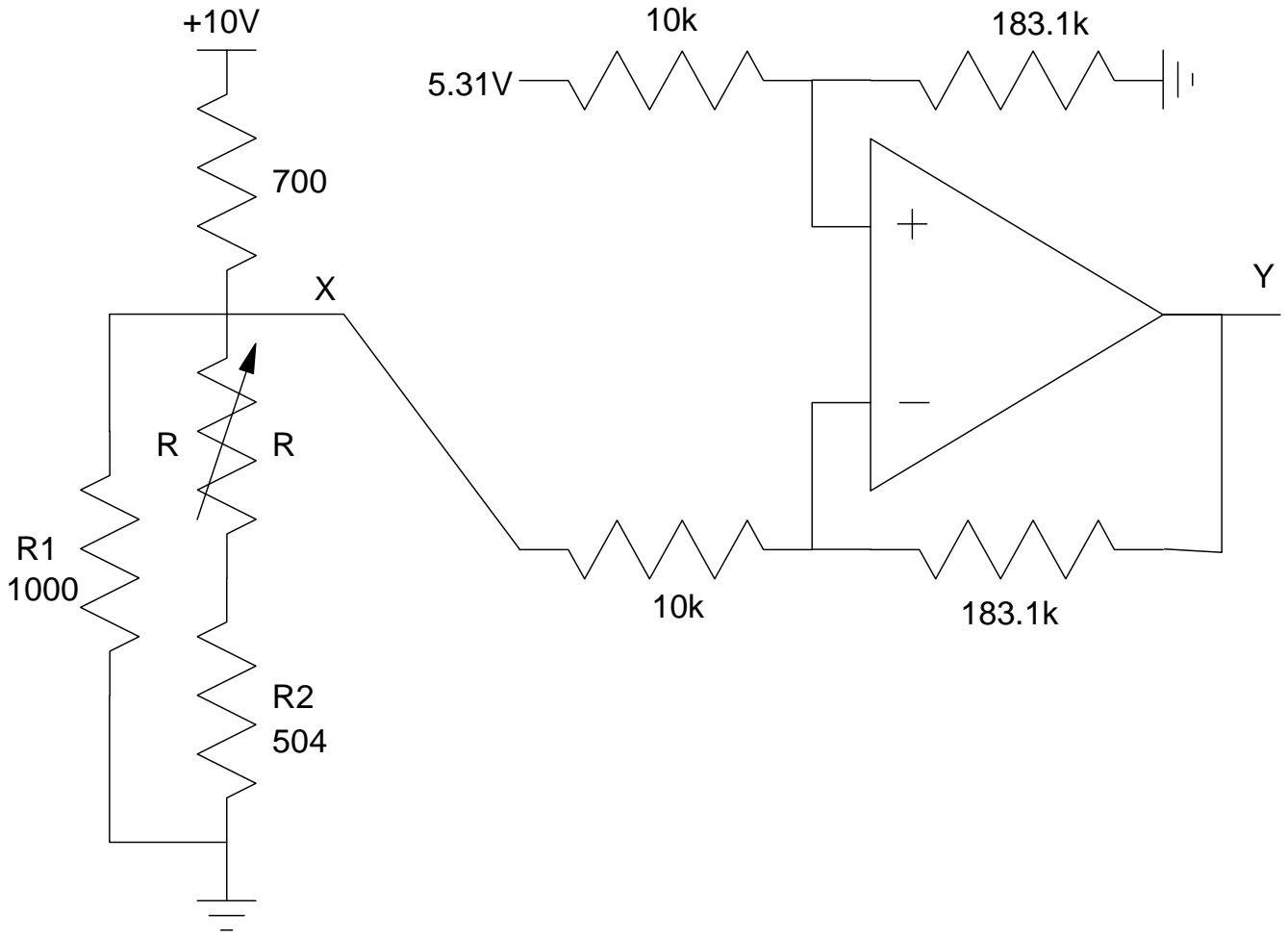

There are other solutions...