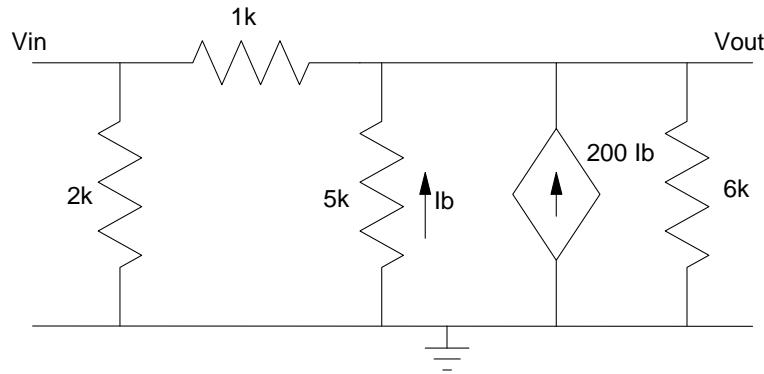


ECE 321 - Homework #4

2-Port Models, Transistor Amplifiers. Due Monday, December 9th

2-Ports

- Determine the 2-port model for the following circuit



Rin: Short Vout. Measure the resistance at Vin

$$R_{in} = 2k \parallel 1k = 666.7\Omega$$


Ai: Apply 1V to Vout. Measure Vin.

From voltage division

$$A_i = \left(\frac{2k}{2k+1k} \right) \cdot 1V = 0.667$$

Rout: Short Vin. Measure the resistance.

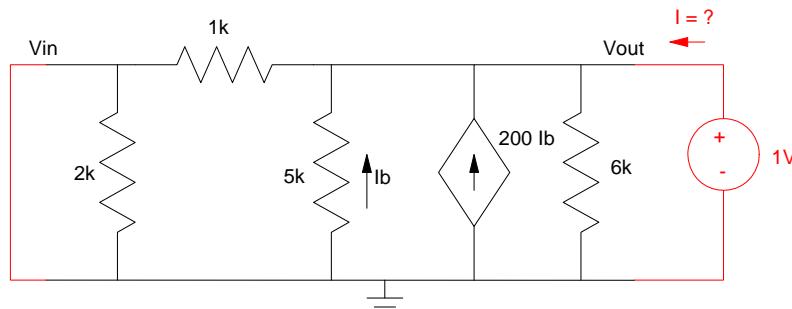
This isn't obvious, so apply a 1V test to Vout and measure the current



$$I = \frac{1}{6k} + \frac{1}{1k} + \frac{1}{5k} + 200 \left(\frac{1}{5k} \right) = 41.37mA$$

$$R_{in} = \frac{1V}{41.37mA} = 24.17\Omega$$

Aout: Apply 1V to Vin. Compute Vout

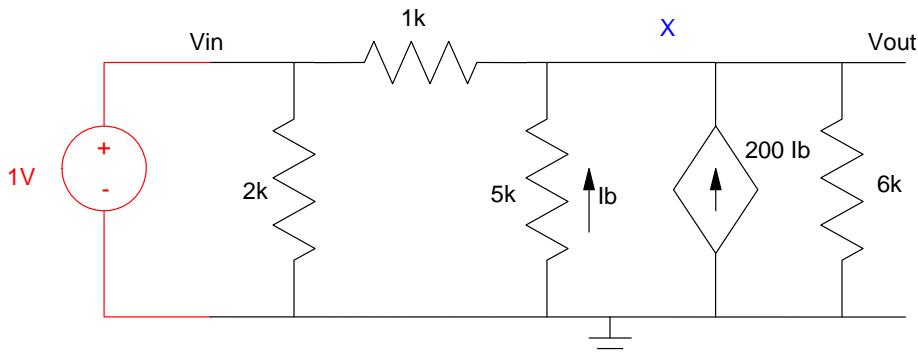


Using voltage nodes


$$\left(\frac{X-1}{1k}\right) + \left(\frac{X}{5k}\right) + 200\left(\frac{X}{5k}\right) + \left(\frac{X}{6k}\right) = 0$$

$$X = 0.02417 = A_o$$


The 2-port model is then

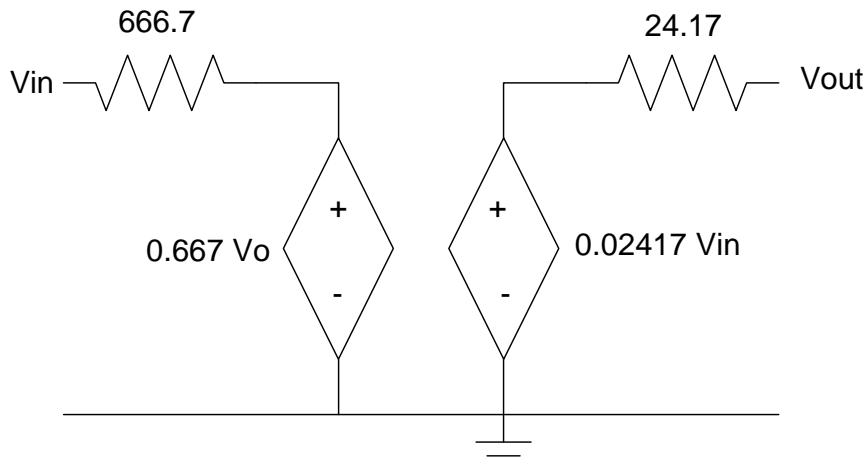

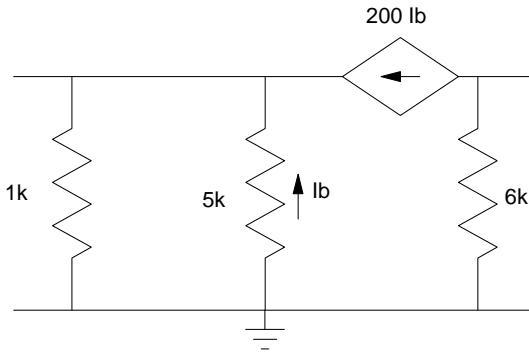2) Determine the 2-port model for the following circuit



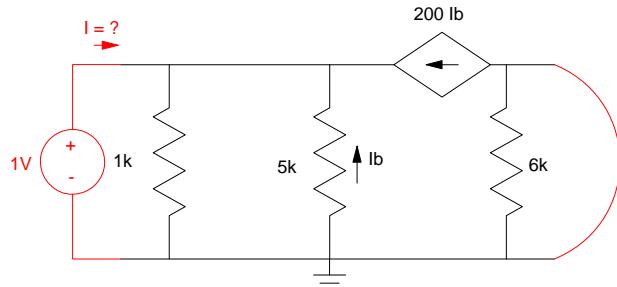Rin: Short Vout. Measure the resistance looking in. This isn't obvious so apply a 1V test voltage




$$I = \frac{1}{1k} + \frac{1}{5k} + 200\left(\frac{1}{5k}\right) = 41.20mA$$

$$R_{in} = \frac{1V}{41.20mA} = 24.27\Omega$$

Ai: Apply 1V at the output. Compute Vin.

Turns out that Vin = 0V


$$Ai = 0.$$

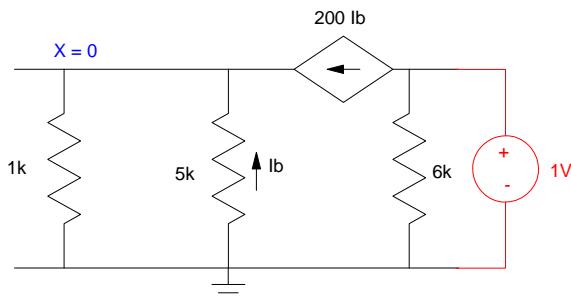

Rout: Short Vin. Compute the resistance at the output

$$R_{out} = 6k$$

Ao: Apply 1V to Vin. Compute Vout

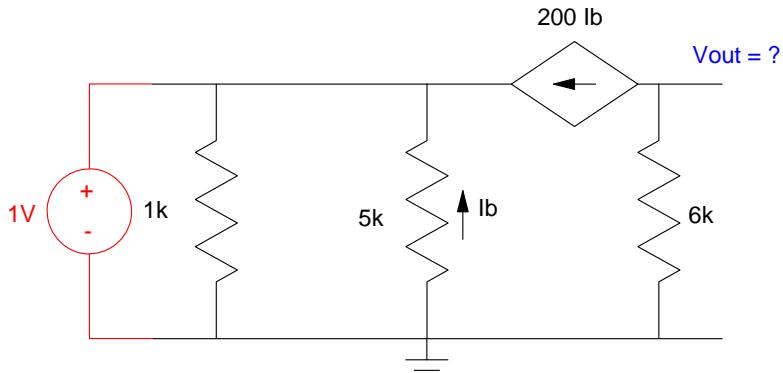


$$I_b = \frac{1V}{5k} = 200\mu A$$


$$200I_b = 40mA$$

$$V_o = 6000 \cdot 40mA = +240$$

The 2-port model is then

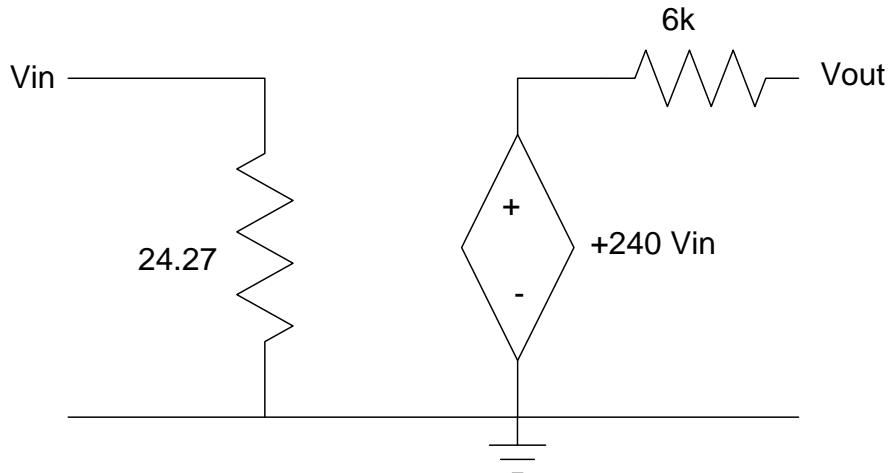

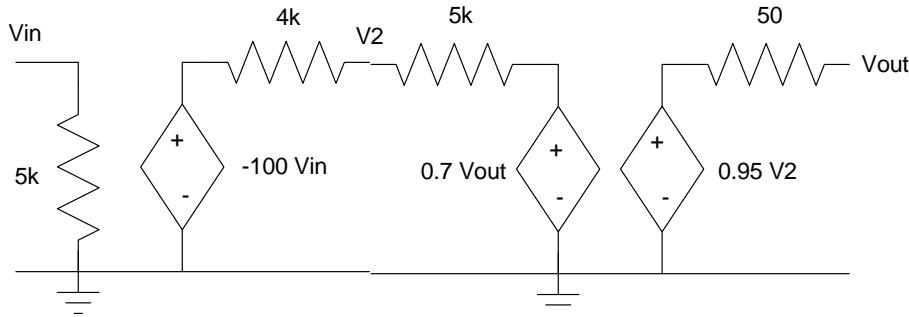3) Determine the 2-port model for the following circuit




By inspection

$$R_{in} = 5k$$

$$A_i = 0$$

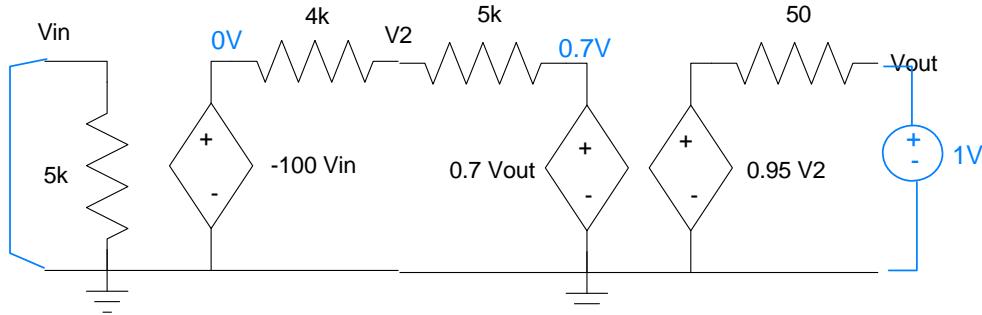R_{out} : Short V_{in} . Measure the resistance at V_{out} . This isn't obvious so add a 1V source to V_{out} and compute the current



V_2 is then

$$V_2 = \left(\frac{4k}{4k+5k} \right) 0.7V = 0.3111V$$


I and R_{out} is then

$$0.95V_2 = 0.2956V$$

$$I = \left(\frac{1V - 0.2956V}{50} \right) = 14.09mA$$

$$R_{out} = \frac{1V}{14.09mA} = 70.98\Omega$$

Ao: Apply 1V to the input. Compute Vout.

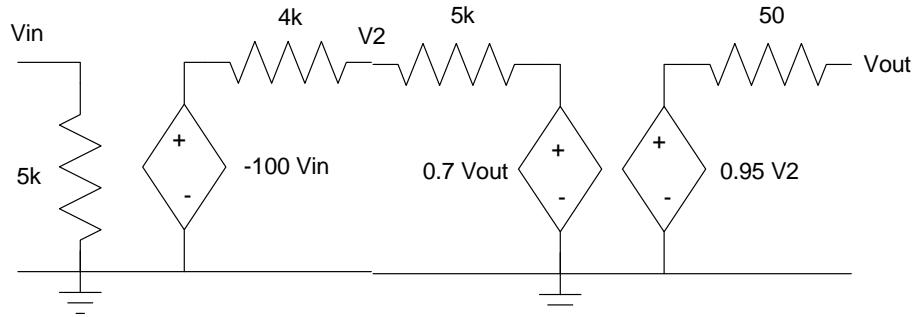

Writing a voltage node at V2

$$\left(\frac{V_2 - (-100)}{4k} \right) + \left(\frac{V_2 - 0.7V_{out}}{5k} \right) = 0$$

$$V_{out} = 0.95V_2$$


Substituting

$$\left(\frac{V_2 - (-100)}{4k} \right) + \left(\frac{V_2 - 0.7(0.95V_2)}{5k} \right) = 0$$

$$V_2 = -78.8644V$$



$$V_{out} = 0.95V_2 = 74.9211V$$

The 2-port model is then

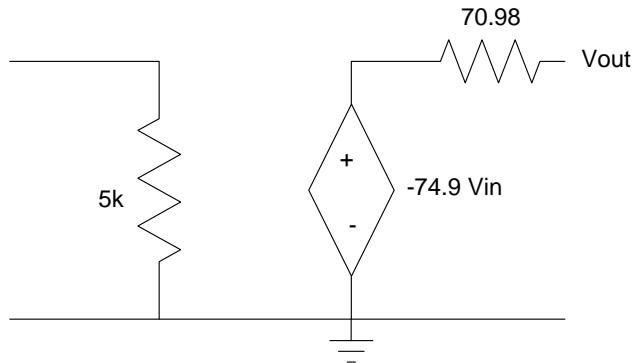

Transistor Amplifiers: DC Analysis

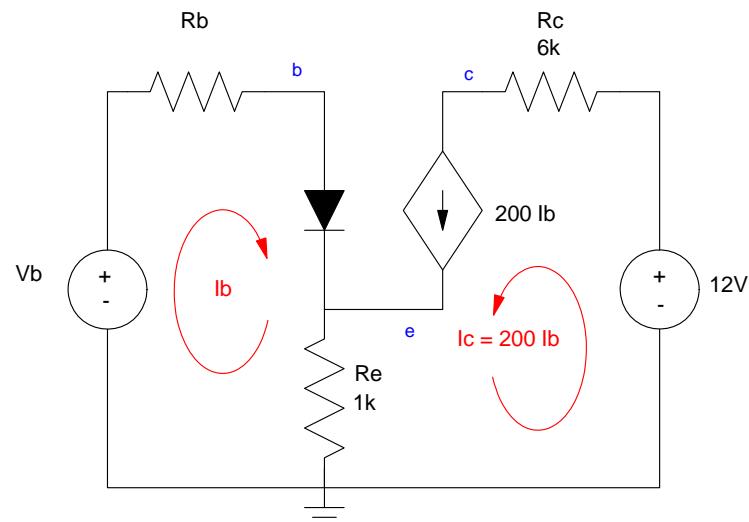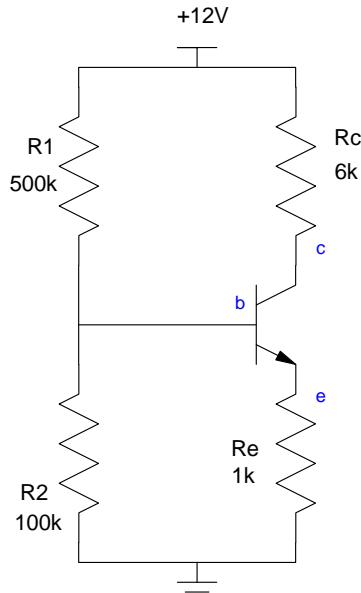4) Determine the Q-point for the following transistor amplifier. Assume 3904 transistors with beta = 200 (nominal)



$$V_b = V_{th} = \left(\frac{100k}{100k+500k} \right) 12V = 2V$$

$$R_b = R_{th} = 100k \parallel 500k = 83.33k$$

Writing the loop equation for Ib

$$-V_b + R_b I_b + 0.7 + 1k \cdot (I_b + 200I_b) = 0$$

$$I_b = \left(\frac{V_b - 0.7}{R_b + (1+200)R_e} \right) = 4.572\mu A$$

$$I_c = 200I_b = 914.4\mu A$$

Vc and Ve are then

$$V_e = R_e(I_b + I_c) = 0.919V$$

$$V_c = 12 - 6000I_c = 6.513V$$

The Q-point is then

$$V_{ce} = V_c - V_e = 5.5494V$$

$$I_c = 914.4\mu A$$

5) Modify the circuit from problem #4 so that

- $V_{ce} = 6.0V$, and
- The Q-point is stabilized for variations in beta

To stabilize the Q-point

$$(1 + \beta)R_e \gg R_b$$

$$201k \gg R_b$$

Let $R_b = 20k$

For $V_{ce} = 6V$

$$6V = 12V - 6000I_c - 1000(I_c + I_b)$$

$$I_c = 856.5\mu A$$

$$I_b = \frac{I_c}{200} = 4.283\mu A$$

V_b is then

$$V_b = R_b I_b + 0.7 + R_e(I_b + I_c)$$

$$V_b = 1.646V$$

R_1 and R_2 are then


$$\left(\frac{R_1 R_2}{R_1 + R_2} \right) = R_b = 20k$$

$$\left(\frac{R_2}{R_1 + R_2} \right) 12V = V_b = 1.646V$$

Solving

$$R_1 = 145.8k$$

$$R_2 = 23.18k$$

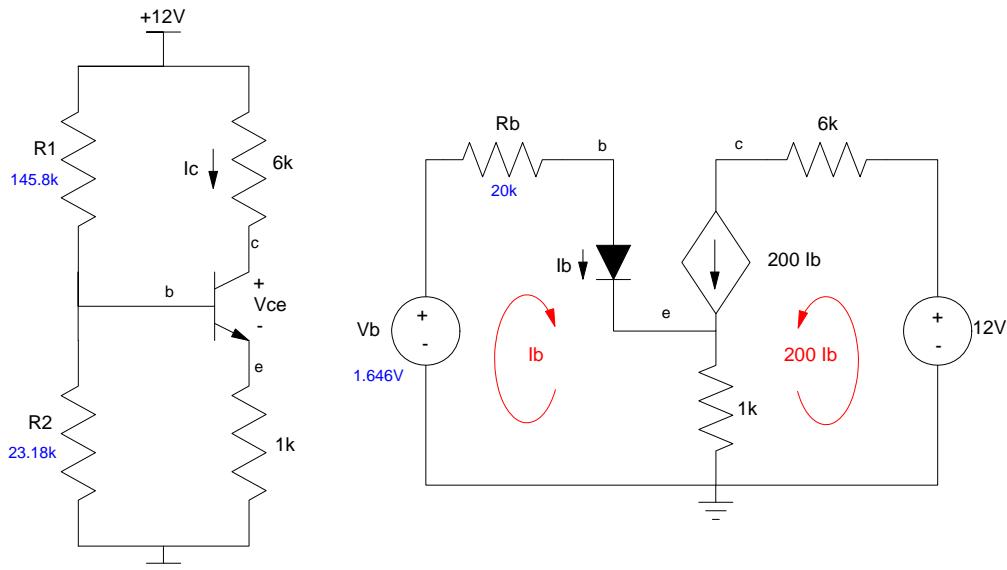


Transistor Amplifiers: AC Analysis

- 6) Draw the small-signal model (i.e. AC model) for a single CE amplifier (shown in red). Determine the 2-port model

$$I_b = 4.572\mu A$$

$$r_f = \left(\frac{0.052}{I_b} \right) = 11.37k$$

The small-signal model is then

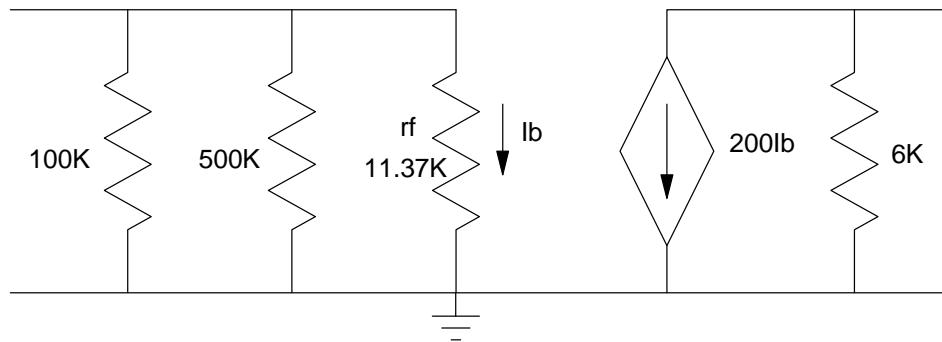

The 2-port parameters are:


$$R_{in} = 100k \parallel 500k \parallel r_f = 10.01k$$

$$A_{in} = 0$$


$$R_{out} = 6k$$

$$A_o = -\frac{\beta R_c}{r_f} = -105.5$$


2-port parameters are then

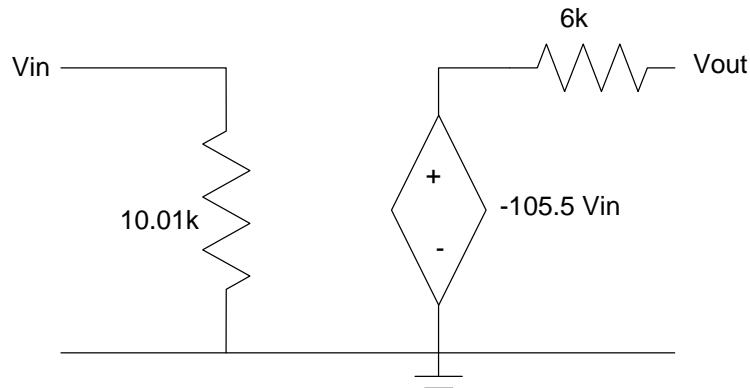

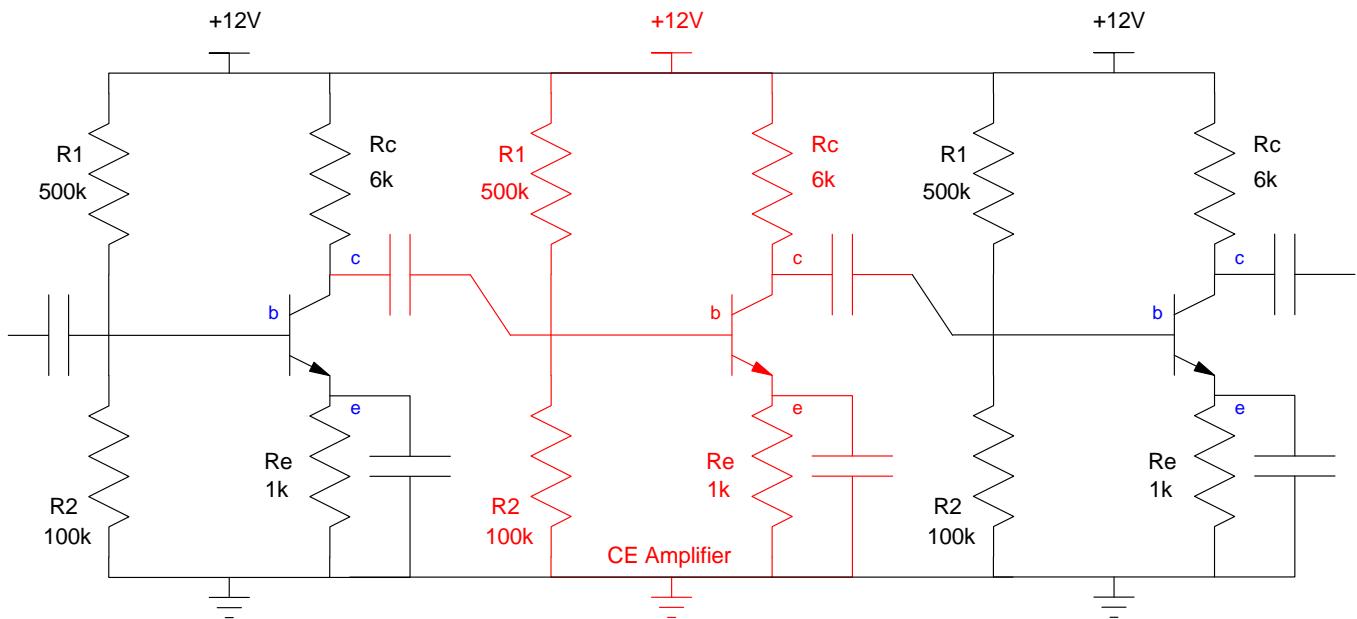7) Determine the 2-port model for three CE amplifiers cascaded back-to-back



Cascade three 2-port models

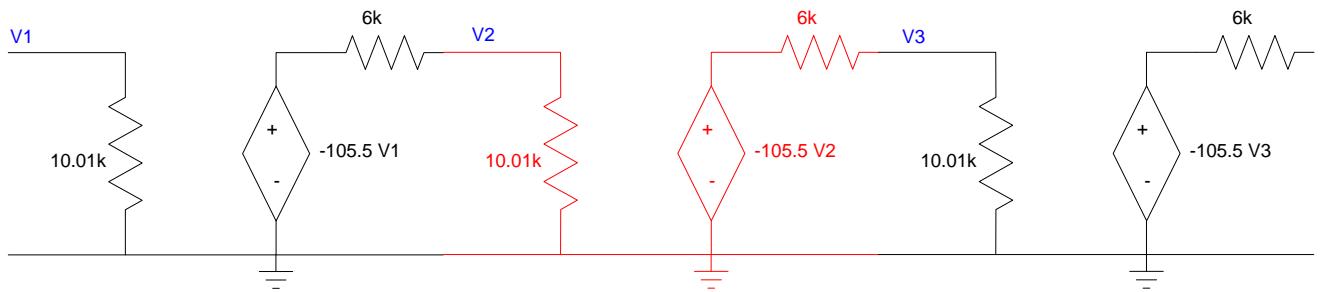

Simplify:


$$R_{in} = 10.01k$$

$$A_i = 0$$

$$R_{out} = 6k$$

$$A_o = (-105.5) \left(\frac{10.01k}{10.01k+6k} \right) (-105.5) \left(\frac{10.01k}{10.01k+6k} \right) (-105.5) = 459,132$$

The 2-port model is then

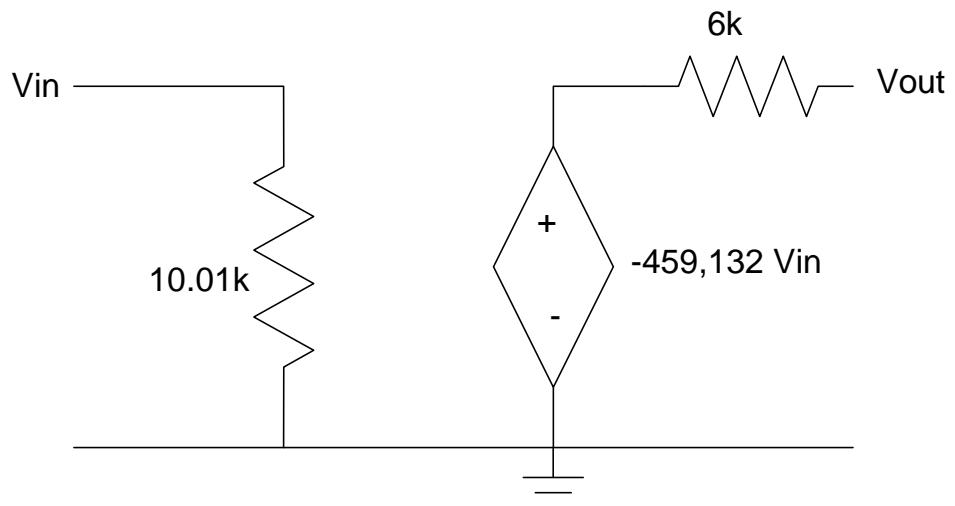

2-port model of three cascaded CE amplifiers