

ECE 321 - Final - Name _____


$R = \underline{\hspace{2cm}} (\text{Your Birth Month}) * 1000 + (\text{Your Birthdate}) * 10$

- For example, Feb 14th would be $R = 2140$ Ohms.

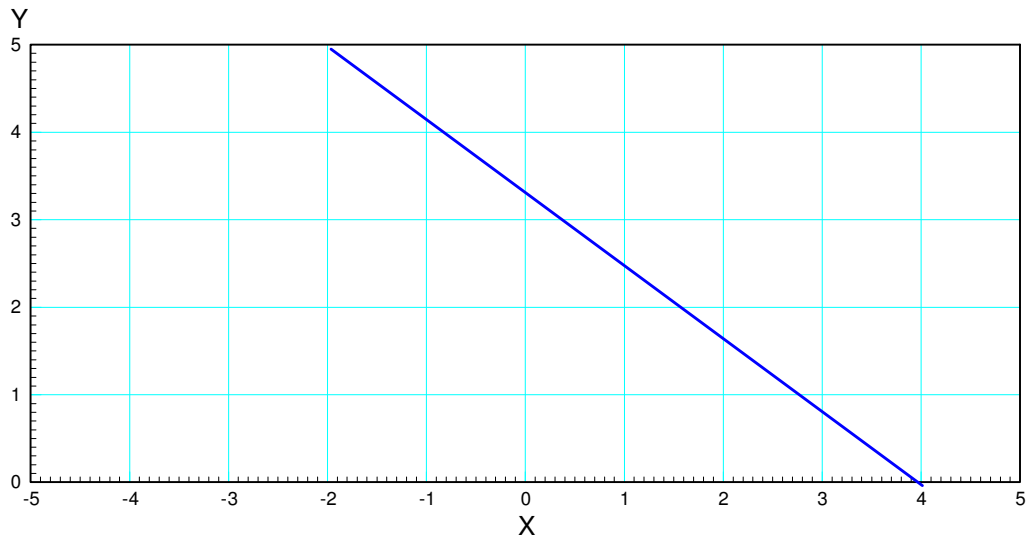1) Amplifiers

1a) Determine the equation for the line, $Y = AX + B$

1b) Design an op-amp circuit to implement $Y = f(X)$. Include R in your answer somewhere (birth month & date)




2) Push-Pull Amplifier

The following circuit can output $-5V$ to $+5V$ using only a single $10V$ power supply. Determine the voltages and currents when $V_{in} = 3V$. Assume 3904/3906 transistors

- $\beta = 200$
- $|V_{be}| = 0.7V$

R	V1	V2	V3	V4	I5

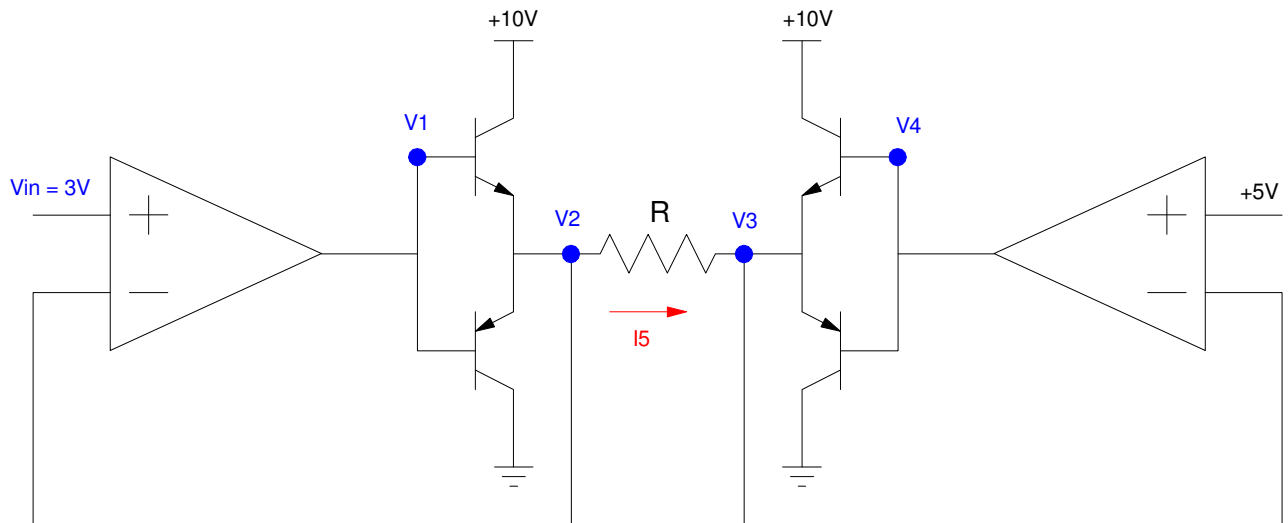$R = \text{birth month} * 1000 + \text{birth day} * 10$. Feb 14th = 2140 Ohms



3) Instrumentation Amplifier



An RTD (type of temperature sensor) has a resistance - temperature relationship of

$$RTD = 2000 \cdot (1 + 0.0043T)\Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- 0V at 0C and
- 10V at +25C

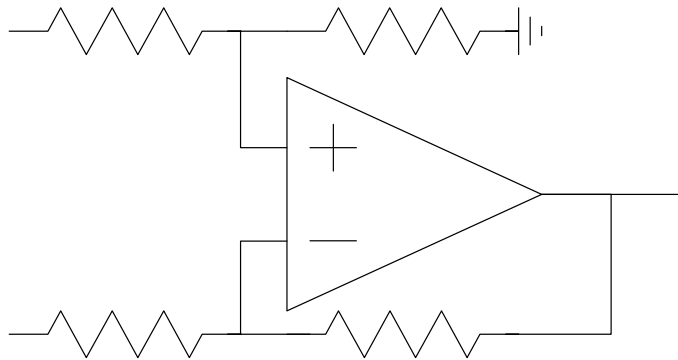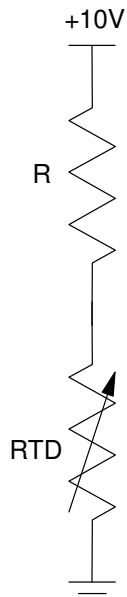Let R be your birth month * 1000 + birth day * 10. Feb 14th = 2140 Ohms



4) Filter: Analysis

Assume X and Y are related by the following transfer function

$$Y = \left(\frac{500(s+2)}{(s+10)(s+30)} \right) X$$

a) What is the differential equation relating X and Y?

b) Determine $y(t)$ assuming

$$x(t) = 5 + 2 \cos(\omega t) + 4 \sin(\omega t)$$

where ω is your birth date (1..31)

5) Filter: Design

Design a circuit so that the gain is

- $0.9 < \text{gain} < 1.1$ for frequencies below 10 rad/sec
- $\text{gain} < 0.3$ for frequencies above 15 rad/sec

Determine the gain of your final design at 10 and 15 rad/sec

6) Filter Design

Design a circuit to implement the following filter:

$$Y = \left(\frac{10.000}{(s^2+10s+R)(s^2+20s+2R)} \right) X$$

where R is your birth month * 1000 + birth date * 10. For example, Feb 14 = 2140



7) CE Amplifier (DC)

Determine the Q-point (V_c , R_c) for the following transistor circuit. Assume a 3904 transistor

- $\beta = 200$
- $|V_{be}| = 0.7$

R	Vb	Rb	Vce	Ic

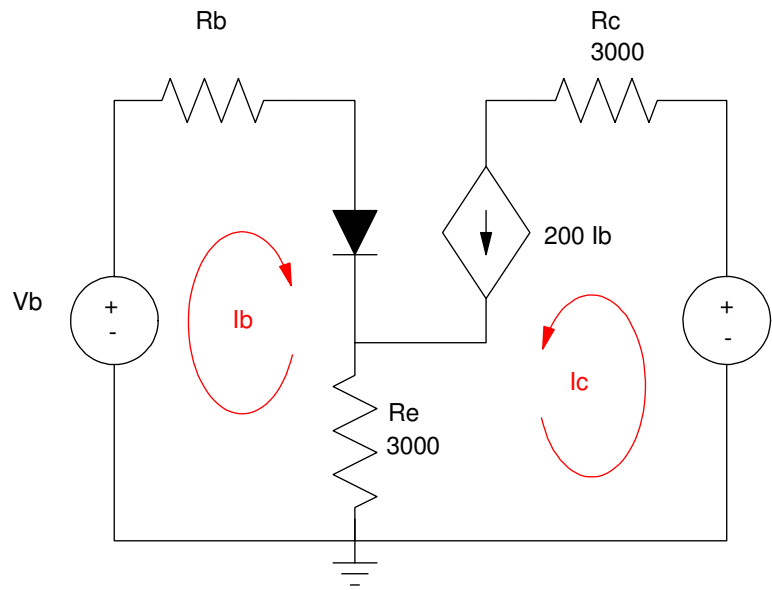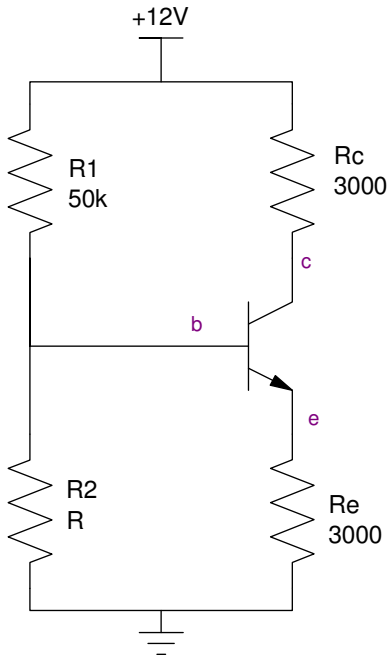R = birth month * 1000 + birth day * 10. For example, Feb 14th = 2140 Ohms



8) CE Amplifier (AC)

Draw the small signal model for this amplifier and the resulting 2-port model. Assume 3904 transistors

- $\beta = 200$
- $V_{be} = 0.7V$

R	R _{in}	A _i	R _{out}	A _o

R = birth month * 1000 + birth day * 10. For example, Feb 14th = 2140 Ohms

